

The Design of Low-Latency Interfaces for Mixed-Timing Systems

Tiberiu Chelcea and Steven M. Nowick

Department of Computer Science
Columbia University

*Keynote Invited Talk: "GALS" Session
IEEE Workshop on Complexity-Effective Design (ISCA-02)
May 26, 2002*

Trends and Challenges

Trends in Chip Design: next decade

- * *"Semiconductor Industry Association (SIA) Roadmap"* (97-8)

Unprecedented Challenges:

- * complexity and scale (= size of systems)
- * clock speeds
- * power management
- * reusability & scalability
- * "time-to-market"

Design becoming unmanageable using a centralized single clock (synchronous) approach....

Trends and Challenges (cont.)

1. Clock Rate:

- * *1980: several MegaHertz*
- * *2001: ~750 MegaHertz - 1+ GigaHertz*
- * *2004: several GigaHertz*

Design Challenge:

- * *"clock skew":* clock must be near-simultaneous across entire chip

Trends and Challenges (cont.)

2. Chip Size and Density:

Total #Transistors per Chip: *60-80% increase/year*

- * *~1970: 4 thousand (Intel 4004)*
- * *today: 10-100+ million*
- * *2004 and beyond: 100 million-1 billion*

Design Challenges:

- * *system complexity, design time, clock distribution*
- * *clock will not reach across chip in 1 cycle*

Trends and Challenges (cont.)

3. Power Consumption

- * Low power: ever-increasing demand
 - * consumer electronics: battery-powered
 - * high-end processors: avoid expensive fans, packaging

Design Challenge:

- * *clock inherently consumes power continuously*
- * “power-down” techniques: only partly effective

Trends and Challenges (cont.)

4. Time-to-Market, Design Re-Use, Scalability

Increasing pressure for faster "*time-to-market*". Need:

- * reusable components: "plug-and-play" design
- * scalable design: easy system upgrades


Design Challenge: mismatch w/ central fixed-rate clock

Trends and Challenges (cont.)

 5. Future Trends: "Mixed Timing" Domains

Chips themselves becoming *distributed systems*....

- * contain many sub-regions, *operating at different speeds:*




Design Challenge: breakdown of single centralized clock control

Introduction


Example: System-on-a-Chip (SoC) Design

- Building entire **large-scale system** on a single chip
- **Benefit:** Higher-level of integration
 - * Improved performance, cost, area
- **Challenges:**
 - * Mixed-timing: moving to multiple timing domains
 - * Performance degradation: synchronization overhead
 - * Complexity, scale, integration
 - * Designing & incorporating of *asynchronous subsystems*

Future Chips

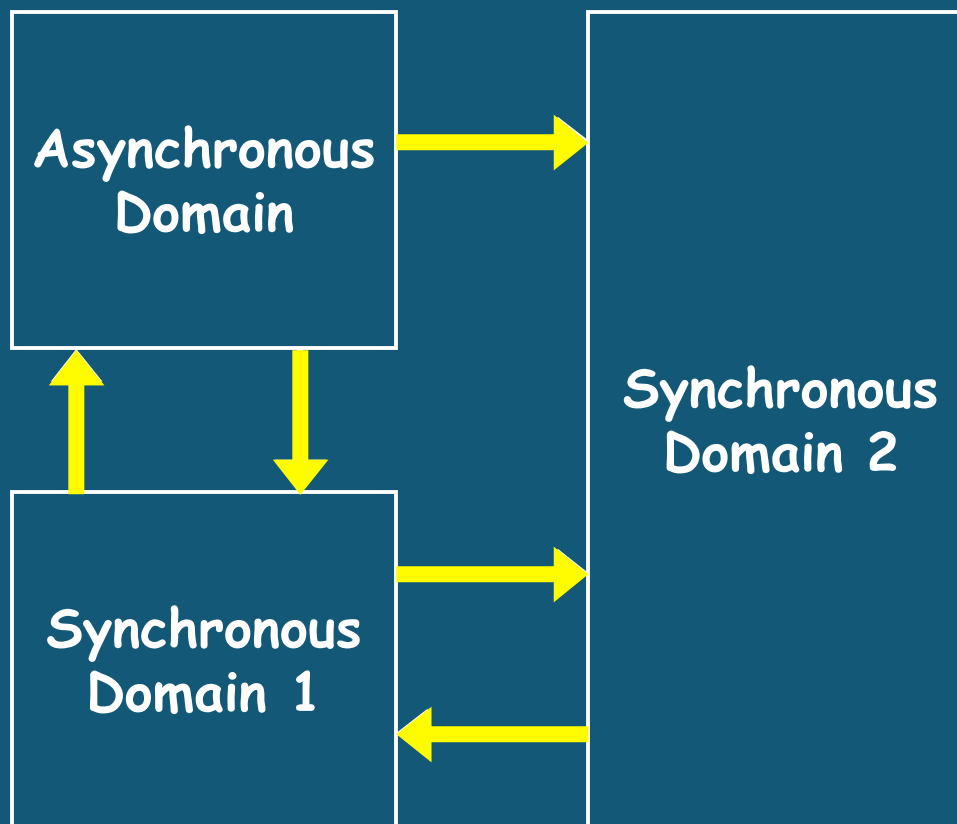

Research Areas

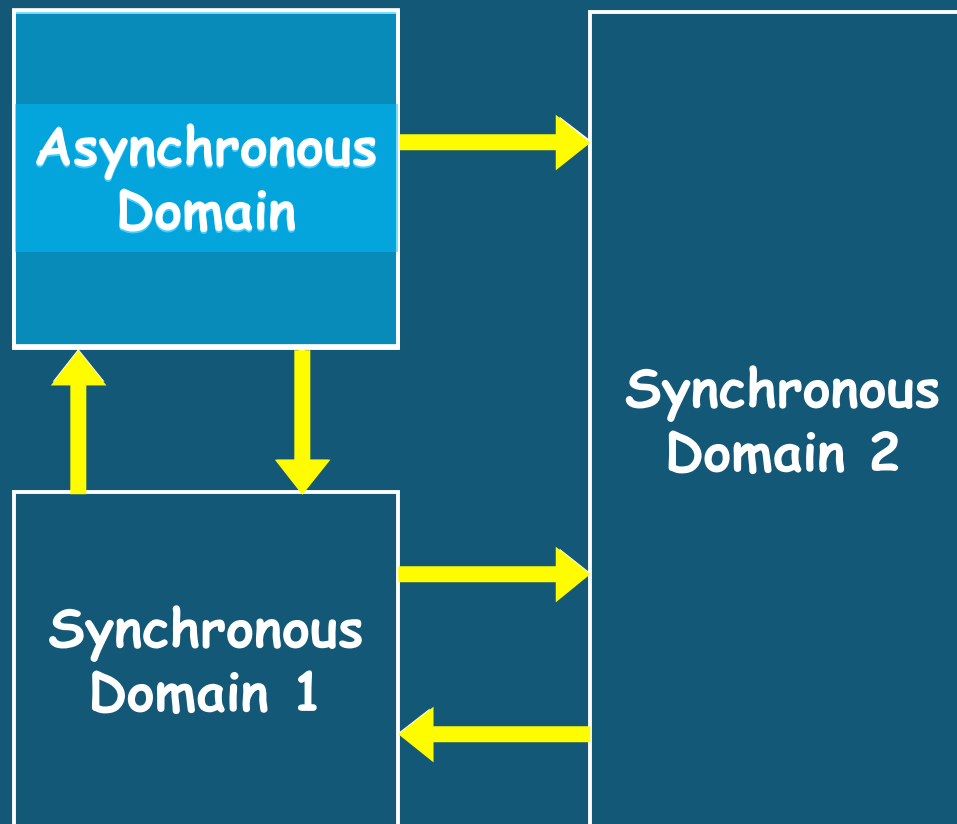

Goal #1: interface mixed-timing domains with low latency

Goal #2: synthesis + optimization of asynchronous systems

Summary: Key Challenges in System Design

Two key issues not yet completely addressed:

1. Communication between **mixed-timing domains**:

- * Goals: **performance and scalability**

2. Synthesis of **large-scale asynchronous systems**:

- * Goals: develop **powerful optimizing CAD tools**,
facilitating “design-space exploration”

Asynchronous Design: Motivation

Need for large-scale asynchronous systems:

- * **Future chips:** likely a mix of async and sync domains

Asynchronous Systems: offer a number of advantages

GALS: “globally-asynchronous, locally-synchronous”

- * **Hybrid style:** introduced by Chapiro [84]
 - * synchronous “processing elements” (“satellites”)
 - * asynchronous communication
- * Recent interest: “Communication-Based Design”
 - * UC Berkeley/Stanford: W. Dally, K. Keutzer, A. Sangiovanni
 - * *orthogonalization of concerns: function vs. communication*

Asynchronous Design: Potential Advantages

- **Modularity:**
 - * Interface easily with sync domains & environment
- **Reusability and scalability:**
 - * Handle wide range of interface speeds \Rightarrow reuse
 - * Scalability: easily add new subsystems
- **Average-case performance:**
 - * Intel RAPPID instruction-length decoder: 3-4x faster than sync design
 - * Differential equation solver: 1.5x faster than sync design
- **Lower power consumption:**
 - * Avoids clock distribution power
 - * Provides automatic "clock gating" ... at *arbitrary granularity*
 - * Digital hearing aid chip: 4-5.5x less power
- **Low electromagnetic interference (EMI):** no regular clock spikes
 - * Philips, commercial 80c51 microcontrollers: in cell phones, pagers

Industrial interest: Intel, Sun, IBM, Philips, Theseus, Fulcrum

Related Work #1: Interfacing in Single Clock Domain

Handling Timing Discrepancies...:

Clock Skew:

- * STARI Chip [M. Greenstreet, ICCD-95]

Use async buffer to smooth out discrepancies between *sender* and *receiver*

- * Skew-Tolerant Domino [M. Horowitz]
- * Clock-Skew Scheduling [E. Friedman]

- * Long interconnect delays [Carloni99]: limited to single clock

Long Interconnect Delays:

- * "Relay Stations" [Carloni, Sangiovanni-Vincentelli, DAC-00]
Break up overlong wires by pipelining communication

Related Work: Interfacing Mixed-Timing Domains

Two common approaches...:

- **Modify Receiver's Clock:**

- ✦ "stretchable" and "pausable" clocks

- ✦ Chapiro84, Yun96, Bormann97, Sjogren/Myers97, Moore02

- ✦ **drawbacks:**
 - Penalties in restarting clock
 - Does not support design reuse

- **Use Synchronization Components:**

- ✦ data/control synchronization

- ✦ Seitz80, Seizovic94, Intel97, Sarmenta95, Kol98

- ✦ **drawbacks:** overheads in throughput, latency, area

Contribution: Mixed-Timing Interfaces

A complete family of mixed-timing FIFO's

Characteristics:

- Low-latency
- Modular and scalable:
 - * Define interfaces for each combination of:
 - * Synchronous or Asynchronous domains
 - * Combine interfaces to design new async/sync FIFO's
- High throughput:
 - * In steady state: no synchronization overhead, no failure probability
 - * Enqueue/Dequeue data items: one/cycle
- Low area overheads

Also, solve issue of long interconnect delays between domains

Contribution: Mixed-Timing Interfaces

Publications

Latest Solution:

IEEE Transactions on VLSI Systems, vol. 12:8, pp. 857-853 (August 2004)

T. Chelcea and S.M. Nowick,
"Robust Interfaces for Mixed-Timing Systems"

IEEE/ACM Design Automation Conference (DAC, June 2001)

T. Chelcea and S.M. Nowick, "Robust Interfaces for Mixed-Timing Systems with Application to Latency-Insensitive Protocols"

Initial Solution:

IEEE Computer Society Workshop on VLSI (WVLSI, April 2000)

T. Chelcea and S.M. Nowick, "A Low-Latency FIFO for Mixed-Clock Systems"

See also:

A. Iyer and D. Marculescu, *ISCA-02*.

Outline

I. Mixed-Timing Interface Circuits

- * Sync/Sync
- * Async/Async
- * Async/Sync

II. Handling Long Interconnect Delays


Experimental Results

Conclusions

Part I


Mixed-Timing Interface Circuits

Mixed-Timing Interfaces: Overview

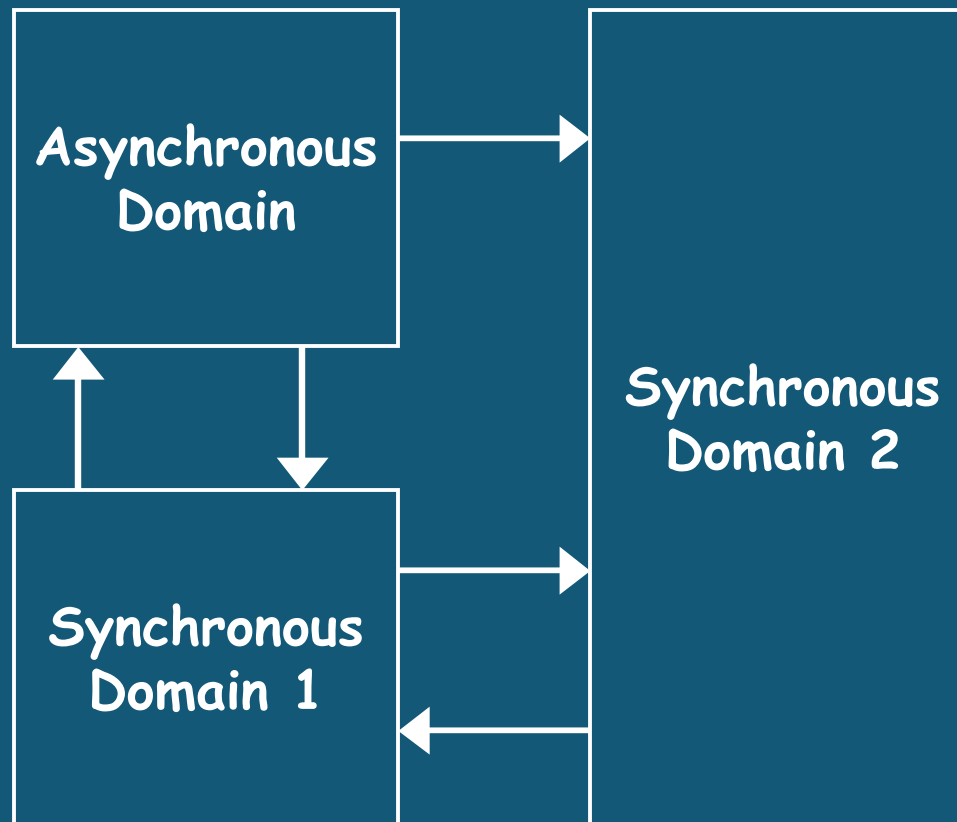

Problem: potential data synchronization errors

Mixed-Timing Interfaces: Overview

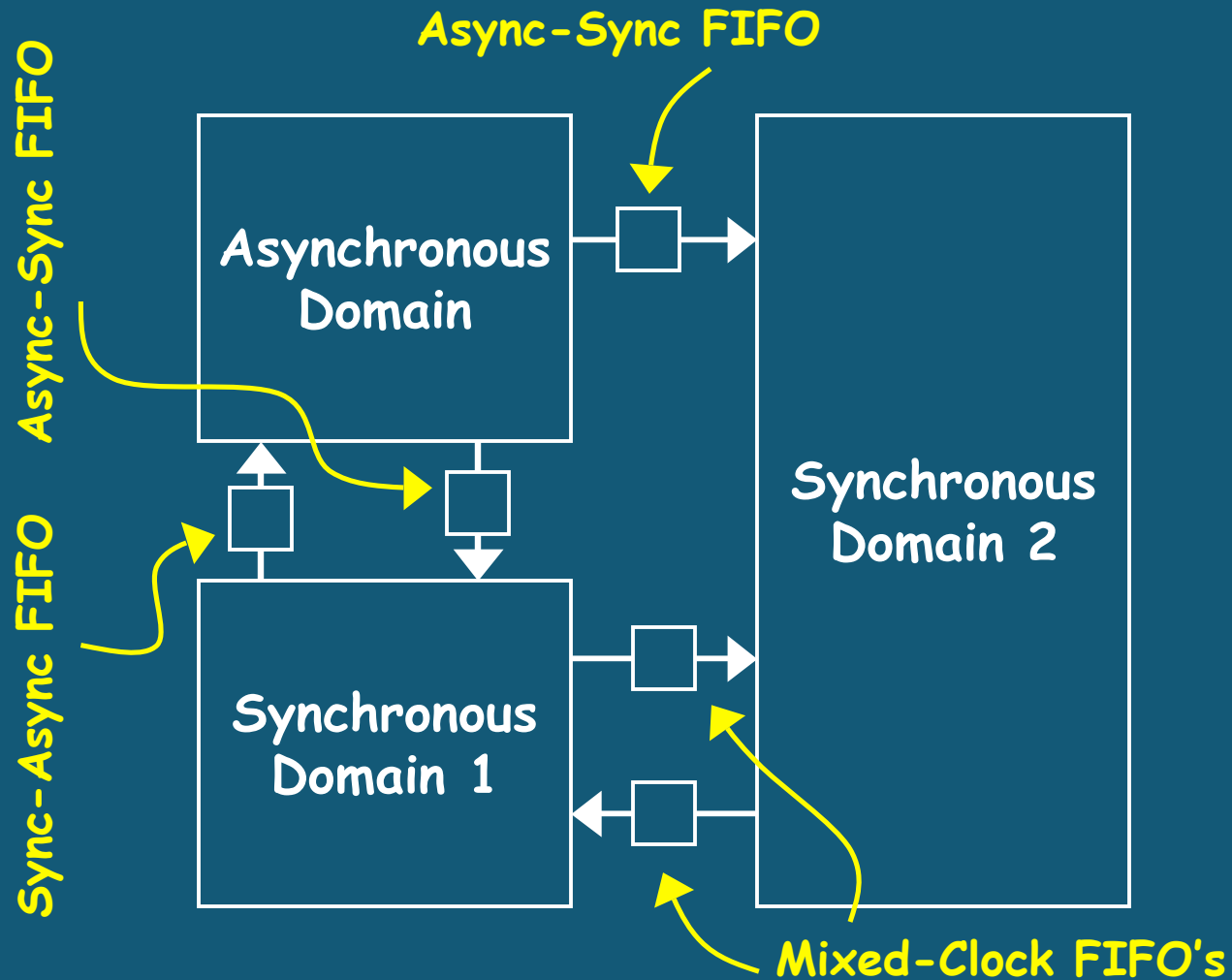


Problem: potential data synchronization errors

Solution: insert mixed-timing FIFO's \Rightarrow safe data transfer


Mixed-Clock FIFO: Block Level

synchronous
put interface

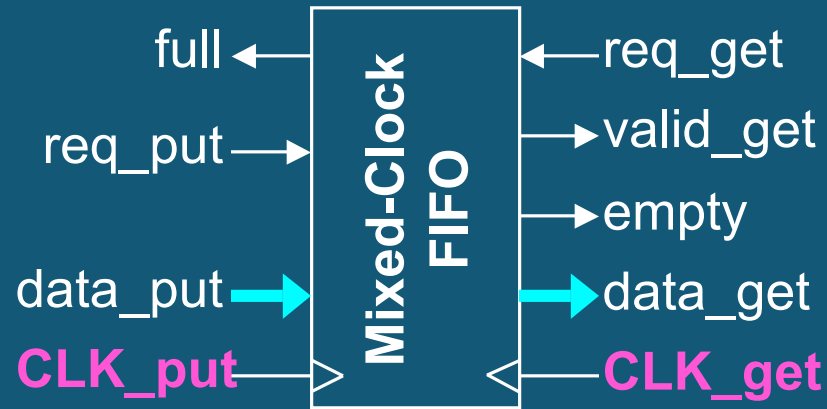

synchronous
get interface

Mixed-Clock FIFO: Block Level

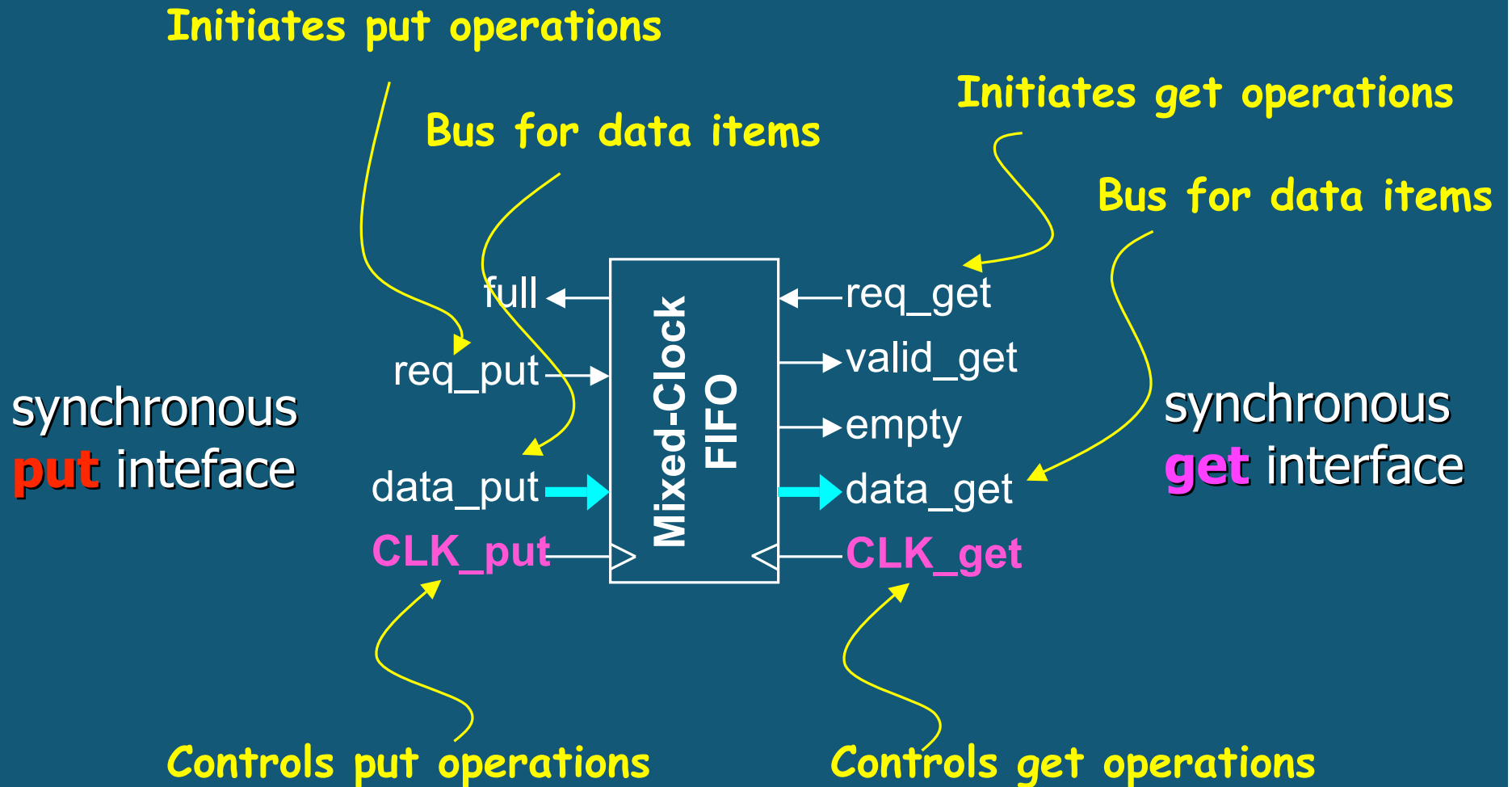


Mixed-Clock FIFO: Block Level

Indicates when FIFO full

Indicates data items validity
(always 1 in this design)


synchronous
put interface

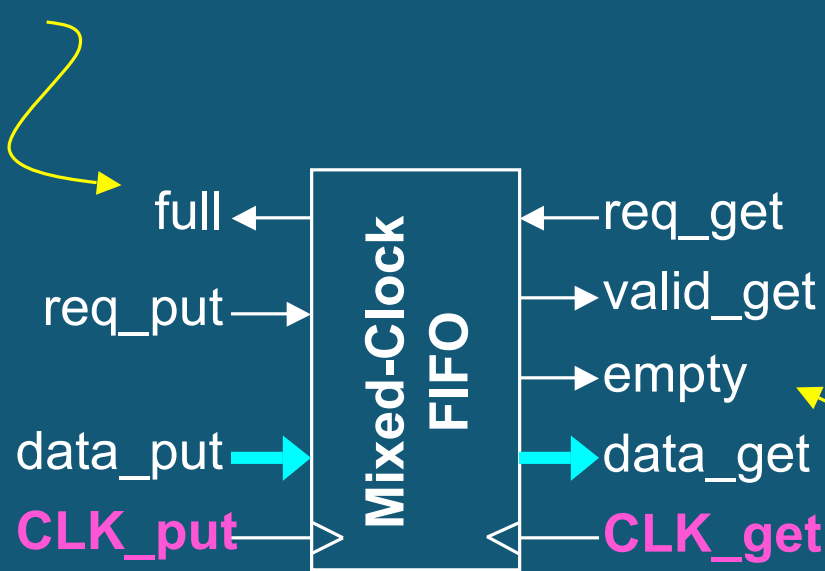

synchronous
get interface


Indicates when FIFO empty

Mixed-Clock FIFO: Architecture

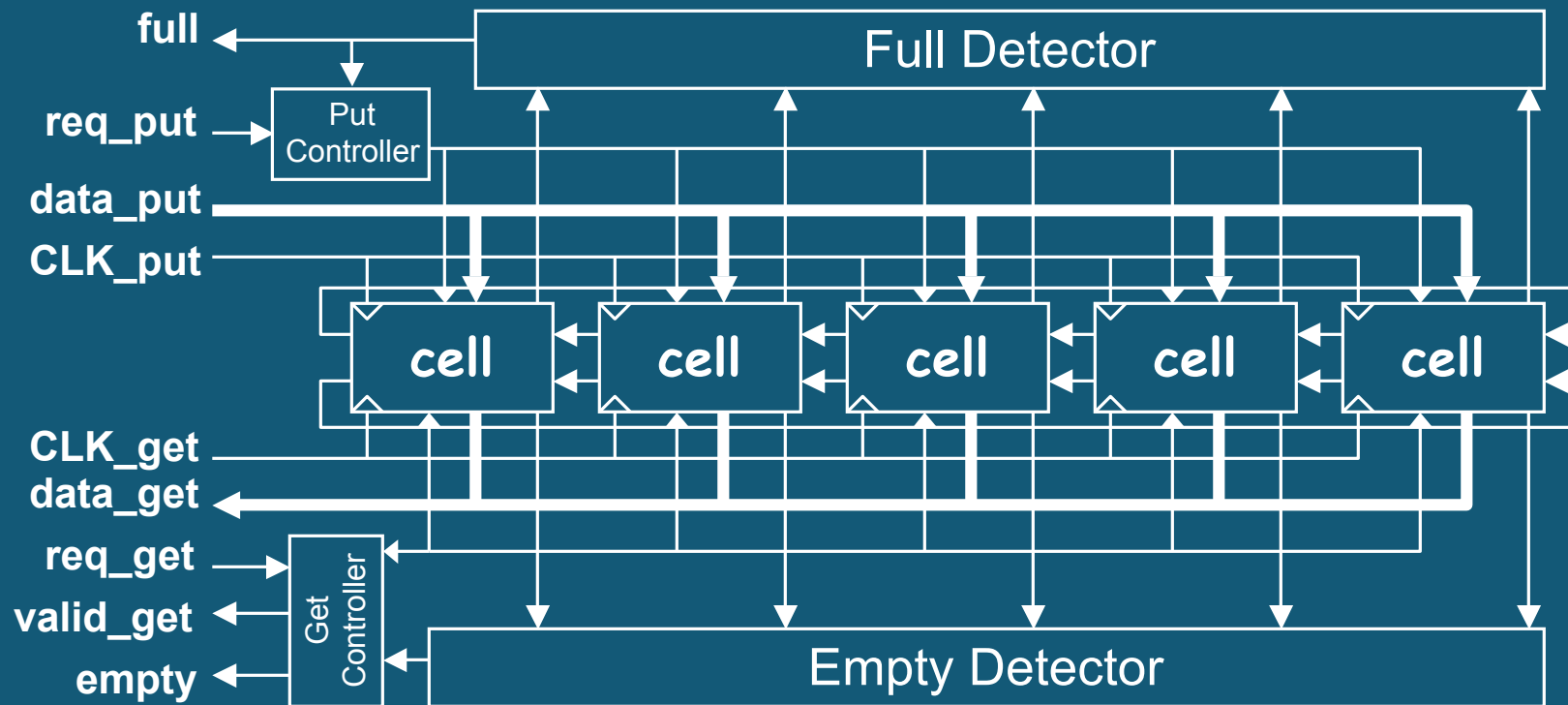

Mixed-Clock FIFO: Architecture

Array of identical cells

 


Token Ring Architecture

Mixed-Clock FIFO: Architecture

Put Interface

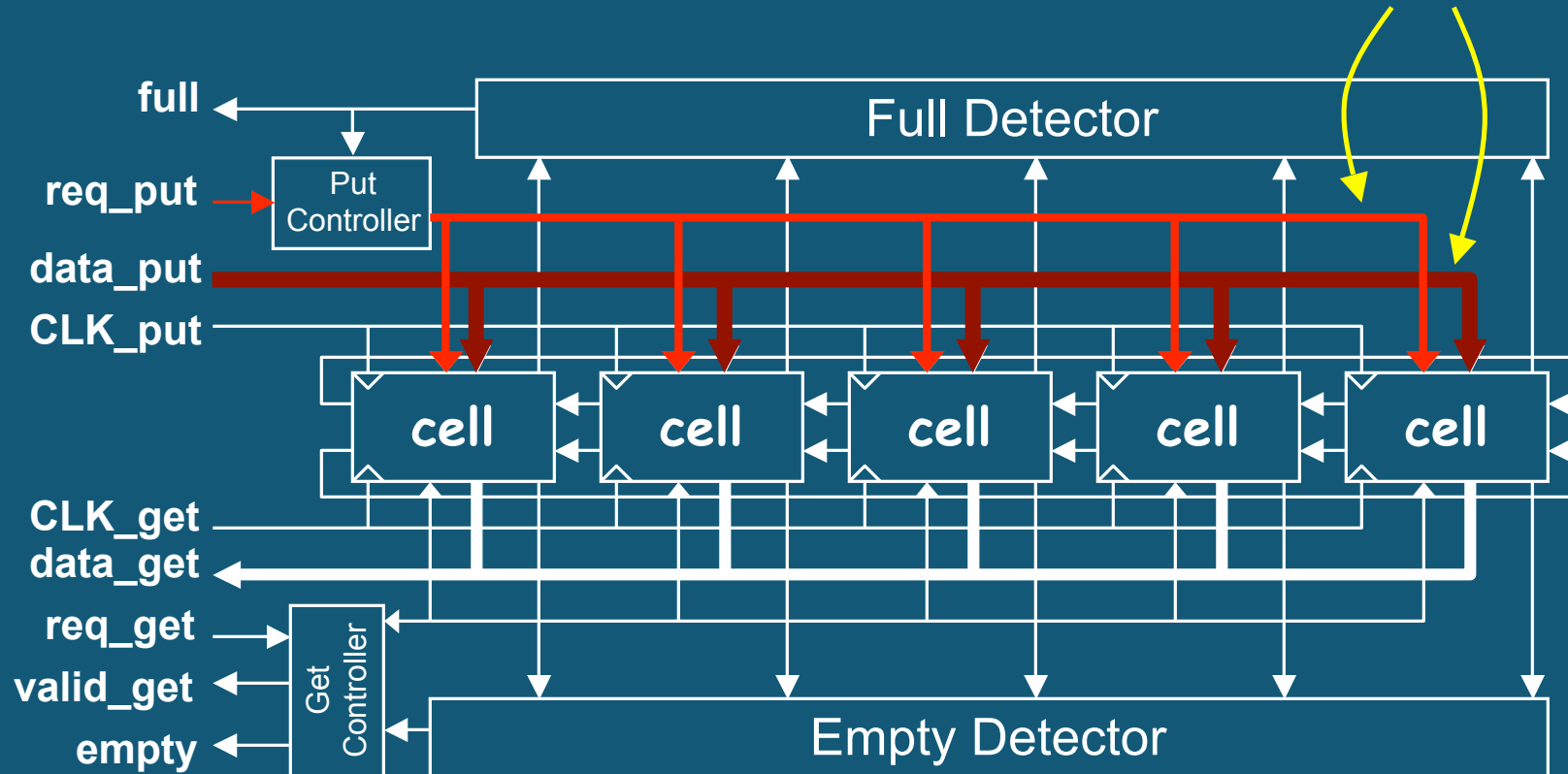
Common Data/Control Buses
for put interface



Mixed-Clock FIFO: Architecture

Put Token Ring

 Put Token: used to enqueue data items
Cell with put token = tail of queue




Mixed-Clock FIFO: Architecture

Put Controller:


- enables & disables put operations
- stalls put interface when FIFO full

Full Detector:

detects when FIFO full

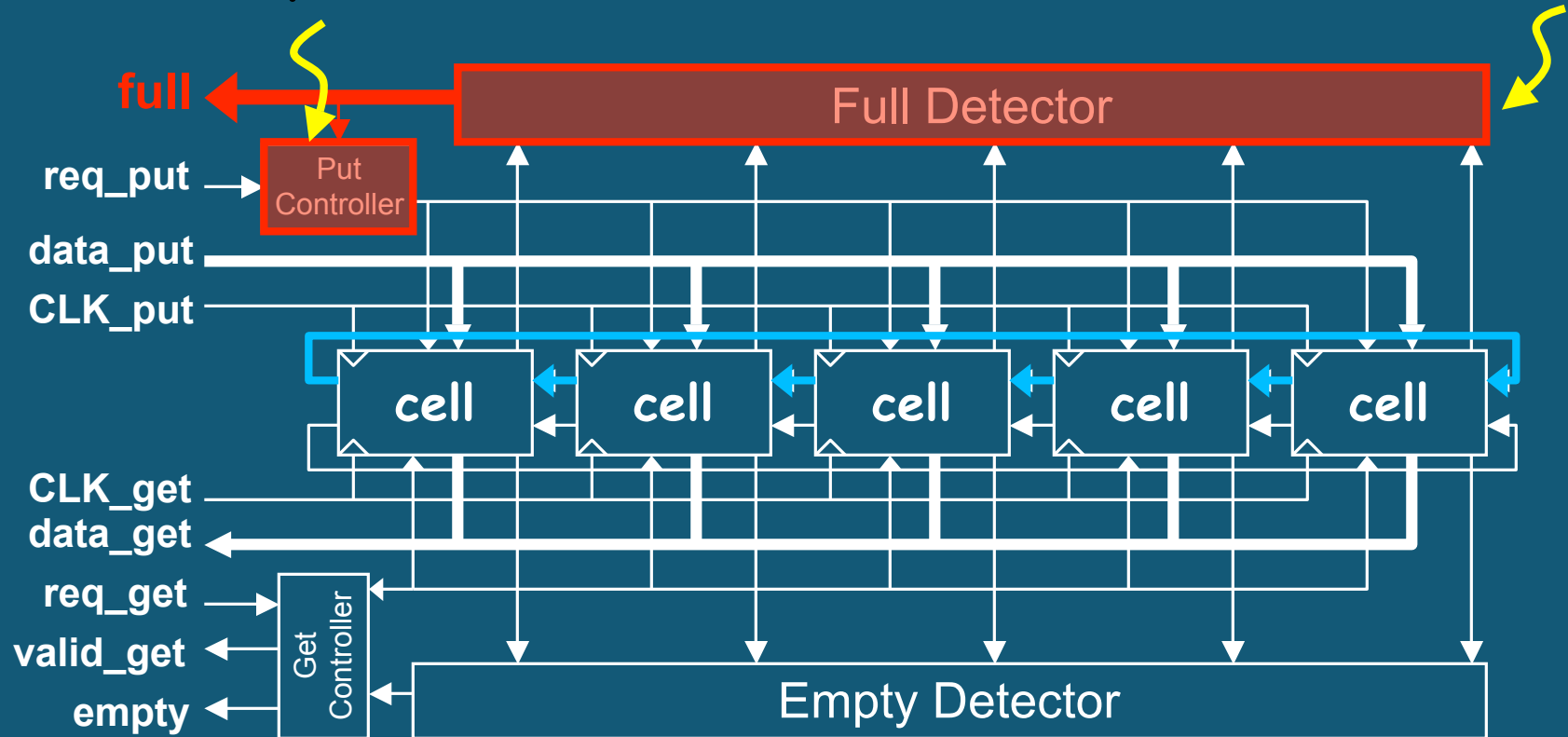

Mixed-Clock FIFO: Architecture

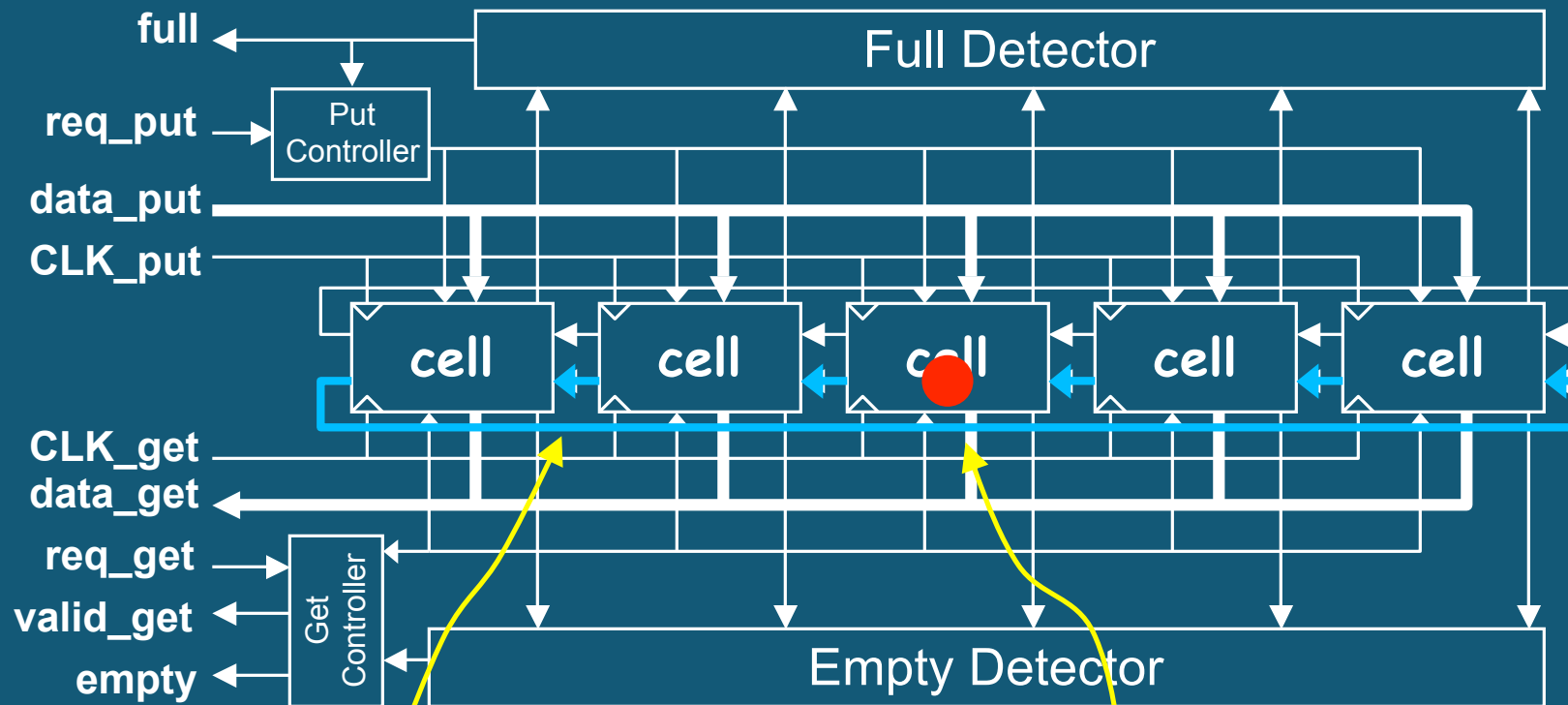


Get Token Ring


Get Token: used to dequeue data items
Cell with get token = head of queue

Get Interface


Mixed-Clock FIFO: Cell Implementation

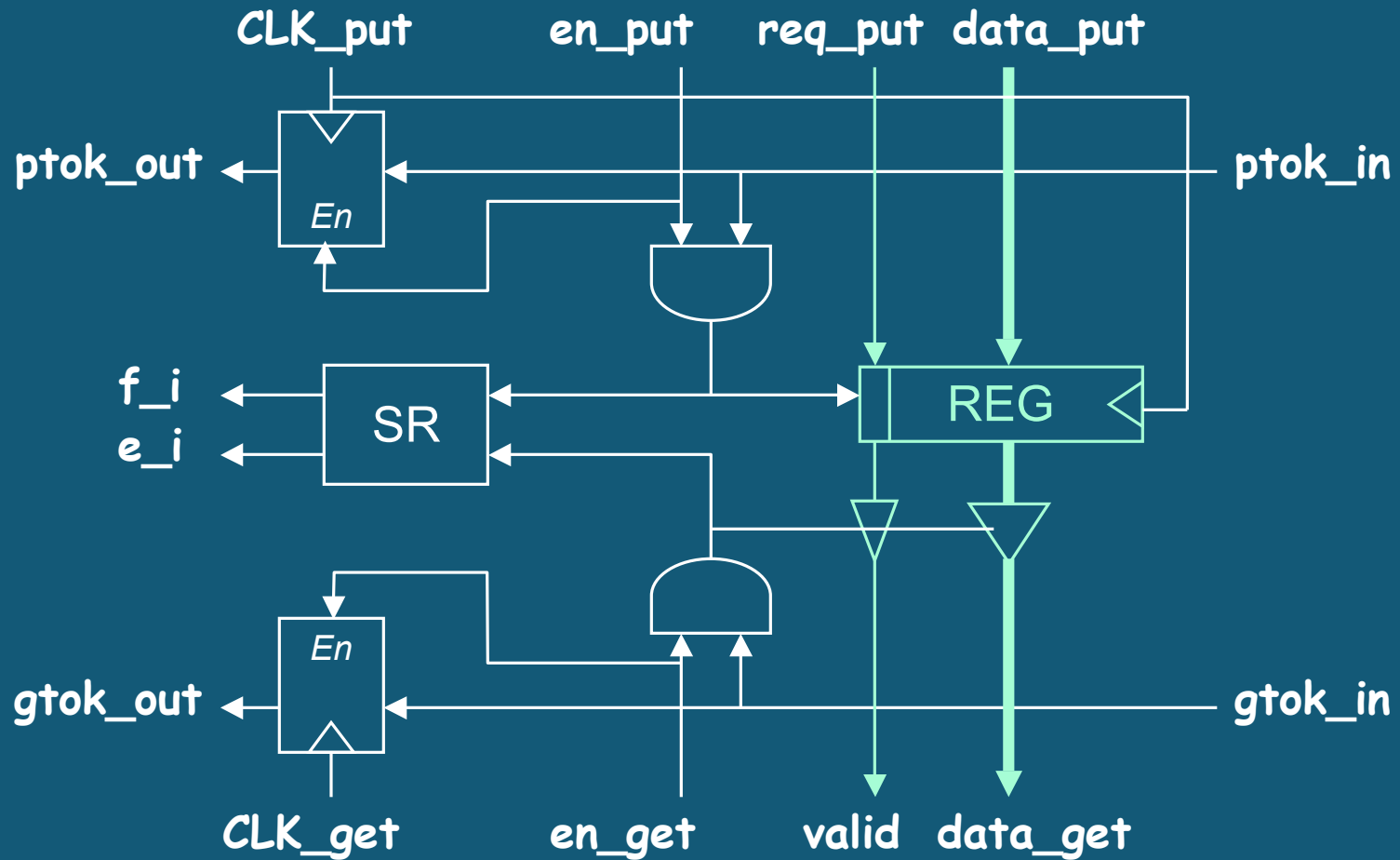


Mixed-Clock FIFO: Cell Implementation

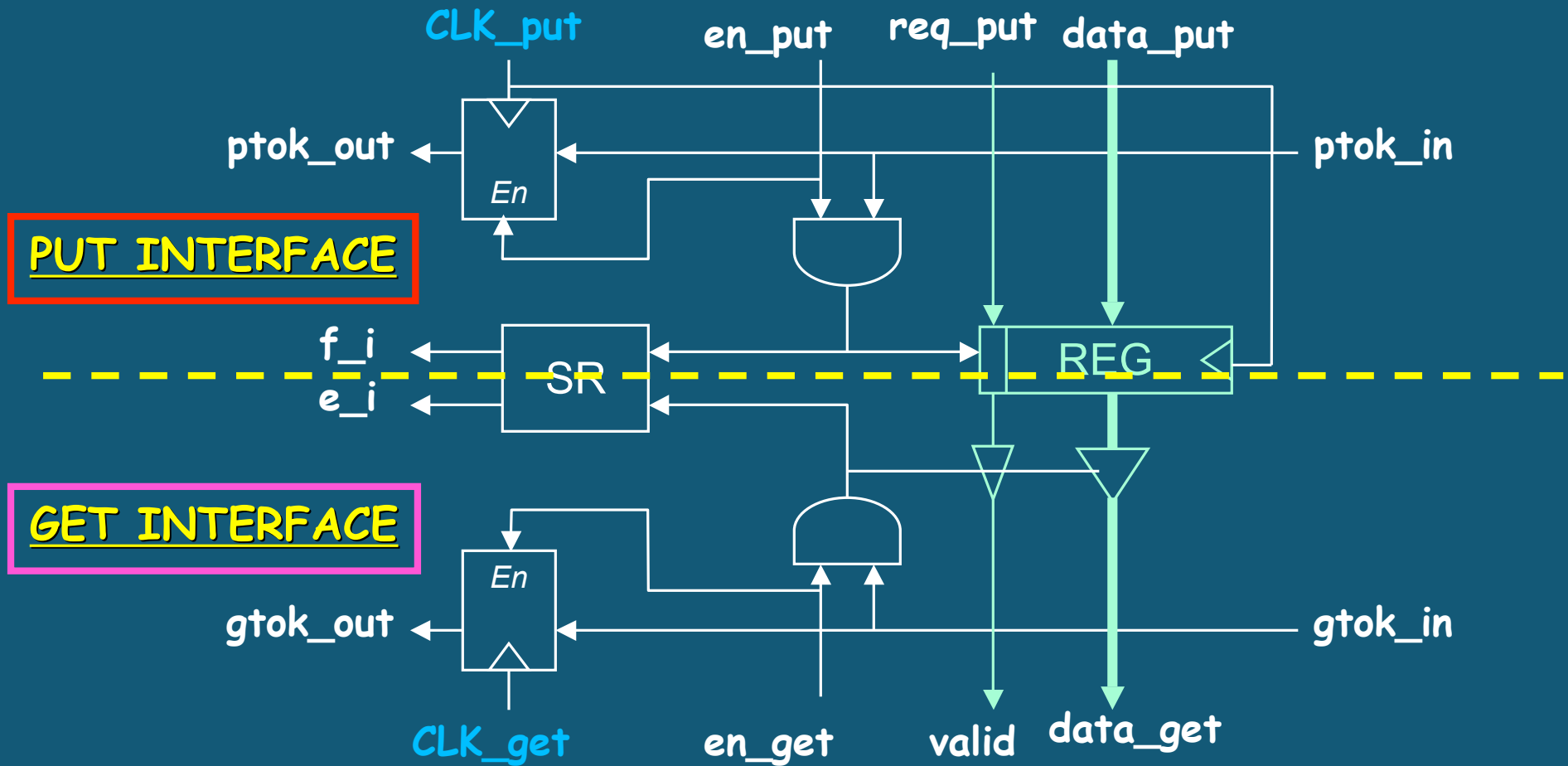


Mixed-Clock FIFO: Cell Implementation

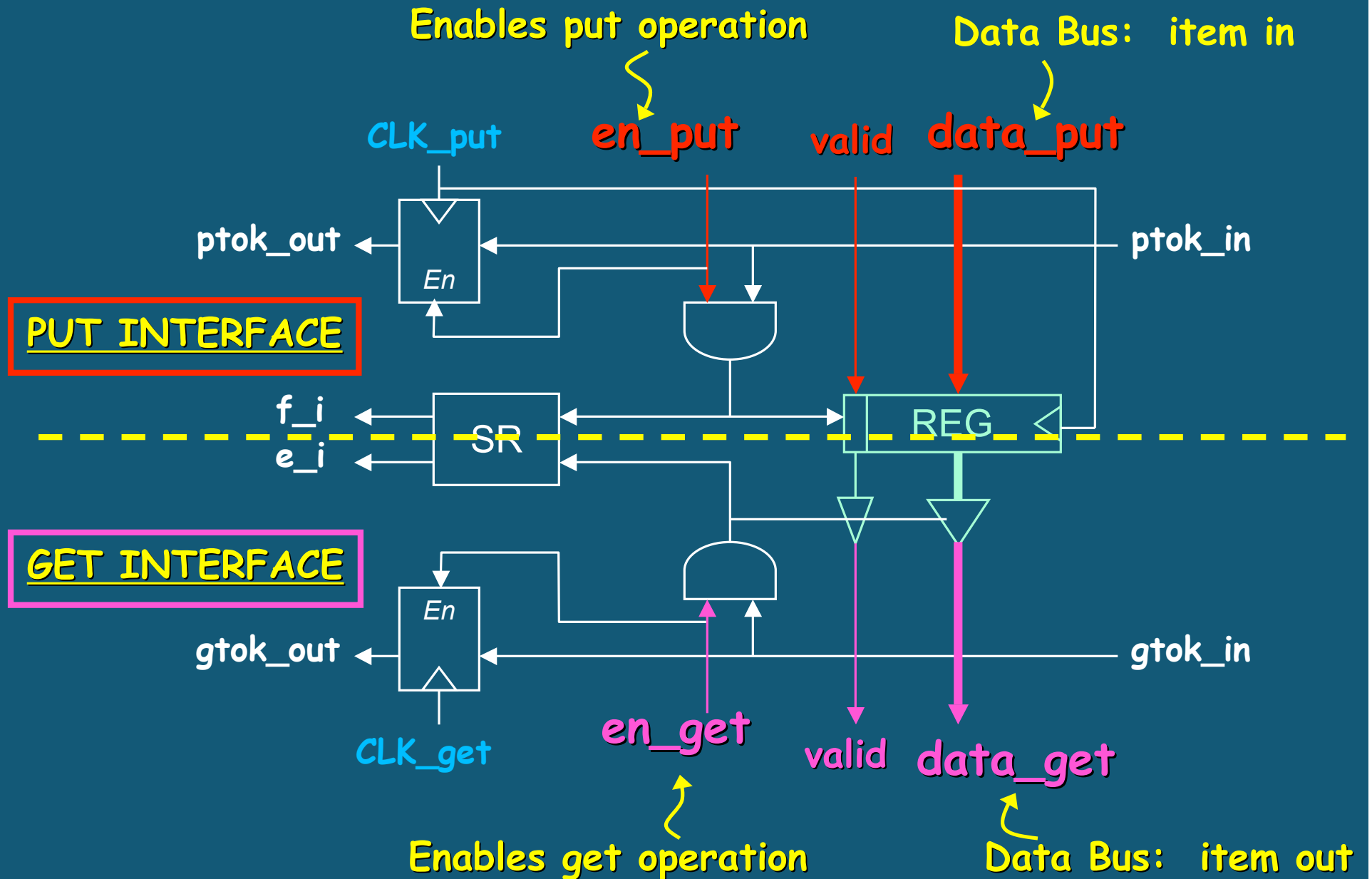

Mixed-Clock FIFO: Cell Implementation

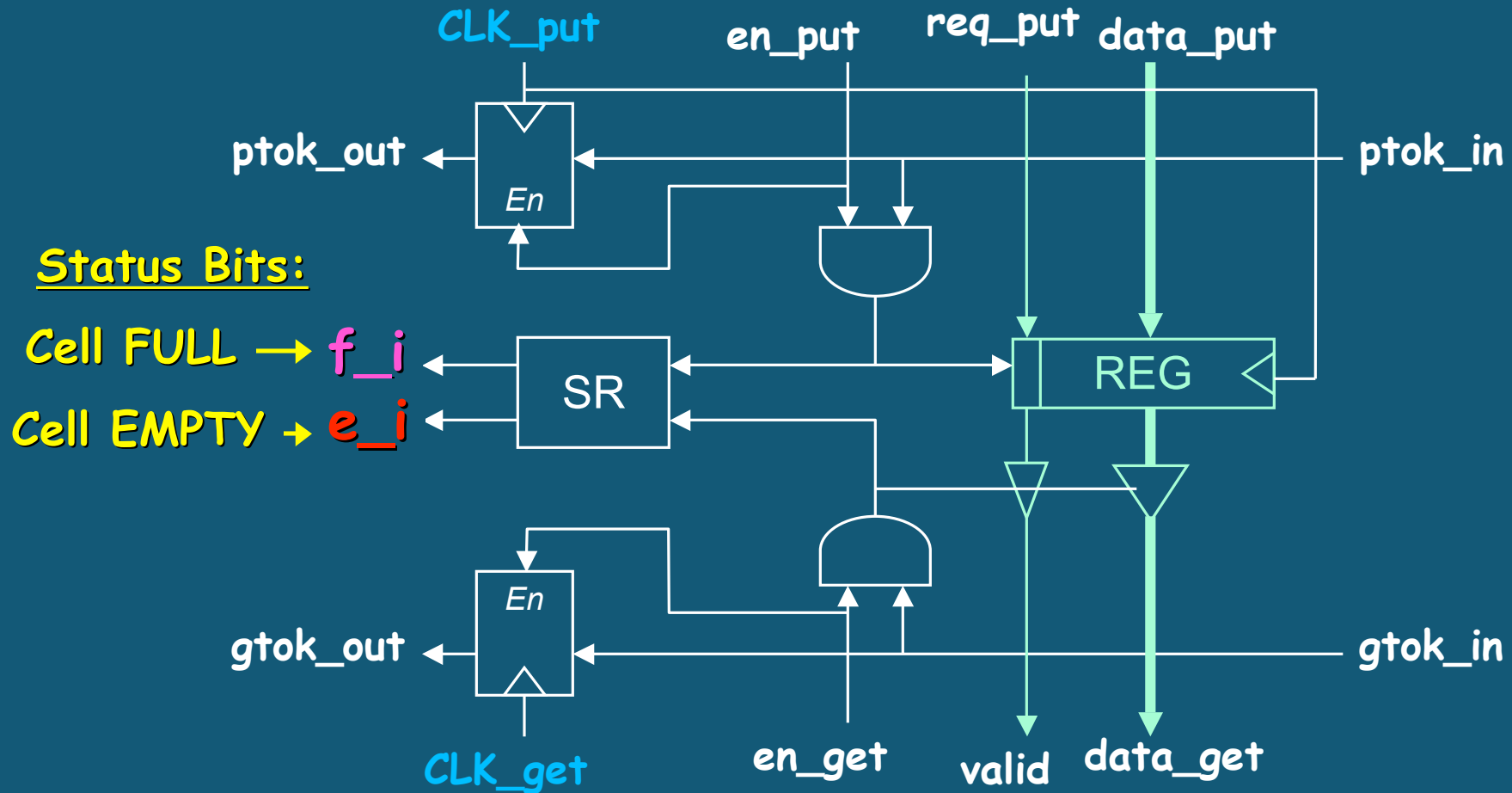


Mixed-Clock FIFO: Cell Implementation

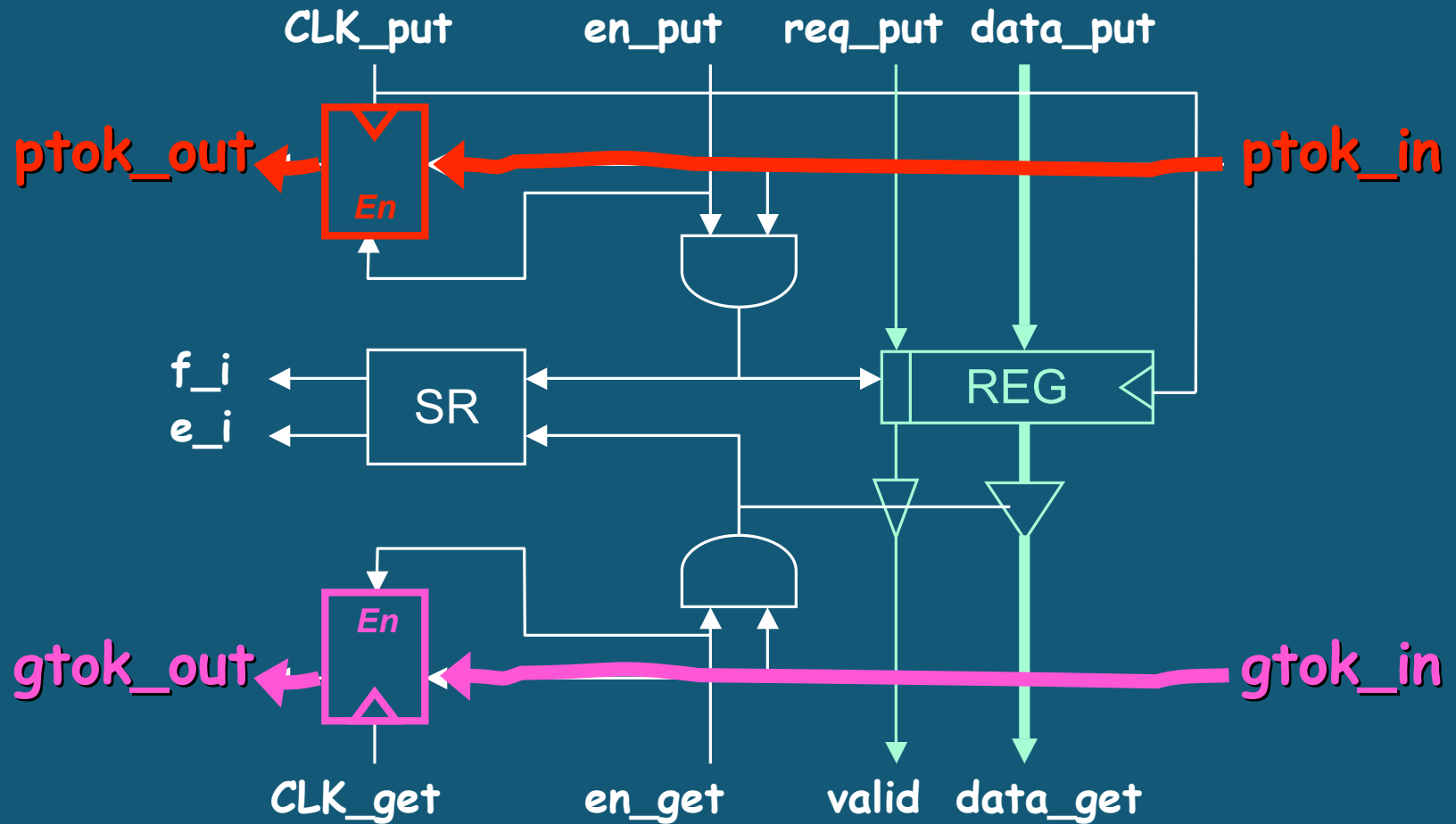

Token Passing:


Mixed-Clock FIFO Cell: Put Operation

Simulation #1: Put Operation

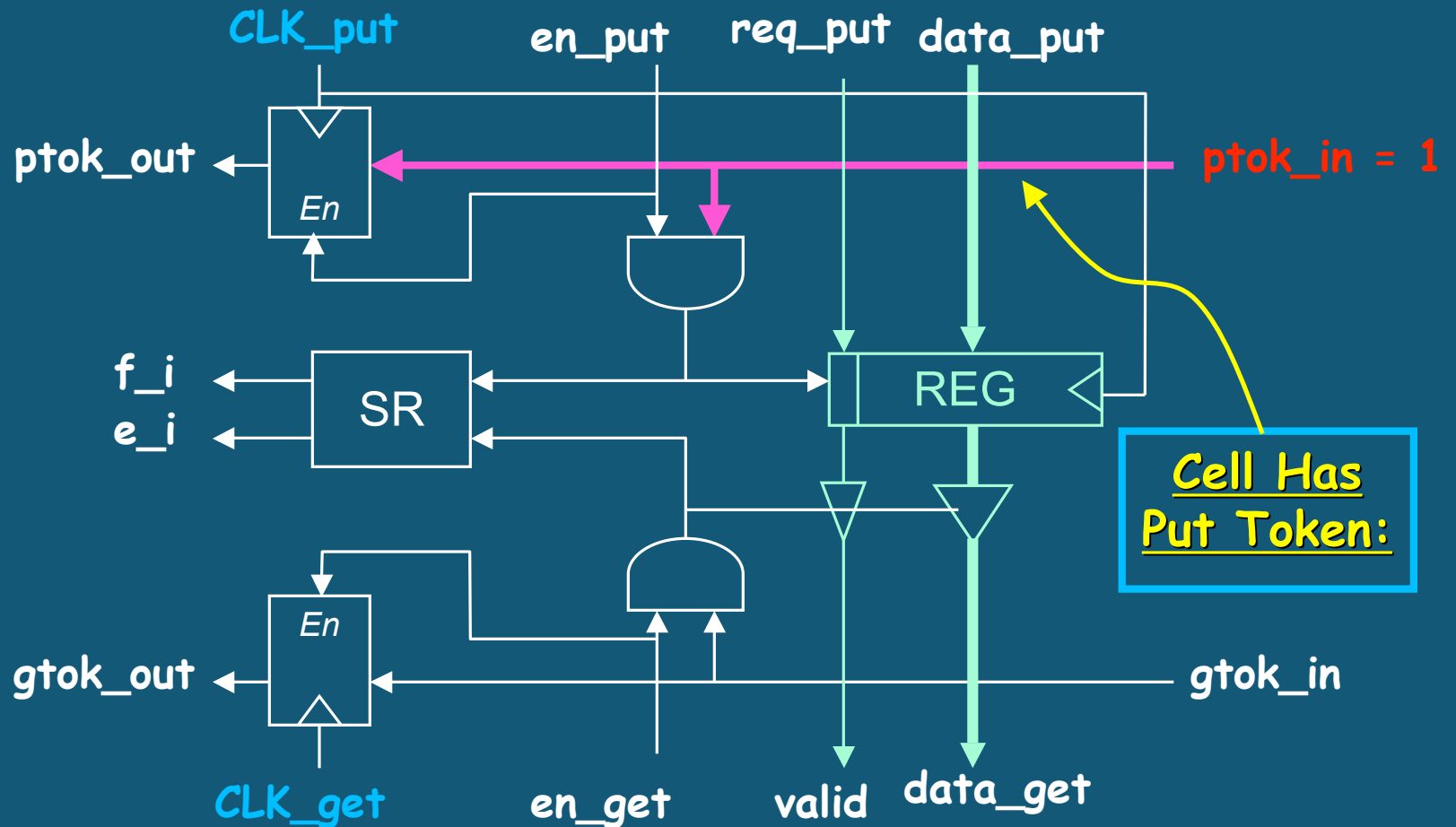


Mixed-Clock FIFO Cell: Put Operation


Put Request Arrives:

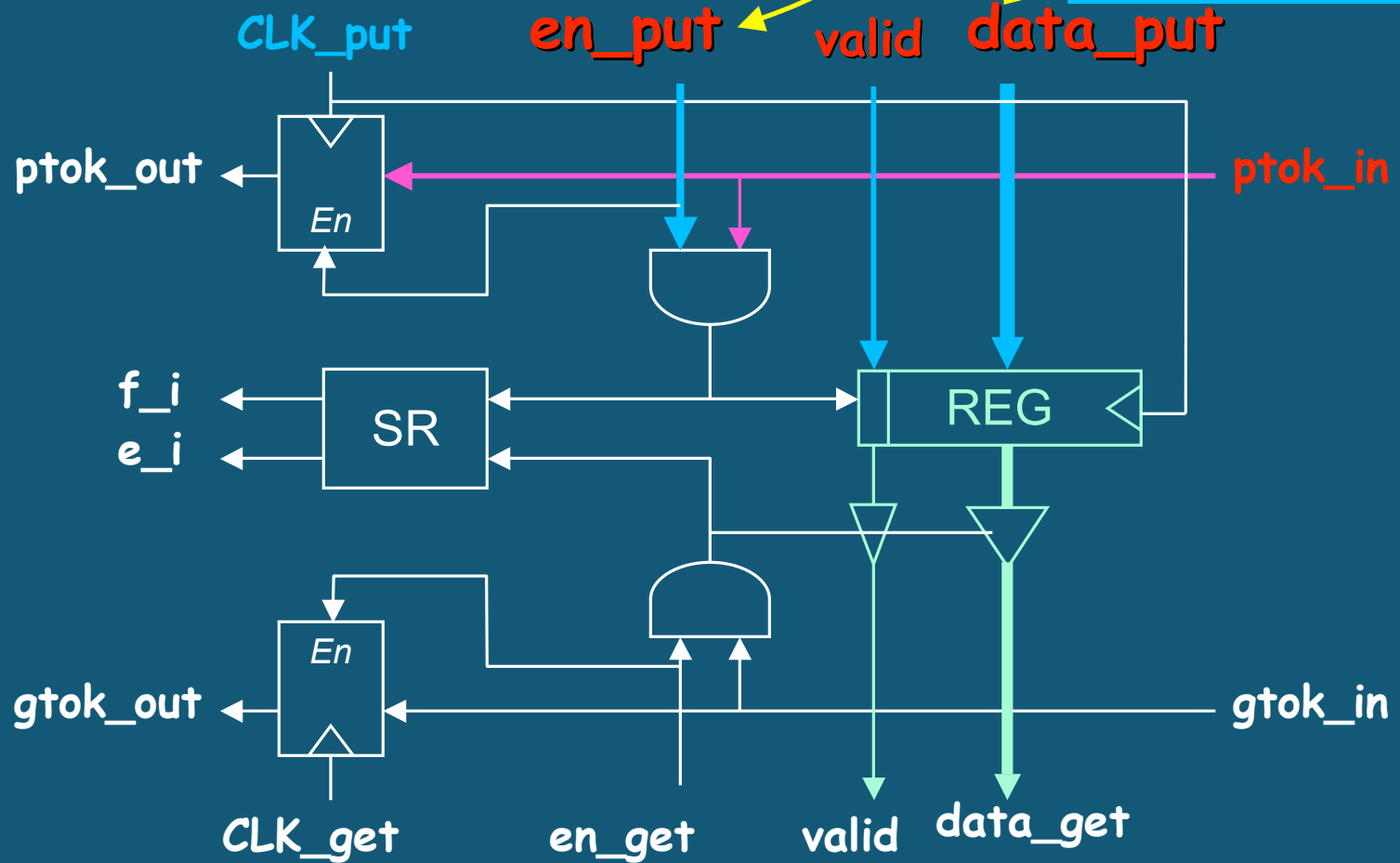

Mixed-Clock FIFO Cell: Put Operation

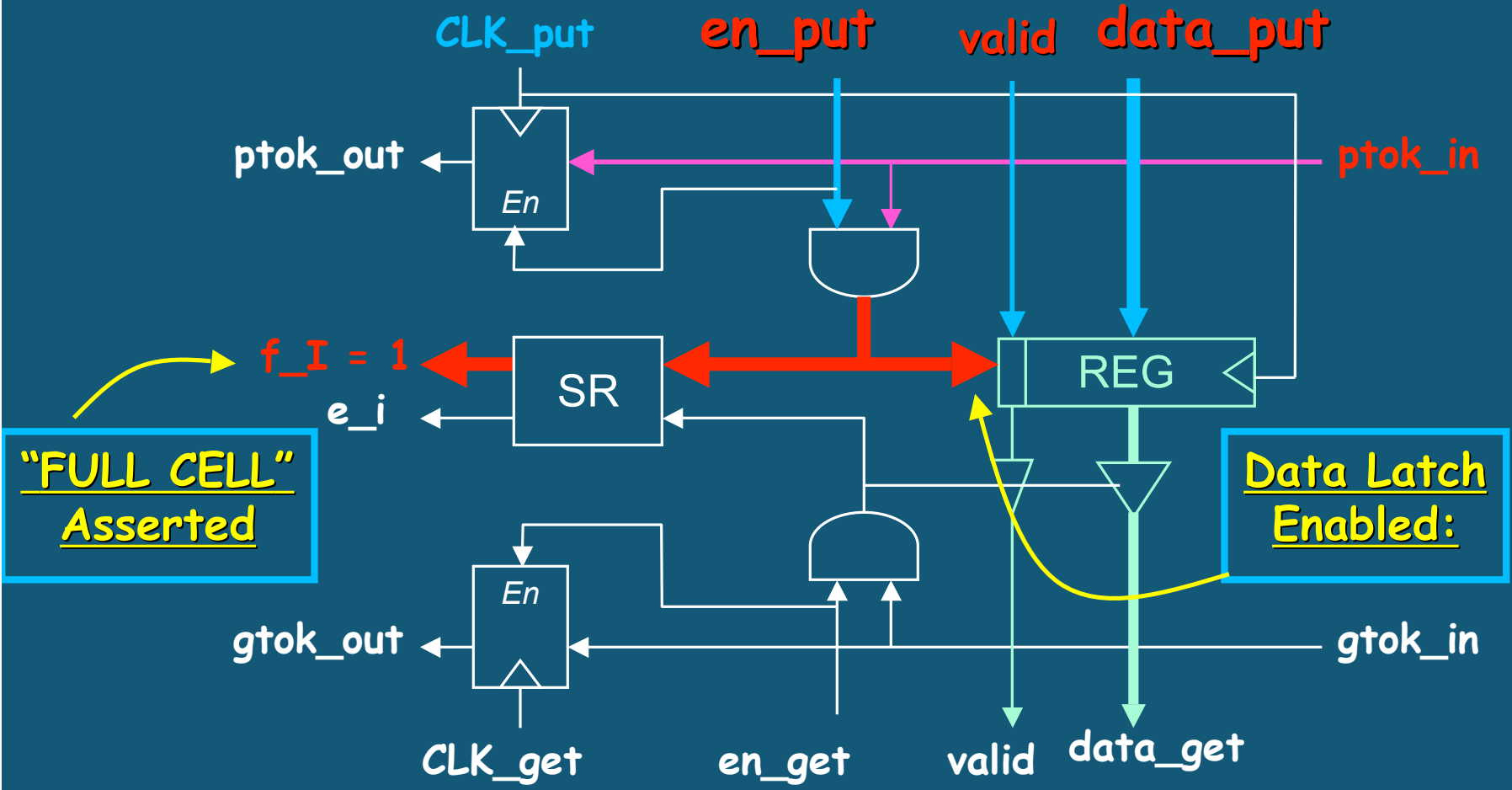


Mixed-Clock FIFO Cell: Put Operation

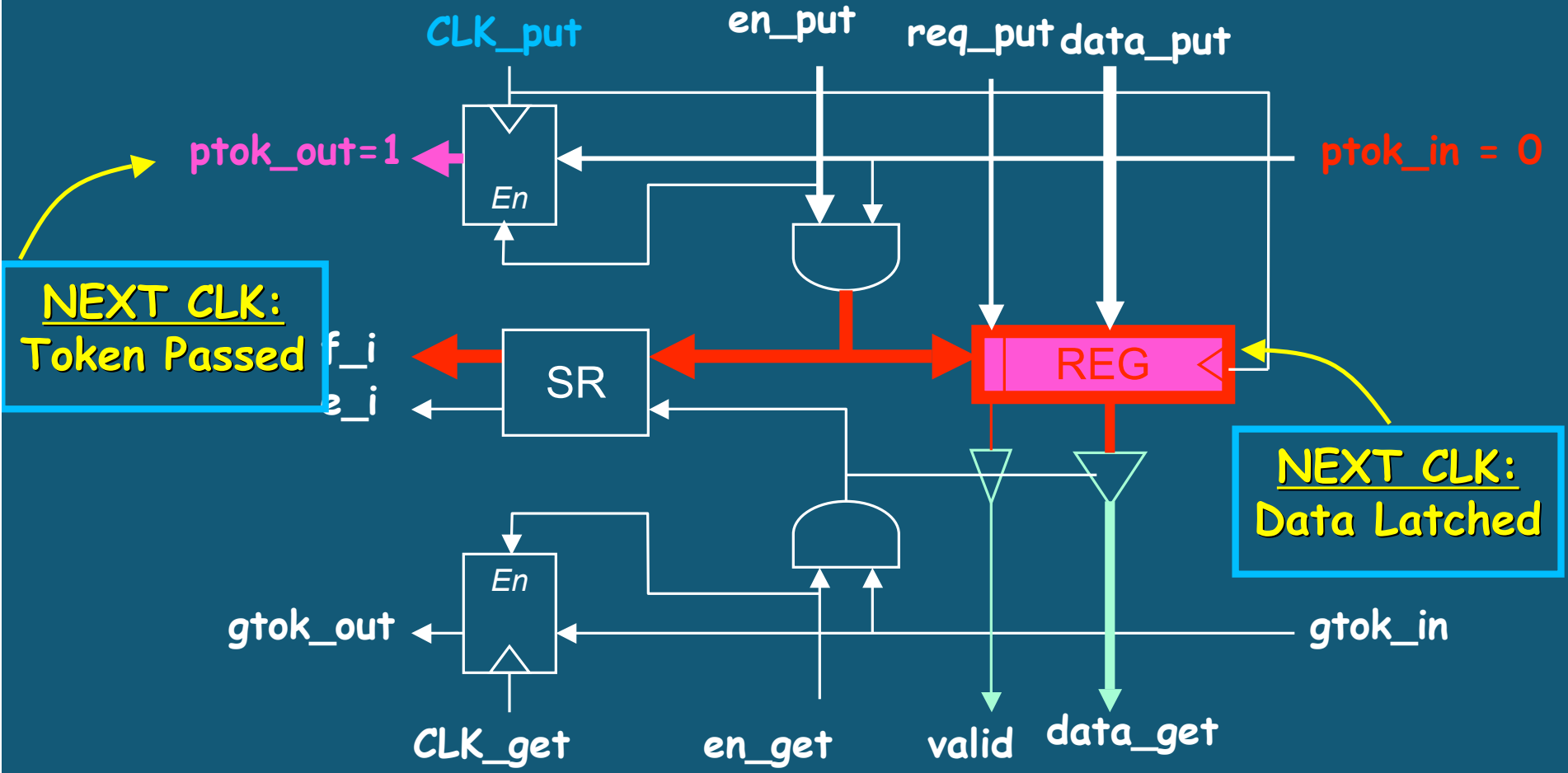


Mixed-Clock FIFO Cell: Get Operation


Simulation #2: Get Operation

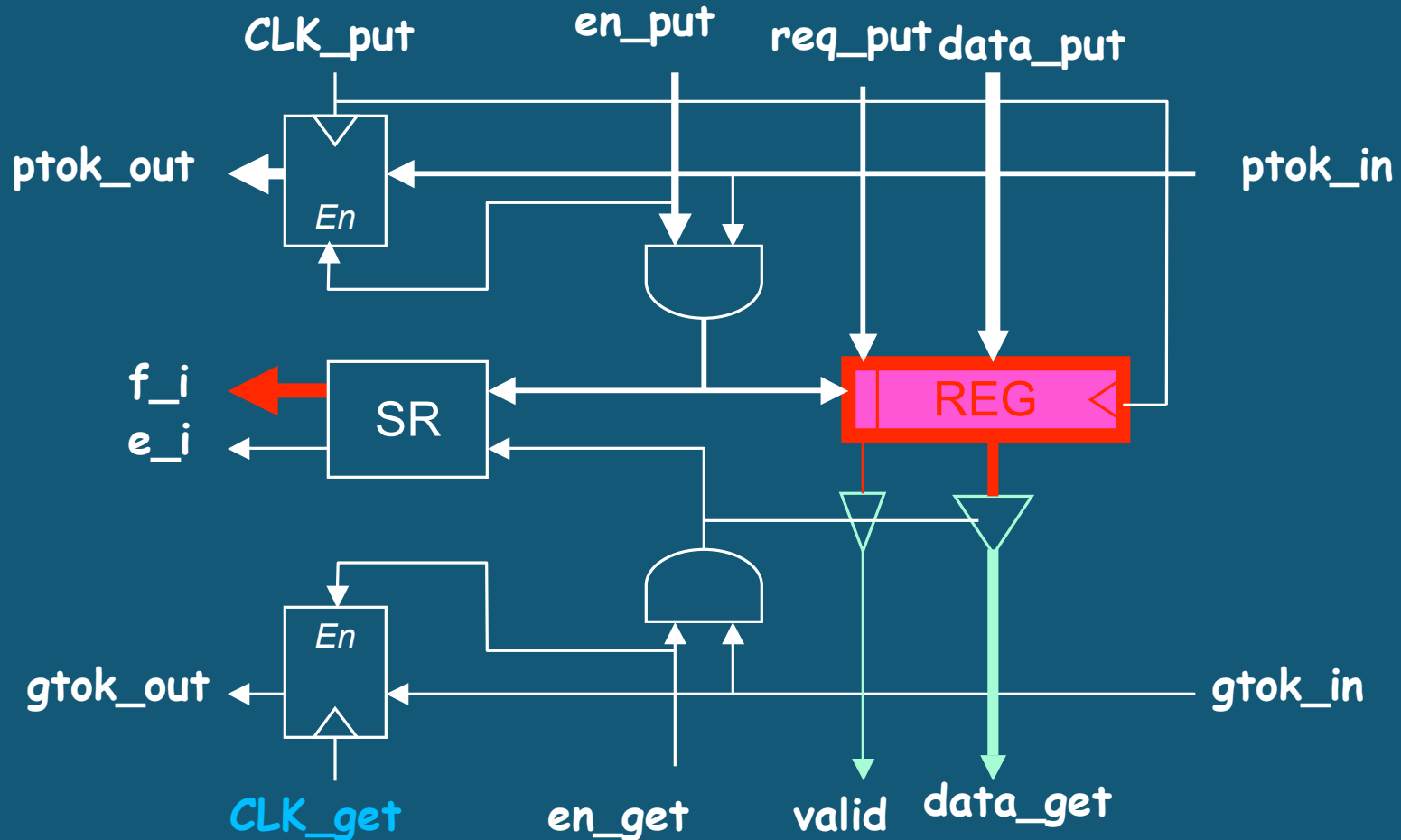

Mixed-Clock FIFO Cell: Get Operation

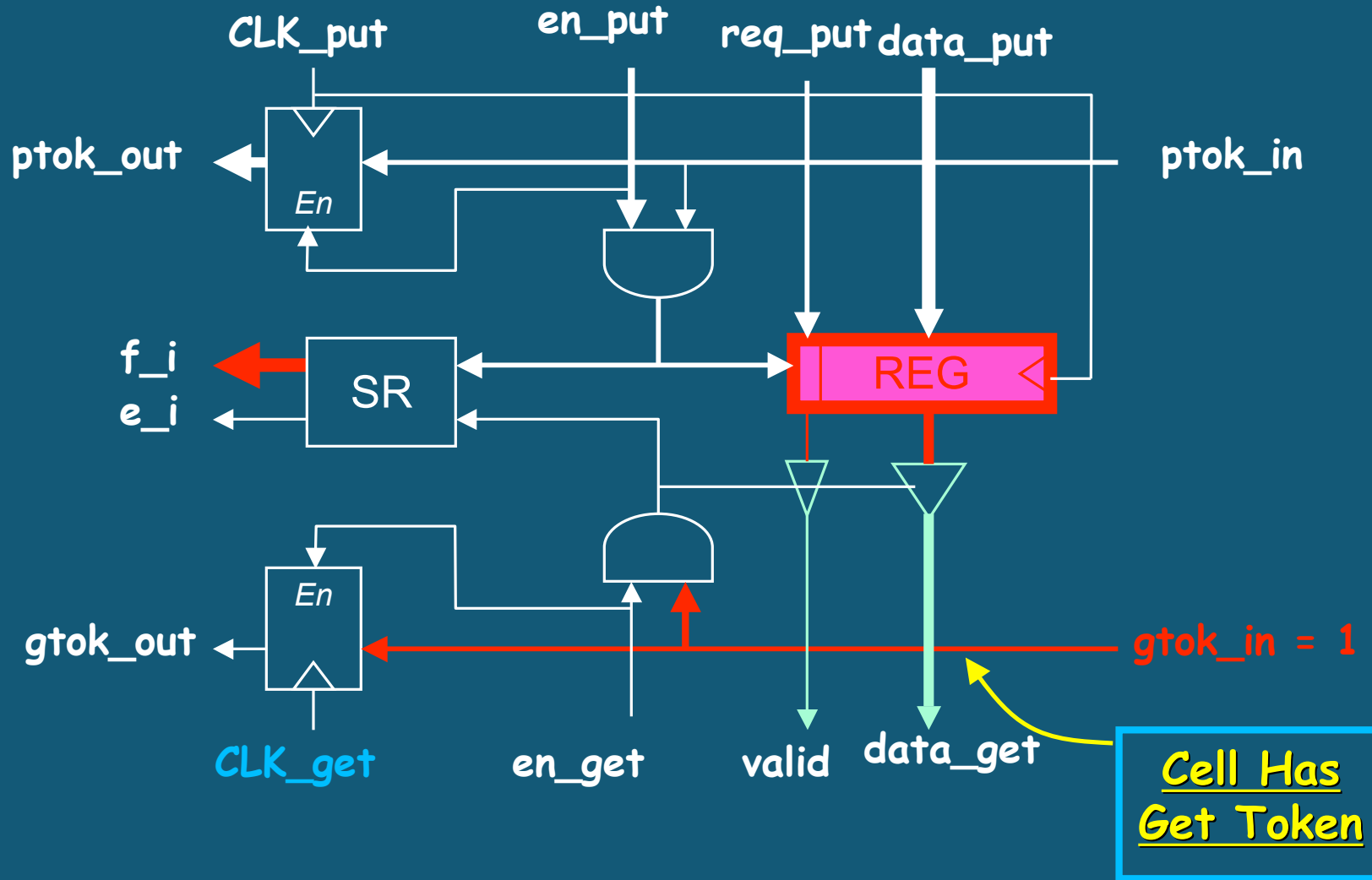


Mixed-Clock FIFO Cell: Get Operation

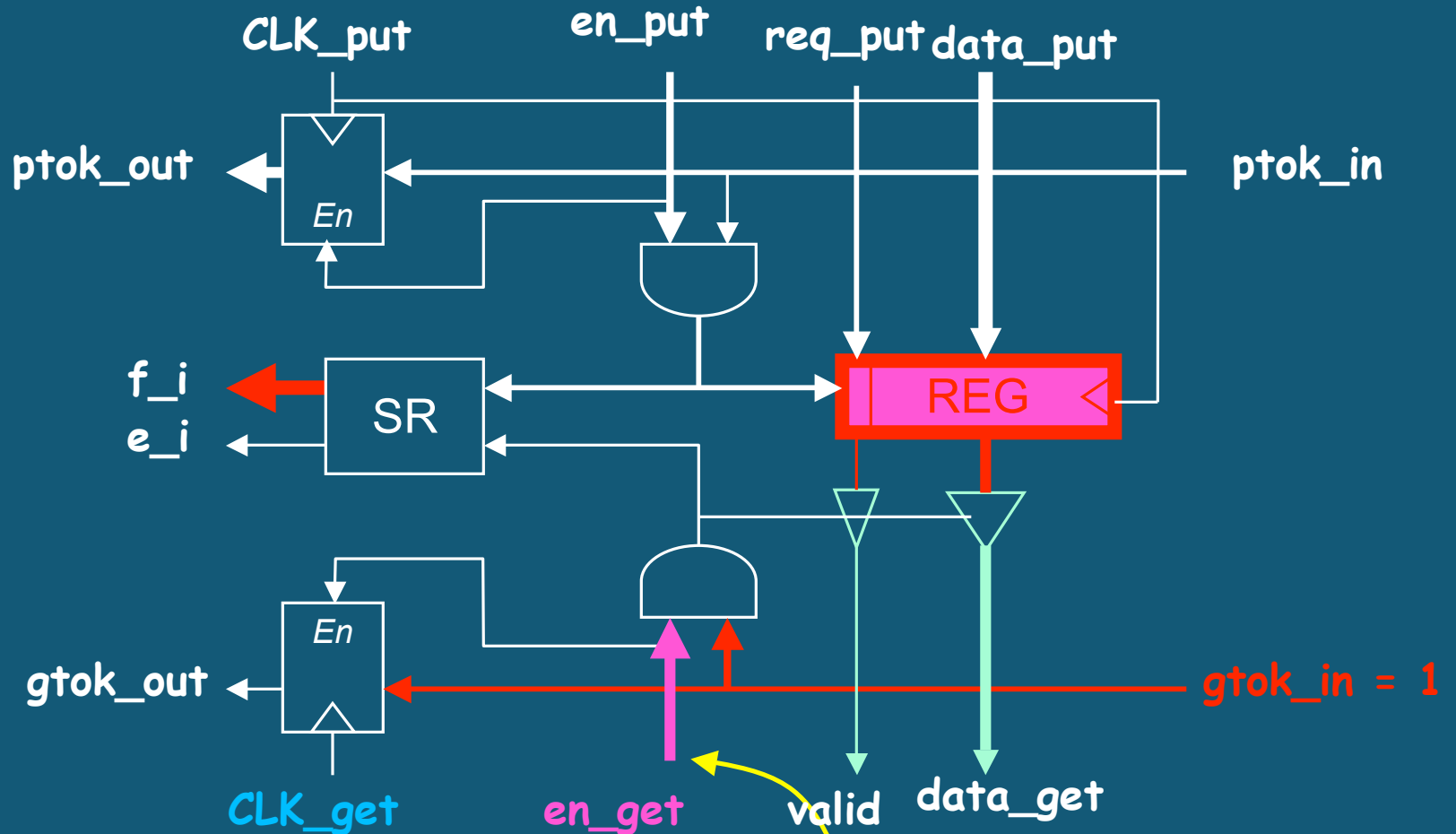


Get Request Arrives

Mixed-Clock FIFO Cell: Get Operation

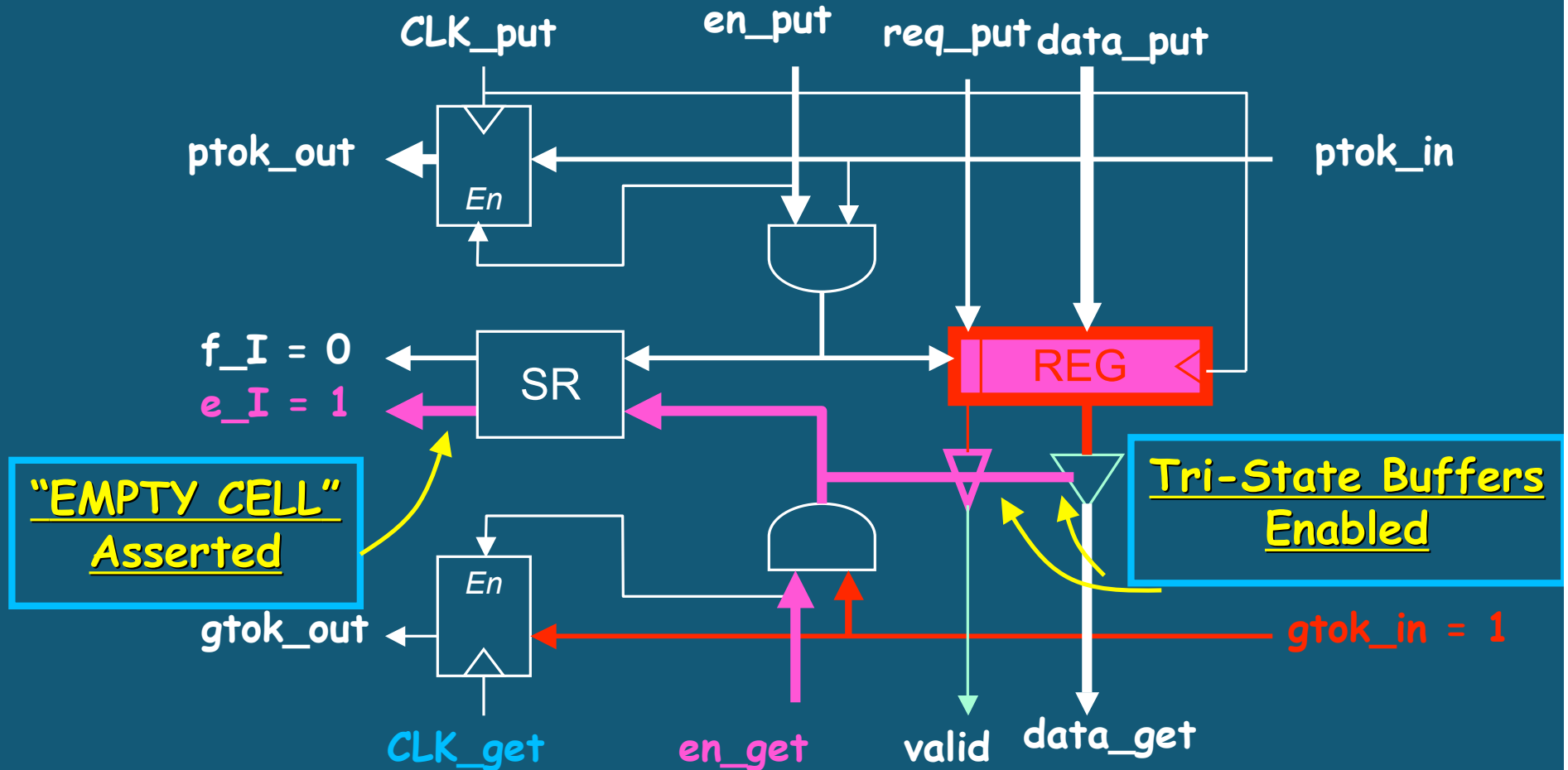


Mixed-Clock FIFO Cell: Get Operation

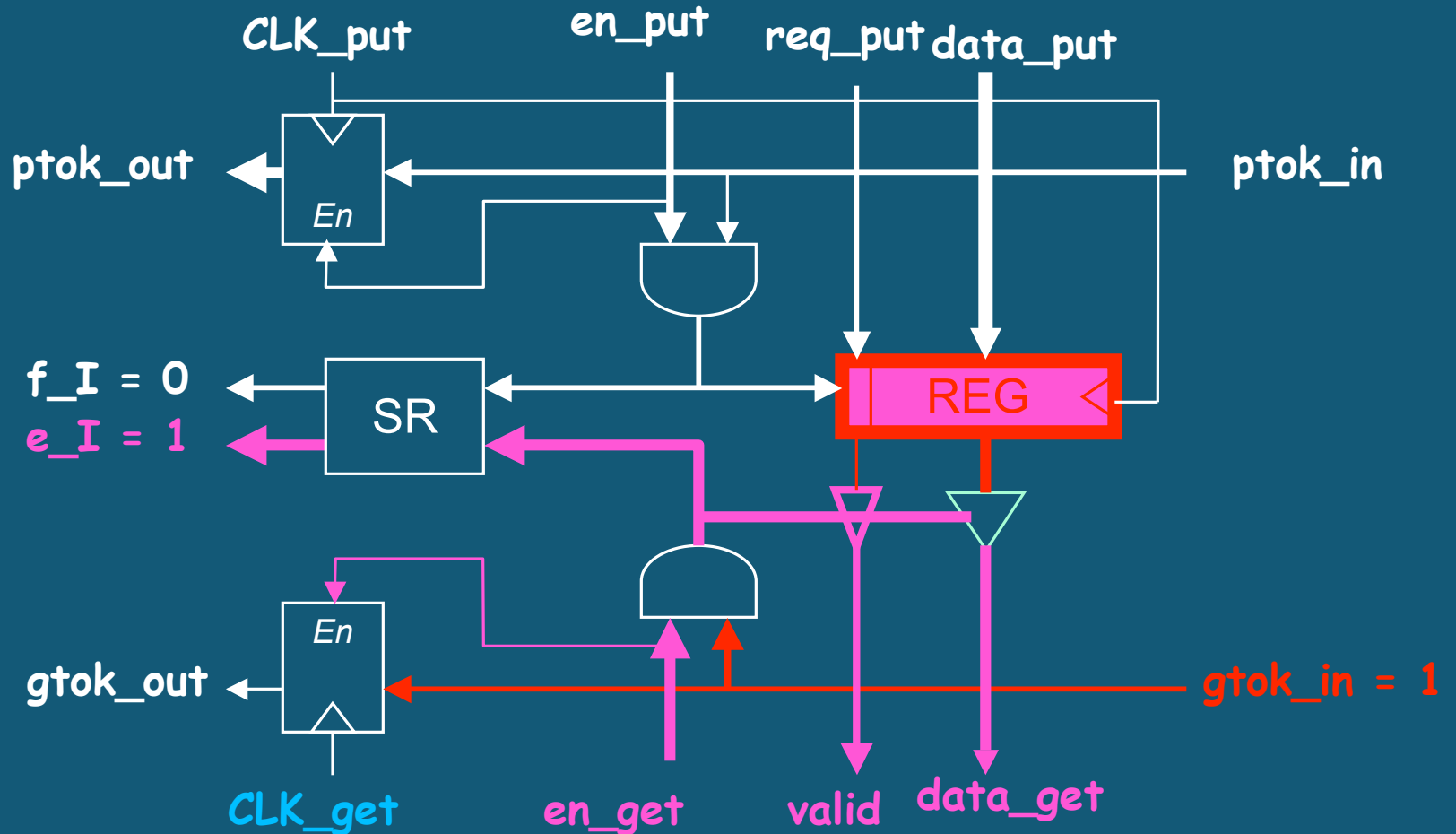

Data Broadcast on Get Bus

Mixed-Clock FIFO Cell: Get Operation

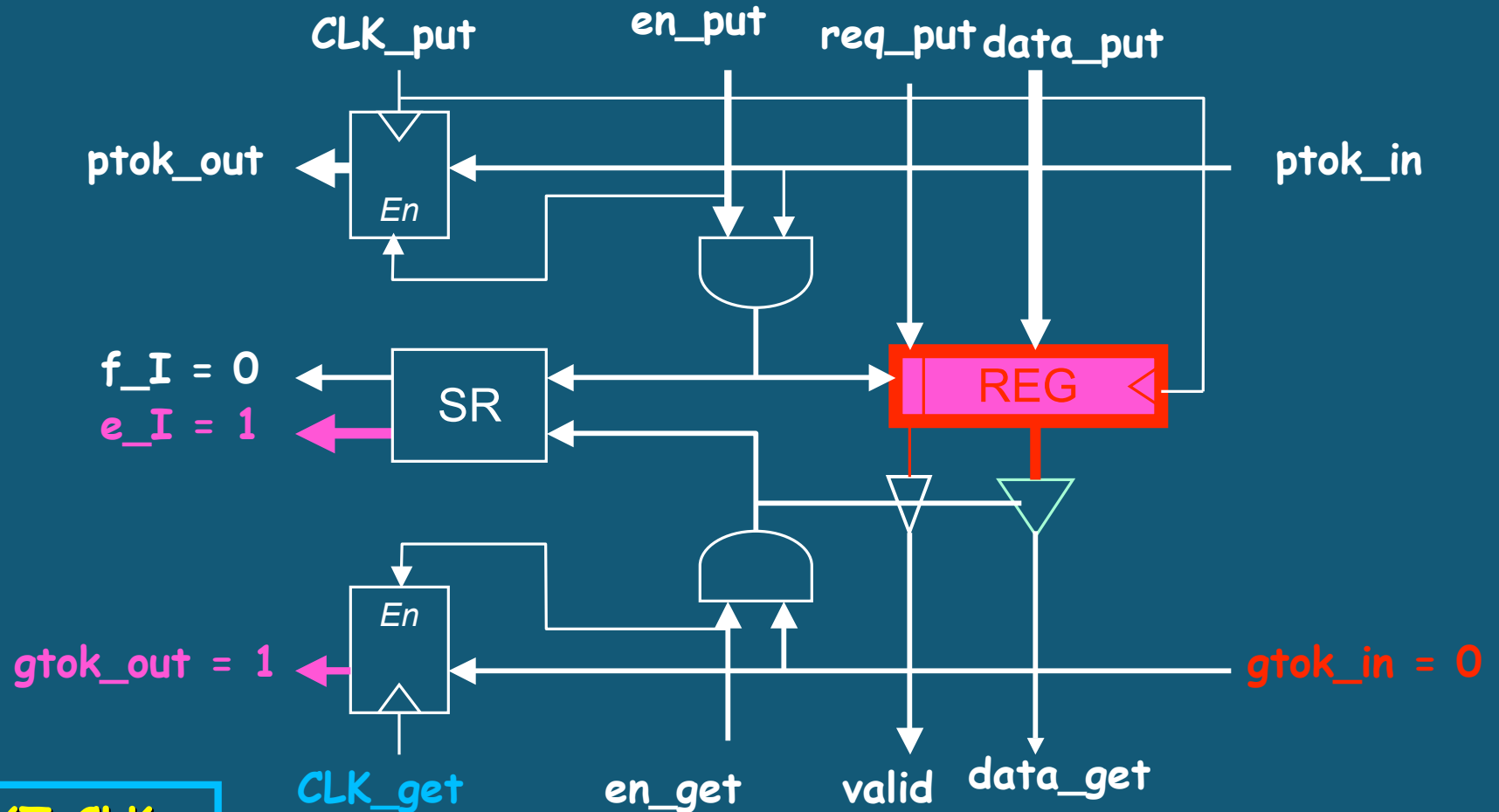

NEXT CLK:
Token Passed

Synchronization Issues: Overview

Challenge: highly concurrent behavior

- * Global FIFO state controlled by two different clocks

Problem #1: Metastability

- * Each FIFO interface needs *clean state signals*

Solution #1: Synchronize "full" & "empty" signals

- * "full" with **CLK_put**
- * "empty" with **CLK_get**

Add 2 synchronizing latches each

Mixed-Clock FIFO: Full/Empty Detectors

Problem #2: FIFO now may underflow/overflow!


* synchronizing latches add extra latency

Solution #2: Change Full/Empty definitions

New FULL: *0 or 1 empty cells left*

New EMPTY: *0 or 1 full cells left*

Synchronizing Latches

 

New Full Detector

Observable full/empty *safely approximate* FIFO's state

Mixed-Clock FIFO: Full/Empty Detectors


Problem #2: FIFO now may underflow/overflow!

* synchronizing latches add extra latency

Solution #2: Change Full/Empty definitions

New FULL: *0 or 1 empty cells left*

New EMPTY: *0 or 1 full cells left*

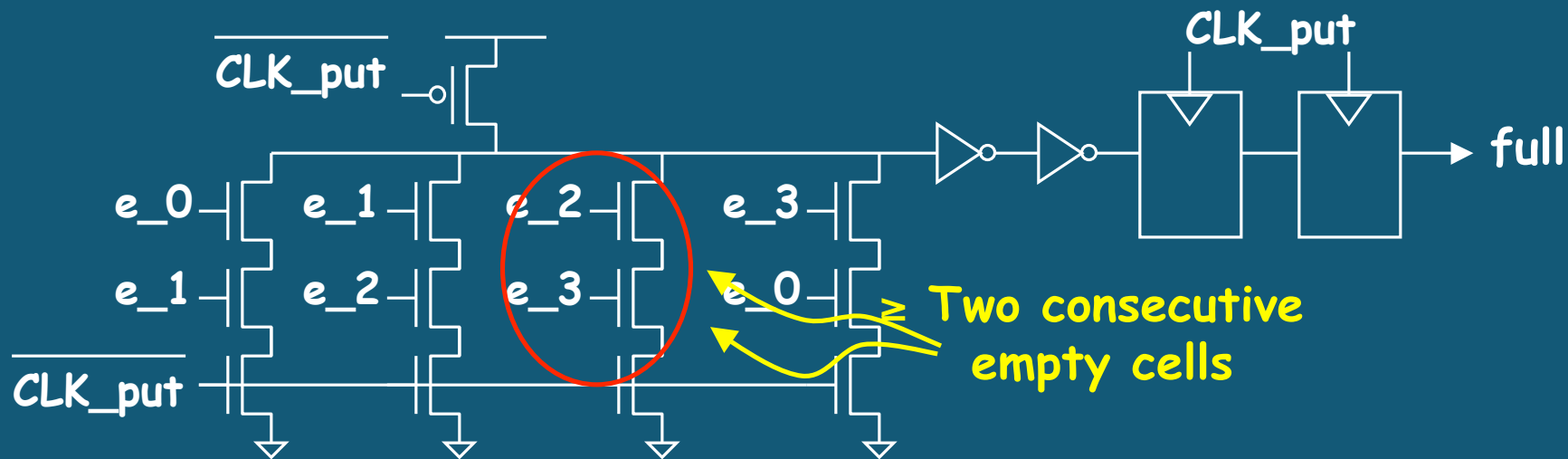

New Full Detector

Observable full/empty *safely approximate* FIFO's state

Mixed-Clock FIFO: Full/Empty Detectors


Problem #2: FIFO now may underflow/overflow!

* synchronizing latches add extra latency

Solution #2: Change Full/Empty definitions

New FULL: *0 or 1 empty cells left*

New EMPTY: *0 or 1 full cells left*

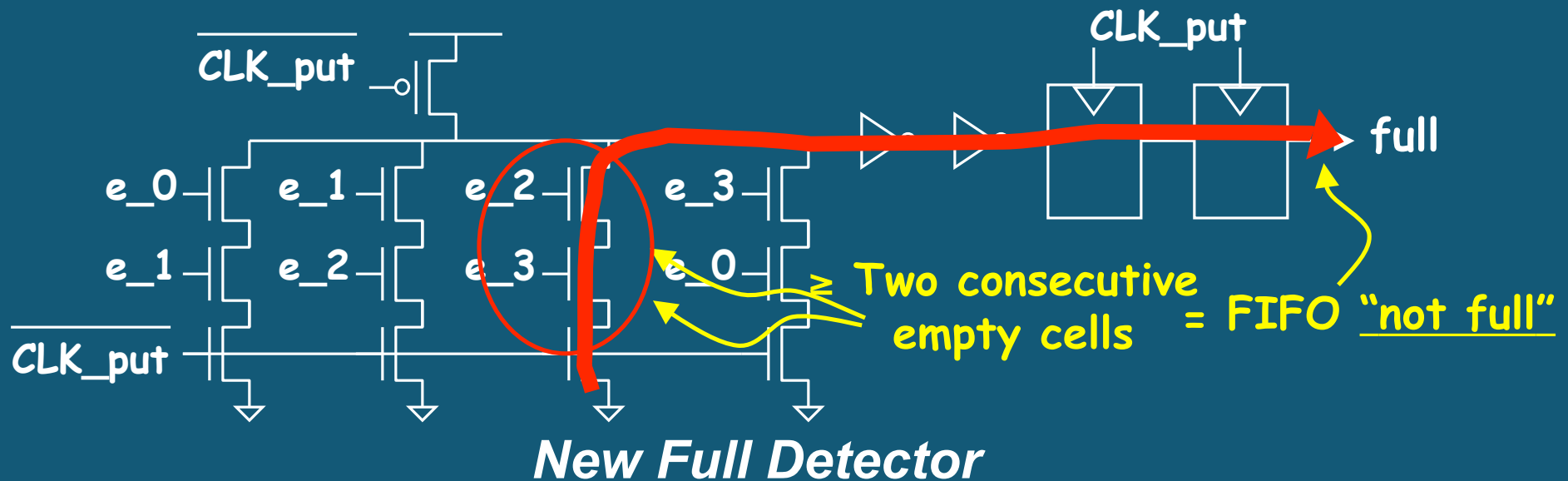

Observable full/empty *safely approximate* FIFO's state

Mixed-Clock FIFO: Full/Empty Detectors


Problem #2: FIFO now may underflow/overflow!

* synchronizing latches add extra latency

Solution #2: Change Full/Empty definitions

New FULL: *0 or 1 empty cells left*

New EMPTY: *0 or 1 full cells left*

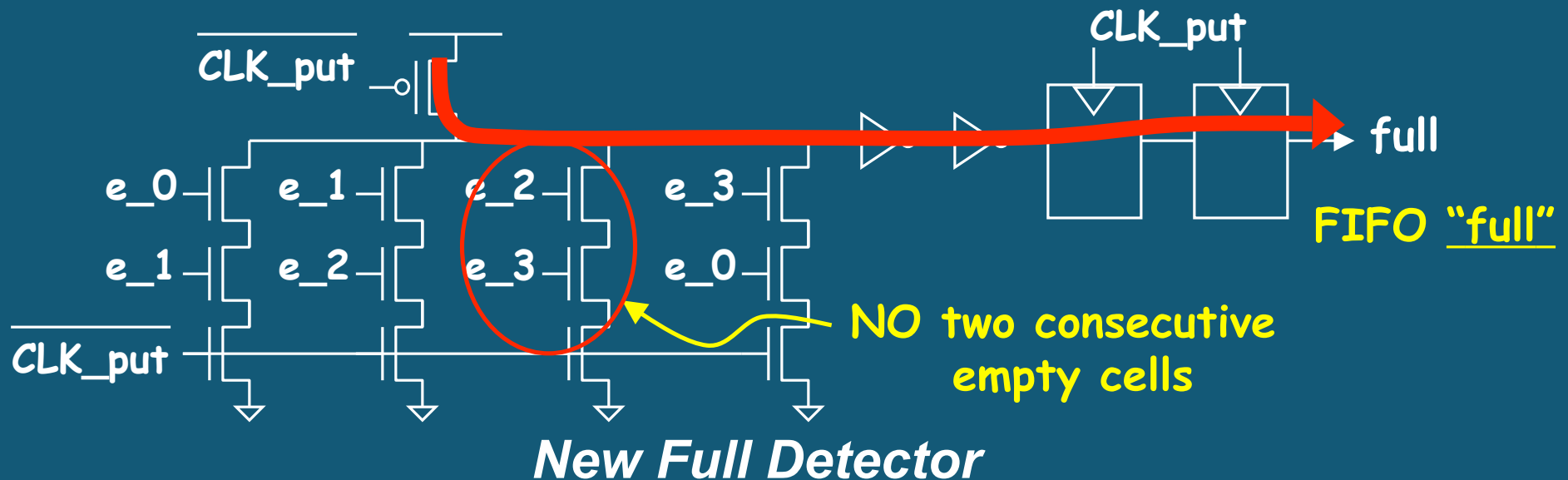

Observable full/empty *safely approximate* FIFO's state

Deadlock Avoidance

Problem #3: potential for **deadlock**

Scenario: only 1 data item in FIFO


- * FIFO still considered "empty" (new definition)
- * Get interface: *cannot dequeue item!*

Solution #3: bi-modal empty detector

- * "New empty" detector (0 or 1 data items)
- * "True empty" detector (0 data items)


Combine two results into single global "empty"

Mixed-Clock FIFO: Deadlock Avoidance


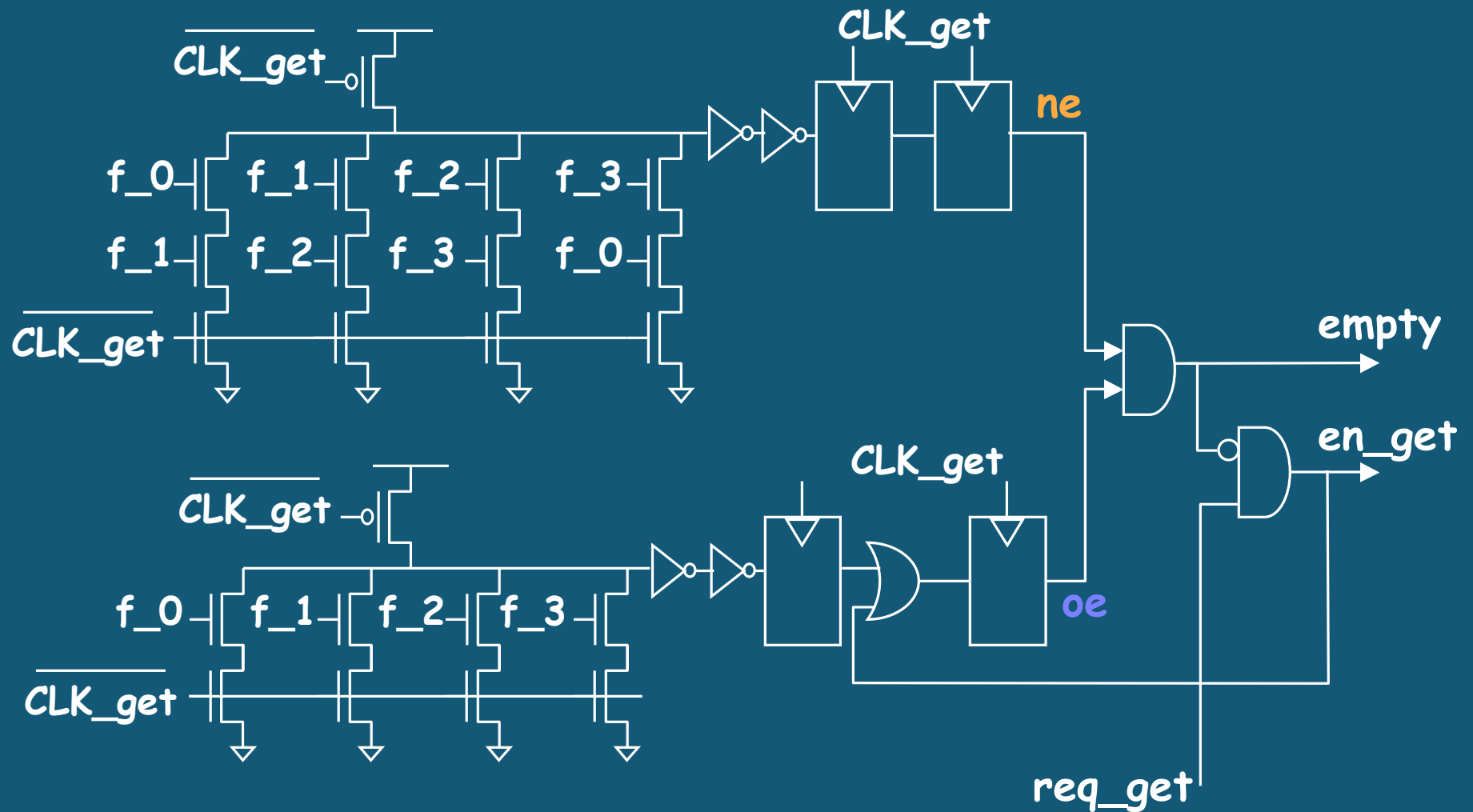


Mixed-Clock FIFO: Deadlock Avoidance


Detects "new empty" (0 or 1 empty cells)

 

Combine into global "empty"

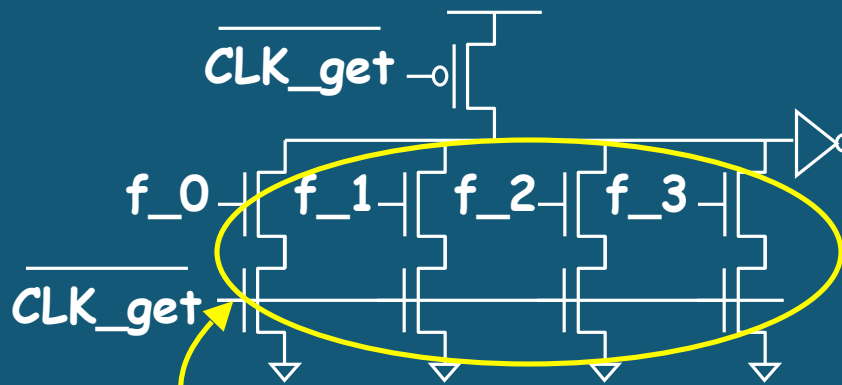 


Detects "true empty" (0 empty cells)

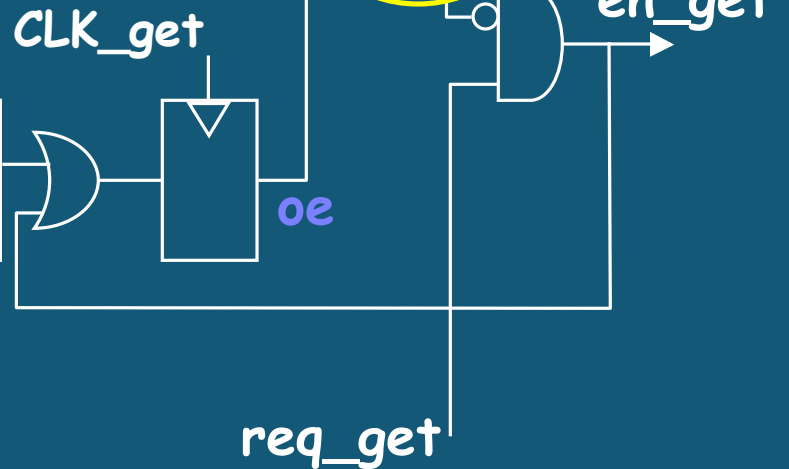

Mixed-Clock FIFO: Deadlock Avoidance

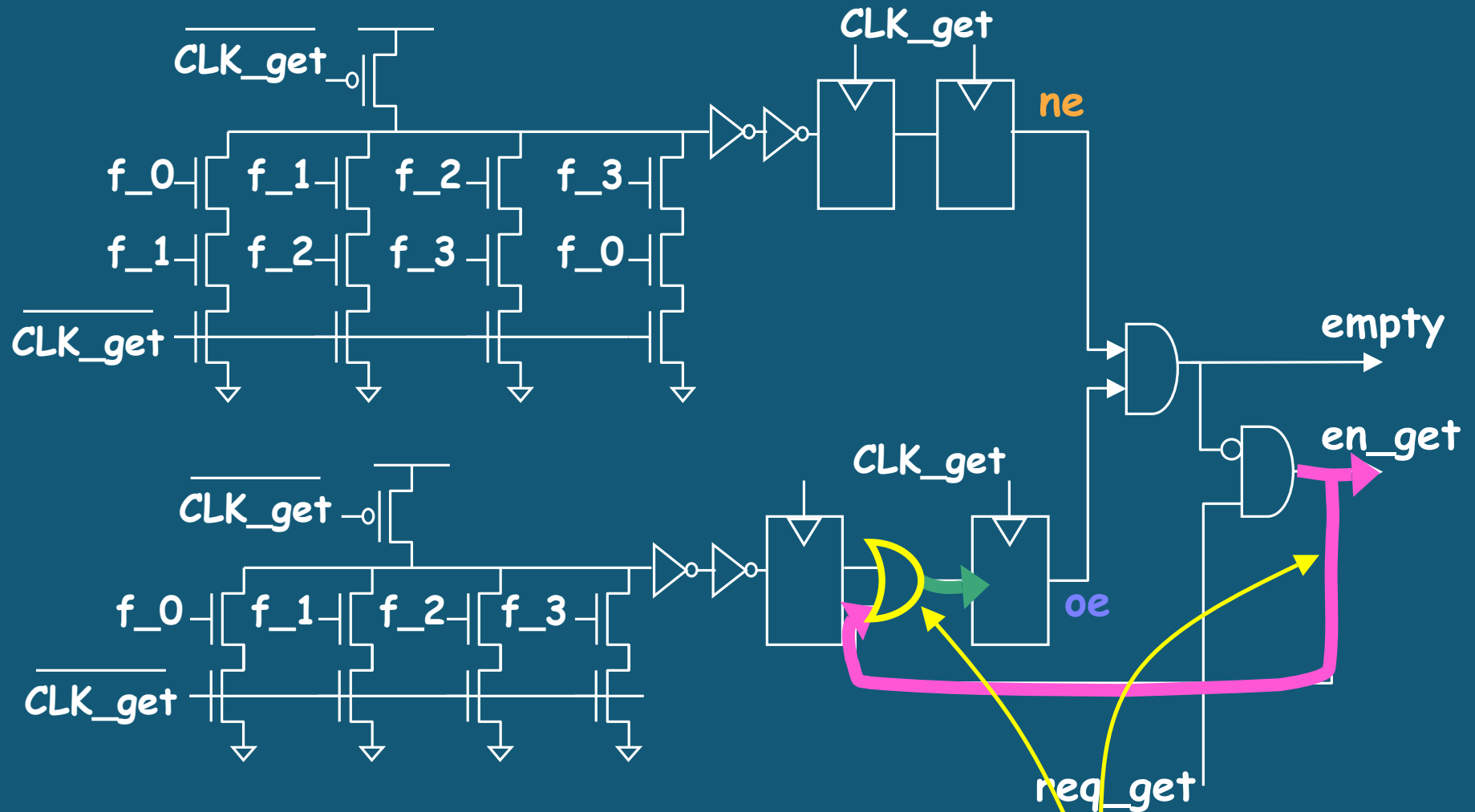
Bi-modal empty detection: select either ne or oe



Reconfigure whenever active get interface

Mixed-Clock FIFO: Deadlock Avoidance

Bi-modal empty detection:

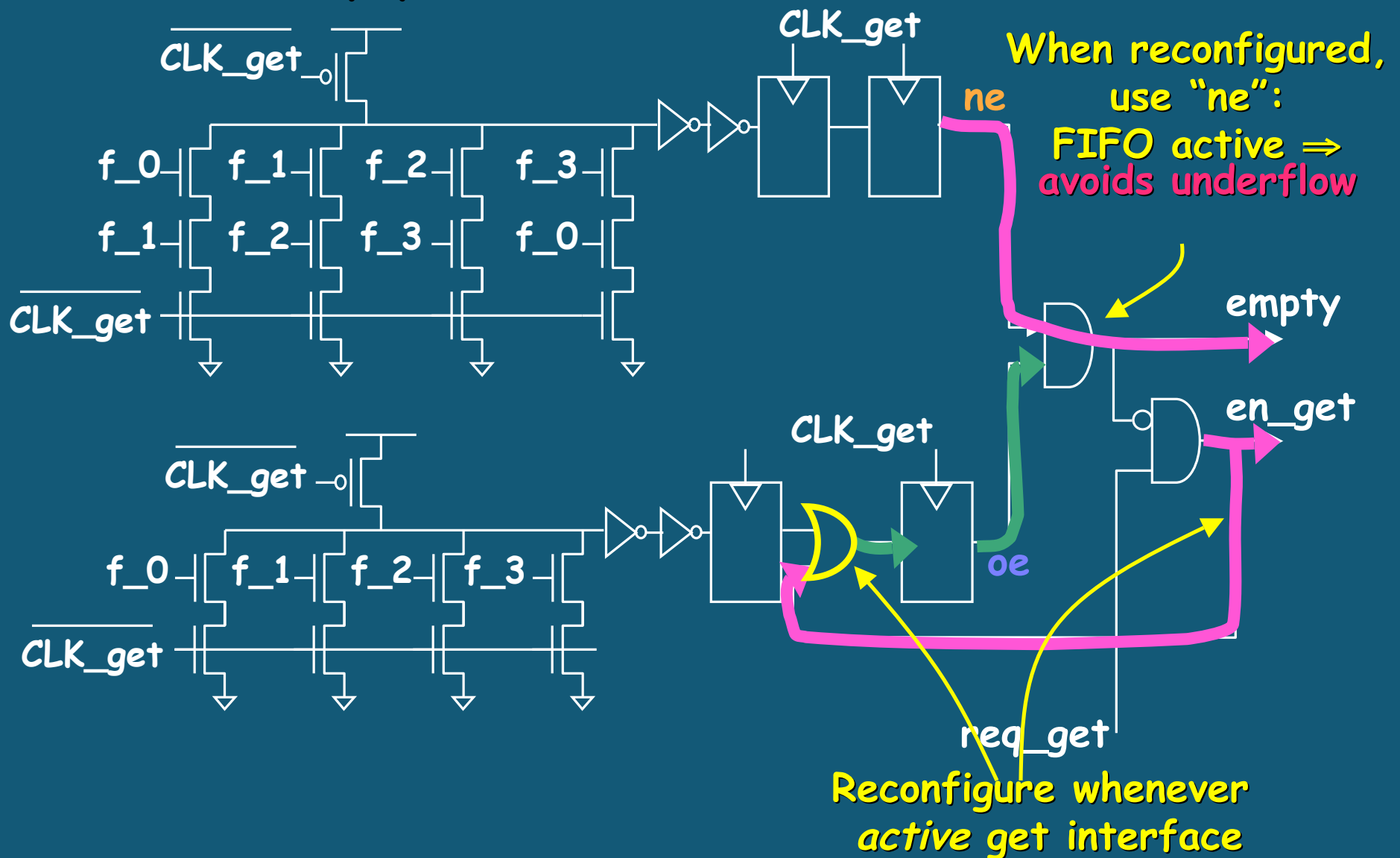


Mixed-Clock FIFO: Deadlock Avoidance

Bi-modal empty detection:

When NOT reconfigured,
use "oe":

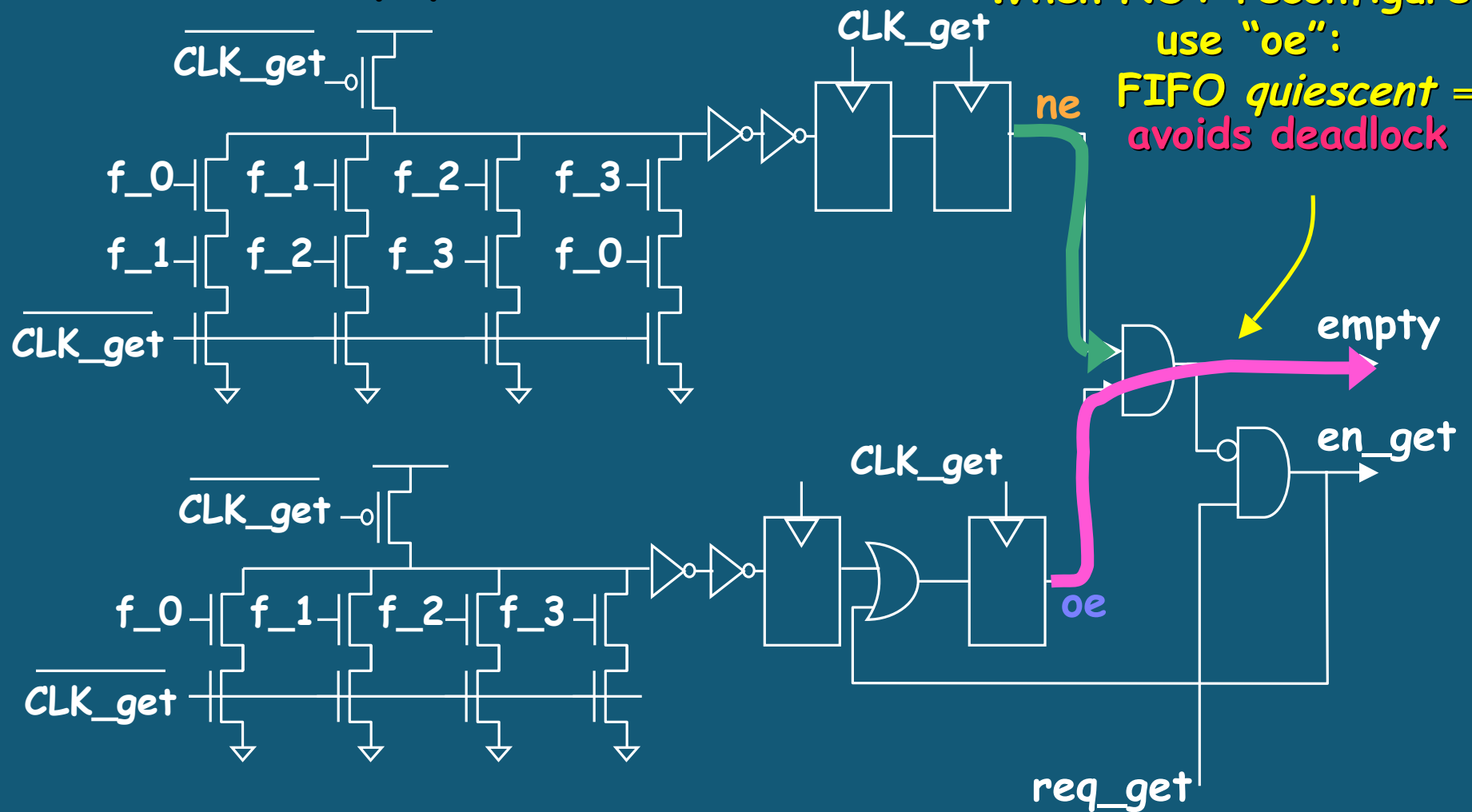FIFO quiescent \Rightarrow
avoids deadlock



Related Work: Intel Mixed-Clock Synchronizer

Intel Patent [1997]: J. Jex, C. Dike, K. Self (5,598,113)

- * Similar FIFO structure
- * Similar notion of "almost full"/"almost empty"

Differences/Limitations: N-stage FIFO


synchronizers required:

- * INTEL: $N+1$
- * US: 3

Interface types:


- * INTEL: only sync-sync
- * US: introduce a complete family (sync+async combinations)

Async-Async FIFO: Architecture

 


Async-Async FIFO: Architecture

Asynchronous Put Part

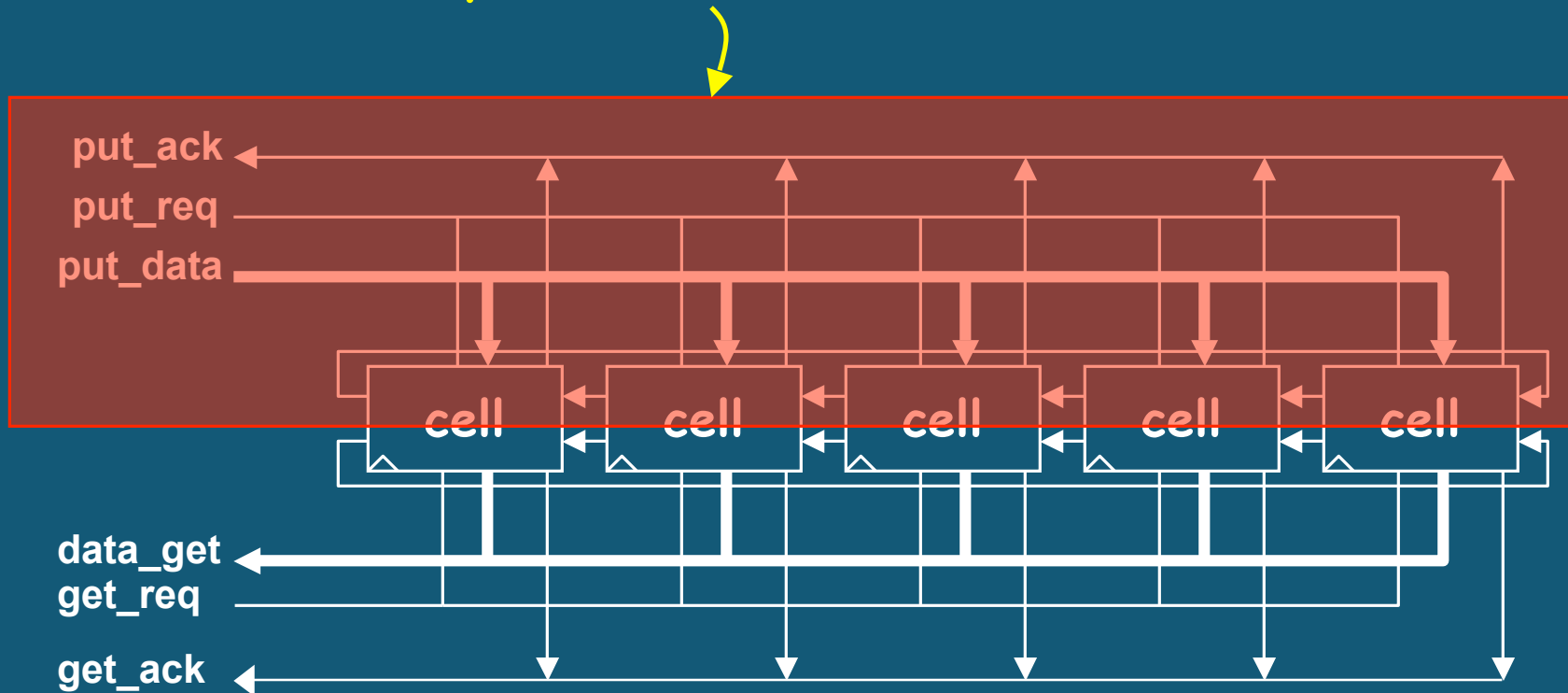


Async-Async FIFO: Architecture

 

Asynchronous Get Part

Async-Async FIFO: Architecture

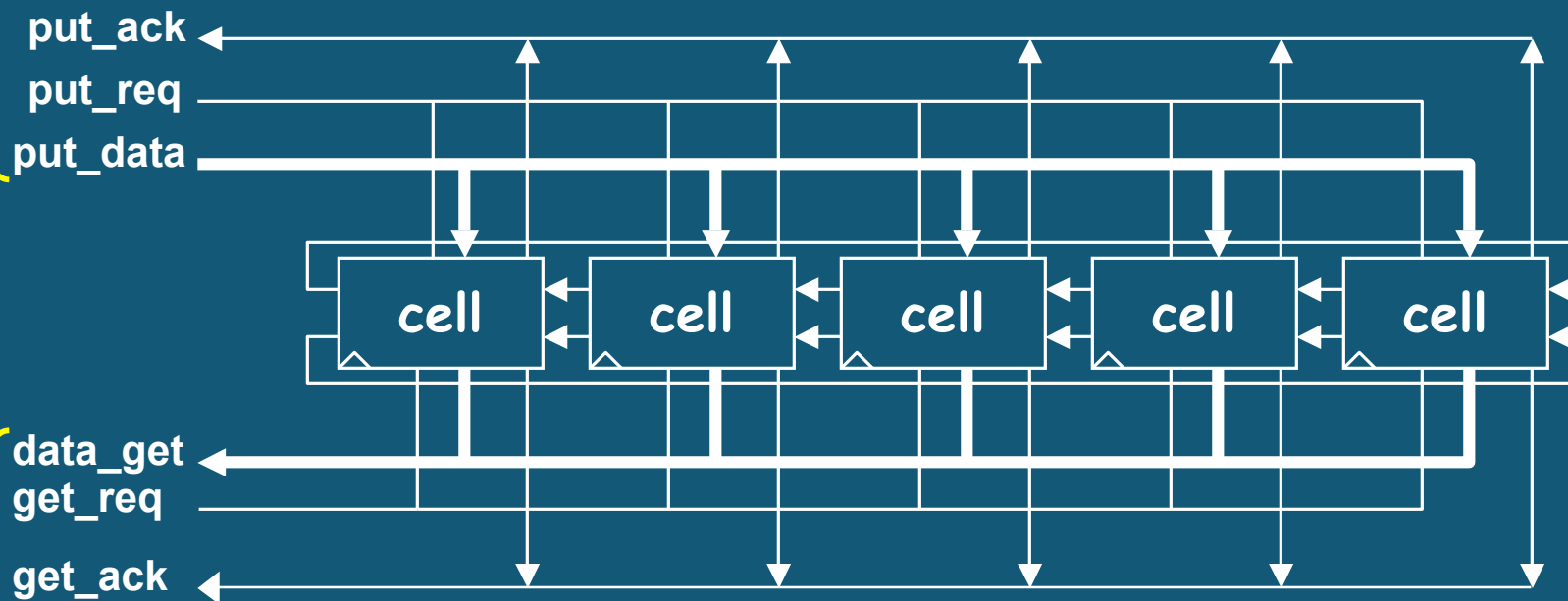
Put Interface: 4-phase bundled data channel



Get Interface: 4-phase bundled data channel


Async-Async FIFO: Architecture

No Detectors or External Controllers

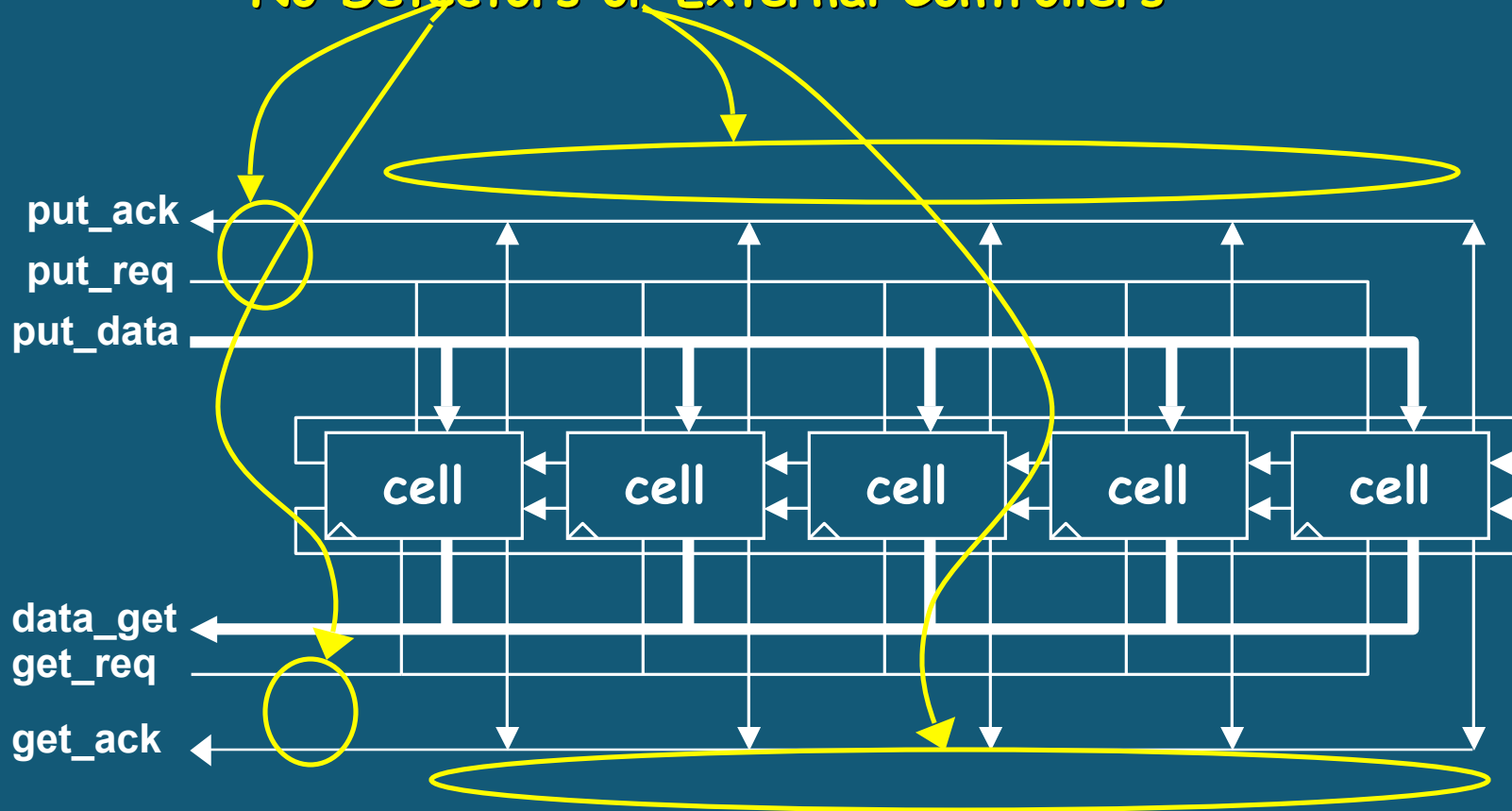


Async-Async FIFO: Architecture

 
When FIFO full, acknowledgment withheld until safe to perform the put operation



Async-Async FIFO Cell

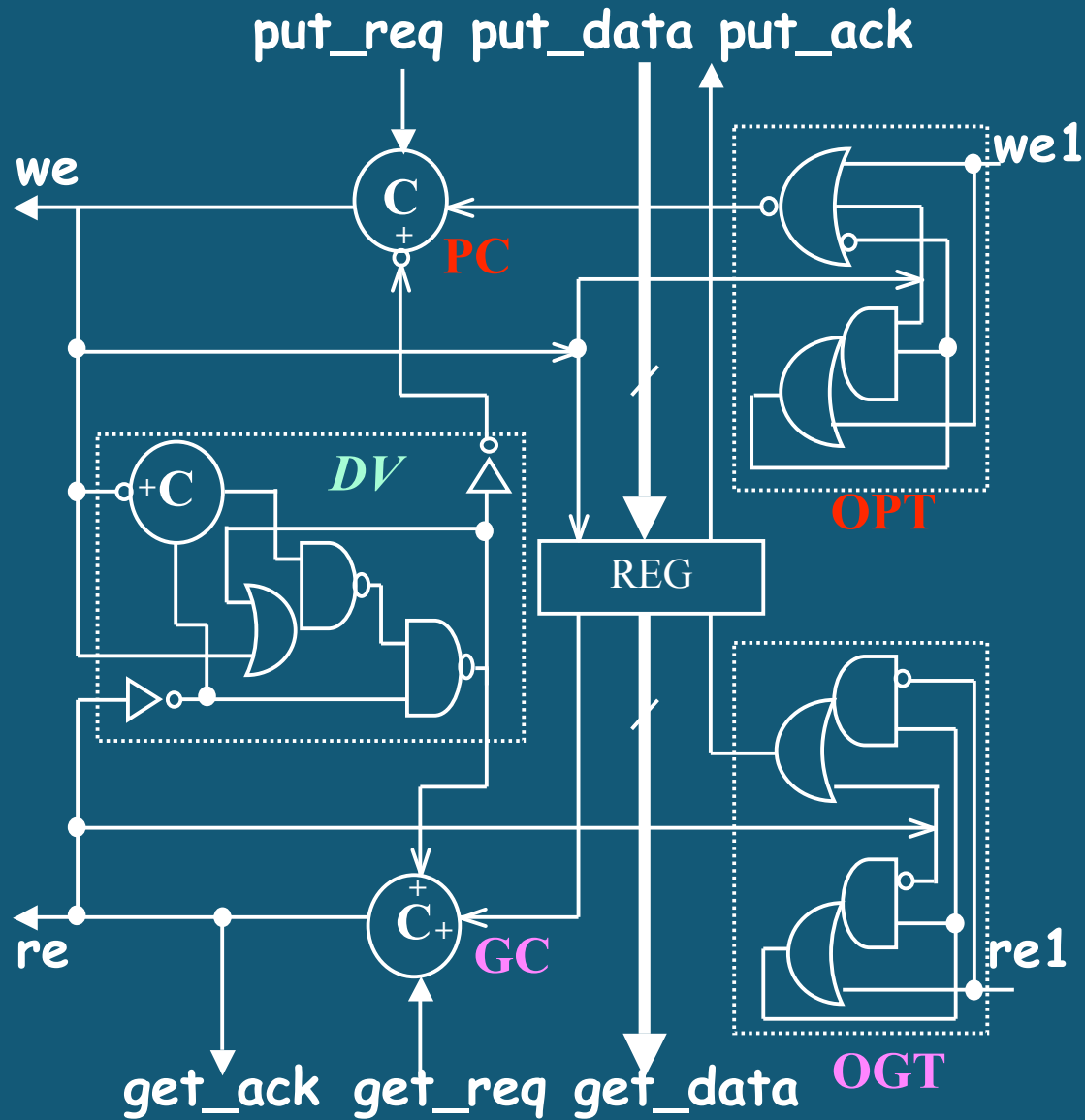


Async-Async FIFO Cell

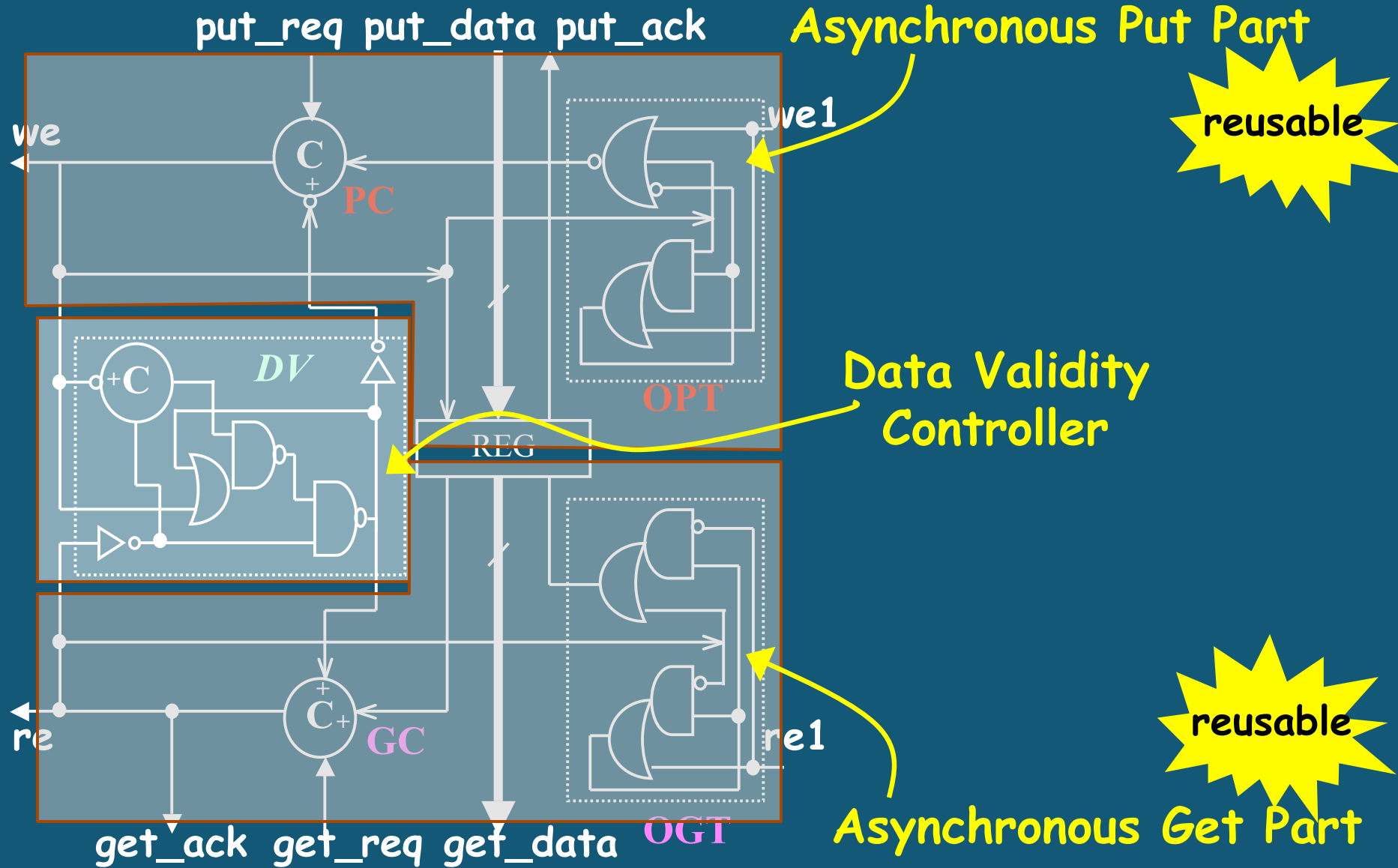


Reusability: Async-Sync FIFO Architecture

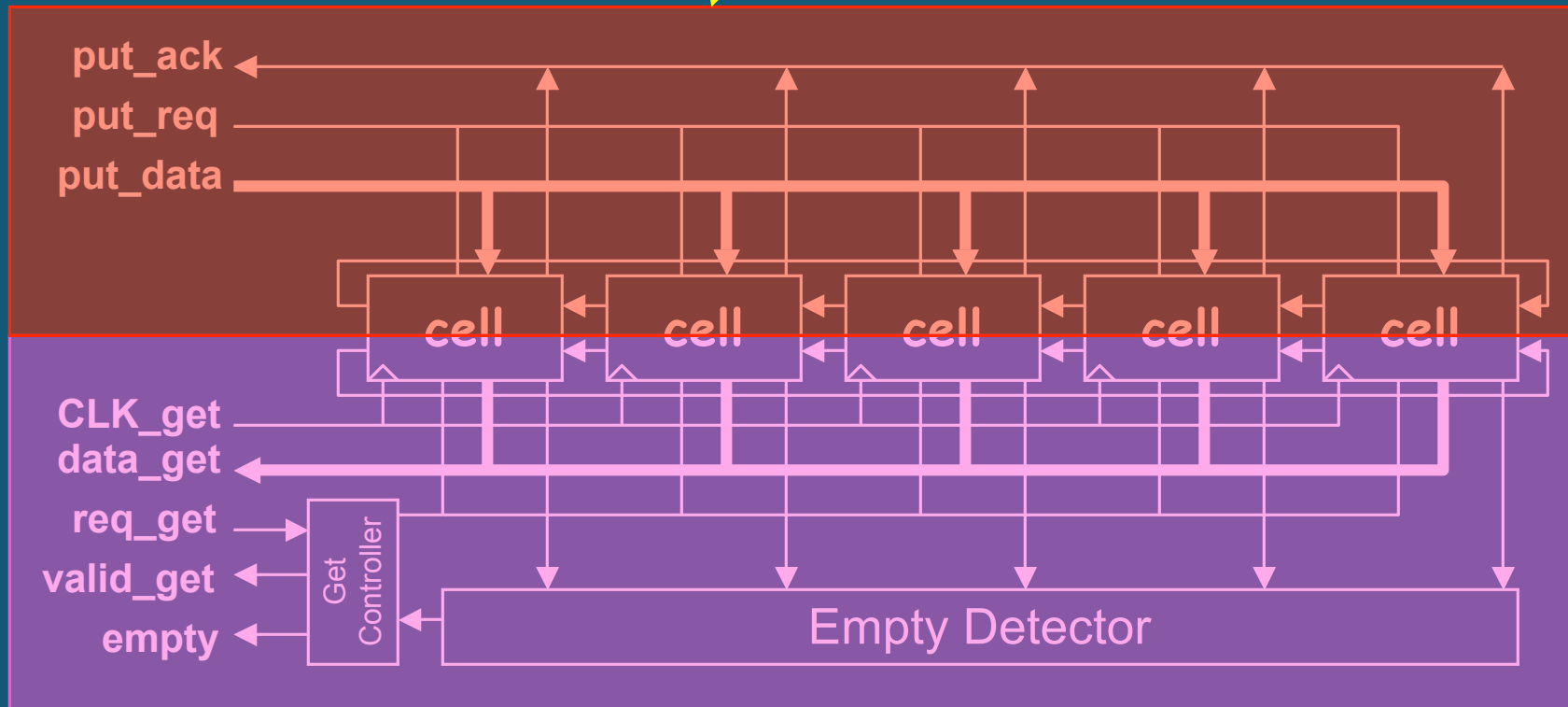Asynchronous Put Interface: exactly as in Async-Async FIFO



Synchronous Get Interface: exactly as in Mixed-Clock FIFO

Reusability: Async-Sync FIFO Cell

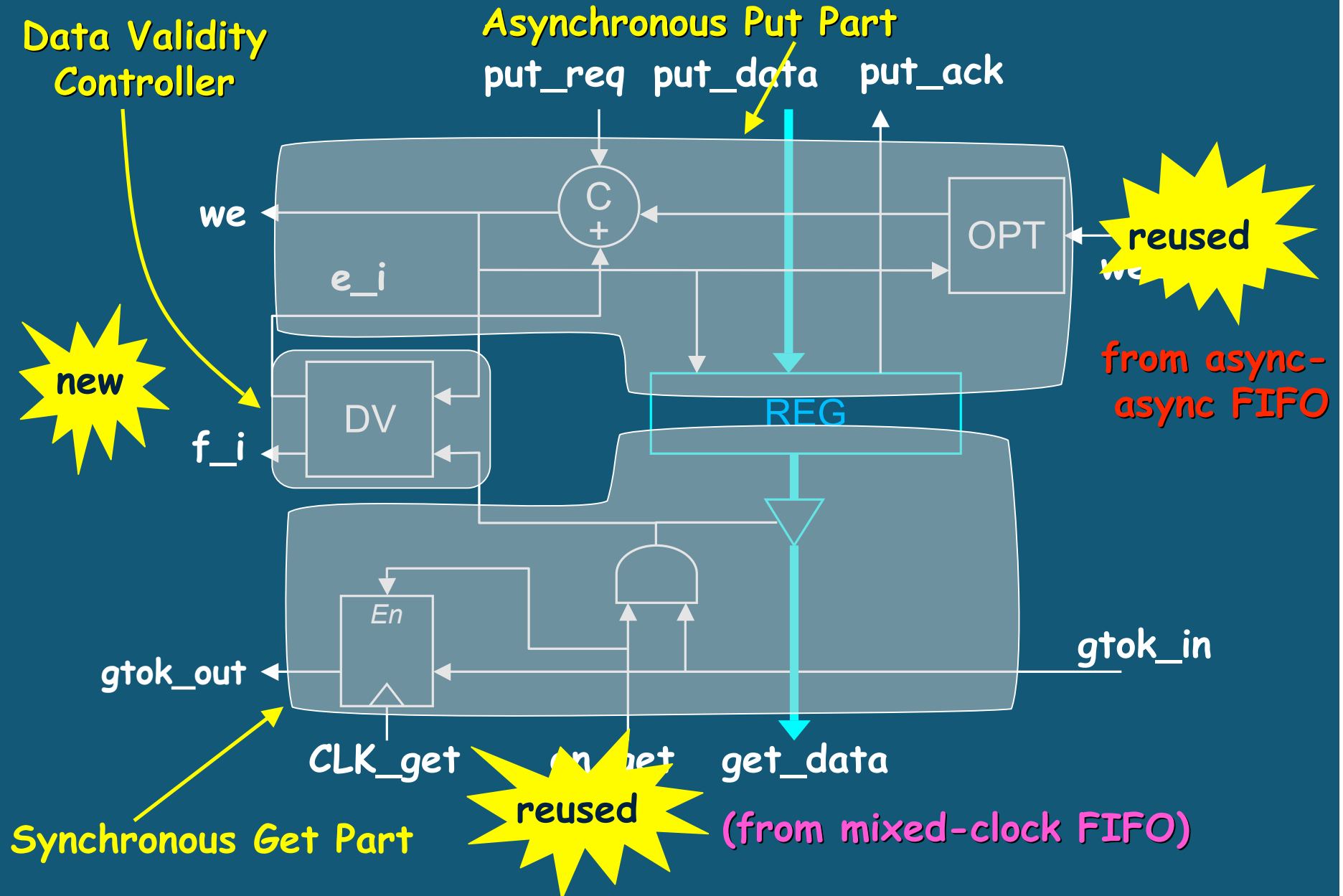


Part II

Handling Long Interconnect Delays

Issues in Handling Long Interconnect

 
Relay Stations: Background [Carloni, Sangiovanni-Vincentelli '99]



Issues in Handling Long Interconnect


Relay Stations Background [Carloni'99]

Delay = > 1 cycle

 


Issues in Handling Long Interconnect

Relay Stations Background [Carloni'99]

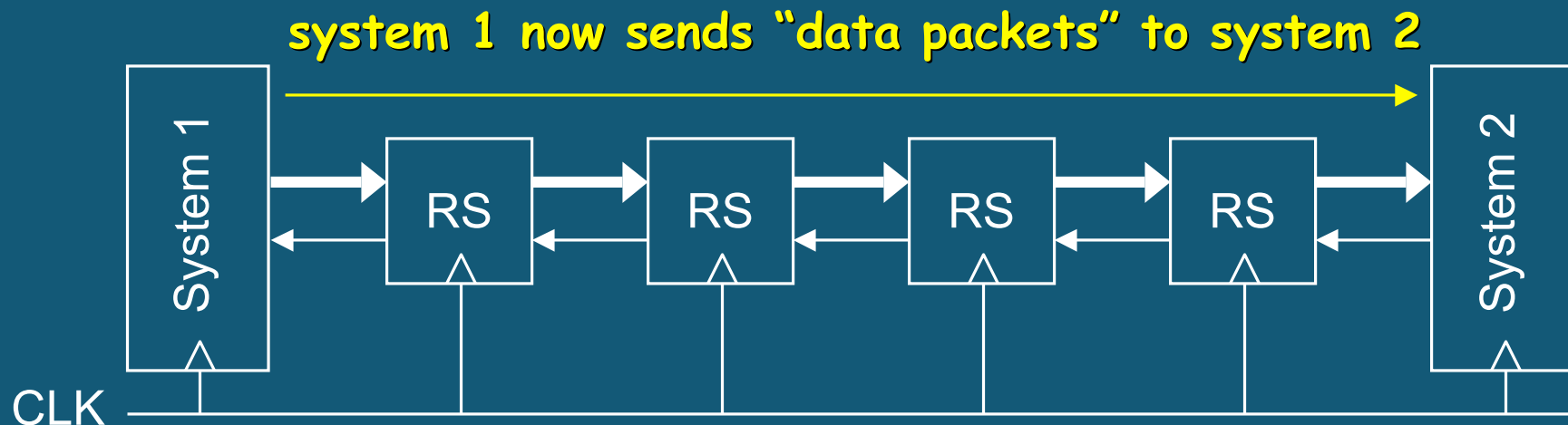


Issues in Handling Long Interconnect

Relay Stations Background [Carloni'99]

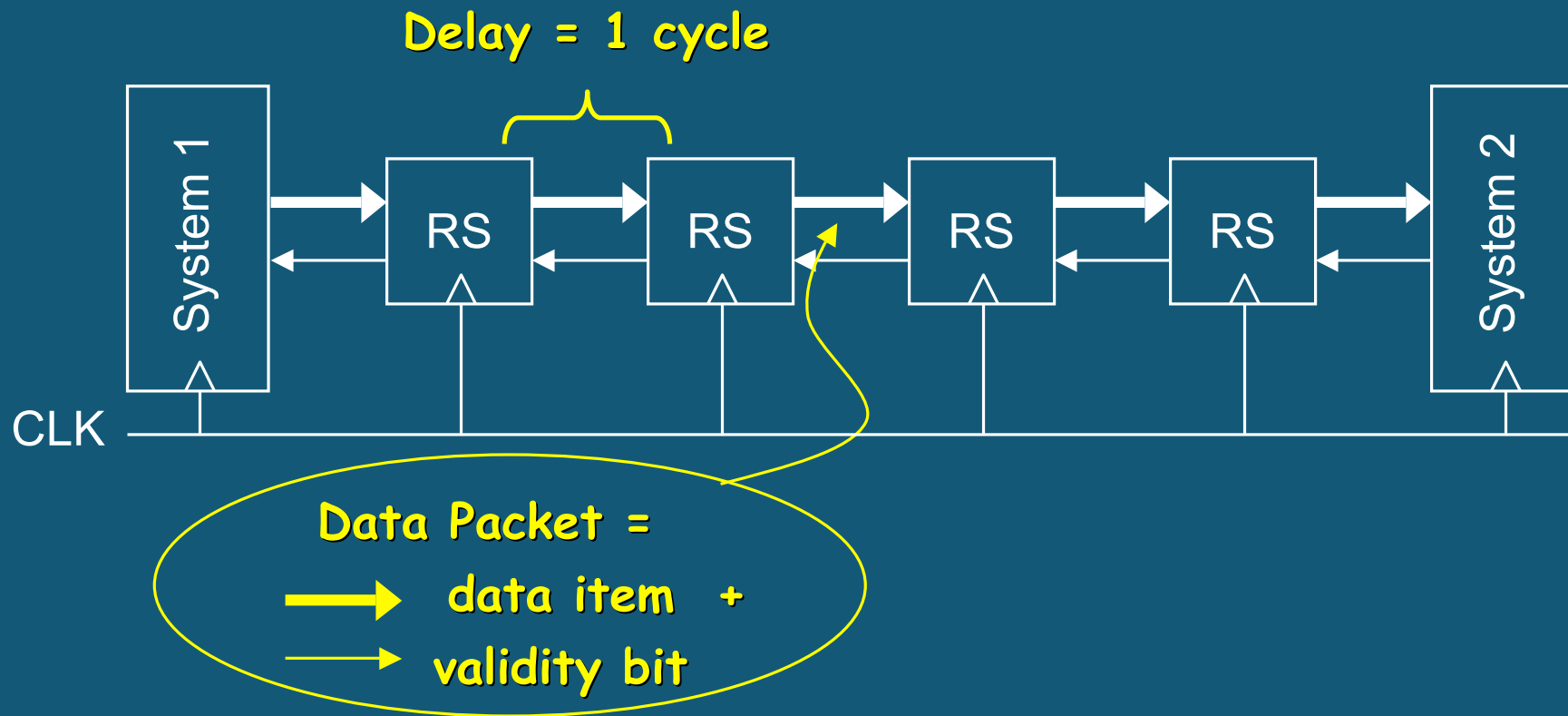

Issues in Handling Long Interconnect


Relay Stations Background [Carloni'99]

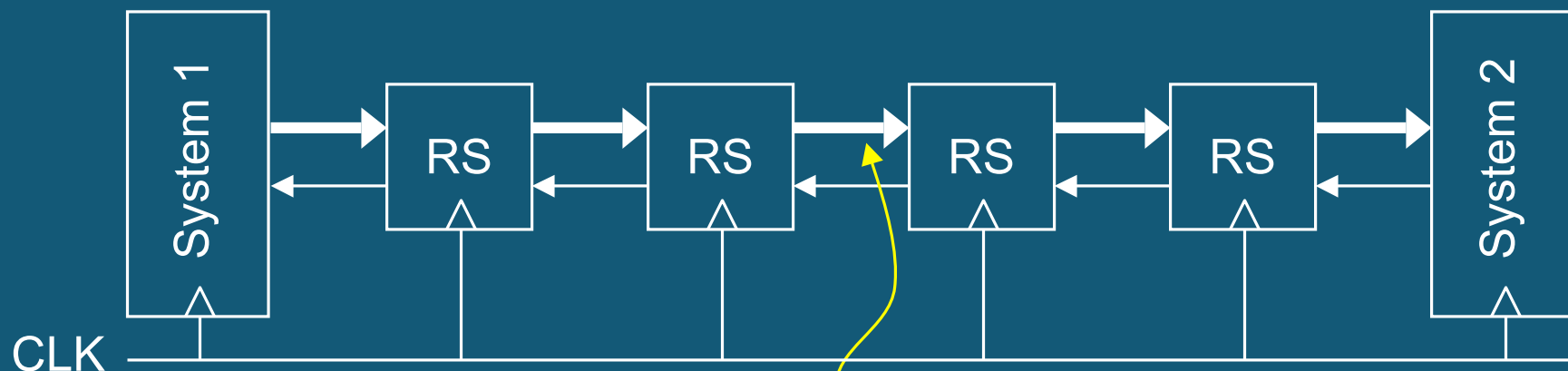

**Steady State: pass data on every cycle
(either valid or invalid)**

Issues in Handling Long Interconnect


Relay Stations Background [Carloni'99]

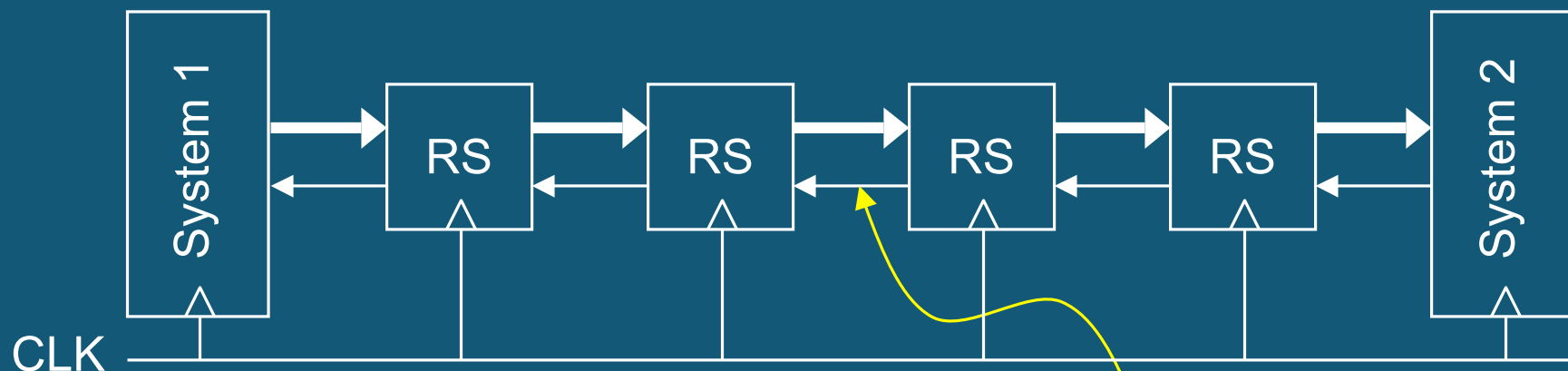

"stop" control = stopIn + stopOut
- apply counter-pressure
- result: stall communication

Problem: Works only for single-clock systems!

Relay Station

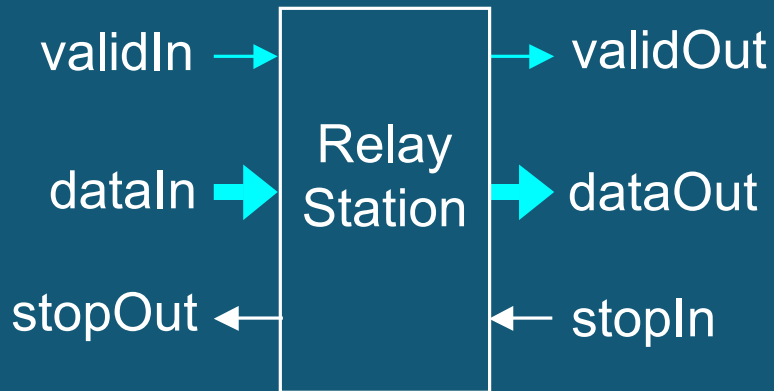


Steady state: always pass data

Data items: both valid & invalid

Stopping mechanism: stopIn
& stopOut

Mixed-Clock FIFO

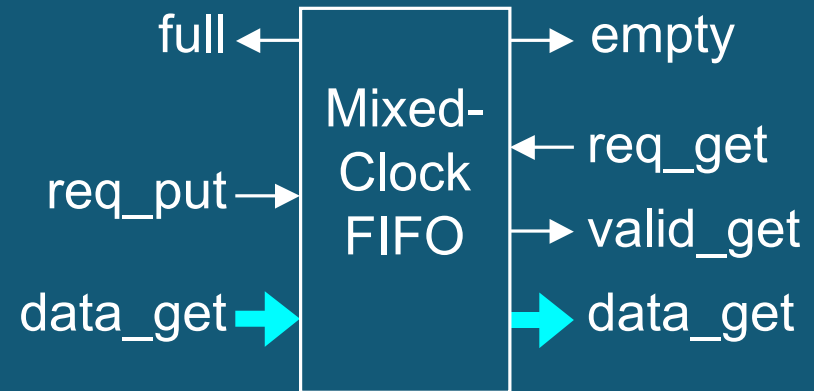


Steady state: only pass data
when requested


Data items: only valid data

Stopping mechanism: none
(only full/empty)

Mixed-Clock Relay Stations (MCRS)

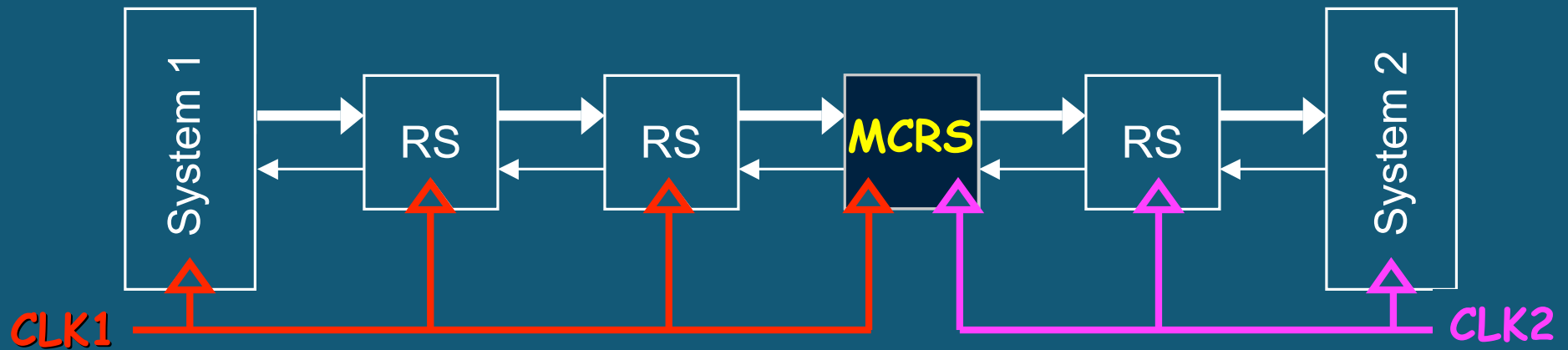

Mixed-Clock Relay Station: derived from Mixed-Clock FIFO
Change ONLY Put and Get Controllers

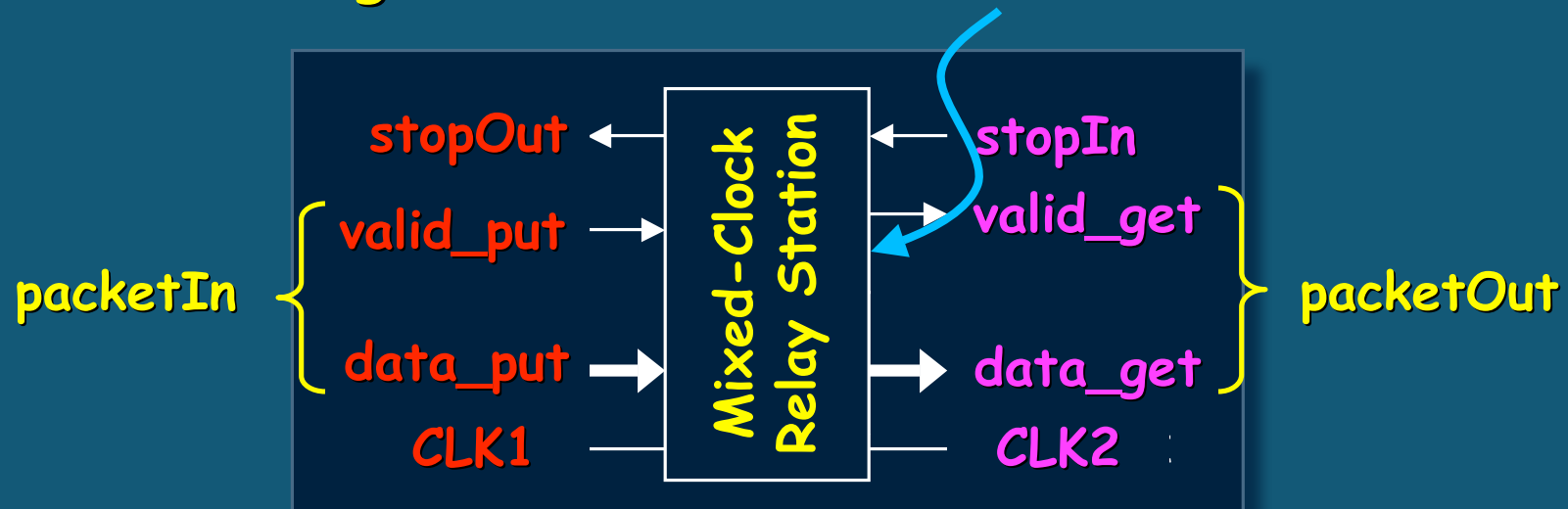

Part III

Experimental Results

Preliminary Results

Each new Mixed-Timing FIFO designed:

- * using both academic and industry tools
 - * **MINIMALIST**: Burst-Mode controllers [Nowick et al. '99]
 - * **PETRIFY**: Petri-Net controllers [Cortadella et al. '97]

Pre-layout simulations in 0.6 μ m HP CMOS technology

Experiments:

- * various FIFO capacities (4/16 cells)
- * 8-bit data items

Preliminary Results: Latency

Experimental setup: 8-bit data items + various FIFO capacities (4, 16)

Latency = time from enqueueing to dequeueing data into an empty FIFO

Version	4-place		16-place	
	Min	Max	Min	Max
Mixed-Clock FIFO	5.43	6.34	6.14	7.17
Async-Async FIFO	1.73		2.29	
Async-Sync FIFO	5.53	6.45	6.47	7.51
Sync-Async FIFO	1.95		2.44	
Mixed-Clock RS	5.48	6.41	6.23	7.28
Async-Sync RS	5.61	6.35	6.57	7.62
Sync-Async RS	1.86		2.43	

Sync receiver \Rightarrow latency not uniquely defined: Min/Max

Preliminary Results: Latency

Experimental setup: 8-bit data items + various FIFO capacities (4, 16)

Latency = time from enqueueing to dequeueing data into an empty FIFO

Version	4-place		16-place	
	Min	Max	Min	Max
Mixed-Clock FIFO	5.43	6.34	6.14	7.17
Async-Async FIFO	1.73		2.29	
Async-Sync FIFO	5.53	6.45	6.47	7.51
Sync-Async FIFO	1.95		2.44	
Mixed-Clock RS	5.48	6.41	6.23	7.28
Async-Sync RS	5.61	6.35	6.57	7.62
Sync-Async RS	1.86		2.43	

Async receiver \Rightarrow lower, unique latency, no synchronization

Preliminary Results: Maximum Operating Rate

Synchronous interfaces: MegaHertz

Asynchronous interfaces: MegaOps/sec

Design	4-place		16-place	
	Put	Get	Put	Get
Mixed-Clock FIFO	565	549	505	484
Async-Async FIFO	423	454	359	357
Async-Sync FIFO	421	549	357	484
Sync-Async FIFO	565	454	505	360
Mixed-Clock RS	580	539	509	475
Async-Sync RS	421	539	357	475
Sync-Async RS	580	454	509	360

Put vs. Get rates:

- sync put faster than sync get
- async put slower than async get

Async vs. Sync rates:

- async slower than sync

Conclusions

Introduced complete family of mixed-timing FIFO's :

- * **sync-sync, async-async, async-sync, sync-async**
- * create FIFO's from *reusable parts*
- * extend to handle **issue of long interconnect delays**


Characteristics:

- **Low-latency**
- **Modular and scalable:** distributed token-ring architecture
- **High throughput:**
 - * steady state: **no synchronization overhead, no failure probability**
 - * enqueue/dequeue data items: one/cycle
- **Low area overheads:** simple design

Extensions:

- * **Deeper synchronizers (more latches) => arbitrary robustness**
- * **powering down of inactive cells**

Relay Station: Implementation

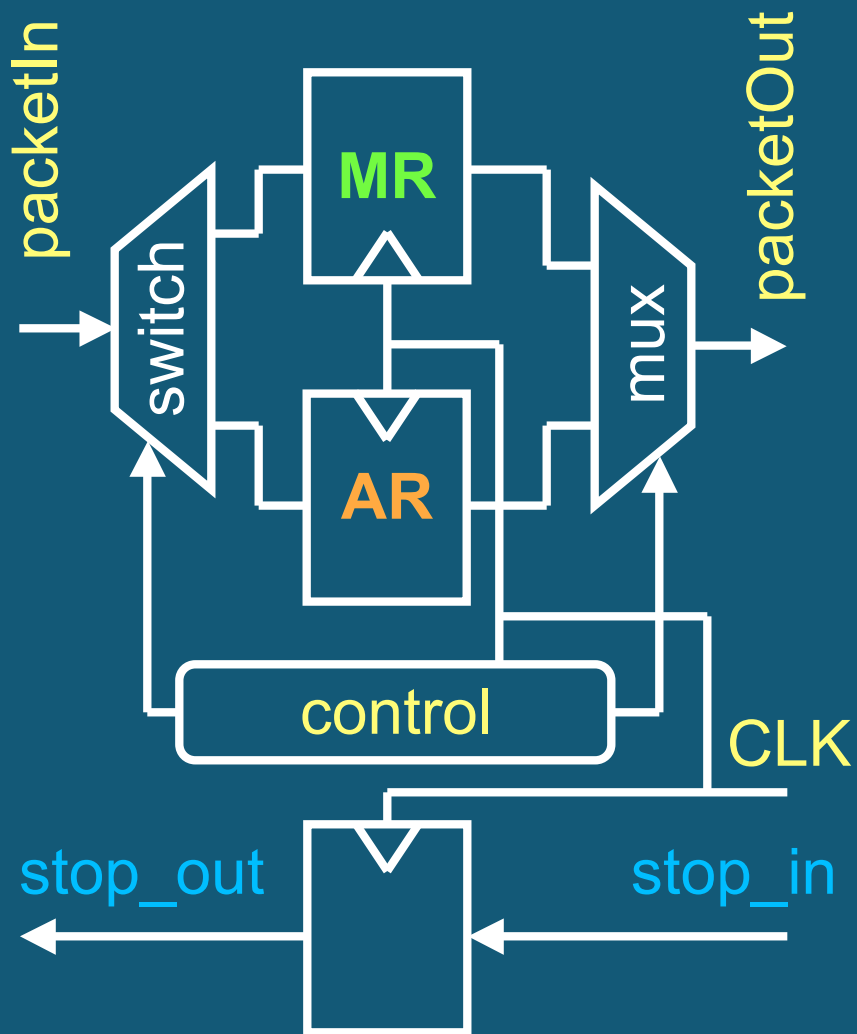

- On every clock cycle:
 - * packet latched in MR
 - * packet passed to next RS by end of clock cycle
 - * **steady state:** pass valid/invalid data items
- Station stopped from right:
 - * stop_in = 1
 - * extra packet latched in AR
 - * stop_out = 1
- Station started (stop_in = 0):
 - * Output packet in MR first
 - * Output packet in AR second
 - * Resume normal operation (stop_out = 0)