 


Digital Design with Synthesizable VHDL

Prof. Stephen A. Edwards
sedwards@cs.columbia.edu

Columbia University
Spring 2008

Why HDLs?




1970s: SPICE transistor-level netlists

An XOR built from four NAND gates

```
.MODEL P PMOS
.MODEL N NMOS


.SUBCKT NAND A B Y Vdd Vss
M1 Y A Vdd Vdd P
M2 Y B Vdd Vdd P
M3 Y A X Vss N
M4 X B Vss Vss N
.ENDS

 X1 A B I1 Vdd 0 NAND
X2 A I1 I2 Vdd 0 NAND
X3 B I1 I3 Vdd 0 NAND
X4 I2 I3 Y Vdd 0 NAND
```



Why HDLs?

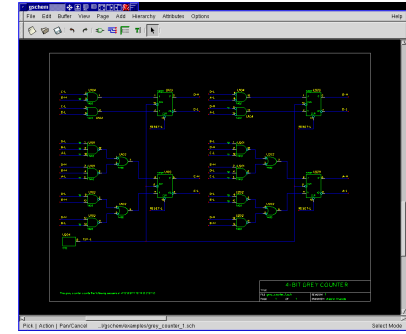1980s: Graphical schematic capture programs




Why HDLs?

1990s: HDLs and Logic Synthesis

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity ALU is
port(
  A: in unsigned(1 downto 0);
  B: in unsigned(1 downto 0);
  Sel: in unsigned(1 downto 0);
  Res: out unsigned(1 downto 0));
end entity ALU;
architecture behv of ALU is begin
process (A,B,Sel) begin
case Sel is
when "00" => Res <= A + B;
when "01" => Res <= A + (not B) + 1;
when "10" => Res <= A and B;
when "11" => Res <= A or B;
when others => Res <= "XX";
end case;
end process;
end behv;
```

 

Two Separate but Equal Languages



Verilog and VHDL
Verilog: More succinct, less flexible, really messy
VHDL: Verbose, very (too?) flexible, fairly messy
Part of languages people actually use identical.
Every synthesis system supports both.

Basic Lexical Rules of VHDL

- Free-form: space only separates tokens.
- Case-insensitive: "VHDL", "vHdL", and "vhdl" are equivalent.
- Comments: from "--" to the end of the line.
- Identifiers: [a-zA-Z](?_[a-zA-Z0-9])*
Examples: X X_or_Y ADDR addr
Illegal: 14M CLK__4 F00_

Literals in VHDL

- Decimal integers*: 1 42 153_1203
- Based integers*: 2#1_0010# 16#F001D#
- Characters: '0' '1' 'X'
- Strings: "101011" "XXXXXX"
- Bit string literals*: B"1001_0101" X"95"
mean "10010101"

*Underscores added for readability are ignored

Combinational Logic in a Dataflow Style

Bits

Logical	True	False
Binary	1	0
Voltage	1.65–3.3V	0–1.65V
Timing Diagram	—	—
VHDL	'1'	'0'

In VHDL, zeros and ones on wires are members of an enumerated type. *They are not Boolean.*

The std_logic_1164 package

```
package std_logic_1164 is
  type std_ulogic is
    ('U', -- Uninitialized
     'X', -- Forcing Unknown
     '0', -- Forcing 0
     '1', -- Forcing 1
     'Z', -- High Impedance
     'W', -- Weak Unknown
     'L', -- Weak 0
     'H', -- Weak 1
     '-' -- Don't care
    );
  -- The std_logic type allows tri-state drivers (preferred)
  subtype std_logic is resolved std_ulogic;
  -- Lots more...
```

Digital Design with Synthesizable VHDL - p. 1

Boolean Operators

The basic ones in VHDL:

a	b	a and b	a or b	not a
'0'	'0'	'0'	'0'	'1'
'0'	'1'	'0'	'1'	'1'
'1'	'0'	'0'	'1'	'0'
'1'	'1'	'1'	'1'	'0'

a	b	a nand b	a nor b	a xor b
'0'	'0'	'1'	'1'	'0'
'0'	'1'	'1'	'0'	'1'
'1'	'0'	'1'	'0'	'1'
'1'	'1'	'0'	'0'	'0'

Digital Design with Synthesizable VHDL - p. 1

Rules of Boolean Algebra (1)

```
-- Precedence
not a or b and c = (not a) or (b and c)

-- Basic relationships
not not a = a
a and '1' = a
a and '0' = '0'
a or '1' = '1'
a or '0' = a
a and a = a
a and not a = '0'
a or a = a
a or not a = '1'
a nand b = not (a and b)
a nor b = not (a or b)
a xor '0' = a
a xor '1' = not a
a xor b = (not a and b) or (a and not b)
```

Digital Design with Synthesizable VHDL - p. 1

Rules of Boolean Algebra (2)

```
-- Commutativity
a and b = b and a
a or b = b or a

-- Associativity
a and (b and c) = (a and b) and c
a or (b or c) = (a or b) or c

-- Distributivity
a and (b or c) = a and b or a and c
a or (b and c) = (a or b) and (a or c)

-- De Morgan's Law
not (a and b) = not a or not b
not (a or b) = not a and not b
```

Digital Design with Synthesizable VHDL - p. 1

A Full Adder: Truth Table

a	b	c	carry	sum	carry <=
0	0	0	0	0	(not a and b and c) or (a and not b and c) or (a and b and not c) or (a and b and c);
0	0	1	0	1	(not a and not b and c) or (a and not b and not c) or (a and b and not c) or (a and b and c);
0	1	0	0	1	(not a and b and not c) or (a and not b and c) or (a and b and not c) or (a and b and c);
0	1	1	1	0	(not a and not b and not c) or (a and not b and not c) or (a and b and not c) or (a and b and c);
1	0	0	0	1	(not a and not b and not c) or (a and not b and not c) or (a and b and not c) or (a and b and c);
1	0	1	1	0	(not a and not b and not c) or (a and not b and not c) or (a and b and not c) or (a and b and c);
1	1	0	1	0	(not a and not b and not c) or (a and not b and not c) or (a and b and not c) or (a and b and c);
1	1	1	1	1	(not a and not b and not c) or (a and not b and not c) or (a and b and not c) or (a and b and c);

Each row represents a minterm

Sum-of-products form: sum of each minterm in which output is true

Digital Design with Synthesizable VHDL - p. 1

Simplifying Using Boolean Rules

```
carry <= (not a and b and c) or (a and not b and c) or
(a and b and not c) or (a and b and c);

<= (a and b and not c) or (a and b and c) or
(not a and b and c) or (a and b and c) or
(a and not b and c) or (a and b and c);

<= (a and b) or (b and c) or (a and c);


sum <= (not a and not b and c) or (not a and b and not c) or
(a and not b and not c) or (a and b and c);

<= (not a) and ((not b and c) or (b and not c)) or
a and ((not b and not c) or (b and c));

<= a xor b xor c;
```

Digital Design with Synthesizable VHDL - p. 1

Structure of a VHDL Module

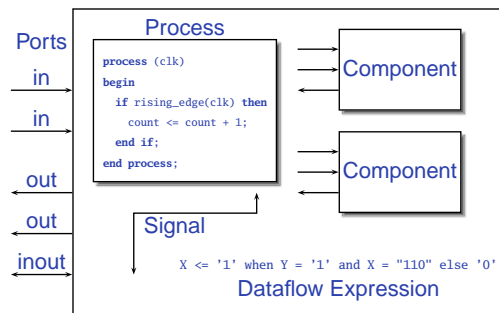


Digital Design with Synthesizable VHDL - p. 1

A Full Adder in VHDL

```
library ieee; -- always needed
use ieee.std_logic_1164.all; -- std_logic, et al.


entity full_adder is -- the interface
  port(a, b, c : in std_logic;
        sum, carry : out std_logic);
end full_adder;

 architecture imp of full_adder is -- the implementation
begin
  sum <= (a xor b) xor c; -- combinational logic
  carry <= (a and b) or (a and c) or (b and c);
end imp;
```



Digital Design with Synthesizable VHDL - p. 1

...After Logic Synthesis

 

Digital Design with Synthesizable VHDL - p. 1

Vectors of Bits

Three standard synthesizable bit vector types:

Type	Library	Logic	Arith.	Neg.
std_logic_vector	ieee_std_1164	✓		
unsigned	numeric_std	✓	✓	
signed	numeric_std	✓	✓	✓

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
```

```
entity vectors is
port (vect : in std_logic_vector(1 downto 0);
      uns1 : in unsigned(7 downto 0);
      sign : out unsigned(15 downto 0));
end entity;
```

Digital Design with Synthesizable VHDL - p. 1

Endianness

The perpetual battle: Is "0" most or least significant?

Little Endian 3 2 1 0 unsigned(3 downto 0)
Big Endian 0 1 2 3 unsigned(0 to 3)

Arguments on both sides will continue forever.

I suggest using Little Endian for vectors.

Digital Design with Synthesizable VHDL - p. 2

Binary and Hexadecimal in VHDL

Decimal	Binary	Hex
0	"0"	x"0"
1	"1"	x"1"
2	"10"	x"2"
3	"11"	x"3"
4	"100"	x"4"
5	"101"	x"5"
6	"110"	x"6"
7	"111"	x"7"
8	"1000"	x"8"
9	"1001"	x"9"
10	"1010"	x"A"
11	"1011"	x"B"
12	"1100"	x"C"
13	"1101"	x"D"
14	"1110"	x"E"
15	"1111"	x"F"
16	"10000"	x"10"
17	"10001"	x"11"
18	"10010"	x"12"
19	"10011"	x"13"

Vector types are arrays of std_logic

Literals are therefore strings of 0's and 1's

```
-- from std_logic_1164
type std_logic_vector is
array (natural range <>) of std_logic;
```

```
--- from numeric_std
type unsigned is
array (natural range <>) of std_logic;
```

```
type signed is
array (natural range <>) of std_logic;
```

Digital Design with Synthesizable VHDL - p. 2

Two's Complement

Decimal	Binary	Hex
-8	"1000"	x"8"
-7	"1001"	x"9"
-6	"1010"	x"A"
-5	"1011"	x"B"
-4	"1100"	x"C"
-3	"1101"	x"D"
-2	"1110"	x"E"
-1	"1111"	x"F"
0	"0000"	x"0"
1	"0001"	x"1"
2	"0010"	x"2"
3	"0011"	x"3"
4	"0100"	x"4"
5	"0101"	x"5"
6	"0110"	x"6"
7	"0111"	x"7"

How do you represent negative numbers?

Two's complement produces simpler logic than sign bit alone.


Idea: Add constant 2^n to negative numbers. Simply discard overflow after addition or subtraction.

An n -bit number represents -2^{n-1} to $2^{n-1} - 1$.

The signed type in numeric_std uses this

Digital Design with Synthesizable VHDL - p. 2

A Hex-to-seven-segment Decoder

 

Digital Design with Synthesizable VHDL - p. 2

VHDL: Hex-to-7-segment Decoder

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all; -- Provides the unsigned type
entity hex7seg is
port ( input : in unsigned(3 downto 0); -- A number
      output : out std_logic_vector(6 downto 0)); -- Just bits
end hex7seg;
architecture combinational of hex7seg is
begin
with input select output <=
"0111111" when x"0", "0000110" when x"1", -- Bad style
"1011011" when x"2", "1001111" when x"3", -- one case
"1100110" when x"4", "1101101" when x"5", -- per line
"1111101" when x"6", "0000111" when x"7", -- preferred
"1111111" when x"8", "1101111" when x"9",
"1110111" when x"A", "1111100" when x"B",
"0111001" when x"C", "1011110" when x"D",
"1111001" when x"E", "1110001" when x"F",
"XXXXXXX" when others;
end combinational;
```

Digital Design with Synthesizable VHDL - p. 2

Four-to-one mux: when .. else

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity multiplexer_4_1 is
port (in0, in1, in2, in3 : in unsigned(15 downto 0);
      s : in unsigned(1 downto 0);
      z : out unsigned(15 downto 0));
end multiplexer_4_1;

architecture comb of multiplexer_4_1 is
begin
z <= in0 when s = "00" else
in1 when s = "01" else
in2 when s = "10" else
in3 when s = "11" else
(others => 'X'); -- Shorthand for "all X's"
end comb;
```

Digital Design with Synthesizable VHDL - p. 2

Four-to-one mux: with...select

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity multiplexer_4_1 is
port (in0, in1, in2, in3 : in unsigned(15 downto 0);
      s0, s1 : in std_logic;
      z : out unsigned(15 downto 0));
end multiplexer_4_1;

architecture comb of multiplexer_4_1 is
signal sels : unsigned(1 downto 0);
begin
sels <= s1 & s0; -- "&" is vector concatenation
with sels select -- would not resolve type if "s1 & s0" here
z <= in0 when "00",
in1 when "01",
in2 when "10",
in3 when "11",
(others => 'X') when others;
```

Digital Design with Synthesizable VHDL - p. 2

Three-to-eight Decoder

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity dec1_8 is
port (
sel : in unsigned(2 downto 0);
res : out unsigned(7 downto 0));
end dec1_8;

architecture comb of dec1_8 is
begin
res <= "00000001" when sel = "000" else
"00000010" when sel = "001" else
"00000100" when sel = "010" else
"00001000" when sel = "011" else
"00010000" when sel = "100" else
"00100000" when sel = "101" else
"01000000" when sel = "110" else
"10000000";
end comb;
```

Digital Design with Synthesizable VHDL - p. 2

Priority Encoder



```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity priority is
    port (
        sel : in std_logic_vector(7 downto 0);
        code : out unsigned(2 downto 0));
end priority;

architecture imp of priority is
begin
    code <= "000" when sel(0) = '1' else
            "001" when sel(1) = '1' else
            "010" when sel(2) = '1' else
            "011" when sel(3) = '1' else
            "100" when sel(4) = '1' else
            "101" when sel(5) = '1' else
            "110" when sel(6) = '1' else
            "111";
end imp;
```

Digital Design with Synthesizable VHDL - p. 2

Integer Arithmetic



```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity adder is
    port (
        A, B : in unsigned(7 downto 0);
        CI : in std_logic;
        SUM : out unsigned(7 downto 0);
        CO : out std_logic);
end adder;

architecture imp of adder is
    signal tmp : unsigned(8 downto 0);
begin
    tmp <= A + B + ("0" & ci); -- trick to promote ci to unsigned
    SUM <= tmp(7 downto 0);
    CO <= tmp(8);
end imp;
```

Digital Design with Synthesizable VHDL - p. 2

A Very Simple ALU

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity alu is
    port (
        A, B : in unsigned(7 downto 0);
        ADD : in std_logic;
        RES : out unsigned(7 downto 0));
end alu;

architecture imp of alu is
begin
    RES <= A + B when ADD = '1' else
           A - B;
end imp;
```

Digital Design with Synthesizable VHDL - p. 3

Arithmetic Comparison

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity comparator is
    port (
        A, B : in unsigned(7 downto 0);
        GE : out std_logic);
end comparator;

architecture imp of comparator is
begin
    GE <= '1' when A >= B else '0';
end imp;
```

Digital Design with Synthesizable VHDL - p. 3

Tri-state drivers

How to use a pin as both an input and output.
Not for internal FPGA signals.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity tri_demo is
    port(addr : out unsigned(15 downto 0); -- output only
         data : inout unsigned(7 downto 0)); -- bidirectional
end tri_demo;

architecture rtl of tri_demo is
    signal oe : std_logic; -- output enable: control direction of data
    signal d_out : unsigned(7 downto 0);
begin
    data <= d_out when oe = '1' else -- Drive data to chip
           (others => 'Z'); -- Read data from external chip
end rtl;
```

Digital Design with Synthesizable VHDL - p. 3

Syntax of Expressions

Logical operators: **and or xor nand nor**
 Relational operators: **= /= < <= > >=**
 Additive operators: **+ - &** (concatenation)
 Multiplicative operators: *** / mod rem**
 Others: **abs not **** (exponentiation)
 Primaries: identifier
 literal
 name(expr to expr)
 name(expr downto expr)
 (choice (| choice) * => expr)

Digital Design with Synthesizable VHDL - p. 3

Summary of Dataflow Modeling

- Conditional signal assignment (when...else)
`target <= (expr when expr else)*
 expr ;`
- Selected signal assignment (with...select)
`with expr select
 target <= (expr when choice (| choice)*,)*
 expr when choice (| choice)* ;`
 A *choice* is a simple expression (i.e., not logical or comparison) or **others**.

Note: **when** does not nest (i.e., it's not an *expr*).

Digital Design with Synthesizable VHDL - p. 3

Hierarchy: Instantiating components (entities)


Hierarchy: port map positional style

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity add2 is
    port (A, B : in unsigned(1 downto 0);
         C : out unsigned(2 downto 0));
end add2;

architecture imp of add2 is
    component full_adder
    port (a, b, c : in std_logic;
         sum, carry : out std_logic);
    end component;

     signal carry : std_logic;
begin
    bit0 : full_adder port map ( A(0), B(0), '0', C(0), carry );
    bit1 : full_adder port map ( A(1), B(1), carry, C(1), C(2) );
end imp;
```



Digital Design with Synthesizable VHDL - p. 3

Hierarchy: port map by-name style

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity add2n is
  port (A, B : in unsigned(1 downto 0);
        C : out unsigned(2 downto 0));
end add2n;
architecture imp of add2n is
  component full_adder
  port (a, b, c : in std_logic;
        sum, carry : out std_logic);
  end component;
  signal carry : std_logic;
begin
  bit0 : full_adder port map (a => A(0), b => B(0), c => '0',
                             sum => C(0), carry => carry);

  bit1 : full_adder port map (a => A(1), b => B(1), c => carry,
                             sum => C(1), carry => C(2));
end imp;
```

Digital Design with Synthesizable VHDL - p. 3

Direct Instantiation (no component)

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity add2 is
  port (A, B : in unsigned(1 downto 0);
        C : out unsigned(2 downto 0));
end add2;

architecture imp of add2 is
  signal carry : std_logic;
begin
  bit0 : entity work.full_adder -- everything in "work" project
  port map ( A(0), B(0), '0', C(0), carry );

  bit1 : entity work.full_adder
  port map ( A(1), B(1), carry, C(1), C(2) );
end imp;

Must be compiled after full_adder.vhd!
```

Digital Design with Synthesizable VHDL - p. 3

Generate: Ripple-carry adder

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity rippleadder is
  port (a, b : in unsigned(3 downto 0);
        cin : in std_logic;
        sum : out unsigned(3 downto 0);
        cout : out std_logic);
end rippleadder;

architecture imp of rippleadder is
  signal c : unsigned(4 downto 0);
begin
  generate G1:
  c(0) <= cin;
  for m in 0 to 3 generate -- expanded at compile time
    sum(m) <= a(m) xor b(m) xor c(m);
    c(m+1) <= (a(m) and b(m)) or (b(m) and c(m)) or
              (a(m) and c(m));
  end generate G1;
  cout <= c(4);
end imp;
```

Digital Design with Synthesizable VHDL - p. 3

Combinational Logic in a Procedural Style

Digital Design with Synthesizable VHDL - p. 4

Processes

Process: sequential code fragment invoked when signal in sensitivity list changes.
A correct, but dumb way to model an inverter:

```
library ieee;
use ieee.std_logic_1164.all;

entity dumb_inv is
  port( a : in std_logic; y : out std_logic );
end dumb_inv;

architecture comb of dumb_inv is
begin
  process (a) -- invoked when signal a changes
  begin
    if a = '1' then y <= '0'; else y <= '1'; end if;
  end process;
end comb;
```

Digital Design with Synthesizable VHDL - p. 4

A 4-to-1 mux in the procedural style

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity pmultiplexer_4_1 is
  port(in0, in1, in2, in3 : in unsigned(15 downto 0);
        s : in unsigned(1 downto 0);
        z : out unsigned(15 downto 0));
end pmultiplexer_4_1;

architecture comb of pmultiplexer_4_1 is
begin
  process (in0, in1, in2, in3, s)
  begin
    z <= (others => 'X'); -- default
    if s = "00" then z <= in0; -- assignment overrides default
    elsif s = "01" then z <= in1;
    elsif s = "10" then z <= in2;
    elsif s = "11" then z <= in3;
    end if;
  end process;
end comb;
```

Digital Design with Synthesizable VHDL - p. 4

A 4-to-1 mux using case

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity cmultiplexer_4_1 is
  port(in0, in1, in2, in3 : in unsigned(15 downto 0);
        s : in unsigned(1 downto 0);
        z : out unsigned(15 downto 0));
end cmultiplexer_4_1;
architecture comb of cmultiplexer_4_1 is
begin
  process (in0, in1, in2, in3, s)
  begin
    case s is
      when "00" => z <= in0;
      when "01" => z <= in1;
      when "10" => z <= in2;
      when "11" => z <= in3;
      when others => z <= (others => 'X');
    end case;
  end process;
```

Digital Design with Synthesizable VHDL - p. 4

An Address Decoder

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity adecoder is
  port(a : in unsigned(15 downto 0);
        ram, rom, video, io : out std_logic);
end adecoder;

architecture proc of adecoder is
begin
  process (a)
  begin
    ram <= '0'; rom <= '0'; video <= '0'; io <= '0';
    if a(15) = '0' then ram <= '1'; -- 0000-7FFF
    elsif a(14 downto 13) = "00" then video <= '1'; -- 8000-9FFF
    elsif a(14 downto 12) = "101" then io <= '1'; -- D000-DFFF
    elsif a(14 downto 13) = "11" then rom <= '1'; -- E000-FFFF
    end if;
  end process;
```

Digital Design with Synthesizable VHDL - p. 4

Summary of Procedural Modeling

- null
- `signal <= expr ;`
- `variable := expr ;`
- `if expr then stmts (elsif expr then stmts)* (else stmts)? end if;`
- `case expr is (when choices => stmts)* end case;`

Note: when...else and with...select not allowed

Digital Design with Synthesizable VHDL - p. 4

Sequential Logic

Digital Design with Synthesizable VHDL - p. 4

Basic D Flip-Flop


```
library ieee;
use ieee.std_logic_1164.all;

entity flipflop is
  port (Clk, D : in std_logic;
        Q      : out std_logic);
end flipflop;

architecture imp of flipflop is
begin

  process (Clk) -- Sensitive only to Clk
  begin
    if rising_edge(Clk) then -- Only on the rising edge of Clk
      Q <= D;
    end if;
  end process;

end imp;
```




Digital Design with Synthesizable VHDL - p. 4

Flip-Flop with Latch Enable

```
library ieee;
use ieee.std_logic_1164.all;
entity flipflop_enable is
  port (Clk, Reset, D, EN : in std_logic;
        Q                  : out std_logic);
end flipflop_enable;

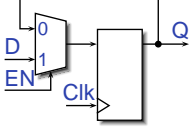architecture imp of flipflop_enable is
begin
  process (Clk)
  begin
    if rising_edge(Clk) then
      if EN = '1' then
        Q <= D;
      end if;
    end if;
  end process;
end imp;
```



Digital Design with Synthesizable VHDL - p. 4

Flip-Flop with Synchronous Reset

```
library ieee;
use ieee.std_logic_1164.all;
entity flipflop_reset is
  port (Clk, Reset, D : in std_logic;
        Q              : out std_logic);
end flipflop_reset;


architecture imp of flipflop_reset is
begin
  process (Clk)
  begin
    if rising_edge(Clk) then
      if Reset = '1' then
        Q <= '0';
      else
        Q <= D;
      end if;
    end if;
  end process;
end imp;
```

Digital Design with Synthesizable VHDL - p. 4

Four-bit binary counter

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity counter is
  port (Clk, Reset : in std_logic;
        Q           : out unsigned(3 downto 0));
end counter;

architecture imp of counter is
  signal count : unsigned(3 downto 0);
begin
  process (Clk)
  begin
    if rising_edge(Clk) then
      if Reset = '1' then count <= (others => '0');
      else count <= count + 1;
      end if;
    end if;
  end process;
  Q <= count; -- copy count to output
end imp;
```



Digital Design with Synthesizable VHDL - p. 5

Eight-bit serial in/out shift register

```
library ieee;
use ieee.std_logic_1164.all;

entity shifter is
  port (Clk, SI : in std_logic;
        SO      : out std_logic);
end shifter;

architecture impl of shifter is
  signal tmp : std_logic_vector(7 downto 0);
begin
  process (Clk)
  begin
    if rising_edge(Clk) then
      tmp <= tmp(6 downto 0) & SI; -- & is concatenation
    end if;
  end process;

  SO <= tmp(7); -- Copy to output
end impl;
```

Digital Design with Synthesizable VHDL - p. 5

Synchronous RAM

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity ram_32_4 is
  port (
    Clk, WE : in std_logic; -- Clock and write enable
    addr    : in unsigned(4 downto 0);
    di      : in unsigned(3 downto 0); -- Data in
    do      : out unsigned(3 downto 0)); -- Data out
end ram_32_4;

architecture imp of ram_32_4 is
  type ram_type is array(0 to 31) of unsigned(3 downto 0);
  signal RAM : ram_type;
begin
  process (Clk) begin
    if rising_edge(Clk) then
      if we = '1' then RAM(TO_INTEGER(addr)) <= di;
        do <= di; -- write-through
      else do <= RAM(TO_INTEGER(addr));
    end if; end if;
  end process;
```

Digital Design with Synthesizable VHDL - p. 5

A small ROM

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity rom_32_4 is
  port (Clk, en : in std_logic;
        addr    : in unsigned(3 downto 0);
        data    : out unsigned(3 downto 0));
end rom_32_4;

architecture imp of rom_32_4 is
  type rom_type is array (0 to 15) of unsigned(3 downto 0);
  constant ROM : rom_type :=
    (X"1", X"2", X"3", X"4", X"5", X"6", X"7", X"8",
     X"9", X"A", X"B", X"C", X"D", X"E", X"F", X"1");
begin
  process (Clk)
  begin
    if rising_edge(Clk) then
      if en = '1' then data <= ROM(TO_INTEGER(addr)); end if;
    end if;
  end process;
end imp;
```

Digital Design with Synthesizable VHDL - p. 5

Variables and Signals

```
library ieee; use ieee.std_logic_1164.all;
entity twoshiftreg is
  port (clk, si1, si2 : in std_logic; so1, so2 : out std_logic);
end twoshiftreg;
architecture imp of twoshiftreg is
  signal sr1 : std_logic_vector(1 downto 0); -- visible globally
begin
  process (clk)
  variable sr2 : std_logic_vector(1 downto 0); -- process-only
  begin
    if rising_edge(clk) then
      sr1(1) <= si1; -- Effect seen only after next clk
      sr1(0) <= sr1(1); -- Any order works
      so1 <= sr1(0);

      sr2(0) <= sr2(0);
      sr2(0) := sr2(1); -- Effect seen immediately
      sr2(1) := si2; -- Must be in this order
    end if;
  end process;
end imp;
```

Digital Design with Synthesizable VHDL - p. 5

Variables vs. Signals

Property	Variables	Signals
Scope	Local to process	Visible throughout architecture
Assignment	Felt immediately (e.g., in next statement)	Only visible after clock rises (i.e., process terminates)

Lesson: use variables to hold temporary results and state to be hidden within a process. Otherwise, use signals.

Digital Design with Synthesizable VHDL - p. 5


Constants: A VGA sync generator

```
library ieee; use ieee.std_logic_1164.all; use ieee.numeric_std.all;
entity sync_gen is
  port (clk : in std_logic; hs, vs : out std_logic);
end sync_gen;

architecture rtl of sync_gen is
  constant HTOTAL : integer := 800; constant HSYNC : integer := 96;
  constant VTOTAL : integer := 525; constant VSYNC : integer := 2;
  signal hcount, vcount : unsigned(9 downto 0);
begin
  process (clk)
  begin
    if rising_edge(clk) then
      if hcount = HTOTAL - 1 then
        hcount <= (others => '0'); hs <= '1';
        if vcount = VTOTAL - 1 then
          vcount <= (others => '0'); vs <= '1';
        else
          if vcount = VSYNC then vs <= '0'; end if;
          vcount <= vcount + 1;
        end if;
      else
        if hcount = HSYNC then hs <= '0'; end if;
        hcount <= hcount + 1;
      end if;
    end if;
  end process;
end rtl;
```

Digital Design with Synthesizable VHDL - p. 5


Rocket Science: FSMs

 

This is a *Mealy* FSM: outputs may depend directly on inputs.

Digital Design with Synthesizable VHDL - p. 5

Moore FSMs

 

This is a *Moore* FSM: outputs come from state bits.

Digital Design with Synthesizable VHDL - p. 5

Coding Moore State Machines

```
library ieee; use ieee.std_logic_1164.all;
entity threecount is
  port (clk, reset, count : in std_logic; at0 : out std_logic);
end threecount;
architecture moore of threecount is
  type states is (ZERO, ONE, TWO); -- States encoded automatically
begin
  process (clk)
  variable state : states;
  begin
    if rising_edge(clk) then
      if reset = '1' then state := ZERO;
      else case state is
            when ZERO => if count = '1' then state := ONE; end if;
            when ONE  => if count = '1' then state := TWO; end if;
            when TWO  => if count = '1' then state := ZERO; end if;
          end case;
      if state = ZERO then at0 <= '1'; else at0 <= '0'; end if;
    end if;
  end process; end moore;
```

Digital Design with Synthesizable VHDL - p. 5


Coding Mealy State Machines

```
architecture mealy of ... is
  type states is (IDLE, STATE1, ...);
  signal state, next_state : states;
begin
  process (clk) -- Sequential process
  begin
    if rising_edge(clk) then state <= next_state; end if;
  end process;

  process (reset, state, i1, i2, ...) -- Combinational process
  begin
    next_state <= state; -- Default: hold
    if reset = '1' then
      next_state <= IDLE;
    else
      case state is
        when IDLE =>
          if i1 = '1' then
            next_state <= STATE1;
          end if;
        when STATE1 =>
          ...
      end case;
    end if;
  end process;
end mealy;
```

Digital Design with Synthesizable VHDL - p. 5


The Traffic Light Controller

 

This controls a traffic light at the intersection of a busy highway and a farm road. Normally, the highway light is green but if a sensor detects a car on the farm road, the highway light turns yellow then red. The farm road light then turns yellow then red until there are no cars or after a long timeout. Then, the farm road light turns yellow then red, and the highway light returns to green. The inputs to the machine are the car sensor, a short timeout signal, and a long timeout signal. The outputs are a timer start signal and the colors of the highway and farm road lights.

Source: Mead and Conway, *Introduction to VLSI Systems*, 1980, p. 85.

FSM for the Traffic Light Controller

 

C: Car sensor
S: Short timeout
L: Long timeout
T: Start timer

St	Hwy	Farm
HG	G	R
HY	Y	R
FG	R	G
FY	R	Y

Traffic Light Controller in VHDL

```
library ieee;
use ieee.std_logic_1164.all;
entity tlc is
  port (clk, reset : in std_logic;
        cars, short, long : in std_logic;
        highway_yellow, highway_red : out std_logic;
        farm_yellow, farm_red : out std_logic;
        start_timer : out std_logic);
end tlc;

architecture imp of tlc is
  type states is (HG, HY, FY, FG);
  signal state, next_state : states;
begin
  process (clk) -- Sequential process
  begin
    if rising_edge(clk) then
      state <= next_state;
    end if;
  end process;
end imp;
```

Digital Design with Synthesizable VHDL - p. 6

TLC in VHDL, continued

```
process (state, reset, cars, short, long)
begin
  if reset = '1' then
    start_timer <= '1'; next_state <= HG;
  else
    case state is
      when HG =>
        highway_yellow <= '0'; highway_red <= '0';
        farm_yellow <= '0'; farm_red <= '1';
        if cars = '1' and long = '1' then
          start_timer <= '1'; next_state <= HY;
        else start_timer <= '0'; next_state <= HG;
        end if;
      when HY =>
        highway_yellow <= '1'; highway_red <= '0';
        farm_yellow <= '0'; farm_red <= '1';
        if short = '1' then
          start_timer <= '1'; next_state <= FG;
        else start_timer <= '0'; next_state <= HY;
        end if;
    end case;
  end if;
end process;
```

Digital Design with Synthesizable VHDL - p. 6

TLC in VHDL, concluded

```
when FG =>
  highway_yellow <= '0'; highway_red <= '1';
  farm_yellow <= '0'; farm_red <= '0';
  if cars = '0' or long = '1' then
    start_timer <= '1'; next_state <= FY;
  else start_timer <= '0'; next_state <= FG;
  end if;
when FY =>
  highway_yellow <= '0'; highway_red <= '1';
  farm_yellow <= '1'; farm_red <= '0';
  if short = '1' then
    start_timer <= '1'; next_state <= HG;
  else start_timer <= '0'; next_state <= FY;
  end if;
end case;
end if;
end process;

end imp;
```

Digital Design with Synthesizable VHDL - p. 6

Digital Design with Synthesizable VHDL - p. 6

Summary of the Three Modeling Styles

Three Modeling Styles: Dataflow (1)

Combinational logic described by expressions

```
-- Simple case
a <= x and y;

-- When...else selector
b <= '1' when x = y else
  '0';

--- With..select selector
with x select
c <=
  '1' when '0',
  '0' when '1',
  'X' when others;
```

Digital Design with Synthesizable VHDL - p. 6

Procedural Combinational (2)

Combinational logic described by statements and expressions

```
process (x, y) -- Should be sensitive to every signal it reads
begin
  a <= x and y;
  if x = y then
    b <= '1';
  else
    b <= '0';
  end if;
  case x of
    '0' => c <= '1';
    '1' => c <= '0';
    others => c <= 'X';
  end case;
end process;
```

Digital Design with Synthesizable VHDL - p. 6


Three Styles: Procedural Sequential

Combinational logic driving flip-flops described by statements and expressions.

```
process (clk) -- Sensitive only to the clock
begin
  if rising_edge(clk) then -- Always check for rising edge
    a <= x and y;
    if x = y then
      b <= '1';
    else
      b <= '0';
    end if;
    case x of
      '0' => c <= '1';
      '1' => c <= '0';
      others => c <= 'X';
    end case;
  end if;
end process;
```

Digital Design with Synthesizable VHDL - p. 6

Ten Commandments of VHDL

 


Digital Design with Synthesizable VHDL - p. 7

I: Thou Shalt Design Before Coding

- Know the structure of what you are designing first.
- Draw a block diagram of the datapath
- Understand the timing (draw diagrams)
- Draw bubble-and-arc diagrams for FSMs
- Only once you have a design should you start coding in VHDL
- VHDL is only a way to ask for component


Digital Design with Synthesizable VHDL - p. 7

Block Diagram of a Character Gen.

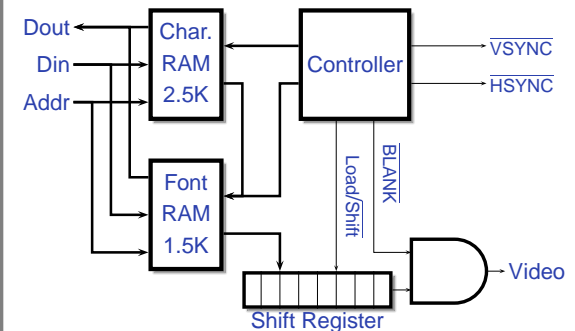


Digital Design with Synthesizable VHDL - p. 7


Pixel-Level Timing

 

Start-of-line Detail

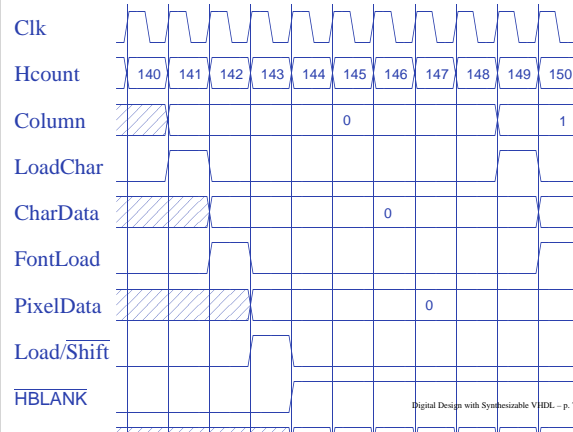

End-of-line detail

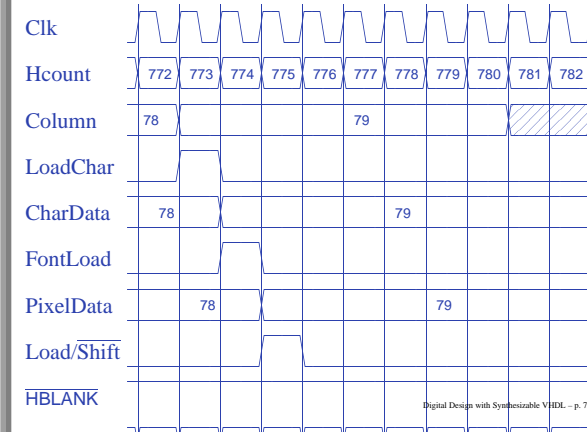

II: Thou Shalt be Synchronous

- One global clock
- Flip-flops generate inputs to combinational logic, which computes inputs to flip-flops
- Exactly one value per signal per clock cycle
- Do not generate asynchronous reset signals; only use them if they are external
- Edge-triggered flip-flops only. Do not use level-sensitive logic.
- Do not generate clock signals. Use multiplexers to create "load enable" signals on flip-flops.

Digital Design with Synthesizable VHDL - p.7

III: Thou Shalt Be Sensitive

Combinational processes: list all process inputs

```


process (state, long)
begin
  if reset = '1' then
    next_state <= HG;
    start_timer <= '1';
  else
    case state is
      when HG =>
        farm_yellow <= '0';
        if cars = '1' and long = '1' then
          next_state <= HY;
        else
          next_state <= HG;
        end if;
      when HY =>
        farm_yellow <= '0';
        if short = '1' then
          next_state <= FG;
        else
          next_state <= HY;
        end if;
    end case;
end process;


```

Digital Design with Synthesizable VHDL - p.7

III: Thou Shalt Be Sensitive

Sequential processes: always include the clock. Include reset if asynchronous, and nothing else.

```


process (Clk, D)
begin
  if rising_edge(Clk) then
    Q <= D;
  end if;
end process;

process (Clk, D, reset)
begin
  if reset = '1' then
    Q <= '0';
  else
    if rising_edge(Clk) then
      Q <= D;
    end if;
  end process;


```

Digital Design with Synthesizable VHDL - p.7

IV: Thou Shalt Assign All Outputs

Synthesis infers level-sensitive latches if sometimes you do not assign an output.

```


process (state, input)
begin
  case state is
    when S1 =>
      if input = '1' then
        output <= '0';
      end if;
    when S2 =>
      output <= '1';
    end case;
end process;


```

```

process (state, input)
begin
  case state is
    when S1 =>
      if input = '1' then
        output <= '0';
      else
        output <= '1';
      end if;
    when S2 =>
      output <= '1';
    end case;
end process;

```

Digital Design with Synthesizable VHDL - p.7

"Default" values are convenient

```

-- OK
process (state, input)
begin
  case state is
    when S1 =>
      if input = '1' then
        output <= '0';
      else
        output <= '1';
      end if;
    when S2 =>
      output <= '1';
    end case;
end process;

```

```

-- Better
process (state, input)
begin
  output <= '1';
  case state is
    when S1 =>
      if input = '1' then
        output <= '0';
      end if;
    end case;
end process;

```

Digital Design with Synthesizable VHDL - p.7

V: Thou Shalt Enumerate States

Better to use an enumeration to encode states:

```

type states is (START, RUN, IDLE, ZAPHOD);
signal current, next : states;

process (current)
begin
  case current is
    when START => ...
    when RUN => ...
    when IDLE => ...
  end case;
end process;

```

Running this produces a helpful error:

```

Compiling vhdl file "/home/cristi/cs4840/lab4/main.vhd" in Library work.
Entity <system> compiled.
ERROR:HDLParasers:813 - "/home/cristi/cs4840/lab4/main.vhd" Line 80.
Enumerated value zaphod is missing in case.
-->

```

Digital Design with Synthesizable VHDL - p.7

VI:



(There is no rule six)

VII: Thou Shalt Avoid Async

Only use asynchronous reset when there is one global signal from outside.

```
-- OK for external Reset
process (Clk, Reset)
begin
  if Reset = '1' then
    Q <= '0';
  else
    if rising_edge(Clk) then
      Q <= D;
    end if;
  end if;
end process;

-- Better
process (Clk)
begin
  if rising_edge(Clk) then
    if Reset = '1' then
      Q <= '0';
    else
      Q <= D;
    end if;
  end if;
end process;
```

Never generate your own asynchronous reset.
Generating a synchronous reset is fine

VIII: Thou Shalt Have One Version

- Never assume signals from the test bench that are not there on the board
- It is hard enough to make simulation match the design; do not make it any harder
- If you must slow down hardware, carefully generate a slower clock and only use that clock globally.

IX: Thou Shalt Not Test For X Or Z

```
architecture behv of ALU is begin
  process (A,B,Sel) begin
    case Sel is
      when "00" => Res <= A + B;
      when "01" => Res <= A + (not B) + 1;
      when "1X" => Res <= A and B;
      when "1Z" => Res <= A or B;
      when others => Res <= "XX";
    end case;
  end process;
end behv;
```

```
architecture behv of ALU is begin
  process(A,B,Sel) begin
    case Sel is
      when "00" => Res <= A + B;
      when "01" => Res <= A + (not B) + 1;
      when "10" => Res <= A and B;
      when "11" => Res <= A or B;
      when others => Res <= "XX";
    end case;
  end process;
end behv;
```

This is legal VHDL, but the synthesized circuit won't behave like you expect.

X: Thou Shalt Not Specify Delays

- The wait statement can delay for a certain amount of time, e.g., "wait 10ns;"
- Only use it in test benches that are not meant to become hardware
- Do not use them in the design of your hardware

Pitfalls: Boolean vs. Std_logic

Don't assign Boolean to std_logic.

```
signal a : std_logic;
signal b : unsigned(7 downto 0);
```

```
a <= b = x"7E"; -- BAD: result is Boolean, not std_logic
```

```
a <= '1' when b = x"7E" else '0'; -- OK
```

Don't test std_logic in a Boolean context.

```
signal a, b, foo : std_logic;
```

```
if a then -- BAD: A is not Boolean
  foo <= '1';
end if;
```

```
b <= '0' when a else '1'; -- BAD: a is not Boolean
```

```
if a = '1' then -- OK
  foo <= '1';
end if;
```

Pitfalls: Inferring a Latch

In a combinational process, make sure all output signals are always assigned.

```
process (x, y)
begin
  if x = '1' then
    y <= '0';
  end if;
  -- BAD: y not assigned when x = '0', synthesis infers a latch
end process;
```

```
process (x, y)
begin
  y <= '1'; -- OK: y is always assigned
  if x = '1' then
    y <= '0';
  end if;
end process
```

Pitfalls: Reading Output Port

```
library ieee;
use ieee.std_logic_1164.all;
entity dont_read_output is
  port ( a : in std_logic;
        x, y : out std_logic );
end dont_read_output;
```

```
architecture BAD of dont_read_output is
begin
  x <= not a;
  y <= not x; -- Error: can't read an output port
end BAD;
```

```
architecture OK of dont_read_output is
signal x_sig : std_logic;
begin
  x_sig <= not a;
  x <= x_sig; -- x_sig just another name for x
  y <= not x_sig; -- OK
end OK;
```

Pitfalls: Complex Port Map Args

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity bad_port_map is end bad_port_map;
```

```
architecture BAD of bad_port_map is
component bar port (x : in unsigned(5 downto 0)); end component;
signal a : unsigned(3 downto 0);
begin
  mybar : bar port map (x => "000" & a); -- BAD
end BAD;
```

```
architecture OK of bad_port_map is
component bar port (x : in unsigned(5 downto 0)); end component;
signal a : unsigned(3 downto 0);
signal aa : unsigned(5 downto 0);
begin
  aa <= "000" & a;
  mybar : bar port map (x => aa); -- OK
end OK;
```

Pitfalls: Combinational Loops

You never really need them.

Drive every signal from exactly one process or concurrent assignment.

Don't build SR latches. Use D flip-flops instead.

Digital Design with Synthesizable VHDL - p. 9

Pitfalls: Clock Gating

Dangerous, difficult to get right.

Use a single, global clock and latch enables to perform the same function.

Digital Design with Synthesizable VHDL - p. 9

Pitfalls: Multiple Clock Domains

If you must, vary the phase and drive clocks directly from flip-flops.

Digital Design with Synthesizable VHDL - p. 9

Writing Testbenches

Digital Design with Synthesizable VHDL - p. 9

Testbenches

One of VHDL's key points: can describe hardware and environment together.

-- Explicit delays are allowed

```
clk <= not clk after 50 ns;
```

```
process
begin
  reset <= '0';
  wait 10 ns;      -- Explicit delay
  reset <= '1';
  wait for a = '1'; -- Delay for an event
  assert b = '1' report "b_did_not_rise" severity failure;
  assert c = '1' report "c=0" severity warning; -- or error or note
  wait for 50 ns; -- Delay for some time
  wait;          -- Halt this process
end process;
```

Digital Design with Synthesizable VHDL - p. 9

Testbench Methodology

- Always put testbench in a separate .vhd file since it cannot be synthesized.
- Instantiate block under test and apply desired inputs (clocks, other stimulus)
- Use **assert** to check conditions
- Try to emulate hardware environment as closely as possible (no special inputs, etc.)

Digital Design with Synthesizable VHDL - p. 9

A Testbench

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity tlc_tb is -- A testbench usually has no ports
end tlc_tb;

architecture tb of tlc_tb is
  signal clk : std_logic := '0'; -- Must initialize!

  -- One signal per port is typical
  signal reset, cars, short, long : std_logic;
  signal farm_red, start_timer : std_logic;
begin

  clk <= not clk after 34.92 ns; -- 14 MHz
```

Digital Design with Synthesizable VHDL - p. 9

A testbench continued

```
-- Apply stimulus and check the results
process
begin
  cars <= '0'; short <= '0'; long <= '0'; reset <= '1';
  wait for 100 ns;
  assert start_timer = '1' report "No_timer" severity error;
  reset <= '0';
  wait for 100 ns;
  assert farm_red = '1' report "Farm_not_red" severity error;
  wait;
end process;

-- Instantiate the Unit Under Test
 uut : entity work.tlc
  port map ( clk => clk,      reset => reset,
            cars => cars,    short => short,
            long => long,    farm_red => farm_red,
            start_timer => start_timer);
```

Digital Design with Synthesizable VHDL - p. 9