

CSEE W3827

Fundamentals of Computer Systems Homework Assignment 3

Profs. Stephen A. Edwards & Martha Kim
Columbia University

Due February 27th, 2012 at 1:10 PM

Write your name **and UNI** on your solutions


Show your work for each problem; we are more interested in how you get the answer than whether you get the right answer.

1. (25 pts.) A sequential circuit with two D flip-flops S_0 and S_1 , two inputs X and Y , and one output Z behaves according to these equations:

$$S'_0 = \bar{X}S_0 + XY \quad S'_1 = \bar{X}S_1 + XS_0 \quad Z = XS_1$$

- Draw the corresponding circuit. Label each of the signals mentioned above.
- Derive the state table (next state and output as a function of present state and input).
- Draw the corresponding bubble-and-arc diagram.

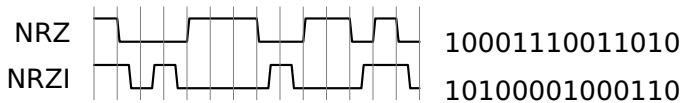2. (15 pts.) Many serial communication protocols, such as USB, use a signaling protocol known as “non return to zero, inverted” (NRZI) in which a “0” is represented as a transition and a “1” as no transition. Below is an example of a normal bit stream (NRZ) and how it would be encoded in NRZI as a waveform on the left and the corresponding bit streams on the right.




- Draw a Mealy bubble-and-arc diagram for an NRZ-to-NRZI protocol converter.
- Choose an encoding for your state machine and write its (encoded) state table.
- Design and draw a circuit implementation of your converter using D flip-flops and gates.

3. (15 pts.) Determine the logic for a synchronous 4-bit decimal counter that counts $0,1,\dots,9,0,1,\dots$ in binary. It should have four outputs Q_1, Q_2, Q_4, Q_8 , (the subscripts indicate the value of each bit) each driven directly by a flip-flop.


Write Boolean expressions of the form $D_i = Q_i \oplus (\dots)$ for each flip-flop's input. (\oplus is XOR)

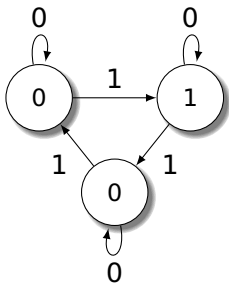4. (15 pts.) Using just three flip-flops and three two-input muxes, draw a circuit for the following Moore state machine with a single input and single output. Use a one-hot encoding. Each state is labeled with the value of the output.



5. (15 pts.)

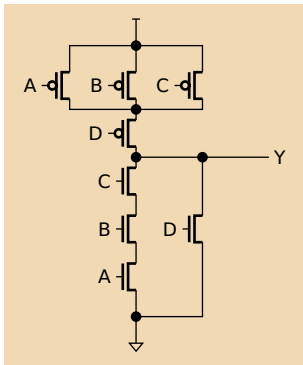- (a) Write a Boolean expression for the function of the following static CMOS gate.



- (b) Draw the schematic for a static CMOS gate that implements $Y = \overline{(A + B)C + D}$

6. (15 pts.) Show how to implement a two-bit priority encoder using the PLA drawn below.

Hint: write the expressions for Y and Z in sum-of-products form then draw crosses to indicate connections on the AND plane.

A	B	C	YZ
0	0	0	00
1	0	0	01
X	1	0	10
X	X	1	11

