


Memory

Stephen A. Edwards

Columbia University

Spring 2012

Early Memories

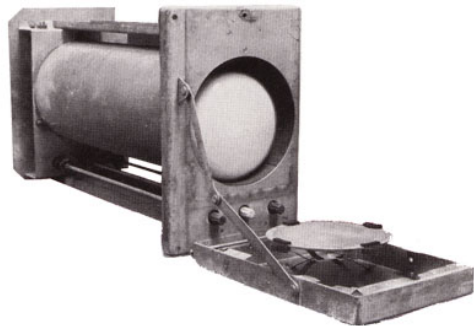

Williams Tube CRT-based random access memory, 1946. Used on the Manchester Mark I. 2048 bits.

Early Memories





Mercury acoustic
delay line.

Used in the EDASC,
1947.


32×17 bits

Early Memories

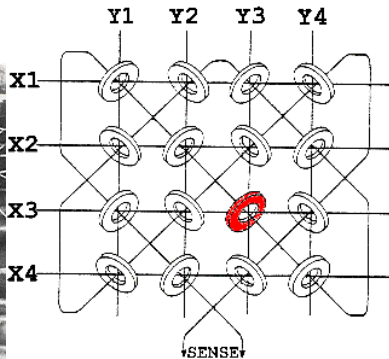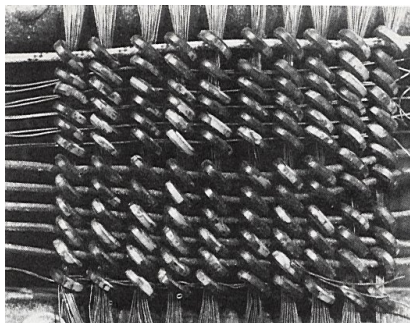


Magnetic core memory, 1952. IBM.

Early Memories

 


Magnetic drum memory. 1950s & 60s. Secondary storage.

Modern Memory Choices




	Family	Programmed	Persistence
	Mask ROM	at fabrication	∞
	PROM	once	∞
	EPROM	1000s, UV	10 years
	FLASH	1000s, block	10 years
	EEPROM	1000s, byte	10 years
	NVRAM	∞	5 years
	SRAM	∞	while powered
	DRAM	∞	64 ms

Implementing ROMs

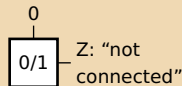


Add. Data

00	011
01	110
10	100
11	010

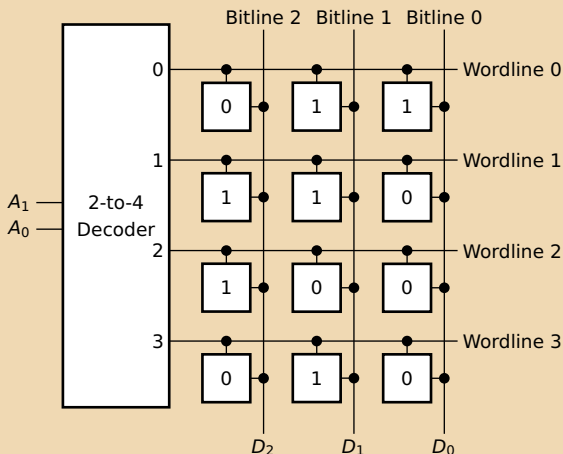


Implementing ROMs

 


Add. Data

00	011
01	110
10	100
11	010

 


Implementing ROMs

 


Add. Data

00	011
01	110
10	100
11	010

 


Implementing ROMs

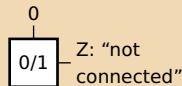


Add. Data


00	011
01	110
10	100
11	010

 

Mask ROM Die Photo

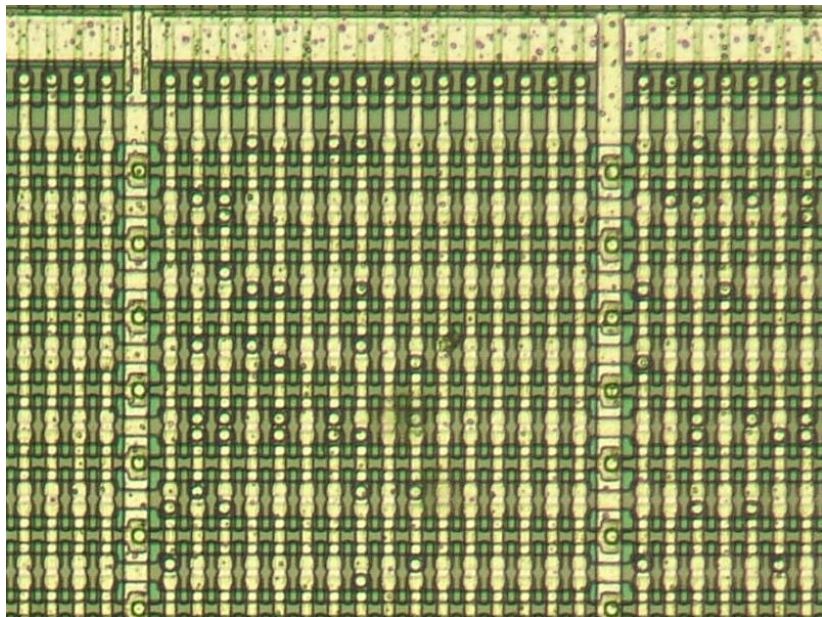


A Floating Gate MOSFET

 


Cross section of a NOR FLASH transistor. Kawai et al., ISSCC 2008 (Renesas)

Floating Gate n-channel MOSFET

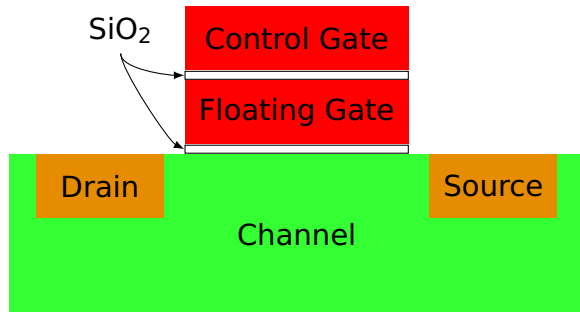


Floating gate uncharged; Control gate at 0V: Off

Floating Gate n-channel MOSFET

 


Floating gate uncharged; Control gate positive: On

Floating Gate n-channel MOSFET

 



Floating gate negative; Control gate at 0V: Off

Floating Gate n-channel MOSFET

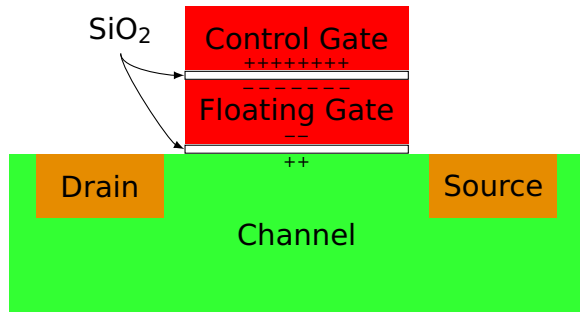


Floating gate negative; Control gate positive: Off


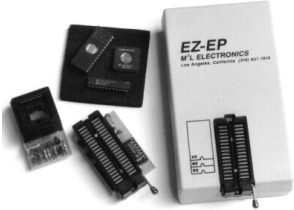
 
EPROMs and FLASH use Floating-Gate MOSFETs



Static Random-Access Memory Cell

 


Layout of a 6T SRAM Cell

   


Weste and Harris. *Introduction to CMOS VLSI Design*.
Addison-Wesley, 2010.


Intel's 2102 SRAM, 1024 × 1 bit, 1972

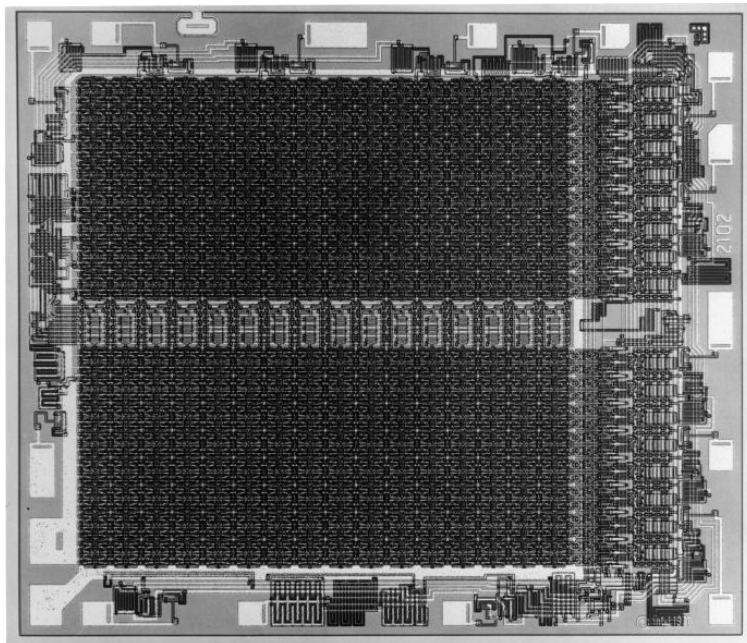


2102 Block Diagram

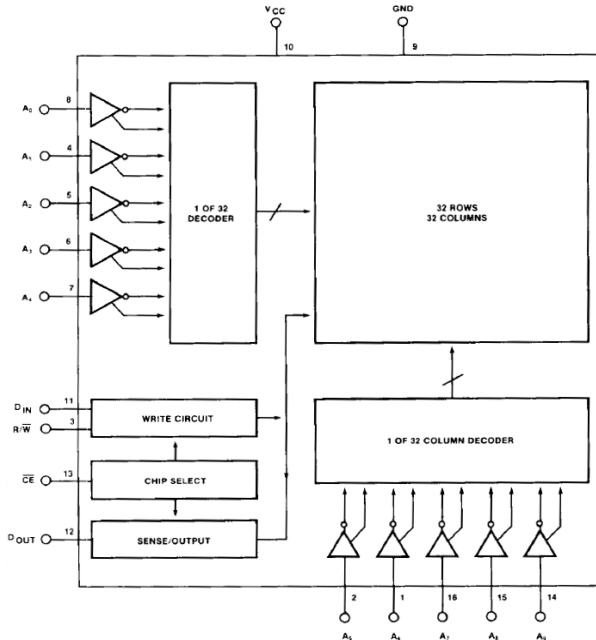



SRAM Timing

 



6264 SRAM Block Diagram

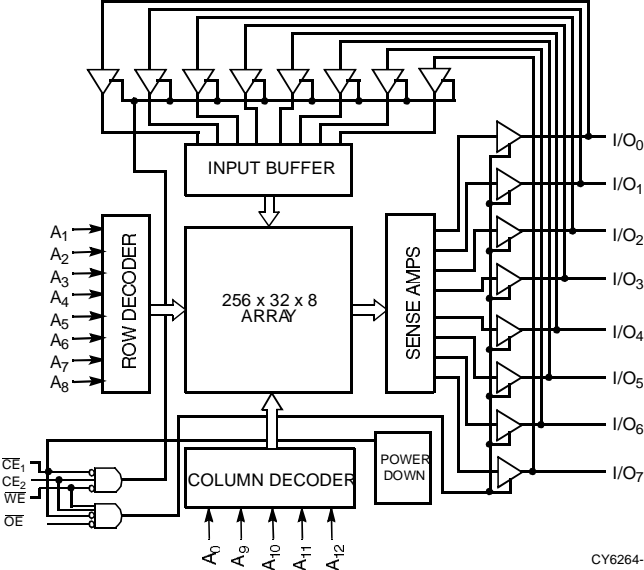


Toshiba TC55V16256J 256K × 16

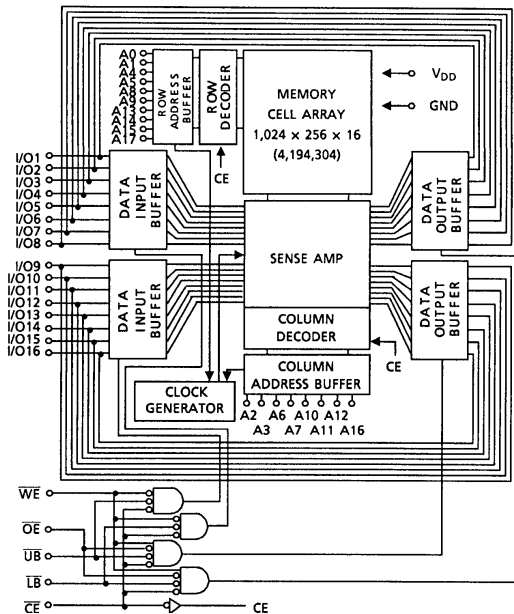 


Dynamic RAM Cell

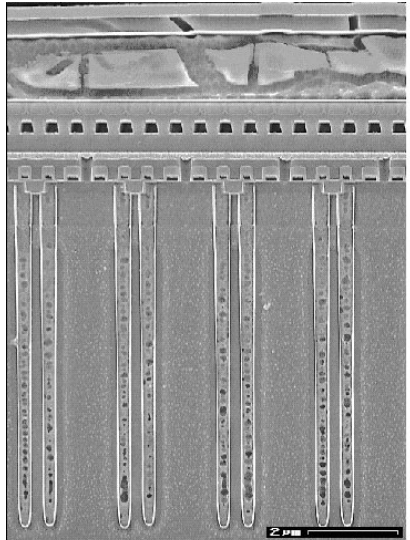 


Ancient (c. 1982) DRAM: 4164 64K × 1

 



Basic DRAM read and write cycles

 

Page Mode DRAM read cycle

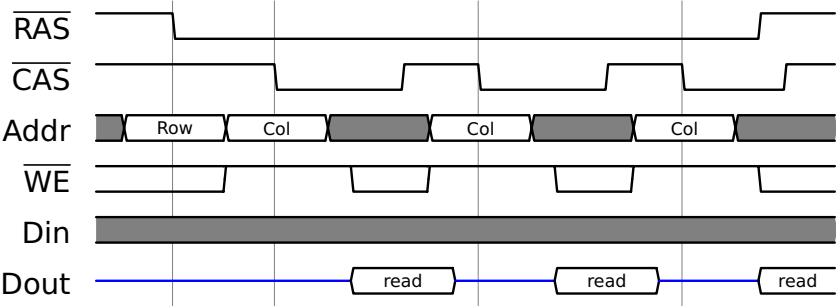

Samsung 8M x 16 SDRAM

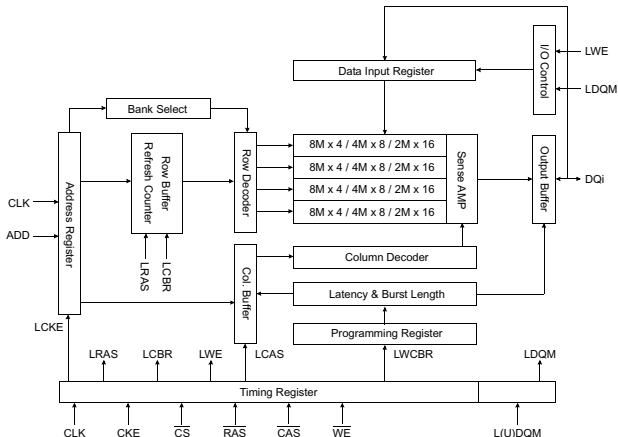 

SDRAM: Control Signals

$\overline{\text{RAS}}$	$\overline{\text{CAS}}$	$\overline{\text{WE}}$	Action
1	1	1	NOP
0	0	0	Load mode register
0	1	1	Active (select row)
1	0	1	Read (select column, start burst)
1	0	0	Write (select column, start burst)
1	1	0	Terminate Burst
0	1	0	Precharge (deselect row)
0	0	1	Auto Refresh

Mode register: selects 1/2/4/8-word bursts, CAS latency, burst on write

SDRAM: Timing with 2-word bursts

