

Fundamentals of Computer Systems

Sequential Logic

Stephen A. Edwards

Columbia University

Summer 2017

State-Holding Elements

- Bistable Elements

- RS Latch

- D Latch

- Positive-Edge-Triggered D Flip-Flop

- D Flip-Flop with Enable

Synchronous Digital Logic

- The Synchronous Paradigm

- Shift Registers

- Counters

Timing in Synchronous Circuits

- Flip-Flop Timing



- Timing in Synchronous Circuits

- Clock Skew





State-Holding Elements

Bistable Elements

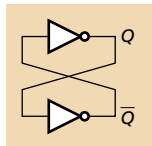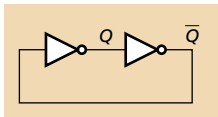


Equivalent circuits; right is more traditional.

Two stable states:

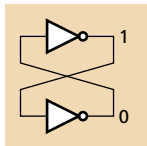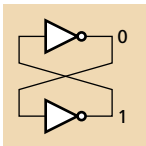


A Bistable in the Wild

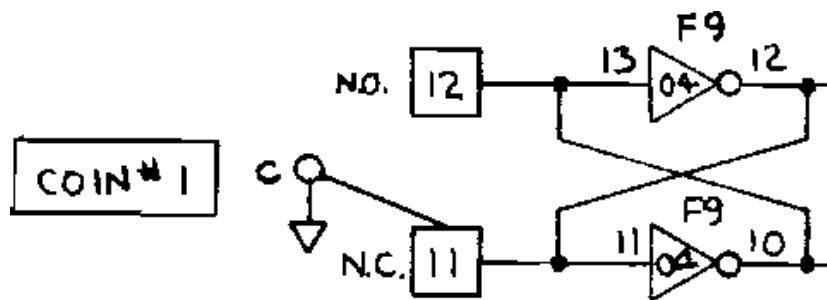

This "debounces" the coin switch.


Breakout, Atari 1976.

RS Latch

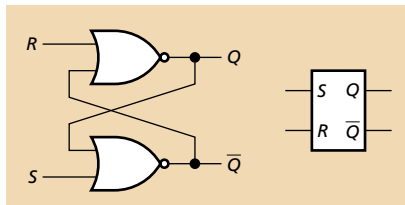

R	S	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		


RS Latch

 

R	S	Q	\bar{Q}	
0	0			
0	1	1	0	Set
1	0			
1	1			

R —
 S —
 Q — Set
 \bar{Q} —

RS Latch

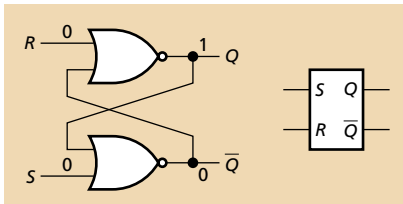

R	S	Q	\bar{Q}	
0	0	Q	\bar{Q}	Hold
0	1	1	0	Set
1	0			
1	1			

R _____


S _____

Q _____


\bar{Q} _____

Hold, State 1


RS Latch

 


R	S	Q	\bar{Q}	
0	0	Q	\bar{Q}	Hold
0	1	1	0	Set
1	0	0	1	Reset
1	1			

 


RS Latch

 


R	S	Q	\bar{Q}	
0	0	Q	\bar{Q}	Hold
0	1	1	0	Set
1	0	0	1	Reset
1	1			

 


RS Latch

 


R	S	Q	\bar{Q}	
0	0	Q	\bar{Q}	Hold
0	1	1	0	Set
1	0	0	1	Reset
1	1	0	0	Bad

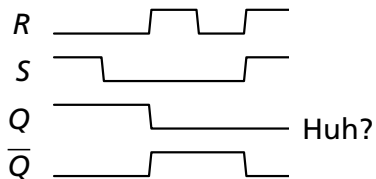


RS Latch

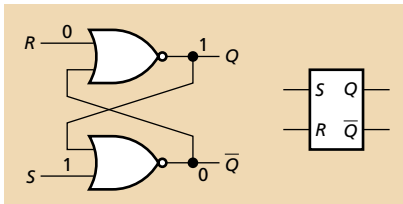


R	S	Q	\bar{Q}	
0	0	Q	\bar{Q}	Hold
0	1	1	0	Set
1	0	0	1	Reset
1	1	0	0	Bad

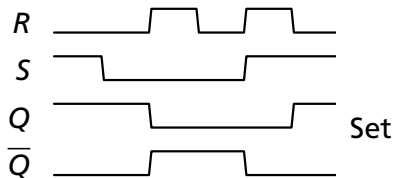

RS Latch

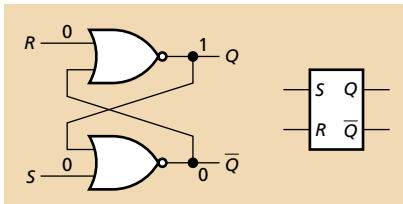


R	S	Q	\bar{Q}	
0	0	Q	\bar{Q}	Hold
0	1	1	0	Set
1	0	0	1	Reset
1	1	0	0	Bad

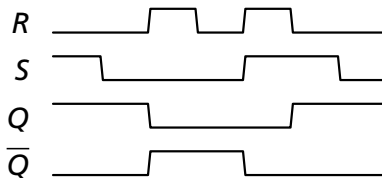


Hold, State 1

RS Latch

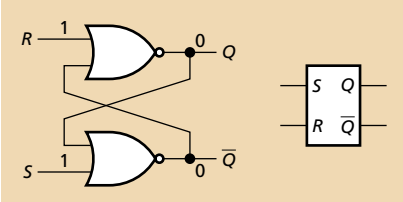


R	S	Q	Q̄	
0	0	Q	Q̄	Hold
0	1	1	0	Set
1	0	0	1	Reset
1	1	0	0	Bad

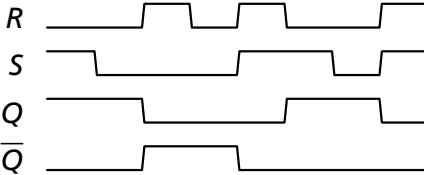


Huh?


RS Latch

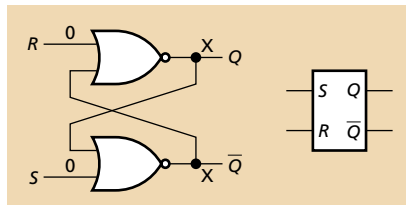

R	S	Q	\bar{Q}	
0	0	Q	\bar{Q}	Hold
0	1	1	0	Set
1	0	0	1	Reset
1	1	0	0	Bad

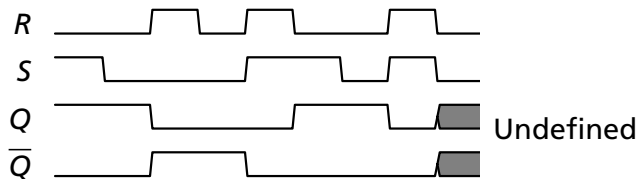


SR Latches in the Wild

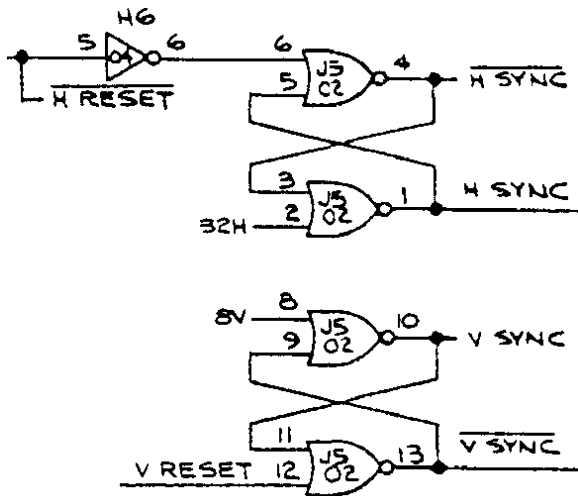

Generates horizontal and vertical synchronization waveforms from counter bits.

Stunt Cycle, Atari 1976.

D Latch

 


inputs		outputs	
C	D	Q	\bar{Q}
0	X	Q	\bar{Q}
1	0	0	1
1	1	1	0

A Challenge

A simple traffic light controller.

 Want the lights to cycle green-yellow-red.



Does this work?




















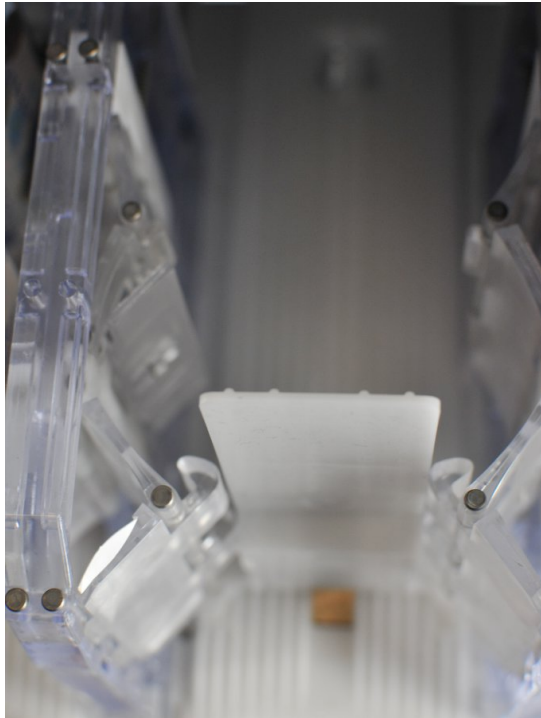

 


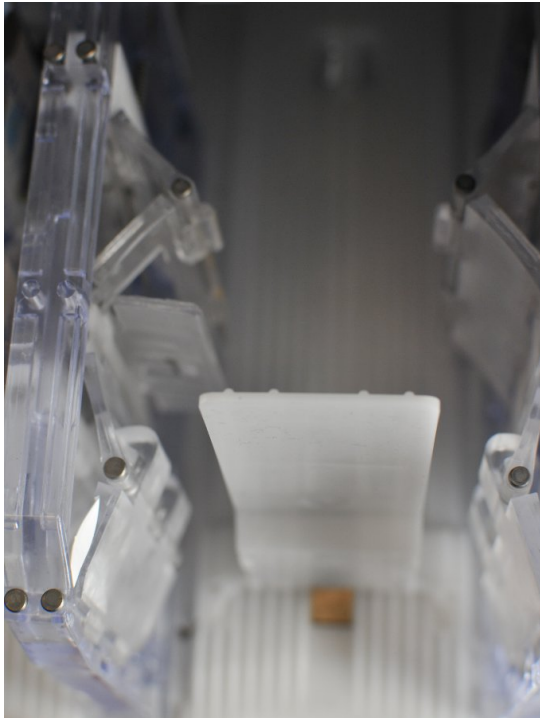

 


 


Positive-Edge-Triggered D Flip-Flop


 


- C _____
- D ██████████
- C_M transparent
- D' ██████████
- C_S opaque
- Q _____



Positive-Edge-Triggered D Flip-Flop

  



Positive-Edge-Triggered D Flip-Flop

  



Positive-Edge-Triggered D Flip-Flop

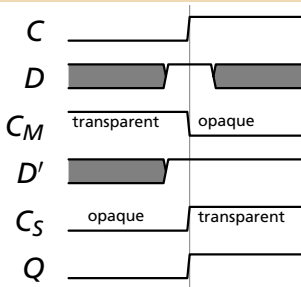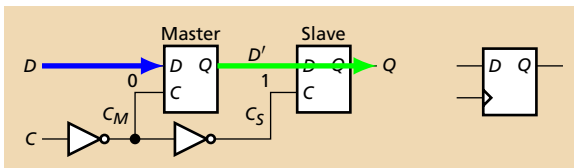

Positive-Edge-Triggered D Flip-Flop

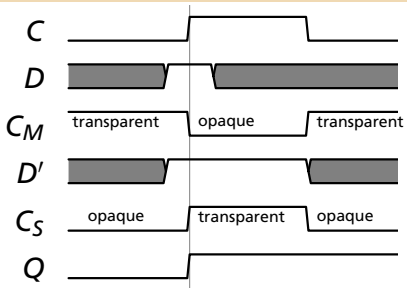 


Positive-Edge-Triggered D Flip-Flop

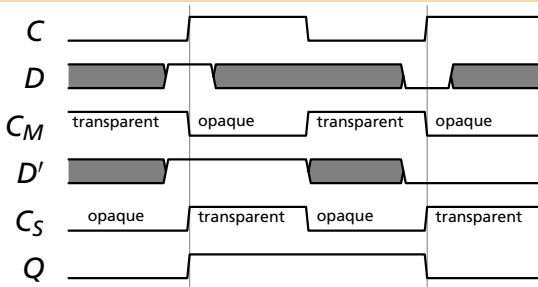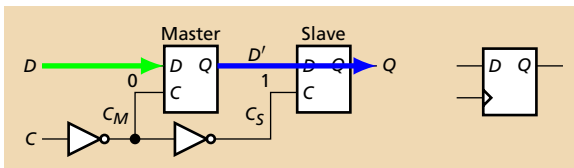

The Traffic Light Controller: A second try

Let's try this again with D flip-flops.

 

CLK ___



R ___

Y ___

G ___



The Traffic Light Controller: A second try

Let's try this again with D flip-flops.

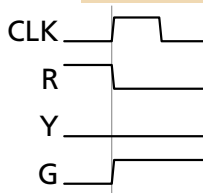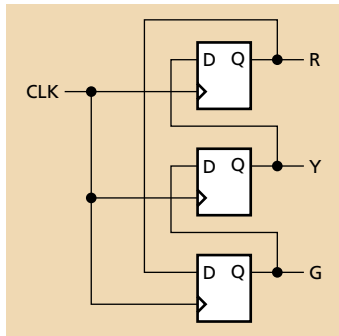



The Traffic Light Controller: A second try

Let's try this again with D flip-flops.

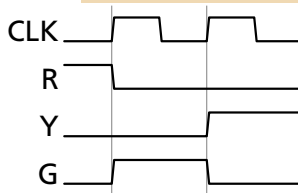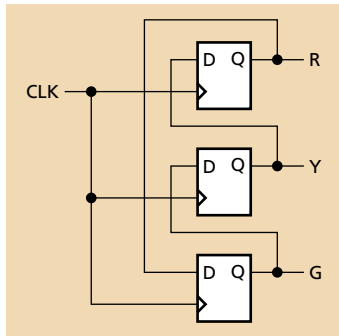



The Traffic Light Controller: A second try

Let's try this again with D flip-flops.

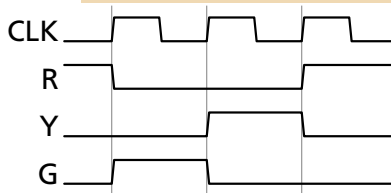 


The Traffic Light Controller: A second try

Let's try this again with D flip-flops.

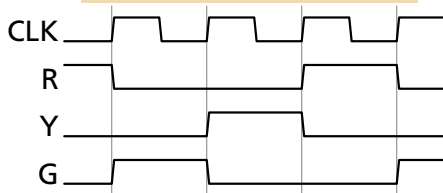
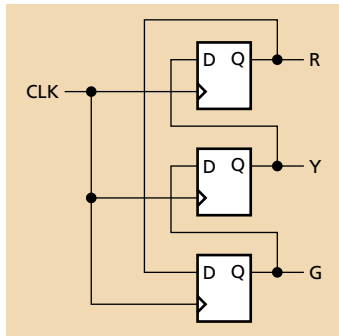


The Traffic Light Controller with Reset


 


CLK _____
RESET _____
R
Y
G



The Traffic Light Controller with Reset

 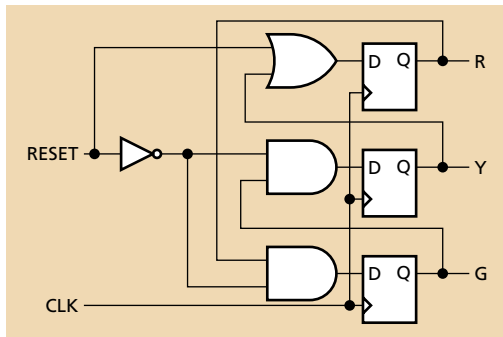



The Traffic Light Controller with Reset

 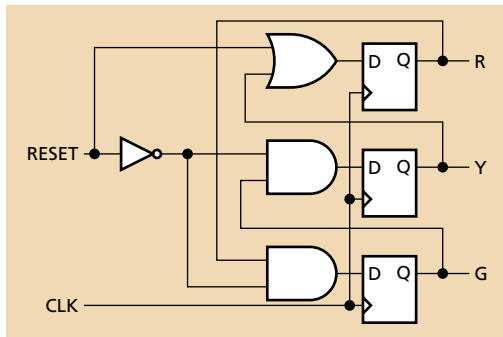



The Traffic Light Controller with Reset

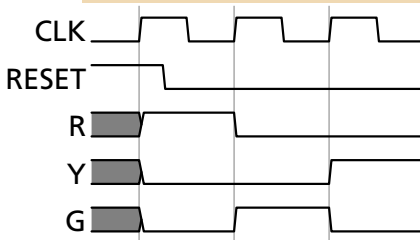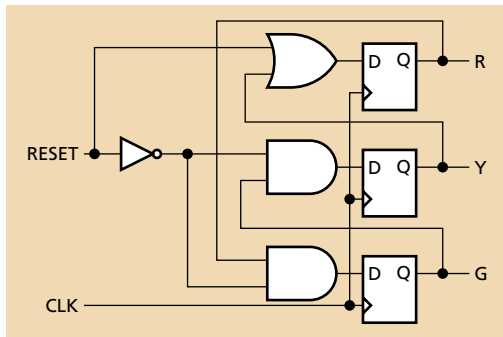


The Traffic Light Controller with Reset

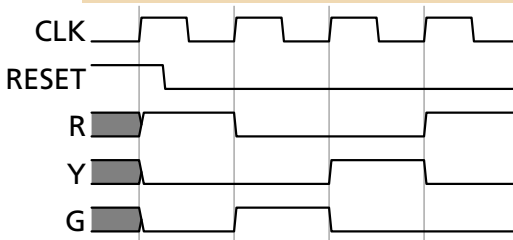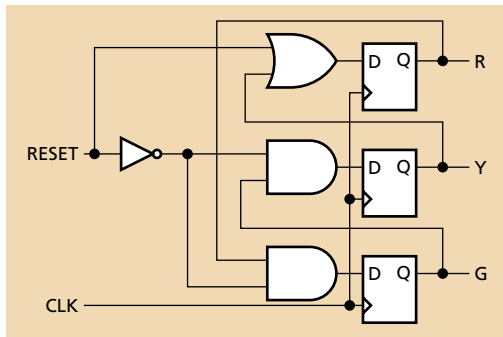


The Traffic Light Controller with Reset

 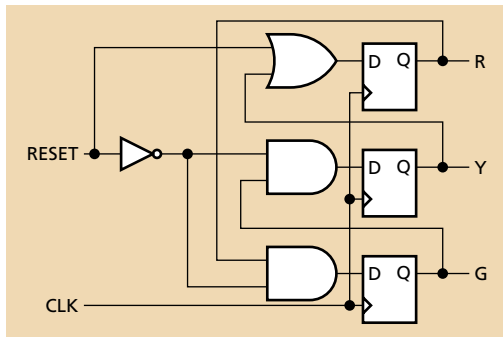

D Flip-Flop with Enable


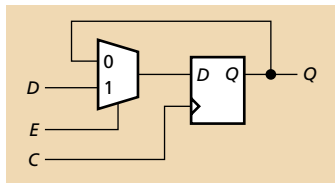


C	E	D	Q
↑	0	X	Q
↑	1	0	0
↑	1	1	1
0	X	X	Q
1	X	X	Q

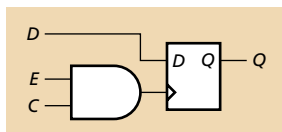


What's wrong with this solution?

Asynchronous Preset/Clear

  

 The Traffic Light Controller w/ Async. Reset




The Synchronous Digital Logic Paradigm


Gates and D
flip-flops only

Each flip-flop
driven by the
same clock

 Every cyclic
path contains
at least one
flip-flop




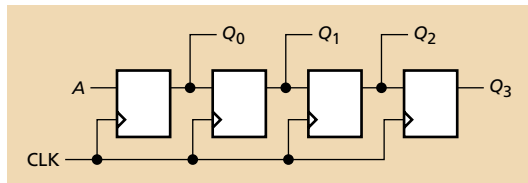Cool Sequential Circuits: Shift Registers



A	Q ₀	Q ₁	Q ₂	Q ₃
0	X	X	X	X
1	0	X	X	X
1	1	0	X	X
0	1	1	0	X
1	0	1	1	0
0	1	0	1	1
0	0	1	0	1
0	0	0	1	0
1	0	0	0	1
0	1	0	0	0

Universal Shift Register

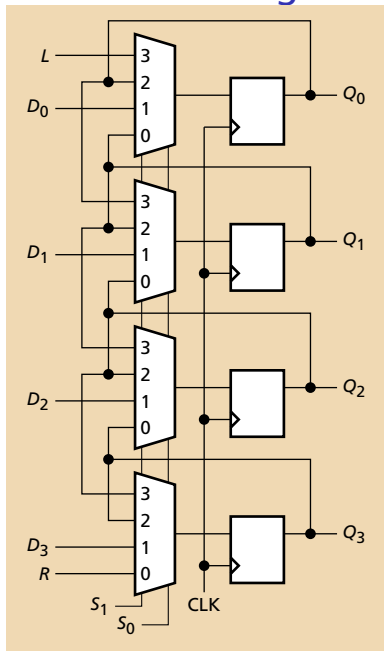


S_1	S_0	Q_3	Q_2	Q_1	Q_0
0	0	R	Q_3	Q_2	Q_1
0	1	D_3	D_2	D_1	D_0
1	0	Q_3	Q_2	Q_1	Q_0
1	1	Q_2	Q_1	Q_0	L


S_1	S_0	Operation
0	0	Shift right
0	1	Load
1	0	Hold
1	1	Shift left

Cool Sequential Circuits: Counters

 Cycle through sequences of numbers, e.g.,



The 74LS163 Synchronous Binary Counter

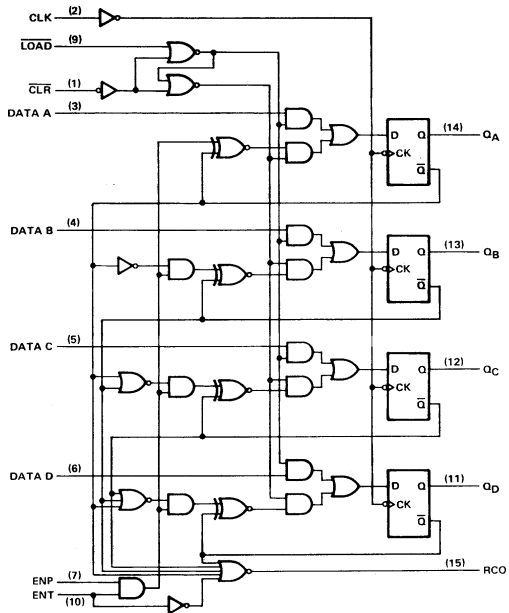

Implementing a 4-bit Binary Counter

Q_{8421}	D_{8421}	D_1	Q_1	D_2	D_4	D_8
0000	0001	1	0 0 1	0 1 0 1	0 0 1 0	0 0 0 0
0001	0010	Q_4 {	1 0 0 1	0 1 0 1	1 1 0 1	0 0 1 0
0010	0011		1 0 0 1	0 1 0 1	1 1 0 1	0 0 1 0
0011	0100		1 0 0 1	0 1 0 1	1 1 0 1	1 1 0 1
0100	0101		1 0 0 1	0 1 0 1	0 0 1 0	1 1 0 1
0101	0110		Q_2			
0110	0111	$D_1 = \bar{Q}_1$				
0111	1000	$D_2 = Q_1 \bar{Q}_2 + \bar{Q}_1 Q_2$				
1000	1001					
1001	1010	$D_4 = Q_1 Q_2 \bar{Q}_4 + \bar{Q}_1 Q_4 + \bar{Q}_2 Q_4$				
1010	1011					
1011	1100	$D_8 = Q_1 Q_2 Q_4 \bar{Q}_8 + \bar{Q}_2 Q_8 + \bar{Q}_1 Q_8 + \bar{Q}_4 Q_8$				Yuck
1100	1101					
1101	1110					
1110	1111					
1111	0000					

Implementing a 4-bit Binary Counter

Q_{8421}	D_{8421}	D_1	Q_1	D_2	D_4	D_8
0000	0001	1	0 0 1	0 1 0 1	0 0 1 0	0 0 0 0
0001	0010	Q_4	$\left\{ \begin{array}{l} 1 0 0 1 \\ 1 0 0 1 \\ 1 0 0 1 \\ 1 0 0 1 \end{array} \right\} Q_8$	0 1 0 1	1 1 0 1	0 0 1 0
0010	0011					
0011	0100					
0100	0101					
0101	0110		Q_2			
0110	0111	Trick: XOR each D with its Q				
0111	1000	$D_1 \oplus Q_1$	Q_1	$D_2 \oplus Q_2$	$D_4 \oplus Q_4$	$D_8 \oplus Q_8$
1000	1001					
1001	1010					
1010	1011	1	1 1 1	0 1 1 0	0 0 1 0	0 0 0 0
1011	1100	Q_4	$\left\{ \begin{array}{l} 1 1 1 1 \\ 1 1 1 1 \\ 1 1 1 1 \\ 1 1 1 1 \end{array} \right\} Q_8$	0 1 1 0	0 0 1 0	0 0 1 0
1100	1101					
1101	1110					
1110	1111					
1111	0000		Q_2			
		$D_1 \oplus Q_1 = 1$		$D_2 \oplus Q_2 = Q_1$		
		$D_4 \oplus Q_4 = Q_1 Q_2$		$D_8 \oplus Q_8 = Q_1 Q_2 Q_4$		

Implementing a 4-bit Binary Counter

Theorem:

If $X \oplus Y = Z$ then $X = Y \oplus Z$

Proof:

$X \oplus Y = Z$ (assumed)

$Y \oplus X \oplus Y = Y \oplus Z$ (apply $Y \oplus$)

$Y \oplus Y \oplus X = Y \oplus Z$ (\oplus commutes)

$X = Y \oplus Z$ ($y \oplus y \oplus x = x$)

So if

$$D_1 \oplus Q_1 = 1$$

$$D_2 \oplus Q_2 = Q_1$$

$$D_4 \oplus Q_4 = Q_1 Q_2$$


$$D_8 \oplus Q_8 = Q_1 Q_2 Q_4,$$

$$D_1 = Q_1 \oplus 1$$

$$D_2 = Q_2 \oplus Q_1$$


$$D_4 = Q_4 \oplus Q_1 Q_2$$

$$D_8 = Q_8 \oplus Q_1 Q_2 Q_4$$

 

Flip-Flop Timing

 
Setup Time: Time before the clock edge after which the data may not change



Flip-Flop Timing

Setup Time: Time before the clock edge after which the data may not change

 
Hold Time: Time after the clock edge after which the data may change



Flip-Flop Timing

Setup Time: Time before the clock edge after which the data may not change

 Hold Time: Time after the clock edge after which the data may change




Minimum Propagation Delay: Time from clock edge to when Q might start changing

Flip-Flop Timing

Setup Time: Time before the clock edge after which the data may not change


 
Hold Time: Time after the clock edge after which the data may change



Minimum Propagation Delay: Time from clock edge to when Q might start changing


Maximum Propagation Delay: Time from clock edge to when Q guaranteed stable

Timing in Synchronous Circuits

  


t_c : Clock period. E.g., 10 ns for a 100 MHz clock

Timing in Synchronous Circuits


 


Sufficient Hold Time?

 


Hold time constraint: how soon after the clock edge can D start changing? Min. FF delay + min. logic delay

Timing in Synchronous Circuits

  


Setup time constraint: when before the clock edge is D guaranteed stable? Max. FF delay + max. logic delay

Clock Skew: What Really Happens

 


Sufficient Hold Time?

 


CLK_2 arrives late: clock skew reduces hold time

Clock Skew: What Really Happens

 

Sufficient Setup Time?

 

CLK_2 arrives early: clock skew reduces setup time