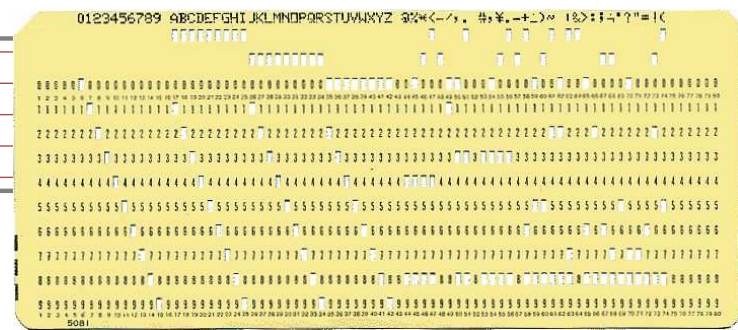


The VHDL Hardware Description Language

Prof. Stephen A. Edwards
sedwards@cs.columbia.edu

Columbia University
Spring 2007

Why HDLs?





1970s: SPICE transistor-level netlists

An XOR built from four NAND gates

```
.MODEL P PMOS
.MODEL N NMOS


.SUBCKT NAND A B Y Vdd Vss
M1 Y A Vdd Vdd P
M2 Y B Vdd Vdd P
M3 Y A X Vss N
M4 X B Vss Vss N
.ENDS
```
  
```
X1 A B I1 Vdd 0 NAND
X2 A I1 I2 Vdd 0 NAND
X3 B I1 I3 Vdd 0 NAND
X4 I2 I3 Y Vdd 0 NAND
```



Why HDLs?

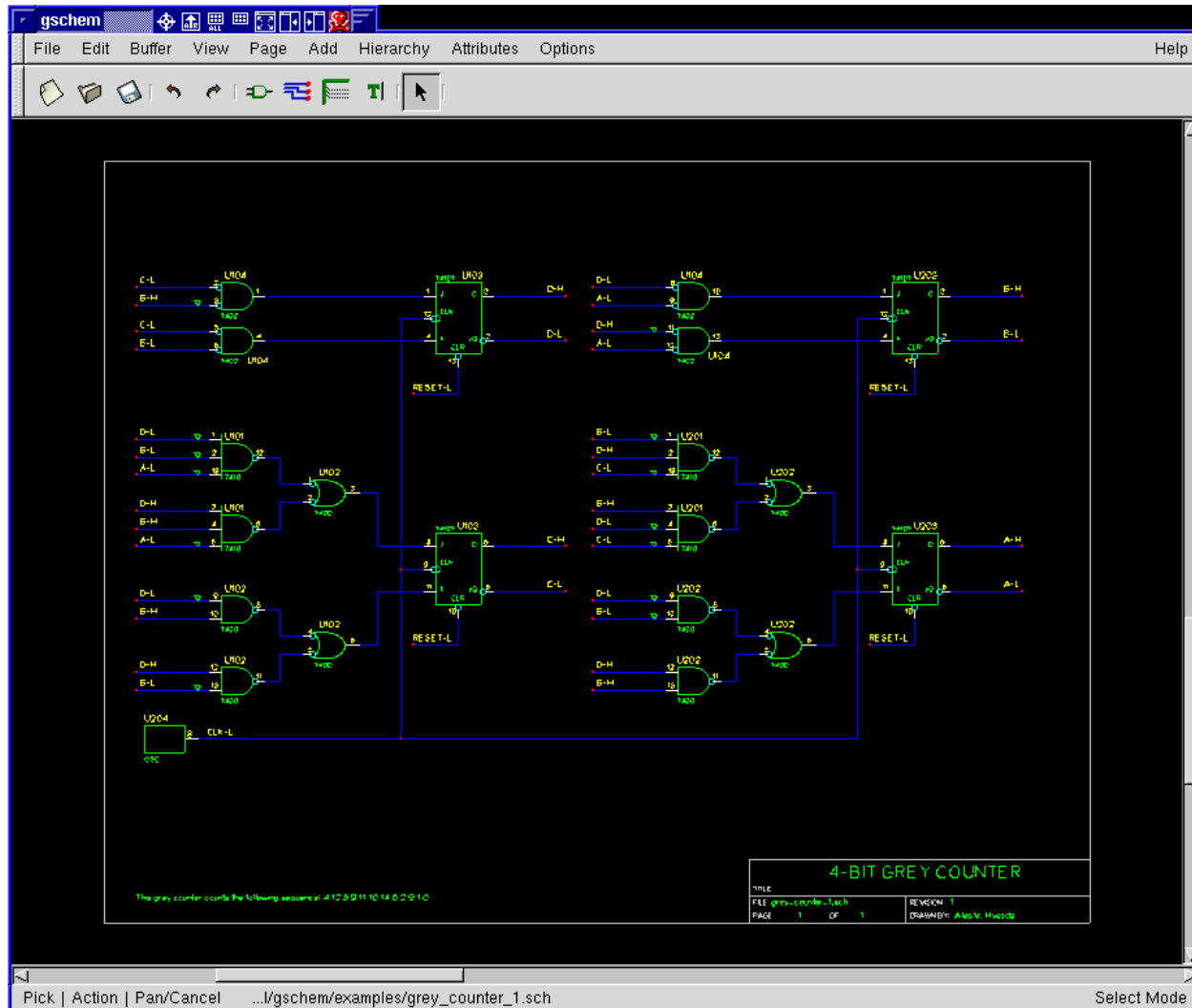
1980s: Graphical schematic capture programs



Why HDLs?

1990s: HDLs and Logic Synthesis

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;
entity ALU is
port(  A:      in std_logic_vector(1 downto 0);
      B:      in std_logic_vector(1 downto 0);
      Sel:    in std_logic_vector(1 downto 0);
      Res:    out std_logic_vector(1 downto 0));
end ALU;
architecture behv of ALU is begin
  process(A,B,Sel) begin
    case Sel is
      when "00" => Res <= A + B;
      when "01" => Res <= A + (not B) + 1;
      when "10" => Res <= A and B;
      when "11" => Res <= A or B;
      when others => Res <= "XX";
    end case;
  end process;
end behv;
```

 

Two Separate but Equal Languages



Verilog and VHDL


Verilog: More succinct, less flexible, really messy

VHDL: Verbose, very (too?) flexible, fairly messy

Part of languages people actually use identical.

Every synthesis system supports both.

VHDL: Hierarchical Models

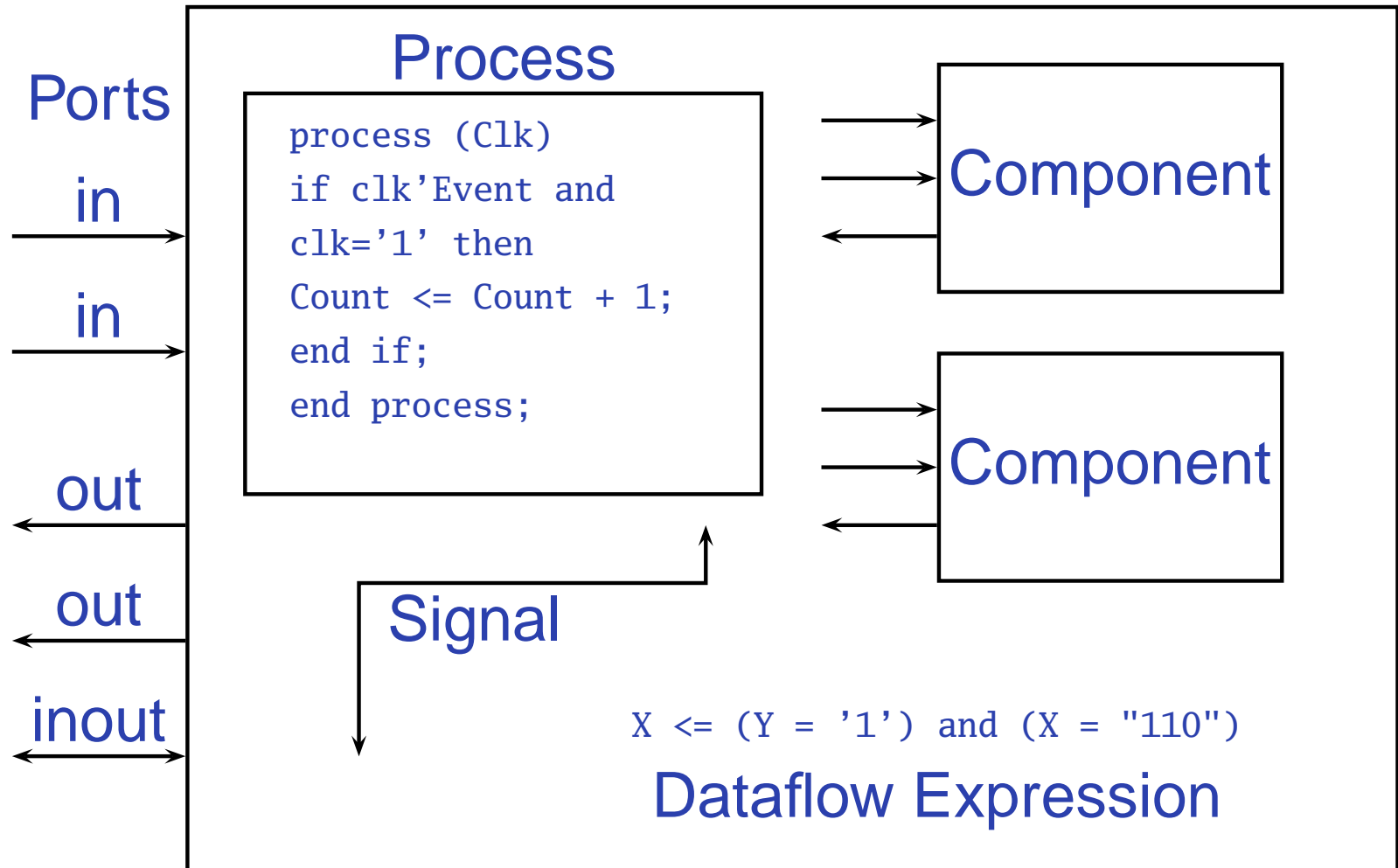


Basic VHDL: Full Adder



```
library ieee;                -- part of IEEE library
use ieee.std_logic_1164.all; -- includes std_ulogic
```

```
entity full_adder is
  port(a, b, c    : in  std_ulogic;
        sum, carry : out std_ulogic);
end full_adder;
```
 
```
architecture imp of full_adder is
begin
  sum    <= (a xor b) xor c;  -- combinational logic
  carry <= (a and b) or (a and c) or (b and c);
end imp;
```




VHDL: Two-bit Counter



```
library ieee;
use ieee.std_logic_1164.all;

entity add2 is
  port (
    A, B : in  std_logic_vector(1 downto 0);
    C     : out std_logic_vector(2 downto 0));
end add2;

architecture imp of add2 is
  component full_adder
    port (
      a, b, c      : in  std_ulogic;
      sum, carry   : out std_ulogic);
  end component;
  signal carry : std_ulogic;
begin
  bit0 : full_adder port map (
    a    => A(0),
    b    => B(0),
    c    => '0',
    sum  => C(0),
    carry => carry);
  bit1 : full_adder port map (
    a    => A(1),
    b    => B(1),
    c    => carry,
    sum  => C(1),
    carry => C(2));
end imp;
```

 

Four-to-one multiplexer: when...else

```
library ieee;
use ieee.std_logic_1164.all;

entity multiplexer_4_1 is
  port(in0, in1 : in  std_ulogic_vector(15 downto 0);
        in2, in3 : in  std_ulogic_vector(15 downto 0);
        s0, s1   : in  std_ulogic;
        z        : out std_ulogic_vector(15 downto 0));
end multiplexer_4_1;

architecture imp of multiplexer_4_1 is
begin
  z <= in0 when (s0 = '0' and s1 = '0') else
        in1 when (s0 = '1' and s1 = '0') else
        in2 when (s0 = '0' and s1 = '1') else
        in3 when (s0 = '1' and s1 = '1') else
        "XXXXXXXXXXXXXXXXXX";
end imp;
```

Four-to-one mux: with...select

```
library ieee;
use ieee.std_logic_1164.all;

entity multiplexer_4_1 is
  port(in0, in1 : in  std_ulogic_vector(15 downto 0);
        in2, in3 : in  std_ulogic_vector(15 downto 0);
        s0, s1   : in  std_ulogic;
        z        : out std_ulogic_vector(15 downto 0));
end multiplexer_4_1;

architecture usewith of multiplexer_4_1 is
  signal sels : std_ulogic_vector(1 downto 0);
begin
  sels <= s1 & s0;  -- Vector concatenation

  with sels select
    z <=
      in0          when "00",
      in1          when "01",
      in2          when "10",
      in3          when "11",
      "XXXXXXXXXXXX" when others;
end usewith;
```

Three-to-eight Decoder

```
library ieee;
use ieee.std_logic_1164.all;

entity dec1_8 is
port (
    sel : in  std_logic_vector(2 downto 0);
    res : out std_logic_vector(7 downto 0));
end dec1_8;

architecture imp of dec1_8 is
begin
    res <= "00000001" when sel = "000" else
           "00000010" when sel = "001" else
           "00000100" when sel = "010" else
           "00001000" when sel = "011" else
           "00010000" when sel = "100" else
           "00100000" when sel = "101" else
           "01000000" when sel = "110" else
           "10000000";
end imp;
```

Priority Encoder



```
library ieee;
use ieee.std_logic_1164.all;

entity priority is
  port (
    sel  : in  std_logic_vector(7 downto 0);
    code : out std_logic_vector(2 downto 0));
end priority;

architecture imp of priority is
begin
  code <= "000" when sel(0) = '1' else
    "001" when sel(1) = '1' else
    "010" when sel(2) = '1' else
    "011" when sel(3) = '1' else
    "100" when sel(4) = '1' else
    "101" when sel(5) = '1' else
    "110" when sel(6) = '1' else
    "111" when sel(7) = '1' else
    "---";          -- "-" is "don't care"
end imp;
```

Integer Arithmetic



```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

entity adder is
  port (
    A, B : in  std_logic_vector(7 downto 0);
    CI   : in  std_logic;
    SUM  : out std_logic_vector(7 downto 0);
    CO   : out std_logic);
end adder;

architecture imp of adder is
  signal tmp : std_logic_vector(8 downto 0);
begin
  tmp <= conv_std_logic_vector((conv_integer(A) +
                                conv_integer(B) +
                                conv_integer(CI)), 9);

  SUM <= tmp(7 downto 0);
  CO  <= tmp(8);
end imp;
```

A Very Simple ALU

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity alu is
  port (
    A, B : in  std_logic_vector(7 downto 0);
    ADD  : in  std_logic;
    RES  : out std_logic_vector(7 downto 0));
end alu;

architecture imp of alu is
begin
  RES <= A + B when ADD = '1' else
        A - B;
end imp;
```

Arithmetic Comparison

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity comparator is
  port (
    A, B : in  std_logic_vector(7 downto 0);
    GE   : out std_logic);
end comparator;

architecture imp of comparator is
begin
  GE <= '1' when A >= B else '0';
end imp;
```

Generate: Ripple-carry adder

```
library ieee;
use ieee.std_logic_1164.all;

entity rippleadder is
  port (a, b : in  std_ulogic_vector(3 downto 0);
        cin  : in  std_ulogic;
        sum  : out std_ulogic_vector(3 downto 0);
        cout : out std_ulogic);
end rippleadder;

architecture imp of rippleadder is
  signal c : std_ulogic_vector(4 downto 0);

begin
  c(0) <= cin;

  G1: for m in 0 to 3 generate          -- at compile time
    sum(m) <= a(m) xor b(m) xor c(m);
    c(m+1) <= (a(m) and b(m)) or (b(m) and c(m)) or
              (a(m) and c(m));
  end generate G1;

  cout <= c(4);

end imp;
```


Basic Flip-Flop



```
library ieee;
use ieee.std_logic_1164.all;

entity flipflop is
  port (Clk, D : in  std_ulogic;
        Q      : out std_ulogic);
end flipflop;

architecture imp of flipflop is
begin

  process (Clk)          -- Process sensitive to Clk
  begin
    if (Clk'event and Clk = '1') then -- Rising edge
      Q <= D;
    end if;
  end process P1;

end imp;
```

Flip-Flop with Synchronous Reset

```
library ieee;
use ieee.std_logic_1164.all;

entity flipflop_reset is
  port (Clk, Reset, D : in  std_ulogic;
        Q           : out std_ulogic);
end flipflop_reset;

architecture imp of flipflop_reset is
begin

  P1: process (Clk)
  begin
    if (Clk'event and Clk = '1') then
      if (Reset = '1') then Q <= '0';
      else Q <= D;
      end if;
    end if;
  end process P1;

end imp;
```

Four-bit binary counter



```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity counter is
  port(
    Clk, Reset : in  std_logic;
    Q          : out std_logic_vector(3 downto 0));
end counter;

architecture imp of counter is
  signal count : std_logic_vector(3 downto 0);
begin
  process (Clk)
  begin
    if (Clk'event and Clk = '1') then
      if (Reset = '1') then
        count <= "0000";
      else
        count <= count + 1;
      end if;
    end if;
  end process;

  Q <= count;          -- copy count to output
end imp;
```

Eight-bit serial in/out shift register

```
library ieee;
use ieee.std_logic_1164.all;

entity shifter is
  port (
    Clk : in  std_logic;
    SI  : in  std_logic;
    SO  : out std_logic);
end shifter;

architecture impl of shifter is
  signal tmp : std_logic_vector(7 downto 0);
begin
  process (Clk)
  begin
    if (Clk'event and Clk = '1') then
      for i in 0 to 6 loop -- unrolled at compile time
        tmp(i+1) <= tmp(i);
      end loop;
      tmp(0) <= SI;
    end if;
  end process;

  SO <= tmp(7); -- Copy to output
end impl;
```

A small RAM



```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity ram_32_4 is
  port (
    Clk : in  std_logic;
    WE  : in  std_logic;          -- Write enable
    EN  : in  std_logic;          -- Read enable
    addr : in  std_logic_vector(4 downto 0);
    di   : in  std_logic_vector(3 downto 0);  -- Data in
    do   : out std_logic_vector(3 downto 0);  -- Data out
  end ram_32_4;

  architecture imp of ram_32_4 is
    type ram_type is array(31 downto 0) of std_logic_vector(3 downto 0);
    signal RAM : ram_type;
  begin
    process (Clk)
    begin
      if (Clk'event and Clk = '1') then
        if (en = '1') then
          if (we = '1') then
            RAM(conv_integer(addr)) <= di;
            do <= di;
          else
            do <= RAM(conv_integer(addr));
          end if;
        end if;
      end if;
    end process;
  end imp;
```

A small ROM



```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity rom_32_4 is
  port (
    Clk  : in  std_logic;
    en   : in  std_logic;          -- Read enable
    addr : in  std_logic_vector(4 downto 0);
    data : out std_logic_vector(3 downto 0));
end rom_32_4;

architecture imp of rom_32_4 is
  type rom_type is array (31 downto 0) of std_logic_vector(3 downto 0);
  constant ROM : rom_type :=
    ("0001", "0010", "0011", "0100", "0101", "0110", "0111", "1000",
     "1001", "1010", "1011", "1100", "1101", "1110", "1111", "0001",
     "0010", "0011", "0100", "0101", "0110", "0111", "1000", "1001",
     "1010", "1011", "1100", "1101", "1110", "1111", "0000", "0010");
begin

  process (Clk)
  begin
    if (Clk'event and Clk = '1') then
      if (en = '1') then
        data <= ROM(conv_integer(addr));
      end if;
    end if;
  end process;
end imp;
```

Rocket Science: FSMs

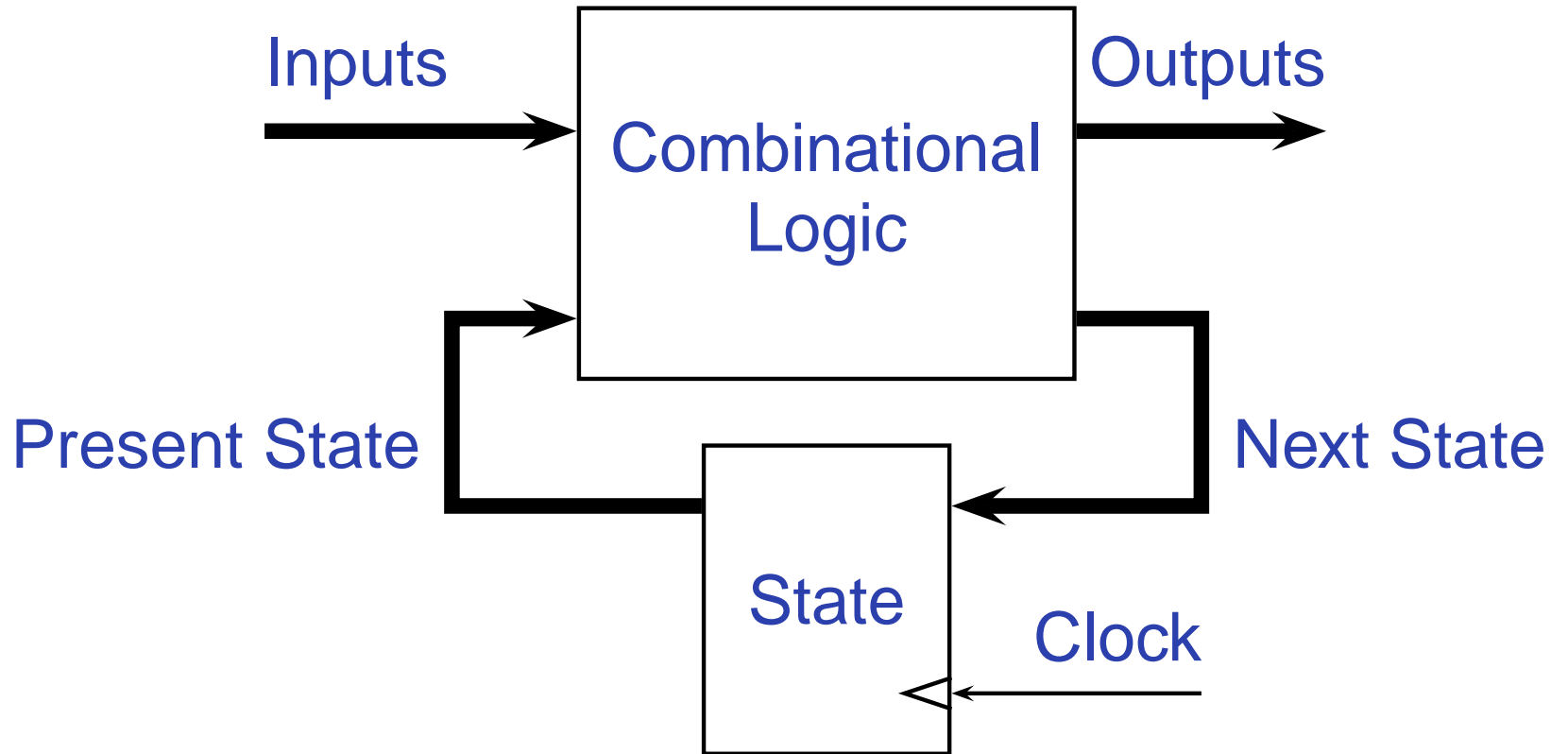 

Structure of FSMs in VHDL

```
entity myFSM is
  port( ... );
end myFSM;


architecture imp of myFSM is
  constant STATE1 := "...";
  constant STATE2 := "...";
  signal current_state, next_state : ...;

  process (clk)          -- State holding element process
  begin
    if (clk'event and clk = '1') then
      current_state <= next_state;
    end if
  end process;

  process (inputs...)    -- Outputs and next state function
  begin
    if (reset = '1') then
      next_state <= STATE1;
    else
      case current_state is
        when STATE1 =>
          output1 <= '1';
          next_state <= STATE2;
        when STATE2 =>
          ...
          next_state <= STATE3;
        end case;
      end if;
    end process;

  end imp;
```



The Traffic Light Controller

 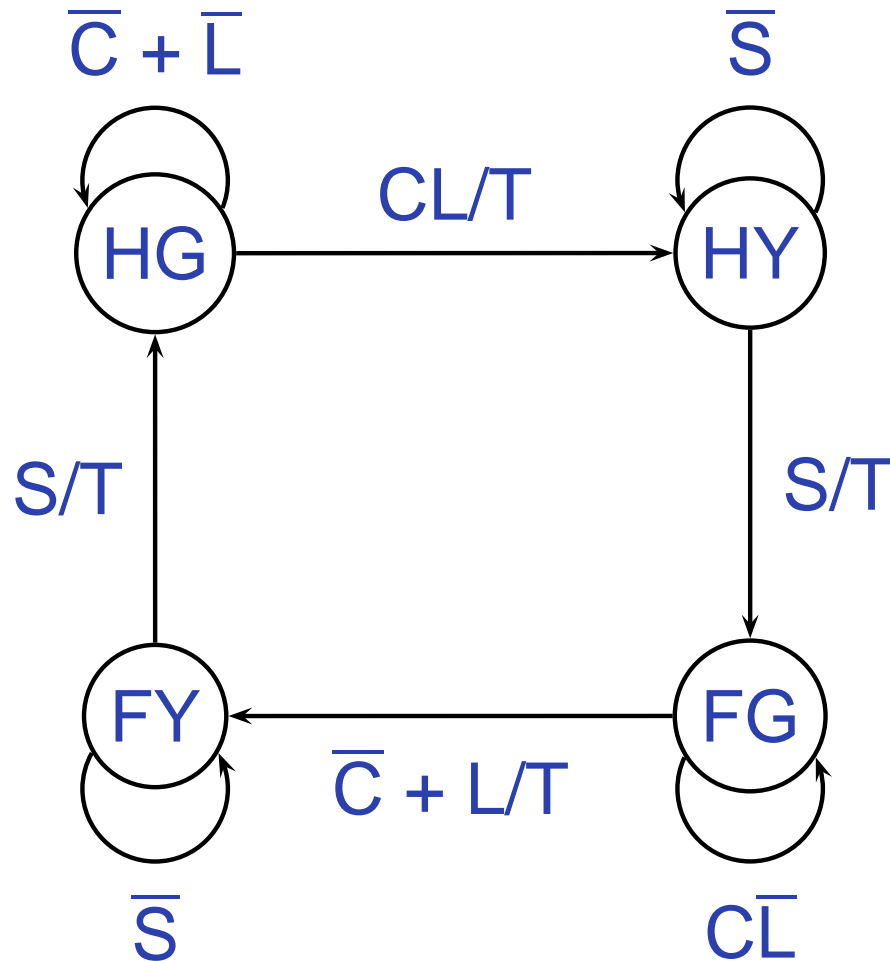

This controls a traffic light at the intersection of a busy highway and a farm road. Normally, the highway light is green but if a sensor detects a car on the farm road, the highway light turns yellow then red. The farm road light then turns green until there are no cars or after a long timeout. Then, the farm road light turns yellow then red, and the highway light returns to green. The inputs to the machine are the car sensor, a short timeout signal, and a long timeout signal. The outputs are a timer start signal and the colors of the highway and farm road lights.

Source: Mead and Conway, *Introduction to VLSI Systems*, 1980, p. 85.

FSM for the Traffic Light Controller



C: Car sensor
 S: Short timeout
 L: Long timeout
 T: Start timer

St	Hwy	Farm
HG	G	R
HY	Y	R
FG	R	G
FY	R	Y

Traffic Light Controller in VHDL (1)

```
library ieee;
use ieee.std_logic_1164.all;

entity tlc is
  port (
    clk           : in  std_ulogic;
    reset         : in  std_ulogic;
    cars          : in  std_ulogic;
    short         : in  std_ulogic;
    long          : in  std_ulogic;
    highway_yellow : out std_ulogic;
    highway_red   : out std_ulogic;
    farm_yellow   : out std_ulogic;
    farm_red      : out std_ulogic;
    start_timer   : out std_ulogic);
end tlc;
```

Traffic Light Controller in VHDL (2)

```
architecture imp of tlc is
  signal current_state, next_state : std_ulogic_vector(1 downto 0);
  constant HG : std_ulogic_vector := "00";
  constant HY : std_ulogic_vector := "01";
  constant FY : std_ulogic_vector := "10";
  constant FG : std_ulogic_vector := "11";
begin

  P1: process (clk)      -- Sequential process
  begin
    if (clk'event and clk = '1') then
      current_state <= next_state;
    end if;
  end process P1;
```

Traffic Light Controller in VHDL (3)

```
-- Combinational process
--   Sensitive to input changes, not clock

P2: process (current_state, reset, cars, short, long)
begin
  if (reset = '1') then
    next_state <= HG;
    start_timer <= '1';
  else
    case current_state is
      when HG =>
        highway_yellow <= '0';
        highway_red     <= '0';
        farm_yellow     <= '0';
        farm_red        <= '1';
        if (cars = '1' and long = '1') then
          next_state <= HY;
          start_timer <= '1';
        else
          next_state <= HG;
          start_timer <= '0';
        end if;
    end case;
  end if;
end process;
```

Traffic Light Controller in VHDL (4)

```
when HY =>
    highway_yellow <= '1';
    highway_red    <= '0';
    farm_yellow    <= '0';
    farm_red       <= '1';
    if (short = '1') then
        next_state <= FG;
        start_timer <= '1';
    else
        next_state <= HY;
        start_timer <= '0';
    end if;

when FG =>
    highway_yellow <= '0';
    highway_red    <= '1';
    farm_yellow    <= '0';
    farm_red       <= '0';
    if (cars = '0' or long = '1') then
        next_state <= FY;
        start_timer <= '1';
    else
        next_state <= FG;
        start_timer <= '0';
    end if;
```


Traffic Light Controller in VHDL (5)

```
when FY =>
    highway_yellow <= '0';
    highway_red    <= '1';
    farm_yellow   <= '1';
    farm_red      <= '0';
    if (short = '1') then
        next_state <= HG;
        start_timer <= '1';
    else
        next_state <= FY;
        start_timer <= '0';
    end if;

when others =>
    next_state <= "XX";
    start_timer <= 'X';
    highway_yellow <= 'X';
    highway_red <= 'X';
    farm_yellow <= 'X';
    farm_red <= 'X';
end case;
end if;
end process P2;

end imp;
```

Ten Commandments of VHDL

 

I: Thou Shalt Design Before Coding

- Know the structure of what you are designing first.
- Draw a block diagram of the datapath
- Understand the timing (draw diagrams)
- Draw bubble-and-arc diagrams for FSMs
- Only once you have a design should you start coding in VHDL
- VHDL is only a way to ask for component

II: Thou Shalt be Synchronous

- One global clock
- Flip-flops generate inputs to combinational logic, which computes inputs to flip-flops
- Exactly one value per signal per clock cycle
- Do not generate asynchronous reset signals; only use them if they are external
- Edge-triggered flip-flops only. Do not use level-sensitive logic.
- Do not generate clock signals. Use multiplexers to create “load enable” signals on flip-flops.

III: Thou Shalt Be Sensitive

Combinational processes: list all process inputs

```
process (current_state, long)
begin
  if (reset = '1') then
    next_state <= HG;
    start_timer <= '1';
  else
    case current_state is
      when HG =>
        farm_yellow <= '0';
        if (cars = '1' and long = '1') then
          next_state <= HY;
        else
          next_state <= HG;
        end if;
      when HY =>
        farm_yellow <= '0';
        if (short = '1') then
          next_state <= FG;
        else
          next_state <= HY;
        end if;
    end case;
  end if;
end process;
```

```
process (current_state, reset, cars, short, long)
begin
  if (reset = '1') then
    next_state <= HG;
    start_timer <= '1';
  else
    case current_state is
      when HG =>
        farm_yellow <= '0';
        if (cars = '1' and long = '1') then
          next_state <= HY;
        else
          next_state <= HG;
        end if;
      when HY =>
        farm_yellow <= '0';
        if (short = '1') then
          next_state <= FG;
        else
          next_state <= HY;
        end if;
    end case;
  end if;
end process;
```

III: Thou Shalt Be Sensitive

Sequential processes: always include the clock.
Include reset if asynchronous, and nothing else.

```
process (Clk, D)
begin
  if (Clk'event and Clk = '1') then
    Q <= D;
  end if;
end process;
```

```
process (Clk, D)
begin
  if (reset = '1') then
    Q <= '0';
  else
    if (Clk'event and Clk = '1') then
      Q <= D;
    end if;
  end if;
end process;
```


```
process (Clk)
begin
  if (Clk'event and Clk = '1') then
    Q <= D;
  end if;
end process;
```

```
process (Clk, reset)
begin
  if (reset = '1') then
    Q <= '0';
  else
    if (Clk'event and Clk = '1') then
      Q <= D;
    end if;
  end if;
end process;
```

IV: Thou Shalt Assign All Outputs

Synthesis infers level-sensitive latches if sometimes you do not assign an output.
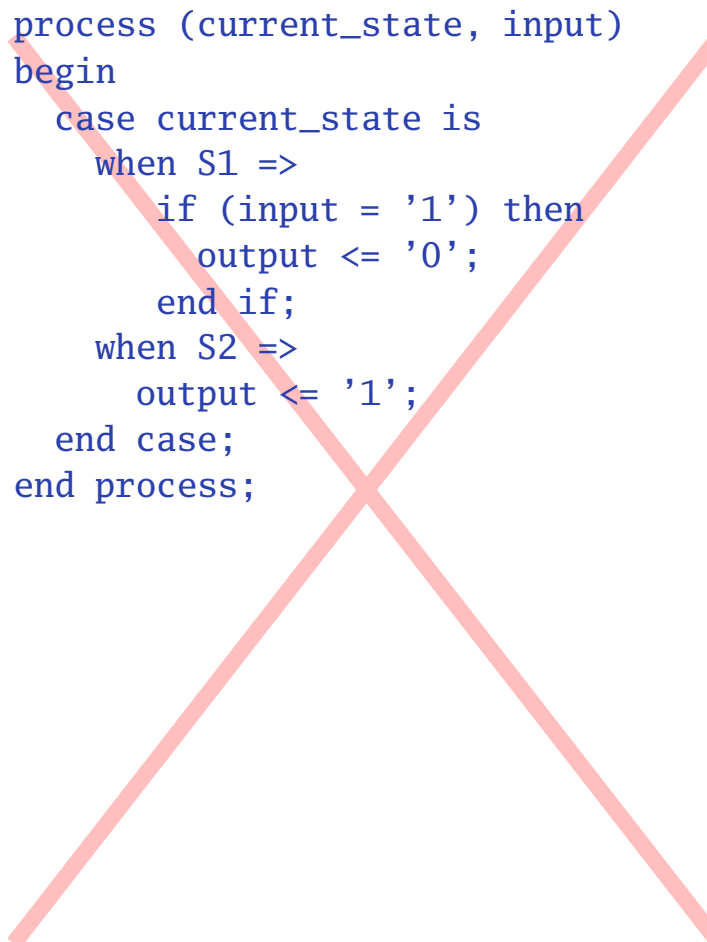
```
process (current_state, input)
begin
  case current_state is
    when S1 =>
      if (input = '1') then
        output <= '0';
      end if;
    when S2 =>
      output <= '1';
    end case;
end process;
```



```
process (current_state, input)
begin
  case current_state is
    when S1 =>
      if (input = '1') then
        output <= '0';
      else
        output <= '1';
      end if;
    when S2 =>
      output <= '1';
    end case;
end process;
```

“Default” values are convenient

-- OK

```
process (current_state, input)
begin
  case current_state is
    when S1 =>
      if (input = '1') then
        output <= '0';
      else
        output <= '1';
      end if;
    when S2 =>
      output <= '1';
  end case;
end process;
```

-- Better

```
process (current_state, input)
begin
  output <= '1';
  case current_state is
    when S1 =>
      if (input = '1') then
        output <= '0';
      end if;
  end case;
end process;
```

V: Thou Shalt Enumerate States

Better to use an enumeration to encode states:

```
type mystate is (START,RUN,IDLE,ZAPHOD);
signal cst : mystate;
signal nxst : mystate;

process(cst)
begin
  case cst is
    when START => ...
    when RUN => ...
    when IDLE => ...
  end case;
end process;
```

Running this produces a helpful error:

```
Compiling vhdl file "/home/cristi/cs4840/lab4/main.vhd" in Library work.
Entity <system> compiled.
ERROR:HDLParasers:813 - "/home/cristi/cs4840/lab4/main.vhd" Line 80.
Enumerated value zaphod is missing in case.
-->
```

VI:



(There is no rule six)

VII: Thou Shalt Avoid Async

Only use asynchronous reset when there is one global signal from outside.

-- OK if Reset is from outside

```
process (Clk, Reset)
begin
  if (Reset = '1') then
    Q <= '0';
  else
    if (Clk'event and Clk = '1') then
      Q <= D;
    end if;
  end if;
end process;
```

-- Better


```
process (Clk)
begin
  if (Clk'event and Clk = '1') then
    if (Reset = '1') then
      Q <= '0';
    else
      Q <= D;
    end if;
  end if;
end process;
```

VIII: Thou Shalt Have One Version

- Never assume signals from the test bench that are not there on the board
- It is hard enough to make simulation match the design; do not make it any harder
- If you must slow down hardware, carefully generate a slower clock and only use that clock globally.

IX: Thou Shalt Not Test For X Or Z
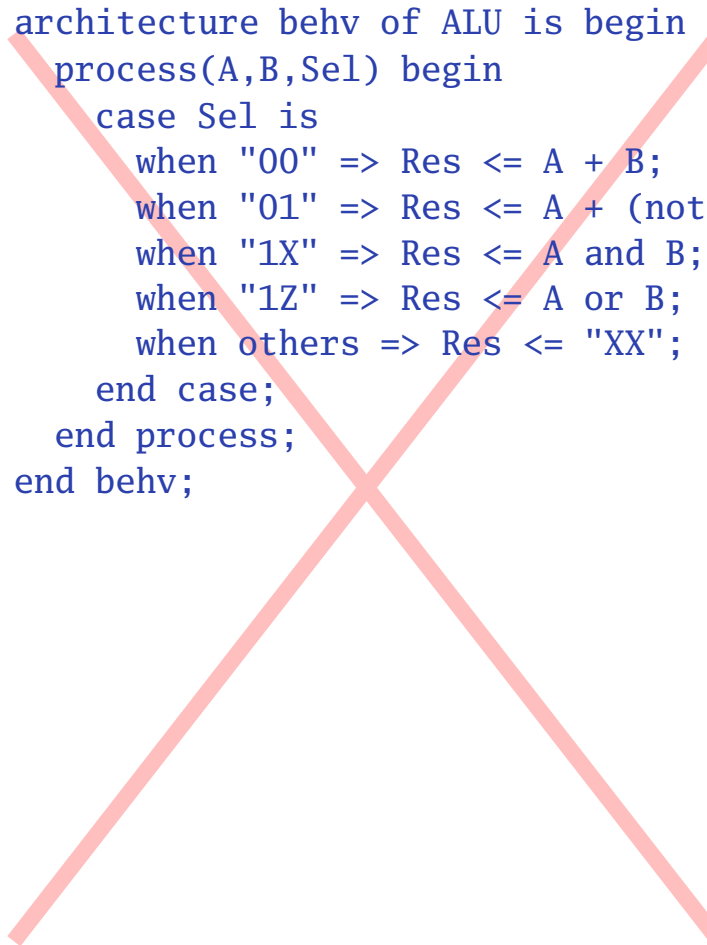
```
architecture behv of ALU is begin
  process(A,B,Sel) begin
    case Sel is
      when "00" => Res <= A + B;
      when "01" => Res <= A + (not B) + 1;
      when "1X" => Res <= A and B;
      when "1Z" => Res <= A or B;
      when others => Res <= "XX";
    end case;
  end process;
end behv;
```



```
architecture behv of ALU is begin
  process(A,B,Sel) begin
    case Sel is
      when "00" => Res <= A + B;
      when "01" => Res <= A + (not B) + 1;
      when "10" => Res <= A and B;
      when "11" => Res <= A or B;
      when others => Res <= "XX";
    end case;
  end process;
end behv;
```

X: Thou Shalt Not Specify Delays

- The `wait` statement can delay for a certain amount of time, e.g., “`wait 10ns;`”
- It is good to use in test benches that are not meant to become hardware
- Do not use them in the design of your hardware