

Fundamentals of Computer Systems



Memory

Stephen A. Edwards


Columbia University

Spring 2012


Atari Space Race, 1973

  

Atari Space Race PCB


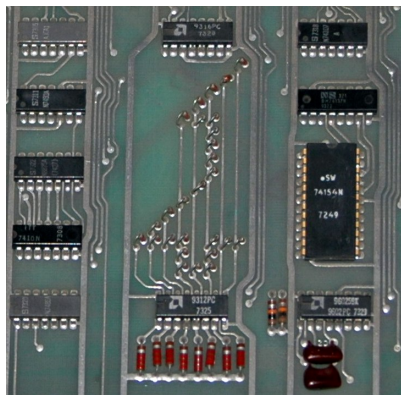


Front

 


Back (mirrored)

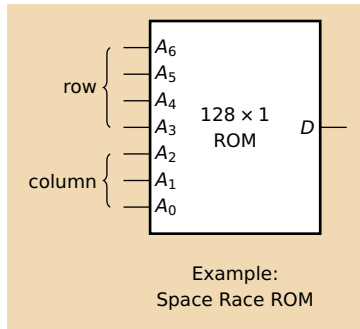 Read-Only Memories: Combinational Functions




Implementing ROMs

 


Add. Data

00	011
01	110
10	100
11	010

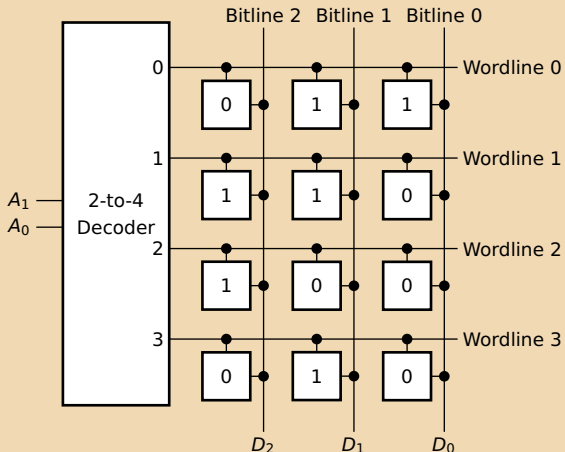


Implementing ROMs

 


Add. Data

00	011
01	110
10	100
11	010

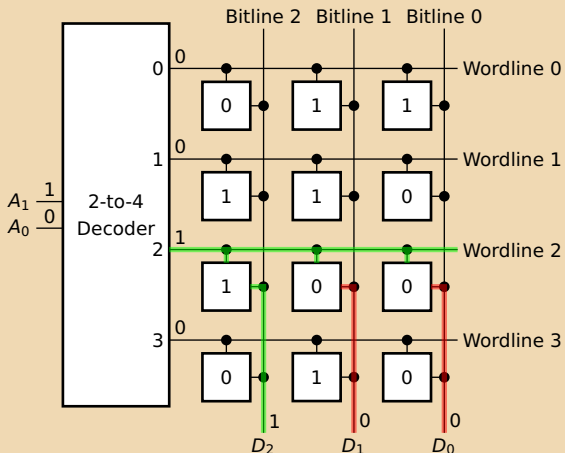


Implementing ROMs

 


Add. Data

00	011
01	110
10	100
11	010

 


Implementing ROMs

 


Add. Data

00	011
01	110
10	100
11	010

 


Atari Space Race Schematic

 


CMOS Mask-Programmed ROMs



Add. Data	
00	011
01	110
10	100
11	010

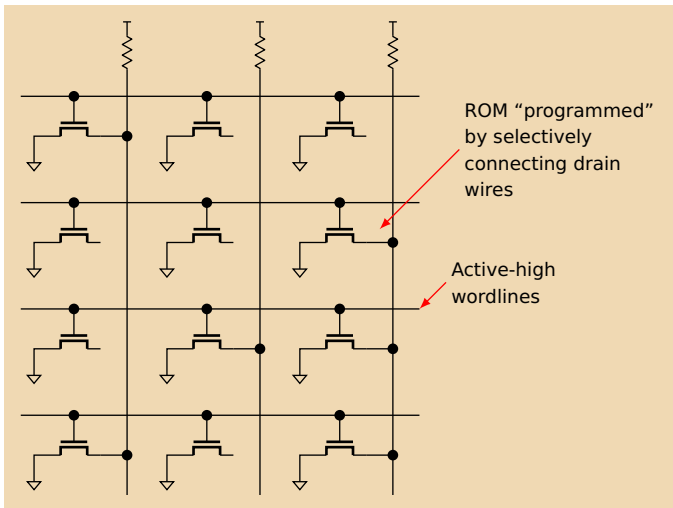

Mask ROM Die Photo

 


Color PROM in Pac-Man

  


00	00	Black
01	07	Red
02	66	Brown
03	EF	Pink
04	00	Black
05	F8	Cyan
06	EA	Light Blue
07	6F	Orange
08	00	Black
09	3F	Yellow
0A	00	Black
0B	C9	Blue
0C	38	Bright Green
0D	AA	Teal
0E	AF	Light Red
0F	F6	Light Purple
10	00	Black
:	:	
1F	00	Black

A Floating Gate MOSFET

 


Cross section of a NOR FLASH transistor. Kawai et al., ISSCC 2008 (Renesas)

Floating Gate n-channel MOSFET

 


Floating gate uncharged; Control gate at 0V: Off

Floating Gate n-channel MOSFET

 


Floating gate uncharged; Control gate positive: On

Floating Gate n-channel MOSFET

 



Floating gate negative; Control gate at 0V: Off

Floating Gate n-channel MOSFET

 


Floating gate negative; Control gate positive: Off


 
 
EPROMs and FLASH use Floating-Gate MOSFETs



Static Random-Access Memory Cell

 


Layout of a 6T SRAM Cell

   


Weste and Harris. *Introduction to CMOS VLSI Design*.
Addison-Wesley, 2010.


Intel's 2102 SRAM, 1024 × 1 bit, 1972

 


2102 Block Diagram

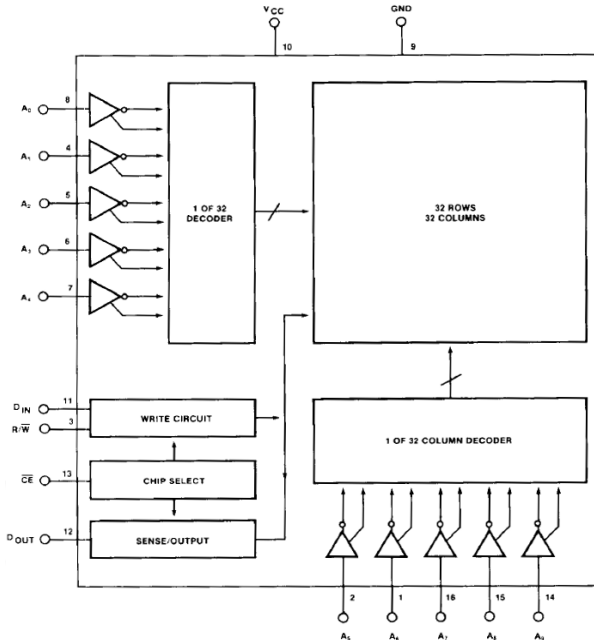


SRAM Timing

 



6264 SRAM Block Diagram

 



Galaga CPU detail (Namco/Midway 1981)

 


Dynamic RAM Cell

  

Our Old Pal, the Space Race ROM

  

Our Old Pal, the Space Race ROM

 


The decoder or
"AND plane"

In a RAM or ROM,
computes every
minterm

Pattern is not
programmable

Our Old Pal, the Space Race ROM

 


The decoder or
“OR plane”

One term for every
output


Pattern is
programmable =
the contents of the
ROM

Our Old Pal, the Space Race ROM

 


Can we do better?


Simplifying the Space Race ROM

 

 Essential minterms mean don't expand these




Our New PAL, the Space Race ROM

 

$$D_0 = 32\bar{1}0$$


Our New PAL, the Space Race ROM

 

$$D_0 = 32\bar{I}_0$$

$$D_1 = 32\bar{I}_1$$

Our New PAL, the Space Race ROM

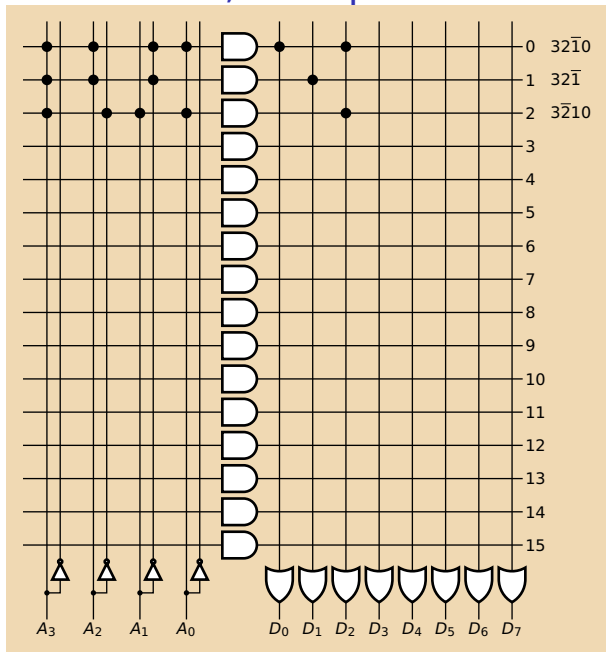


$$D_0 = 32\bar{1}0$$

$$D_1 = 32\bar{1}$$

$$D_2 = 3\bar{2}10 + 32\bar{1}0$$

Our New PAL, the Space Race ROM

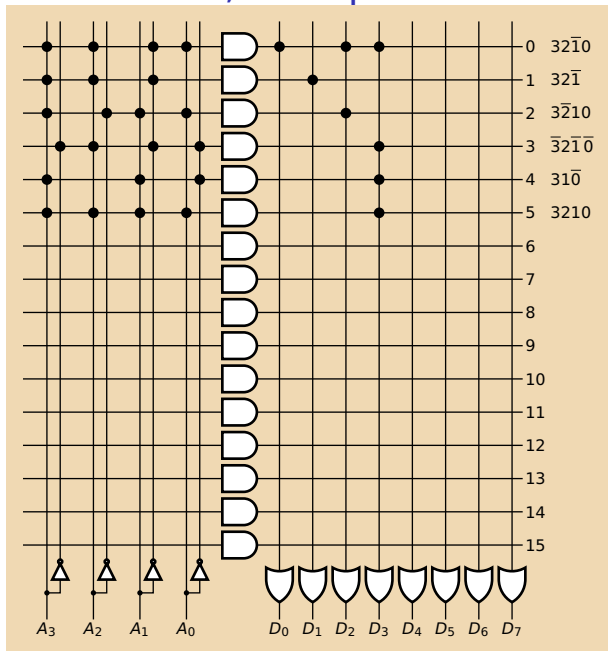


$$D_0 = 32\bar{1}0$$

$$D_1 = 32\bar{1}$$

$$D_2 = 3\bar{2}10 + 32\bar{1}0$$

$$D_3 = \bar{3}\bar{2}\bar{1}\bar{0} + 31\bar{0} + 3\bar{2}\bar{1}0 + 3210$$

Our New PAL, the Space Race ROM

 

$$D_0 = 3\bar{2}\bar{1}0$$


$$D_1 = 3\bar{2}\bar{1}$$

$$D_2 = 3\bar{2}10 + 3\bar{2}\bar{1}0$$

$$D_3 = \bar{3}\bar{2}\bar{1}\bar{0} + 31\bar{0} + 3\bar{2}\bar{1}0 + 3210$$

$$D_4 = \bar{3}\bar{2}10 + \bar{3}\bar{2}\bar{1}\bar{0} + 3\bar{2}\bar{1}0 + 3210$$

Our New PAL, the Space Race ROM

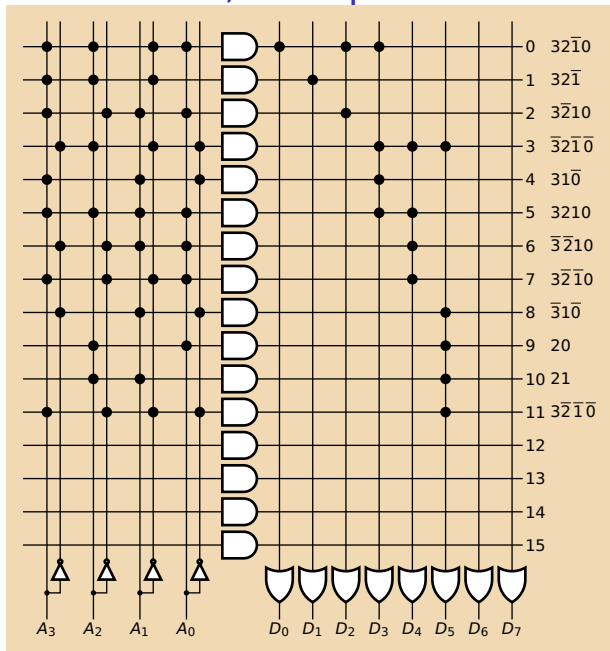

$$D_0 = 32\bar{1}0$$

$$D_1 = 32\bar{1}$$


$$D_2 = 3\bar{2}10 + 32\bar{1}0$$

$$D_3 = \bar{3}2\bar{1}\bar{0} + 31\bar{0} + 32\bar{1}0 + 3210$$

$$D_4 = \bar{3}\bar{2}10 + \bar{3}2\bar{1}\bar{0} + 3\bar{2}\bar{1}0 + 3210$$

$$D_5 = \bar{3}\bar{1}\bar{0} + 20 + 21 + \bar{3}2\bar{1}\bar{0} + 3\bar{2}\bar{1}\bar{0}$$

Our New PAL, the Space Race ROM

 

$$D_0 = 32\bar{1}0$$

$$D_1 = 32\bar{1}$$

$$D_2 = 3\bar{2}10 + 32\bar{1}0$$


$$D_3 = \bar{3}2\bar{1}\bar{0} + 31\bar{0} + 32\bar{1}0 + 3210$$

$$D_4 = \bar{3}\bar{2}10 + \bar{3}2\bar{1}\bar{0} + 3\bar{2}\bar{1}0 + 3210$$

$$D_5 = \bar{3}1\bar{0} + 20 + 21 + \bar{3}2\bar{1}\bar{0} + 3\bar{2}\bar{1}0$$

$$D_6 = \bar{3}\bar{2}\bar{1}0 + 32\bar{1}0$$

Our New PAL, the Space Race ROM

 

$$D_0 = 32\bar{1}0$$

$$D_1 = 32\bar{1}$$

$$D_2 = 3\bar{2}10 + 32\bar{1}0$$

$$D_3 = \bar{3}2\bar{1}\bar{0} + 31\bar{0} + 32\bar{1}0 + 3210$$

$$D_4 = \bar{3}\bar{2}10 + \bar{3}2\bar{1}\bar{0} + 3\bar{2}\bar{1}0 + 3210$$


$$D_5 = \bar{3}1\bar{0} + 20 + 21 + \bar{3}2\bar{1}\bar{0} + 3\bar{2}\bar{1}\bar{0}$$

$$D_6 = \bar{3}\bar{2}\bar{1}0 + 32\bar{1}0$$

$$D_7 = \bar{3}\bar{2}\bar{1}\bar{0} + 32\bar{1}0$$

Saved two ANDs

A 22V10 PAL: Programmable AND/Fixed OR

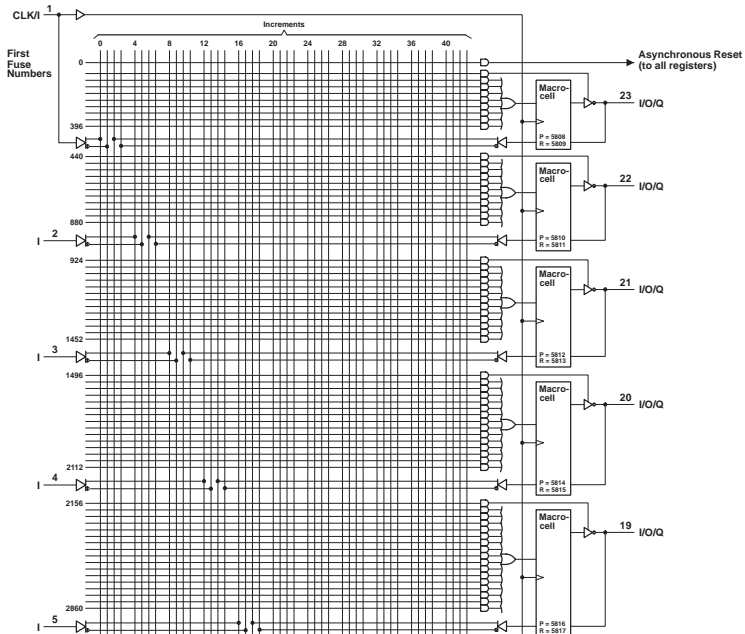

Field-Programmable Gate Arrays (FPGAs)

