

# Bresenham's Line Algorithm in Hardware


Stephen A. Edwards

Columbia University

Spring 2013


# Bresenham's Line Algorithm

Objective: Draw a line...

 


# Bresenham's Line Algorithm

...with well-approximating pixels...

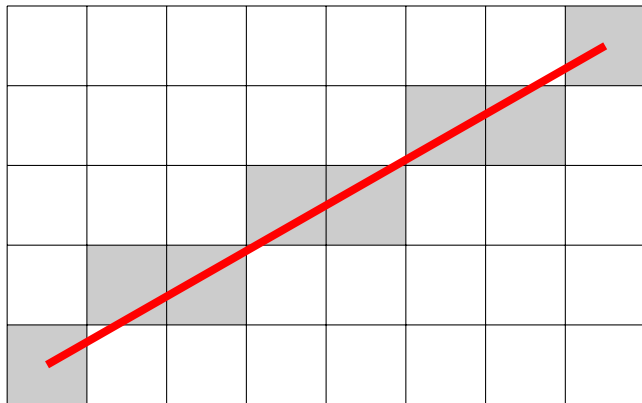

# Bresenham's Line Algorithm

...by maintaining error information..

 



## The Pseudocode from Wikipedia

```
function line(x0, y0, x1, y1)
  dx := abs(x1-x0)
  dy := abs(y1-y0)
  if x0 < x1 then sx := 1 else sx := -1
  if y0 < y1 then sy := 1 else sy := -1
  err := dx-dy

  loop
    setPixel(x0,y0)
    if x0 = x1 and y0 = y1 exit loop
    e2 := 2*err
    if e2 > -dy then
      err := err - dy
      x0 := x0 + sx
    end if
    if e2 < dx then
      err := err + dx
      y0 := y0 + sy
    end if
  end loop
```

## My C Code

```
void line(Uint16 x0, Uint16 y0, Uint16 x1, Uint16 y1)
{
    Sint16 dx, dy; // Width and height of bounding box
    Uint16 x, y; // Current point
    Sint8 sx, sy; // -1 or 1
    Sint16 err; // Loop-carried value
    Sint16 e2; // Temporary variable
    int right, down; // Boolean

    dx = x1 - x0; right = dx > 0; if (!right) dx = -dx;
    dy = y1 - y0; down = dy > 0; if (down) dy = -dy;
    err = dx + dy; x = x0; y = y0;
    for (;;) {
        plot(x, y);
        if (x == x1 && y == y1) break; // Reached the end
        e2 = err << 1; // err * 2
        if (e2 > dy) { err += dy; if (right) x++; else x--;}
        if (e2 < dx) { err += dx; if (down) y++; else y--;}
    }
}
```

## Datapath for $dx$ , $dy$ , *right*, and *down*

```
void line(Uint16 x0, Uint16 y0,
         Uint16 x1, Uint16 y1)
{
    Sint16 dx;    // Width of bounding box
    Sint16 dy;    // Height of BB (neg)
    Uint16 x, y;  // Current point
    Sint8  sx, sy; // -1 or 1
    Sint16 err;   // Loop-carried value
    Sint16 e2;    // Temporary variable
    int right;    // Boolean
    int down;     // Boolean


    dx = x1 - x0;
    right = dx > 0;
    if (!right) dx = -dx;
    dy = y1 - y0;
    down = dy > 0;
    if (down) dy = -dy;

    err = dx + dy;
    x = x0; y = y0;

    for (;;) {
        plot(x, y);
        if (x == x1 && y == y1)
            break;
        e2 = err << 1;
        if (e2 > dy) {
            err += dy;
            if (right) x++;
            else x--;
        }
        if (e2 < dx) {
            err += dx;
            if (down) y++;
            else y--;
        }
    }
}
```


 
## Datapath for $dx$ , $dy$ , *right*, and *down*




```
dx = x1 - x0;  
right = dx > 0;  
if (!right) dx = -dx;  
dy = y1 - y0;  
down = dy > 0;  
if (down) dy = -dy;
```

```
err = dx + dy;  
x = x0; y = y0;
```

```
for (;;) {  
    plot(x, y);  
    if (x == x1 && y == y1)  
        break;  
    e2 = err << 1;  
    if (e2 > dy) {  
        err += dy;  
        if (right) x++;  
        else x--;  
    }  
    if (e2 < dx) {  
        err += dx;  
        if (down) y++;  
        else y--;  
    }  
}
```
 
## Datapath for $dx$ , $dy$ , *right*, and *down*




```
x1x0 <= x1 - x0;  
y1y0 <= y1 - y0;
```

```
right <= not x1x0(10);  
down <= not y1y0(10);
```

```
dx <= x1x0 when right = '1'  
      else -x1x0;  
dy <= -y1y0 when down = '1'  
      else y1y0;
```

# Datapath for *err*

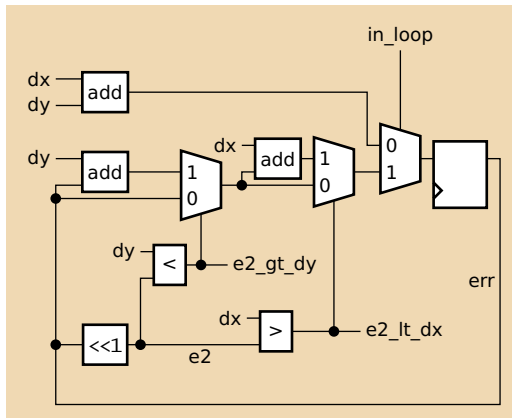


```
dx = x1 - x0;
right = dx > 0;
if (!right) dx = -dx;
dy = y1 - y0;
down = dy > 0;
if (down) dy = -dy;
```

```
err = dx + dy;
x = x0; y = y0;
```

```
for (;;) {
    plot(x, y);
    if (x == x1 && y == y1)
        break;
    e2 = err << 1;
    if (e2 > dy) {
        err += dy;
        if (right) x++;
        else x--;
    }
    if (e2 < dx) {
        err += dx;
        if (down) y++;
        else y--;
    }
}
```

## Datapath for *err*

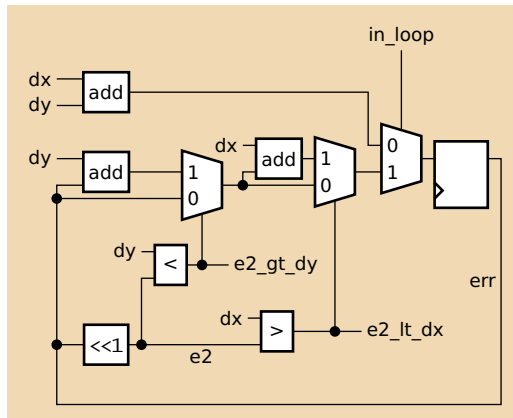

```
err_next <=
  ("0" & dx) + ("0" & dy)
  when in_loop = '0'
  else err2;
```

```
err2 <= err1 + dx
  when e2_lt_dx = '1'
  else err1;
```


```
err1 <= err + dy
  when e2_gt_dy = '1'
  else err;
```

```
e2 <=
  err(10 downto 0) & "0";
```

```
e2_gt_dy <=
  '1' when e2 > dy
  else '0';
```

```
e2_lt_dx <=
  '1' when e2 < dx
  else '0';
```

# Datapath for x and y

 


```
dx = x1 - x0;
right = dx > 0;
if (!right) dx = -dx;
dy = y1 - y0;
down = dy > 0;
if (down) dy = -dy;
```

```
err = dx + dy;
x = x0; y = y0;
```

```
for (;;) {
    plot(x, y);
    if (x == x1 && y == y1)
        break;
    e2 = err << 1;
    if (e2 > dy) {
        err += dy;
        if (right) x++;
        else x--;
    }
    if (e2 < dx) {
        err += dx;
        if (down) y++;
        else y--;
    }
}
```

# Datapath for x and y

 

```
x_next <=
    x0 when in_loop = '0'
    else xb;
xb <= xa when e2_gt_dy = '1'
    else x;
xa <= x + 1 when right = '1'
    else x - 1;
y_next <=
    y0 when in_loop = '0'
    else yb;
yb <= ya when e2_lt_dx = '1'
    else y;
ya <= y + 1 when down = '1'
    else y - 1;
break <=
    '1' when x = x1 and y = y1
    else '0';
```

```
process (clk)
begin
    if rising_edge(clk) then
        err <= err_next;
        x <= x_next;
        y <= y_next;
    end if;
end process;
```

# Interface and Types


```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity lines is
  port (
    clk          : in  std_logic;
    rst          : in  std_logic;
    x0, y0, x1, y1 : in  signed(10 downto 0);
    x_p, y_p     : out signed(10 downto 0);
    start       : in  std_logic;
    done, plot  : out std_logic);
end lines;

architecture datapath of lines is
  signal x1x0, y1y0, dx, dy          : signed(10 downto 0);
  signal down, right, e2_lt_dx, e2_gt_dy : std_logic;
  signal in_loop, break             : std_logic;


  signal err, err1, err2, e2, err_next : signed(11 downto 0);
  signal x, y, x_next, y_next,
         xa, xb, ya, yb             : signed(10 downto 0);
```

# Timing

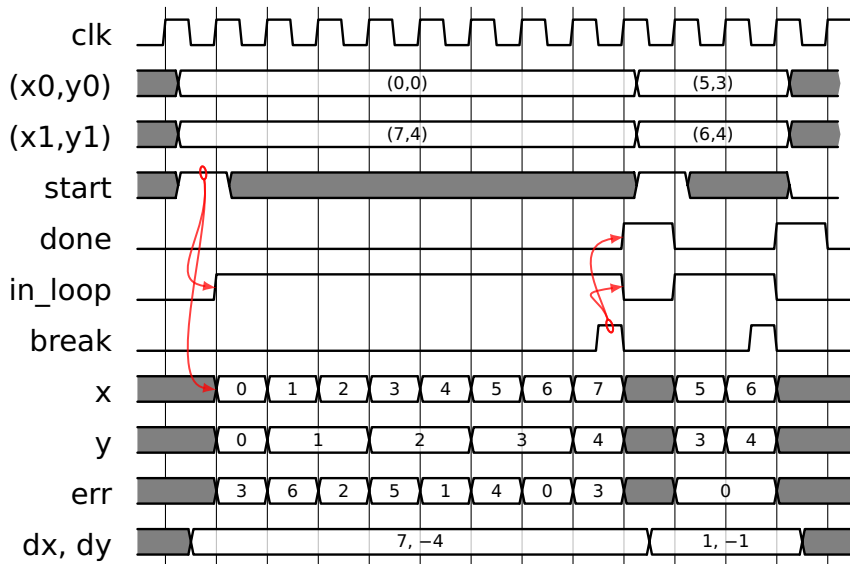



# Control FSM

 

# Control FSM in VHDL

```
type states is (IDLE_STATE, RUNNING_STATE, DONE_STATE);  
signal state : states;  
  
fsm : process (clk)  
begin  
  if rising_edge(clk) then  
    if rst = '1' then  
      state <= IDLE_STATE;  
    else  
      case state is  
        when IDLE_STATE =>  
          if start = '1' then state <= RUNNING_STATE; end if;  
        when RUNNING_STATE =>  
          if break = '1' then state <= DONE_STATE;    end if;  
        when DONE_STATE =>  
          if start = '1' then state <= RUNNING_STATE;  
            else state <= IDLE_STATE;    end if;  
      end case; end if; end if; end process;  
  
in_loop <= '1' when state = RUNNING_STATE else '0';  
done    <= '1' when state = DONE_STATE    else '0';  
plot    <= in_loop;
```

# The Framebuffer

```
component fbmem port (  
    data      : in std_logic_vector(0 downto 0);  
    rdaddress : in std_logic_vector(18 downto 0);  
    rdclock   : in std_logic;  
    wraddress : in std_logic_vector(18 downto 0);  
    wrclock   : in std_logic;  
    wren      : in std_logic;  
    q         : out std_logic_vector(0 downto 0));  
end component;  
  
frame_buffer_memory : fbmem port map (  
    rdaddress => std_logic_vector(rdaddress(18 downto 0)),  
    rdclock   => VGA_CLK,  
    q         => q,  
    data      => data,  
    wraddress => std_logic_vector(wraddress(18 downto 0)),  
    wrclock   => clk,  
    wren      => wren);  
  
read_data <= '1' when q(0) = '1'      else '0';  
data      <= "1" when write_data = '1' else "0";  
  
rdaddress <= ("0000000000" & VGA_X) +  
             (VGA_Y & "0000000") + (VGA_Y & "0000000000");  
wraddress <= ("0000000000" & VGA_XW) +  
             (VGA_YW & "0000000") + (VGA_YW & "0000000000");
```