

Fundamentals of Computer Systems


Memory

Stephen A. Edwards


Columbia University

Summer 2016


Atari Space Race, 1973

 

Atari Space Race PCB


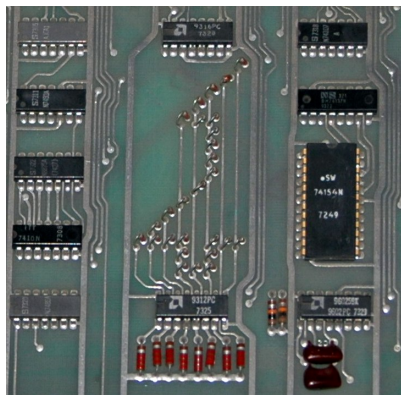


Front

 


Back (mirrored)

  
Read-Only Memories: Combinational Functions




Implementing ROMs

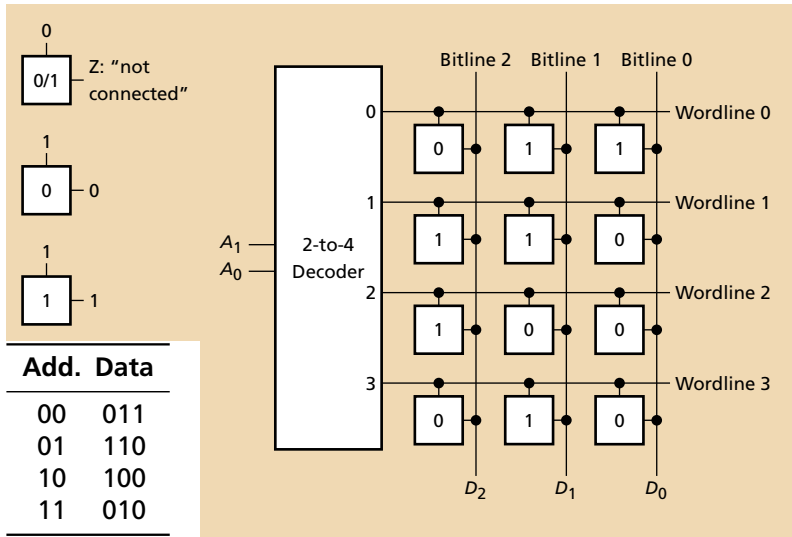

Implementing ROMs

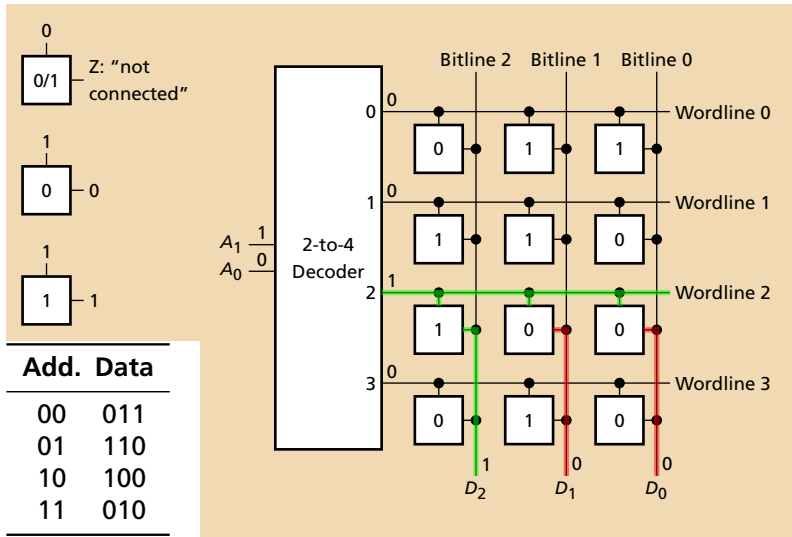


Implementing ROMs

 


Addr. Data

00	011
01	110
10	100
11	010

 


Implementing ROMs

 


Add. Data


00	011
01	110
10	100
11	010

 

Atari Space Race Schematic

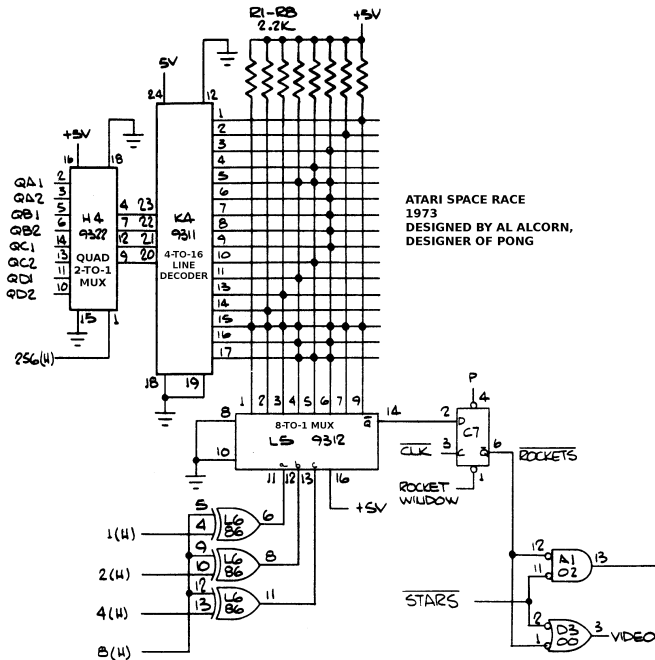

 
The 1971 DEC M792-YB Bootstrap Diode Matrix




32-word, 16-bit (64-byte) ROM diode matrix

CMOS Mask-Programmed ROMs



Add. Data	
00	011
01	110
10	100
11	010

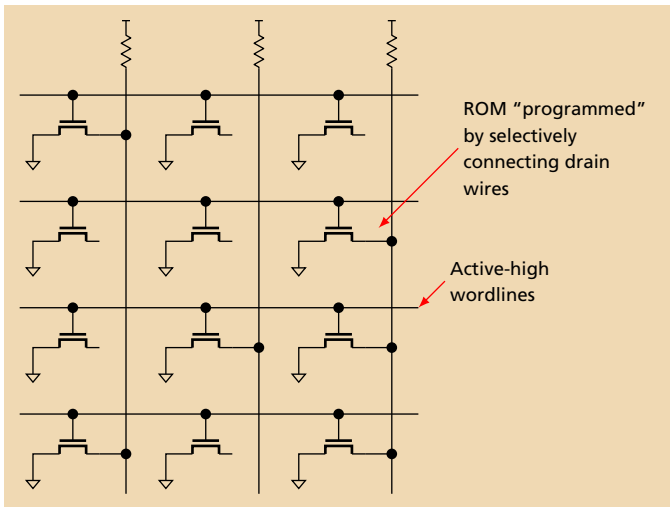

Mask ROM Die Photo

 


Color PROM in Pac-Man

  


00	00	█
01	07	█
02	66	█
03	EF	█
04	00	█
05	F8	█
06	EA	█
07	6F	█
08	00	█
09	3F	█
0A	00	█
0B	C9	█
0C	38	█
0D	AA	█
0E	AF	█
0F	F6	█
10	00	█
⋮	⋮	
1F	00	█

A Floating Gate MOSFET

 


Cross section of a NOR FLASH transistor. Kawai et al., ISSCC 2008 (Renesas)

Floating Gate n-channel MOSFET

 


Floating gate uncharged; Control gate at 0V: Off

Floating Gate n-channel MOSFET

 


Floating gate uncharged; Control gate positive: On

Floating Gate n-channel MOSFET

 



Floating gate negative; Control gate at 0V: Off

Floating Gate n-channel MOSFET

 


Floating gate negative; Control gate positive: Off


 
 
EPROMs and FLASH use Floating-Gate MOSFETs



Static Random-Access Memory Cell

 


Layout of a 6T SRAM Cell

   


Weste and Harris. *Introduction to CMOS VLSI Design*. Addison-Wesley, 2010.


Intel's 2102 SRAM, 1024 × 1 bit, 1972

 


2102 Block Diagram

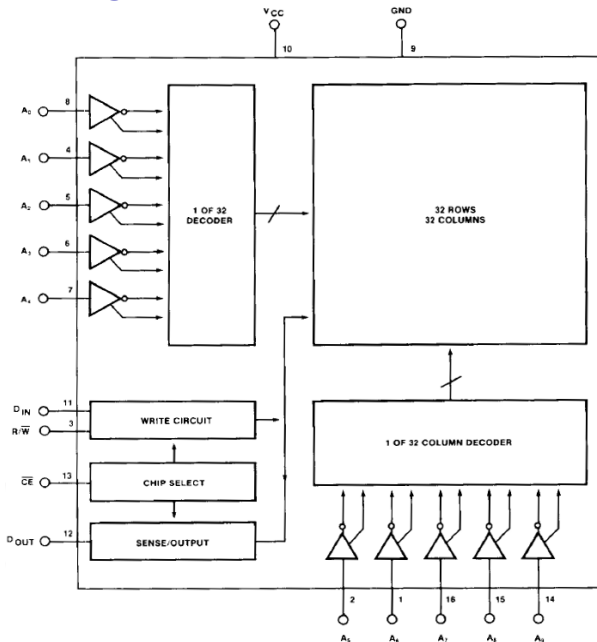


SRAM Timing

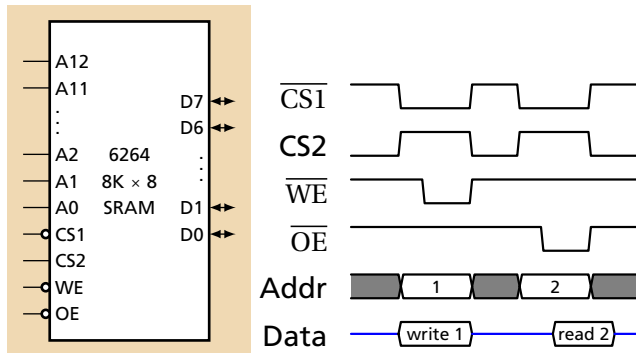



6264 SRAM Block Diagram

 



Galaga CPU detail (Namco/Midway 1981)

 


Dynamic RAM Cell

  

Our Old Pal, the Space Race ROM

  

Our Old Pal, the Space Race ROM

 


The decoder or
"AND plane"

In a RAM or ROM,
computes every
minterm

Pattern is not
programmable

Our Old Pal, the Space Race ROM

 


The decoder or "OR plane"

One term for every output


Pattern is programmable = the contents of the ROM

Our Old Pal, the Space Race ROM

 

Can we do better?


Simplifying the Space Race ROM

 

Essential minterms mean don't expand these




Our New PAL, the Space Race ROM

 

$$D_0 = 32\bar{1}0$$


Our New PAL, the Space Race ROM

 

$$D_0 = 32\bar{1}0$$

$$D_1 = 32\bar{1}$$

Our New PAL, the Space Race ROM

 


$$D_0 = 3\bar{2}10$$

$$D_1 = 3\bar{2}1$$

$$D_2 = 3\bar{2}10 + 3\bar{2}10$$

Our New PAL, the Space Race ROM

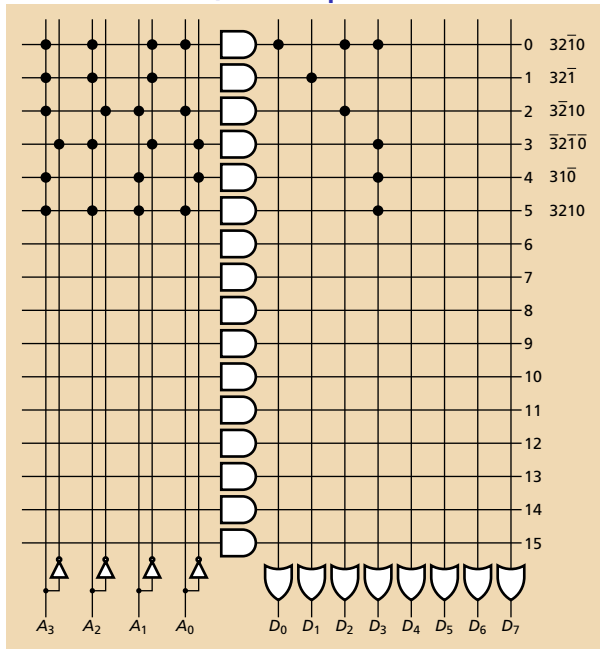


$$D_0 = 3\bar{2}\bar{1}0$$

$$D_1 = 3\bar{2}\bar{1}$$

$$D_2 = \bar{3}\bar{2}10 + 3\bar{2}\bar{1}0$$

$$D_3 = \bar{3}\bar{2}\bar{1}0 + 31\bar{0} + 3\bar{2}\bar{1}0 + 3210$$

Our New PAL, the Space Race ROM

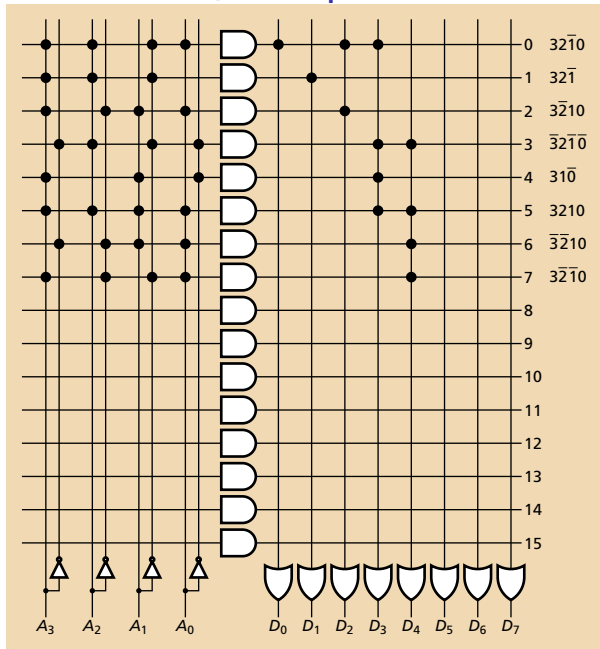

$$D_0 = 32\bar{1}0$$


$$D_1 = 32\bar{1}\bar{1}$$

$$D_2 = 3\bar{2}10 + 32\bar{1}0$$

$$D_3 = \bar{3}2\bar{1}0 + 31\bar{0} + 32\bar{1}0 + 3210$$

$$D_4 = \bar{3}210 + \bar{3}2\bar{1}0 + 3\bar{2}\bar{1}0 + 3210$$

Our New PAL, the Space Race ROM

 

$$D_0 = 3\bar{2}\bar{1}0$$

$$D_1 = 3\bar{2}\bar{1}$$


$$D_2 = \bar{3}\bar{2}\bar{1}0 + 3\bar{2}\bar{1}0$$

$$D_3 = \bar{3}\bar{2}\bar{1}0 + 3\bar{1}0 + \bar{3}\bar{2}\bar{1}0 + 3\bar{2}\bar{1}0$$

$$D_4 = \bar{3}\bar{2}\bar{1}0 + \bar{3}\bar{2}\bar{1}0 + \bar{3}\bar{2}\bar{1}0 + 3\bar{2}\bar{1}0$$

$$D_5 = \bar{3}\bar{1}0 + 20 + 21 + \bar{3}\bar{2}\bar{1}0 + \bar{3}\bar{2}\bar{1}0$$

Our New PAL, the Space Race ROM

 

$$D_0 = 3\bar{2}\bar{1}0$$

$$D_1 = 3\bar{2}\bar{1}$$

$$D_2 = 3\bar{2}\bar{1}0 + 3\bar{2}\bar{1}0$$


$$D_3 = \bar{3}\bar{2}\bar{1}\bar{0} + 3\bar{1}\bar{0} + 3\bar{2}\bar{1}0 + 3\bar{2}\bar{1}0$$

$$D_4 = \bar{3}\bar{2}\bar{1}0 + \bar{3}\bar{2}\bar{1}\bar{0} + \bar{3}\bar{2}\bar{1}0 + 3\bar{2}\bar{1}0$$

$$D_5 = \bar{3}\bar{1}\bar{0} + 20 + 21 + \bar{3}\bar{2}\bar{1}0 + \bar{3}\bar{2}\bar{1}0$$

$$D_6 = \bar{3}\bar{2}\bar{1}0 + 3\bar{2}\bar{1}0$$

Our New PAL, the Space Race ROM

 

$$D_0 = 3210$$

$$D_1 = 321$$

$$D_2 = 3210 + 3210$$

$$D_3 = \bar{3}2\bar{1}\bar{0} + 31\bar{0} + 32\bar{1}0 + 3210$$

$$D_4 = \bar{3}2\bar{1}0 + \bar{3}2\bar{1}\bar{0} + 32\bar{1}0 + 3210$$


$$D_5 = \bar{3}1\bar{0} + 20 + 21 + \bar{3}2\bar{1}\bar{0} + 32\bar{1}\bar{0}$$

$$D_6 = \bar{3}2\bar{1}\bar{0} + 3210$$

$$D_7 = \bar{3}2\bar{1}\bar{0} + 3210$$

Saved two ANDs

A 22V10 PAL: Programmable AND/Fixed OR

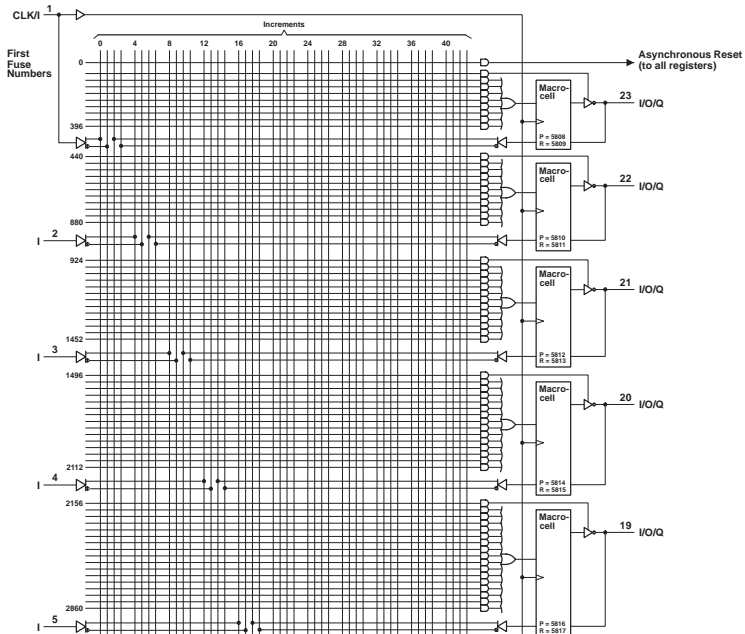

Field-Programmable Gate Arrays (FPGAs)

