

Fundamentals of Computer Systems



Memory

Stephen A. Edwards


Columbia University

Summer 2021


Atari Space Race, 1973

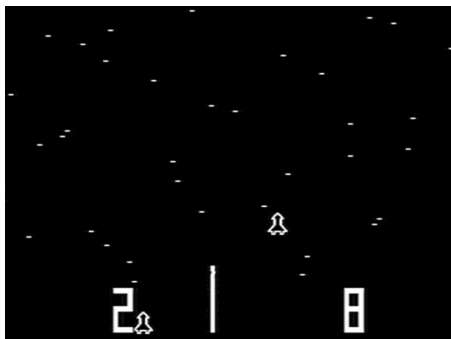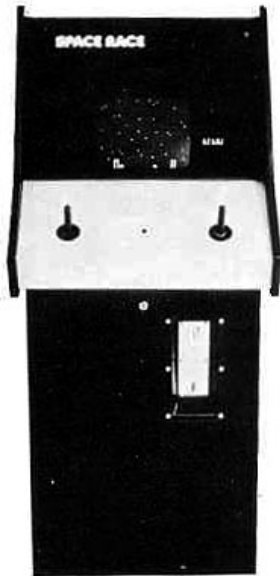

Atari Space Race PCB


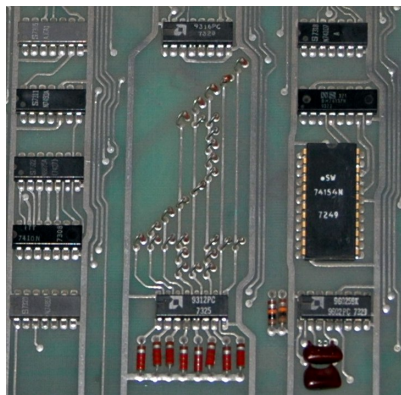


Front

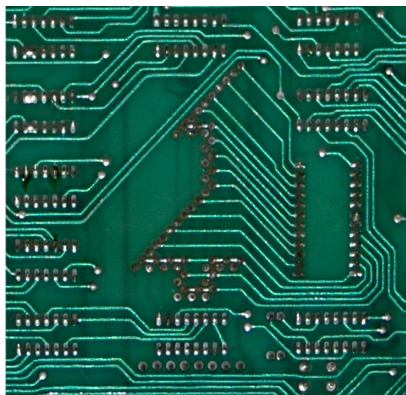


Back (mirrored)

  
Read-Only Memories: Combinational Functions




Implementing ROMs

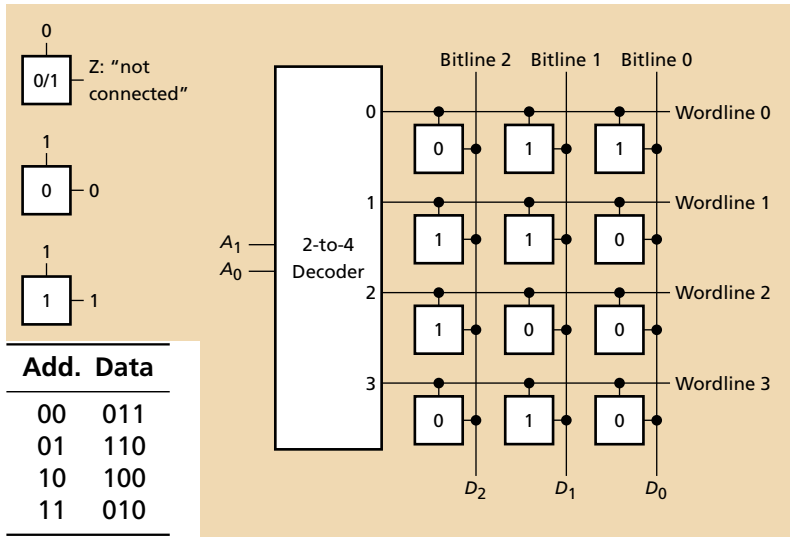

Implementing ROMs

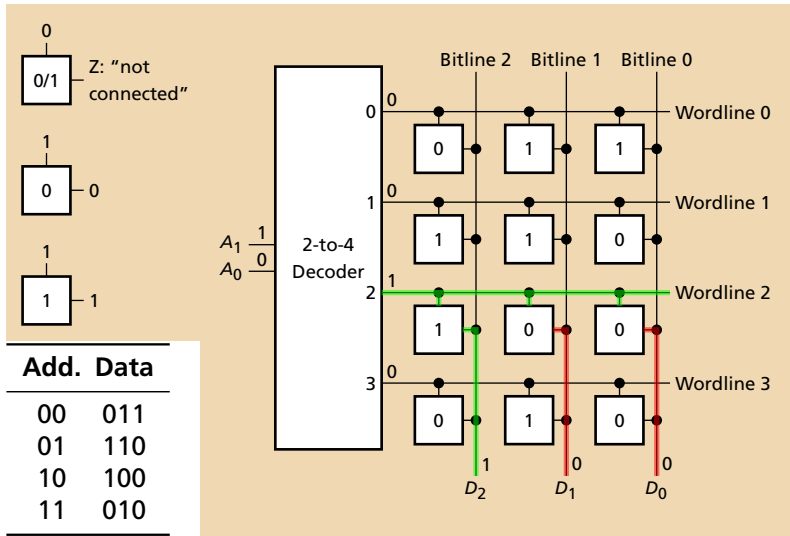


Implementing ROMs

 


Add. Data


00	011
01	110
10	100
11	010

 

Implementing ROMs

 

 
The 1971 DEC M792-YB Bootstrap Diode Matrix




32-word, 16-bit (64-byte) ROM diode matrix

CMOS Mask-Programmed ROMs



Add. Data	
00	011
01	110
10	100
11	010

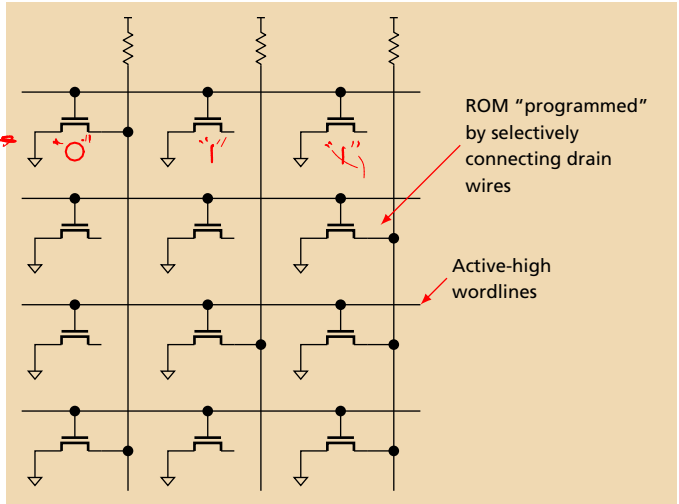

Mask ROM Die Photo

 


Color PROM in Pac-Man

  


A	0	
00	00	█
01	07	█
02	66	█
03	EF	█
04	00	█
05	F8	█
06	EA	█
07	6F	█
08	00	█
09	3F	█
0A	00	█
0B	C9	█
0C	38	█
0D	AA	█
0E	AF	█
0F	F6	█
10	00	
⋮	⋮	
1F	00	

A Floating Gate MOSFET

 


Cross section of a NOR FLASH transistor. Kawai et al., ISSCC 2008 (Renesas)

Floating Gate n-channel MOSFET

 


Floating gate uncharged; Control gate at 0V: Off

Floating Gate n-channel MOSFET

 


Floating gate uncharged; Control gate positive: On

Floating Gate n-channel MOSFET

 

Floating gate negative; Control gate at 0V: Off



Floating Gate n-channel MOSFET

 

Floating gate negative; Control gate positive: Off


EPROMs and FLASH use Floating-Gate MOSFETs

Floating gates


 
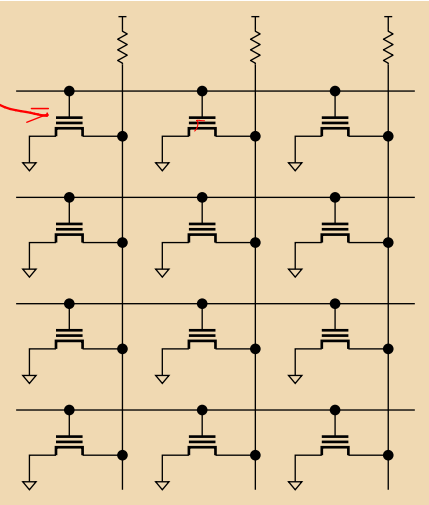


Static Random-Access Memory Cell

Bistable element

 


Layout of a 6T SRAM Cell

  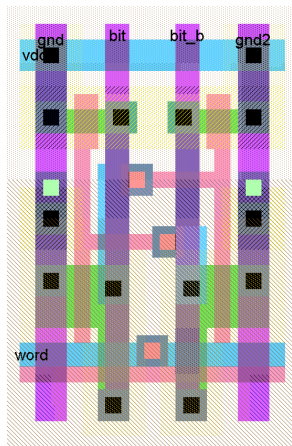

Weste and Harris. *Introduction to CMOS VLSI Design*. Addison-Wesley, 2010.

Intel's 2102 SRAM, 1024 × 1 bit, 1972

 


512
bits


16
rows

92 columns


2102 Block Diagram

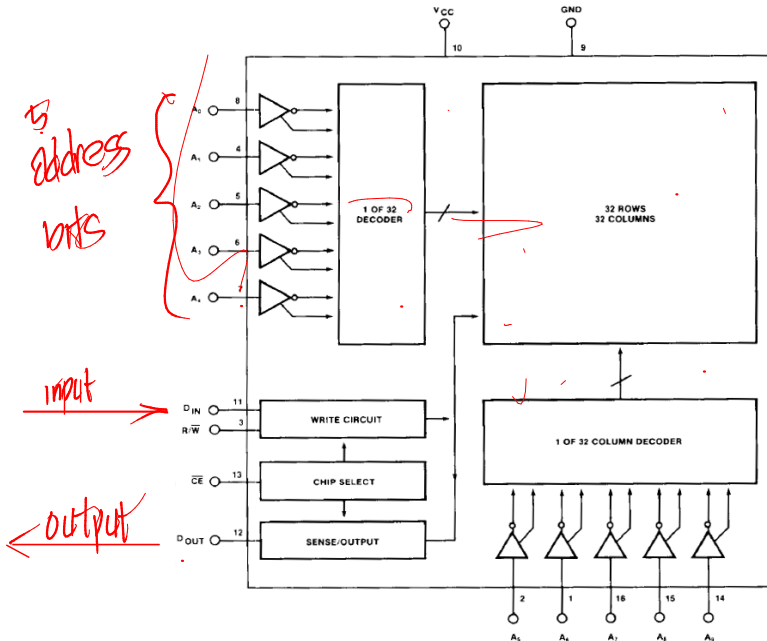


SRAM Timing

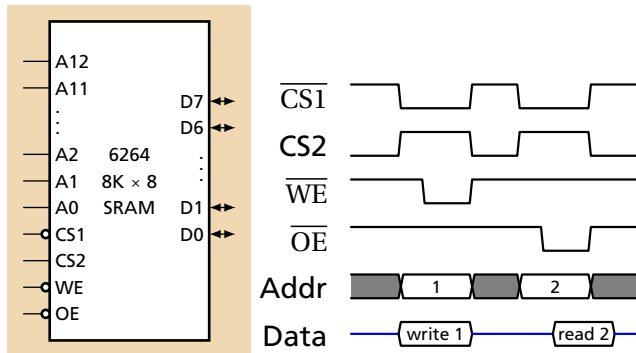

6264 SRAM Block Diagram

 


Galaga CPU detail (Namco/Midway 1981)

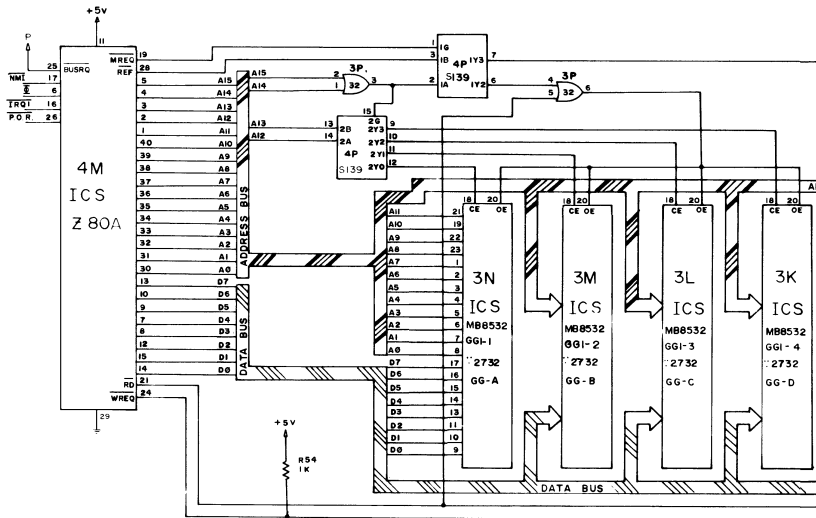


Dynamic RAM Cell

DRAM


 


1T


1C1R

 

Our Old Pal, the Space Race ROM

  

Our Old Pal, the Space Race ROM

 


The decoder or
"AND plane"

In a RAM or ROM,
computes every
minterm

Pattern is not
programmable

Our Old Pal, the Space Race ROM

 


The decoder or “OR plane”

One term for every output


Pattern is programmable = the contents of the ROM

Our Old Pal, the Space Race ROM

 

Can we do better?

Simplifying the Space Race ROM

 


Essential minterms

mean don't expand these




Our New PAL, the Space Race ROM

 

$$D_0 = 32\bar{1}0$$


Our New PAL, the Space Race ROM

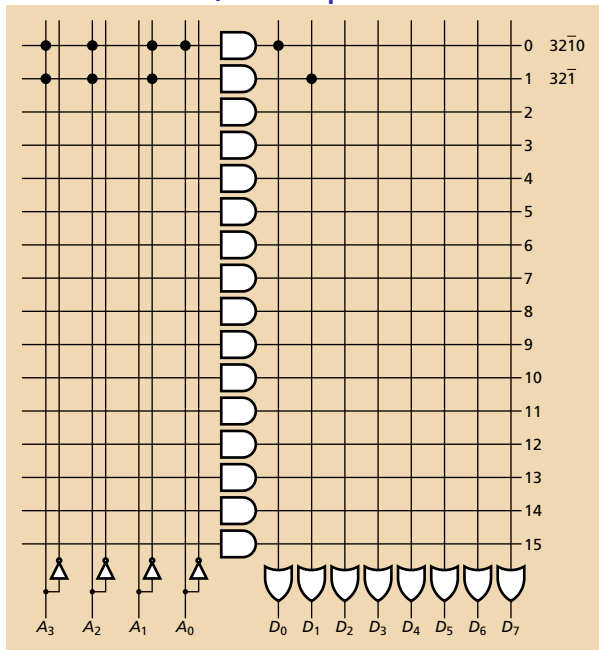

$$D_0 = 32\bar{1}0$$

$$D_1 = 32\bar{1}$$

Our New PAL, the Space Race ROM

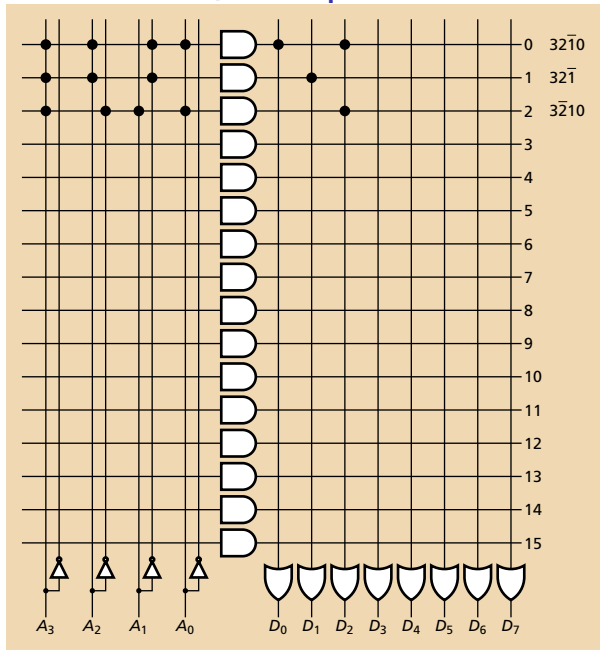


$$D_0 = 3\bar{2}\bar{1}0$$

$$D_1 = 3\bar{2}\bar{1}$$

$$D_2 = 3\bar{2}\bar{1}0 + 3\bar{2}10$$

Our New PAL, the Space Race ROM

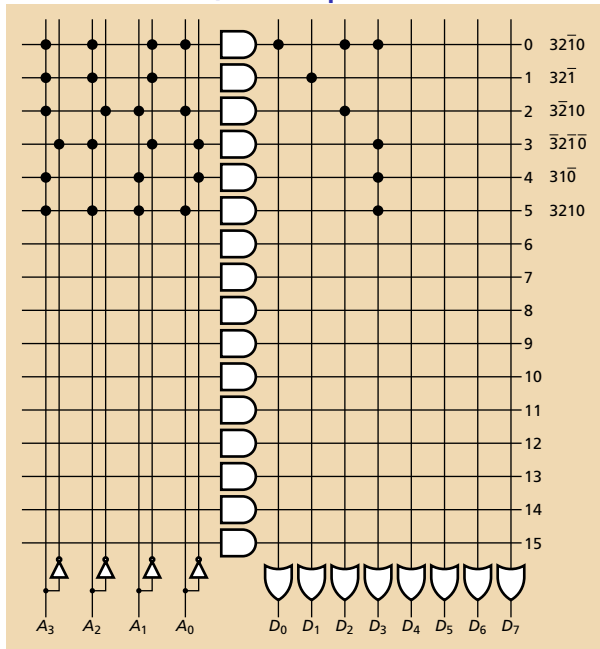


$$D_0 = 32\bar{1}0$$

$$D_1 = 32\bar{1}$$

$$D_2 = 3\bar{2}10 + 32\bar{1}0$$

$$D_3 = \bar{3}2\bar{1}0 + 31\bar{0} + 32\bar{1}0 + 3210$$

Our New PAL, the Space Race ROM

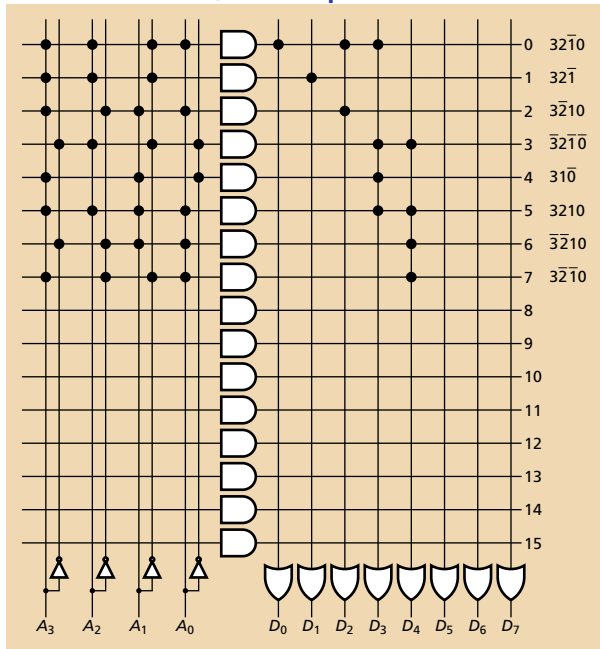

$$D_0 = 32\bar{1}0$$


$$D_1 = 32\bar{1}$$

$$D_2 = 3\bar{2}10 + 32\bar{1}0$$

$$D_3 = \bar{3}2\bar{1}0 + 31\bar{0} + 3\bar{2}10 + 3210$$

$$D_4 = \bar{3}\bar{2}10 + \bar{3}2\bar{1}0 + \bar{3}\bar{2}\bar{1}0 + 3210$$

Our New PAL, the Space Race ROM

 

$$D_0 = 32\bar{1}0$$

$$D_1 = 32\bar{1}$$


$$D_2 = 3\bar{2}10 + 32\bar{1}0$$

$$D_3 = \bar{3}2\bar{1}0 + 31\bar{0} + 32\bar{1}0 + 3210$$

$$D_4 = \bar{3}\bar{2}10 + \bar{3}2\bar{1}0 + 3\bar{2}\bar{1}0 + 3210$$

$$D_5 = \bar{3}1\bar{0} + 20 + 21 + \bar{3}2\bar{1}0 + 32\bar{1}0$$

Our New PAL, the Space Race ROM

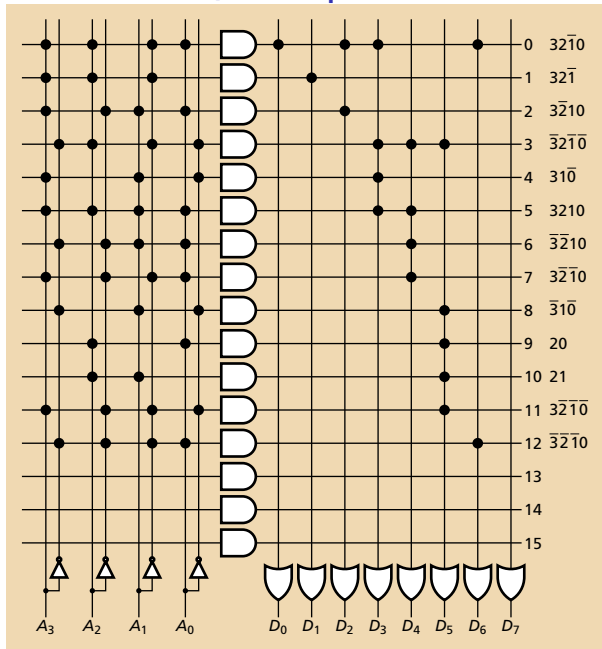

$$D_0 = \bar{3}\bar{2}\bar{1}0$$

$$D_1 = 3\bar{2}\bar{1}$$

$$D_2 = \bar{3}\bar{2}10 + 3\bar{2}\bar{1}0$$


$$D_3 = \bar{3}\bar{2}\bar{1}\bar{0} + 3\bar{1}\bar{0} + \bar{3}\bar{2}10 + 3210$$

$$D_4 = \bar{3}\bar{2}10 + \bar{3}\bar{2}\bar{1}\bar{0} + \bar{3}\bar{2}\bar{1}0 + 3210$$

$$D_5 = \bar{3}\bar{1}\bar{0} + 20 + 21 + \bar{3}\bar{2}\bar{1}\bar{0} + \bar{3}\bar{2}\bar{1}0$$

$$D_6 = \bar{3}\bar{2}\bar{1}0 + 3\bar{2}\bar{1}0$$

Our New PAL, the Space Race ROM

 

$$D_0 = 32\bar{1}0$$

$$D_1 = 32\bar{1}$$

$$D_2 = 3\bar{2}10 + 32\bar{1}0$$

$$D_3 = \bar{3}2\bar{1}0 + 31\bar{0} + 32\bar{1}0 + 3210$$

$$D_4 = \bar{3}\bar{2}10 + \bar{3}2\bar{1}0 + \bar{3}2\bar{1}0 + 32\bar{1}0 + 3210$$


$$D_5 = \bar{3}1\bar{0} + 20 + 21 + \bar{3}2\bar{1}0 + \bar{3}2\bar{1}0$$

$$D_6 = \bar{3}\bar{2}\bar{1}0 + 32\bar{1}0$$

$$D_7 = \bar{3}\bar{2}\bar{1}0 + 32\bar{1}0$$

Saved two ANDs

A 22V10 PAL: Programmable AND/Fixed OR

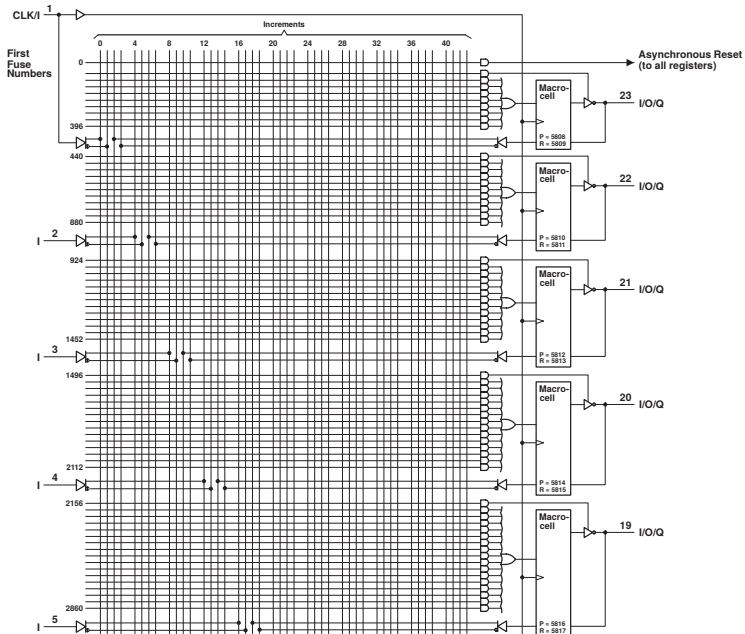

Field-Programmable Gate Arrays (FPGAs)

