

Understand Video Games; Understand Everything

Stephen A. Edwards

Columbia University



The Subject of this Lecture

0

The Subjects of this Lecture


0

1


But let your communication be, Yea, yea; Nay, nay: for whatsoever is more than these cometh of evil.

— Matthew 5:37

Engineering Works Because of Abstraction

 

Application Software	COMS 3157, 4156, et al.
Operating Systems	COMS W4118
Architecture	COMS W3827
Micro-Architecture	COMS W3827
Logic	COMS W3827
Digital Circuits	COMS W3827
Analog Circuits	ELEN 3331
Devices	ELEN 3106
Physics	ELEN 3106 et al.

 

There are only 10 types
of people in the world:
Those who understand binary
and those who don't.

Boolean Logic

AN INVESTIGATION

OF

THE LAWS OF THOUGHT,


ON WHICH ARE FOUNDED

THE MATHEMATICAL THEORIES OF LOGIC
AND PROBABILITIES.

BY

GEORGE BOOLE, LL.D.

 PROFESSOR OF MATHEMATICS IN QUEEN'S COLLEGE, CORK.



George Boole
1815–1864

LONDON:
WALTON AND MABERY,
UPPER GOWER-STREET, AND IVY-LANE, PATERNOSTER-ROW.
CAMBRIDGE: MACMILLAN AND CO.

1854.

Boole's Intuition Behind Boolean Logic

Variables X, Y, \dots represent classes of things

No imprecision: A thing either is or is not in a class

If X is “sheep”
and Y is “white
things,” XY are
all white sheep,

$$XY = YX$$

and

$$XX = X.$$

If X is “men”
and Y is
“women,” $X + Y$
is “both men
and women,”

$$X + Y = Y + X$$

and

$$X + X = X.$$

If X is “men,” Y
is “women,” and
 Z is “European,”
 $Z(X + Y)$ is
“European men
and women”
and

$$Z(X+Y) = ZX+ZY.$$

Simplifying a Boolean Expression

“You are a New Yorker if you were born in New York or were not born in New York and lived here ten years.”

$X = \text{born in New York}$

$Y = \text{lived here ten years}$

$$X + (\bar{X} \cdot Y)$$

Axioms

$$X + Y = Y + X$$

$$X \cdot Y = Y \cdot X$$

$$X + (Y + Z) = (X + Y) + Z$$

$$X \cdot (Y \cdot Z) = (X \cdot Y) \cdot Z$$

$$X + (X \cdot Y) = X$$

$$X \cdot (X + Y) = X$$

$$X \cdot (Y + Z) = (X \cdot Y) + (X \cdot Z)$$

$$X + (Y \cdot Z) = (X + Y) \cdot (X + Z)$$

$$X + \bar{X} = 1$$

$$X \cdot \bar{X} = 0$$

Lemma:

$$\begin{aligned} X \cdot 1 &= X \cdot (X + \bar{X}) \\ &= X \cdot (X + Y) \text{ if } Y = \bar{X} \\ &= X \end{aligned}$$

Simplifying a Boolean Expression

“You are a New Yorker if you were born in New York or were not born in New York and lived here ten years.”

$X = \text{born in New York}$

$Y = \text{lived here ten years}$

$$\begin{aligned} X + (\bar{X} \cdot Y) \\ = (X + \bar{X}) \cdot (X + Y) \end{aligned}$$

Axioms

$$\begin{aligned} X + Y &= Y + X \\ X \cdot Y &= Y \cdot X \\ X + (Y + Z) &= (X + Y) + Z \\ X \cdot (Y \cdot Z) &= (X \cdot Y) \cdot Z \\ X + (X \cdot Y) &= X \\ X \cdot (X + Y) &= X \\ X \cdot (Y + Z) &= (X \cdot Y) + (X \cdot Z) \\ X + (Y \cdot Z) &= (X + Y) \cdot (X + Z) \\ X + \bar{X} &= 1 \\ X \cdot \bar{X} &= 0 \end{aligned}$$

Lemma:

$$\begin{aligned} X \cdot 1 &= X \cdot (X + \bar{X}) \\ &= X \cdot (X + Y) \text{ if } Y = \bar{X} \\ &= X \end{aligned}$$

Simplifying a Boolean Expression

“You are a New Yorker if you were born in New York or were not born in New York and lived here ten years.”

$X = \text{born in New York}$

$Y = \text{lived here ten years}$

$$X + (\bar{X} \cdot Y)$$

$$= (X + \bar{X}) \cdot (X + Y)$$

$$= 1 \cdot (X + Y)$$

Axioms

$$X + Y = Y + X$$

$$X \cdot Y = Y \cdot X$$

$$X + (Y + Z) = (X + Y) + Z$$

$$X \cdot (Y \cdot Z) = (X \cdot Y) \cdot Z$$

$$X + (X \cdot Y) = X$$

$$X \cdot (X + Y) = X$$

$$X \cdot (Y + Z) = (X \cdot Y) + (X \cdot Z)$$

$$X + (Y \cdot Z) = (X + Y) \cdot (X + Z)$$

$$\color{red}{X + \bar{X} = 1}$$

$$X \cdot \bar{X} = 0$$

Lemma:

$$\begin{aligned} X \cdot 1 &= X \cdot (X + \bar{X}) \\ &= X \cdot (X + Y) \text{ if } Y = \bar{X} \\ &= X \end{aligned}$$

Simplifying a Boolean Expression

“You are a New Yorker if you were born in New York or were not born in New York and lived here ten years.”

$X = \text{born in New York}$

$Y = \text{lived here ten years}$

$$\begin{aligned} X + (\bar{X} \cdot Y) \\ &= (X + \bar{X}) \cdot (X + Y) \\ &= 1 \cdot (X + Y) \\ &= X + Y \end{aligned}$$






Axioms

$$\begin{aligned} X + Y &= Y + X \\ X \cdot Y &= Y \cdot X \\ X + (Y + Z) &= (X + Y) + Z \\ X \cdot (Y \cdot Z) &= (X \cdot Y) \cdot Z \\ X + (X \cdot Y) &= X \\ X \cdot (X + Y) &= X \\ X \cdot (Y + Z) &= (X \cdot Y) + (X \cdot Z) \\ X + (Y \cdot Z) &= (X + Y) \cdot (X + Z) \\ X + \bar{X} &= 1 \\ X \cdot \bar{X} &= 0 \end{aligned}$$

Lemma:


$$\begin{aligned} X \cdot 1 &= X \cdot (X + \bar{X}) \\ &= X \cdot (X + Y) \text{ if } Y = \bar{X} \\ &= X \end{aligned}$$

Alternate Notations for Boolean Logic

     Operator	Math	Engineer	Schematic
Copy	x	X	 or 
Complement	$\neg x$	\bar{X}	
AND	$x \wedge y$	XY or $X \cdot Y$	
OR	$x \vee y$	$X + Y$	


Expressions to Schematics

$$F = \bar{X}Y + X\bar{Y}$$

 


Expressions to Schematics

$$F = \bar{X}Y + X\bar{Y}$$

 


Expressions to Schematics

$$F = \bar{X}Y + X\bar{Y}$$

 


Expressions to Schematics

$$F = \bar{X}Y + X\bar{Y}$$

 


Expressions to Schematics

$$F = \bar{X}Y + X\bar{Y}$$

 

Expressions to Schematics
 
$$F = \bar{X}Y + X\bar{Y} = (X + Y)(\bar{X} + \bar{Y})$$



The Decimal Positional Numbering System



Ten figures: 0 1 2 3 4 5 6 7 8 9

$$7 \times 10^2 + 3 \times 10^1 + 0 \times 10^0 = 730_{10}$$

$$9 \times 10^2 + 9 \times 10^1 + 0 \times 10^0 = 990_{10}$$

Why base ten?



Binary



DEC PDP-8/I, c. 1968

Dec	Bin
0	0
1	1
2	10
3	11
4	100
5	101
6	110
7	111
8	1000
9	1001
10	1010

$$\begin{aligned}
 \text{PC} &= 0 \times 2^{11} + 1 \times 2^{10} + 0 \times 2^9 + 1 \times 2^8 + 1 \times 2^7 + 0 \times 2^6 + \\
 &\quad 1 \times 2^5 + 1 \times 2^4 + 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 \\
 &= 1469_{10}
 \end{aligned}$$

Binary Addition Algorithm

$$\begin{array}{r} 10011 \\ +11001 \\ \hline \end{array}$$

$$1 + 1 = \textcolor{red}{10}$$

+	0	1
0	00	01
1	01	10
10	10	11

Binary Addition Algorithm

$$\begin{array}{r} & 1 \\ & 10011 \\ + & 11001 \\ \hline & 0 \end{array}$$

$$\begin{array}{rcl} 1 + 1 & = & 10 \\ 1 + 1 + 0 & = & 10 \end{array}$$

+	0	1
0	00	01
1	01	10
10	10	11

Binary Addition Algorithm

$$\begin{array}{r} 11 \\ 10011 \\ +11001 \\ \hline 00 \end{array}$$

$$\begin{aligned} 1 + 1 &= 10 \\ 1 + 1 + 0 &= 10 \\ 1 + 0 + 0 &= 01 \end{aligned}$$

+	0	1
0	00	01
1	01	10
10	10	11

Binary Addition Algorithm

$$\begin{array}{r} 011 \\ 10011 \\ +11001 \\ \hline 100 \end{array}$$

$$\begin{aligned} 1 + 1 &= 10 \\ 1 + 1 + 0 &= 10 \\ 1 + 0 + 0 &= 01 \\ 0 + 0 + 1 &= 01 \end{aligned}$$

+	0	1
0	00	01
1	01	10
10	10	11

Binary Addition Algorithm

$$\begin{array}{r} 0011 \\ 10011 \\ +11001 \\ \hline 1100 \end{array}$$

$$\begin{aligned} 1 + 1 &= 10 \\ 1 + 1 + 0 &= 10 \\ 1 + 0 + 0 &= 01 \\ 0 + 0 + 1 &= 01 \\ 0 + 1 + 1 &= 10 \end{aligned}$$

+	0	1
0	00	01
1	01	10
10	10	11

Binary Addition Algorithm

$$\begin{array}{r} \textcolor{red}{10011} \\ 10011 \\ + \textcolor{blue}{11001} \\ \hline \textcolor{blue}{101100} \end{array}$$

$$\begin{aligned} 1 + 1 &= \textcolor{red}{10} \\ 1 + 1 + 0 &= \textcolor{red}{10} \\ 1 + 0 + 0 &= \textcolor{red}{01} \\ 0 + 0 + 1 &= \textcolor{red}{01} \\ 0 + 1 + 1 &= \textcolor{red}{10} \end{aligned}$$

+	0	1
0	00	01
1	01	10
10	10	11



Arithmetic Circuits

Arithmetic: Addition

Adding two one-bit numbers:


A and B

Produces a two-bit result:

C S

(carry and sum)

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

Half Adder



Male Adder



Full Adder

In general,
you need to
add *three*
bits:



$$\begin{array}{r} \textcolor{red}{111000} \\ 111010 \\ + 11100 \\ \hline 1010110 \end{array}$$

$$\begin{aligned} 0 + 0 &= 00 \\ 0 + 1 + 0 &= 01 \\ 0 + 0 + 1 &= 01 \\ 0 + 1 + 1 &= 10 \\ 1 + 1 + 1 &= 11 \\ 1 + 1 + 0 &= 10 \end{aligned}$$


$C_i A B$	$C_o S$
000	0 0
001	0 1
010	0 1
011	1 0
100	0 1
101	1 0
110	1 0
111	1 1

  

A Four-Bit Ripple-Carry Adder

  

PONG

 

PONG, Atari 1973

Built from TTL logic gates; no computer, no software

Launched the video arcade game revolution

Horizontal Ball Control in PONG

M	L	R	A	B
0	0	0	X	X
0	0	1	0	1
0	1	0	0	1
0	1	1	X	X
1	0	0	X	X
1	0	1	1	0
1	1	0	1	1
1	1	1	X	X

The ball moves either left or right.

Part of the control circuit has three inputs: M ("move"), L ("left"), and R ("right").

It produces two outputs A and B .

Here, "X" means "I don't care what the output is; I never expect this input combination to occur."

Horizontal Ball Control in PONG

M	L	R	A	B
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	0	0
1	0	0	0	0
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

Assume all the X's are 0's:

$$A = M\bar{L}R + M\bar{L}\bar{R}$$

$$B = \bar{M}\bar{L}R + \bar{M}\bar{L}\bar{R} + M\bar{L}\bar{R}$$

3 inv + 4 AND3 + 1 OR2 + 1 OR3

Horizontal Ball Control in PONG

M	L	R	A	B
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	1	0

Choosing better values for the X's:

$$A = ML + MR$$

$$B = \overline{MR}$$

3 NAND2

Horizontal Ball Control in PONG

M	L	R	A	B
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	1	1
1	0	1	1	0
1	1	0	1	1
1	1	1	1	0


Being even more clever:

$$A = M$$


$$B = \overline{MR}$$

1 NAND2

The Actual Pong Circuit

 

Pong,
Atari, 1972

 

Winner,
Midway, 1973

HORIZONTAL DIRECTION

Karnaugh Maps

Basic trick: put “similar” variable values near each other so simple functions are obvious

<i>M</i>	<i>L</i>	<i>R</i>	<i>A</i>	<i>B</i>
0	0	0	X	X
0	0	1	0	1
0	1	0	0	1
0	1	1	X	X
1	0	0	X	X
1	0	1	1	0
1	1	0	1	1
1	1	1	X	X

The *M*'s are already arranged nicely

Karnaugh Maps

Basic trick: put “similar” variable values near each other so simple functions are obvious

<i>M</i>	<i>L</i>	<i>R</i>	<i>A</i>	<i>B</i>	
0	0	0	X	X	Let's rearrange the <i>L</i> 's by permuting two pairs of rows
0	0	1	0	1	
0	1	0	0	1	
0	1	1	X	X	
1	0	0	X	X	
1	0	1	1	0	
	1	1	0	1	
	1	1	1	X	

Karnaugh Maps

Basic trick: put “similar” variable values near each other so simple functions are obvious

<i>M</i>	<i>L</i>	<i>R</i>	<i>A</i>	<i>B</i>	
0	0	0	X	X	Let's rearrange the <i>L</i> 's by permuting two pairs of rows
0	0	1	0	1	
0	1	0	0	1	
0	1	1	X	X	
1	0	0	X	X	
1	0	1	1	0	
			1	1	0
			1	1	1
			1	X	X

Karnaugh Maps

Basic trick: put “similar” variable values near each other so simple functions are obvious

<i>M</i>	<i>L</i>	<i>R</i>	<i>A</i>	<i>B</i>	
0	0	0	X	X	Let's rearrange the <i>L</i> 's by permuting two pairs of rows
0	0	1	0	1	
0	1	0	0	1	
0	1	1	X	X	
1	0	0	X	X	
1	0	1	1	0	1 1 0 1 1
					1 1 X X

Karnaugh Maps

Basic trick: put “similar” variable values near each other so simple functions are obvious

<i>M</i>	<i>L</i>	<i>R</i>	<i>A</i>	<i>B</i>
0	0	0	X	X
0	0	1	0	1
0	1	0	0	1
0	1	1	X	X

Let's rearrange the
L's by permuting two
pairs of rows

1	0	0	X	X	1	1	0	1	1
1	0	1	1	0	1	1	1	X	X

Karnaugh Maps

Basic trick: put “similar” variable values near each other so simple functions are obvious

<i>M</i>	<i>L</i>	<i>R</i>	<i>A</i>	<i>B</i>			
0	0	0	X	X	Let's rearrange the <i>L</i> 's by permuting two pairs of rows		
0	0	1	0	1			
0	1	0	0	1			
0	1	1	X	X			
			1	1	0	1	1
			1	1	1	X	X
1	0	0	X	X			
1	0	1	1	0			

Karnaugh Maps

Basic trick: put “similar” variable values near each other so simple functions are obvious

<i>M</i>	<i>L</i>	<i>R</i>	<i>A</i>	<i>B</i>			
0	0	0	X	X	Let's rearrange the <i>L</i> 's by permuting two pairs of rows		
0	0	1	0	1			
0	1	0	0	1			
0	1	1	X	X			
			1	1	0	1	1
			1	1	1	X	X
1	0	0	X	X			
1	0	1	1	0			

Karnaugh Maps

Basic trick: put “similar” variable values near each other so simple functions are obvious

<i>M</i>	<i>L</i>	<i>R</i>	<i>A</i>	<i>B</i>	
0	0	0	X	X	Let's rearrange the <i>L</i> 's by permuting two pairs of rows
0	0	1	0	1	
0	1	0	0	1	
0	1	1	X	X	
	1	1	0	1	1
	1	1	1	X	X
1	0	0	X	X	
1	0	1	1	0	

Karnaugh Maps

Basic trick: put “similar” variable values near each other so simple functions are obvious

<i>M</i>	<i>L</i>	<i>R</i>	<i>A</i>	<i>B</i>	
0	0	0	X	X	Let's rearrange the <i>L</i> 's by permuting two pairs of rows
0	0	1	0	1	
0	1	0	0	1	
0	1	1	X	X	
1	1	0	1	1	
1	1	1	X	X	
1	0	0	X	X	
1	0	1	1	0	

Karnaugh Maps

Basic trick: put “similar” variable values near each other so simple functions are obvious

<i>M</i>	<i>L</i>	<i>R</i>	<i>A</i>	<i>B</i>	
0	0	0	X	X	The <i>R</i> 's are really crazy; let's use the second dimension
0	0	1	0	1	
0	1	0	0	1	
0	1	1	X	X	
1	1	0	1	1	
1	1	1	X	X	
1	0	0	X	X	
1	0	1	1	0	

Karnaugh Maps

Basic trick: put “similar” variable values near each other so simple functions are obvious

M	L	R	A	B
0	0	0	x_0	x_1
0	1	0	0_x	1_x
1	1	0	1_x	1_x
1	0	0	x_1	x_0

The R 's are really crazy; let's use the second dimension

Karnaugh Maps

Basic trick: put “similar” variable values near each other so simple functions are obvious

M	L	R	A	B
00	00	01	X0	X1
00	11	01	0X	1X

The *R*'s are really crazy; let's use the second dimension

11 11 01 1X 1X

11 00 01 X1 X0

Karnaugh Maps

Basic trick: put “similar” variable values near each other so simple functions are obvious

M	L	R	A	B
00	00	01	X0	X1
00	11	01	0X	1X
11	11	01	1X	1X
11	00	01	X1	X0

Diagram illustrating the grouping of variables in a Karnaugh map:

- The first two columns (M and L) are grouped together by a red bracket labeled *MR*.
- The last two columns (A and B) are grouped together by a red bracket labeled *M*.

Maurice Karnaugh's Maps

The Map Method for Synthesis of Combinational Logic Circuits


M. KARNAUGH

NONMEMBER AIEE


THE SEARCH for simple abstract techniques to be applied to the design of switching systems is still, despite some recent advances, in its early stages. The problem in this area which has been attacked most energetically is that of the synthesis of efficient combinational that is, nonsequential, logic circuits.

be convenient to describe other methods in terms of Boolean algebra. Whenever the term "algebra" is used in this paper, it will refer to Boolean algebra, where addition corresponds to the logical connective "or," while multiplication corresponds to "and."

The minimizing chart,² developed at

 

(A)

 


(B)

Fig. 2. Graphical representations of the input conditions for three and for four variables

The Seven-Segment Decoder Example



W	X	Y	Z	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1
1	0	1	0	X	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X	X
1	1	1	1	0	0	0	0	0	0	0

 

Karnaugh Map for Seg. a

W	X	Y	Z	a
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	0

$$Z = \overbrace{\begin{matrix} 1 & 0 & 1 & 1 \\ 0 & 1 & 1 & 1 \\ X & X & 0 & X \\ 1 & 1 & X & X \end{matrix}}^W}^X Y$$

The Karnaugh Map Sum-of-Products Challenge


Cover all the 1's and none of the 0's using **as few literals** (gate inputs) as possible.

Few, large rectangles are good.

Covering X's is optional.

Karnaugh Map for Seg. a

W	X	Y	Z	a
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	0

 

The minterm solution: cover each 1 with a single implicant.


$$a = \overline{W}\overline{X}Y\overline{Z} + \overline{W}\overline{X}YZ + \overline{W}\overline{X}Y\overline{Z} + \\ \overline{W}X\overline{Y}Z + \overline{W}XY\overline{Z} + \overline{W}XY\overline{Z} + \\ W\overline{X}\overline{Y}\overline{Z} + W\overline{X}\overline{Y}Z$$

$$8 \times 4 = 32 \text{ literals}$$

$$4 \text{ inv} + 8 \text{ AND4} + 1 \text{ OR8}$$

Karnaugh Map for Seg. a

W	X	Y	Z	a
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	0

 

Merging implicants helps

Recall the distributive law:
 $AB + AC = A(B + C)$


$$a = \overline{W}\overline{X}\overline{Y}\overline{Z} + \overline{W}Y + \overline{W}XZ + W\overline{X}\overline{Y}$$

$4 + 2 + 3 + 3 = 12$ literals

4 inv + 1 AND4 + 2 AND3 + 1 AND2
+ 1 OR4

Karnaugh Map for Seg. a

W	X	Y	Z	a
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	0

 

Missed one: Remember this is actually a torus.


$$a = \overline{X}\overline{Y}\overline{Z} + \overline{W}Y + \\ \overline{W}XZ + W\overline{X}\overline{Y}$$

$3 + 2 + 3 + 3 = 11$ literals

4 inv + 3 AND3 + 1 AND2 + 1 OR4

Karnaugh Map for Seg. a

W	X	Y	Z	a
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	0

 

Taking don't-cares into account, we can enlarge two implicants:


$$a = \overline{X}\overline{Z} + \overline{W}Y + \overline{W}XZ + W\overline{X}$$

$$2 + 2 + 3 + 2 = 9 \text{ literals}$$

$$3 \text{ inv} + 1 \text{ AND3} + 3 \text{ AND2} + 1 \text{ OR4}$$

Karnaugh Map for Seg. a

W	X	Y	Z	a
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	0

 

Can also compute the complement of the function and invert the result.

Covering the 0's instead of the 1's:


$$\bar{a} = \overline{W}\overline{X}\overline{Y}Z + X\overline{Y}\overline{Z} + WY$$

$$4 + 3 + 2 = 9 \text{ literals}$$


$$\begin{aligned} & 5 \text{ inv} + 1 \text{ AND4} + 1 \text{ AND3} + 1 \text{ AND2} \\ & + 1 \text{ OR3} \end{aligned}$$

Karnaugh Map for Seg. a

W	X	Y	Z	a
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	0

 

 To display the score, PONG used a chip with this:





Decoders


Decoders

Input: n -bit binary number


Output: 1-of- 2^n one-hot code

2-to-4 in out		3-to-8 decoder in out		4-to-16 decoder in out	
00	0001	000	00000001	0000	000000000000000000000001
01	0010	001	00000010	0001	000000000000000000000010
10	0100	010	00000100	0010	0000000000000000000000100
11	1000	011	00001000	0011	00000000000000000000001000
		100	00010000	0100	00000000000010000
		101	00100000	0101	0000000000100000
		110	01000000	0110	00000000001000000
		111	10000000	0111	00000000010000000
				1000	00000001000000000
				1001	00000010000000000
				1010	00000100000000000
				1011	00001000000000000
				1100	00010000000000000
				1101	00100000000000000
				1110	01000000000000000
				1111	10000000000000000

The 74138 3-to-8 Decoder

 

A '138 Spotted in the Wild

 


Pac-Man (Midway, 1980)



Multiplexers


The Two-Input Multiplexer

 

S	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


$$\begin{matrix} & \overset{A}{\overbrace{0 \ 1 \ 1}} & 0 \\ S \langle & \underset{B}{\overbrace{0 \ 0 \ 1 \ 1}} & \end{matrix}$$

S	B	A	Y
0	X	0	0
0	X	1	1
1	0	X	0
1	1	X	1

 

S	Y
0	A
1	B

Two-input Muxes in the Wild

 



Quad 2-to-1 mux 3B selects color from a sprite or the background

Pac-Man (Midway, 1980)





State-Holding Elements

Bistable Elements

  


Equivalent circuits; right is more traditional.

Two stable states:

  


A Bistable in the Wild

 

This “debounces” the coin switch.


Breakout, Atari 1976.

SR Latches in the Wild

 


Generates horizontal and vertical synchronization waveforms from counter bits.
Stunt Cycle, Atari 1976.


Atari Space Race, 1973

 

Atari Space Race PCB

 

Front

 


Back (mirrored)

Implementing ROMs

Add. Data


00	011
01	110
10	100
11	010

 


Implementing ROMs

Add. Data


00	011
01	110
10	100
11	010

 

Atari Space Race Schematic


 


 The 1971 DEC M792-YB Bootstrap Diode Matrix



32-word, 16-bit (64-byte) ROM diode matrix

Color PROM in Pac-Man

  


00	00	BLACK
01	07	RED
02	66	BROWN
03	EF	PINK
04	00	BLACK
05	F8	CYAN
06	EA	LIGHT BLUE
07	6F	ORANGE
08	00	BLACK
09	3F	YELLOW
0A	00	BLACK
0B	C9	BLUE
0C	38	GREEN
0D	AA	TEAL
0E	AF	ORANGE RED
0F	F6	LAVENDER
10	00	BLACK
:	:	
1F	00	BLACK

HIGH SCORE

360


4600

 

HIGH SCORE

360

4600

 


MARIO
000700

0x01


WORLD
8-1

TIME
242


0 0

 

NINTENDO

 


3RD
1:24:00

 


TIME
0:13:15

TUNNELS

 


©1982 TEXAS INSTRUMENTS


TMS9918 Video Display Processor

 


TMS9918 Video Display Processor

 


Nintendo NES/Famicom

 

TMS9918 Pattern Generation

 

TMS9918 Sprite Generation

 

TMS9918 Sprite Attribute Table Entry

BYTE		BIT							
		0	1	2	3	4	5	6	7
	0	VERTICAL POSITION							
	1	HORIZONTAL POSITION							
	2	NAME							
	3	EARLY CLOCK BIT	0	0	0		COLOR CODE		