


# Vintage Computing with FPGAs

Stephen A. Edwards

VCF East, May , 2018



MOS Technology KIM-1  
c. 1976

 

Altera Cyclone II FPGA  
c. 2004

# Software Emulation



# SIMH

```
void mos6502::Op_ADC(uint16_t src)
{
    uint8_t m = Read(src);
    unsigned int tmp = m + A + (IF_CARRY() ? 1 : 0);
    SET_ZERO(!(tmp & 0xFF));
    if (IF_DECIMAL()) {
        if (((A & 0xF) + (m & 0xF) + (IF_CARRY() ? 1 : 0)) > 9)
            tmp += 6;
        SET_NEGATIVE(tmp & 0x80);
        SET_OVERFLOW(!((A ^ m) & 0x80) && ((A ^ tmp) & 0x80));
        if (tmp > 0x99)
            tmp += 96;
        SET_CARRY(tmp > 0x99);
    } else {
        SET_NEGATIVE(tmp & 0x80);
        SET_OVERFLOW(!((A ^ m) & 0x80) && ((A ^ tmp) & 0x80));
        SET_CARRY(tmp > 0xFF);
    }
    A = tmp & 0xFF;
}
```


Source: <https://github.com/gianlucag/mos6502>

Emulation software tricks original software into thinking it is running on original hardware
 
# What is an FPGA?

A Field Programmable Gate Array:

A configurable circuit; not a stored-program computer




LUT: 16-element lookup table


Source: <http://evergreen.loyola.edu/dhhoe/www/HoeResearchFPGA.htm>
 
# Using a LUT to Implement a Circuit

If the circuit has fewer than 4 inputs, write the truth table and load it in the LUT:



Pong, Atari, 1972

 

M	L	R	A
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

## The Main FPGA Players



formerly known as



Classic duopoly, good for customers: neck-and-neck technology

Altera Cyclone II

EP2C5T144

c. 2004


Very-low end;  
completely  
obsolete

Dirt cheap: \$16  
board

"Only" 4608 LEs

14 KB memory


144 pins (89 I/O)

 
 
# Minimal EP2C5T144 Development Board

Altera FPGA Cyclone II  
EP2C5T144 Minimum System  
Board Development Board


\$16 on Banggood.com. Also  
Amazon, eBay, dx.com,  
AliExpress, etc.



- 50 MHz oscillator
- JTAG programming connector
- EPCS4SI8 4 Mb serial configuration flash
- Active Serial connector for programming
- +5V power jack
- 3.3V (I/O) and 1.2V (core) voltage regulators
- 3 LEDs, 1 pushbutton switch

 
# The Design Flow

```
module comb1(  
    input logic [3:0] a, b,  
    input logic s,  
    output logic [3:0] y);  
  
    always_comb  
        if (s)  
            y = a + b;  
        else  
            y = a & b;  
  
    endmodule
```



JTAG

System Verilog

 


# A Taste of SystemVerilog: A Full Adder

// Full adder

```
module full_adder(input logic a, b, c,
                    output logic sum, carry);
    assign sum = a ^ b ^ c;
    assign carry = a & b | a & c | b & c;
endmodule
```

Module name  
Input port  
Data type:  
single bit  
Port name

 Single-line comment  
Systems are built from modules  
"Continuous assignment" expresses combinational logic



Logical Expression




# An XOR Built Hierarchically

```
module mynand2(input logic a, b,  
                output logic y);  
    assign y = ~(a & b);  
endmodule  
  
module myxor2(input logic a, b,  
                output logic y);  
    logic abn, aa, bb;  
    mynand2 n1(a, b, abn),  
            n2(a, abn, aa),  
            n3(abn, b, bb),  
            n4(aa, bb, y);  
endmodule
```

Declare internal wires

n1: A mynand2 connected to a, b, and abn

 

# A Decimal-to-Seven-Segment Decoder

always\_comb:  
combinational  
logic in an  
imperative style

Multiway  
conditional

4'd5: decimal "5"  
as a four-bit  
binary number

Mandatory

```
module dec7seg(input logic [3:0] a,
                 output logic [6:0] y);
    always_comb
        case (a)
            4'd0:    y = 7'b111_1110;
            4'd1:    y = 7'b011_0000;
            4'd2:    y = 7'b110_1101;
            4'd3:    y = 7'b111_1001;
            4'd4:    y = 7'b011_0011;
            4'd5:    y = 7'b101_1011;
            4'd6:    y = 7'b101_1111;
            4'd7:    y = 7'b111_0000;
            4'd8:    y = 7'b111_1111;
            4'd9:    y = 7'b111_0011;
        default: y = 7'b000_0000;
    endcase
endmodule
```

seven-bit  
binary vector  
(\_ is ignored)


"blocking  
assignment":  
use in always\_comb

# Imperative Combinational Logic

```
module comb1(
    input logic [3:0] a, b,
    input logic s,
    output logic [3:0] y);

    always_comb
        if (s)
            y = a + b;
        else
            y = a & b;

endmodule
```

 

Both  $a + b$  and  $a \& b$  computed, mux selects the result.

# An Address Decoder

```
module adecode(input logic [15:0] address,
                output logic RAM, ROM,
                output logic VIDEO, IO);

    always_comb begin
        {RAM, ROM, VIDEO, IO} = 4'b 0;
        if (address[15])
            RAM = 1;
        else if (address[14:13] == 2'b 00 )
            VIDEO = 1;
        else if (address[14:12] == 3'b 101)
            IO = 1;
        else if (address[14:13] == 2'b 11 )
            ROM = 1;
    end

endmodule
```

Vector concatenation

Default:  
all zeros

Select bit 15

Select bits 14, 13, & 12

# A D-Flip-Flop

always\_ff introduces sequential logic

```
module mydff(input logic clk,  
              input logic d,  
              output logic q);
```

Copy d to q


```
    always_ff @(posedge clk)
```

```
        q <= d;
```

```
    endmodule
```

Triggered by the rising edge of clk

 
Non-blocking assignment:  
happens "just after" the rising edge



# A Four-Bit Binary Counter


```
module count4(input logic clk,  
              output logic [3:0] count);  
  
    always_ff @(posedge clk)  
        count <= count + 4'd1;  
  
endmodule
```

Width optional  
but good style

 
 
# Quartus

"Lite"/"Web edition" free good enough for our use  
Quartus 13.0sp1 last to support the Cyclone II



# Quartus 13.0sp1 on Ubuntu 16.04, 64 bit

Installer is a 32-bit binary; needs 32-bit libraries

```
# sudo apt install -y lib32z1  
# sudo ./setup.sh
```

Install to /opt/altera/13.0sp1

Set up environment:

```
# PATH=$PATH:/opt/altera/13.0sp1/quartus/bin  
# quartus --64bit
```

# Ubuntu 16.04 USB Blaster Permissions

Nothing today doesn't require a programming dongle; JTAG, active serial



```
# lsusb  
Bus 001 Device 087: ID 09fb:6001 Altera Blaster
```

Create the file /etc/udev/rules.d/51-altera.rules

```
ATTR{idVendor}=="09fb", ATTR{idProduct}=="6001",  
MODE="0666"
```

Fixes "Unable to lock chain (Insufficient port permissions)" errors from jtagconfig

# "Hello World" for an FPGA

- hello.qpf Project file; mostly the name
- hello.qsf Settings file: device type, pin assignments
- hello.sdc Timing constraints: 50 MHz clock
- hello.sv System Verilog specification of "guts"

Use the GUI or run at the command line:

```
quartus_sh --64bit --flow compile hello  
quartus_pgm -c 1 -m as -o "pv;hello.pof"
```

```
# hello.qpf
QUARTUS_VERSION = "13.0"
DATE = "11:17:07 May 17, 2018"
PROJECT_REVISION = "hello"
```

```
# hello.qsf
set_global_assignment -name FAMILY "Cyclone II"
set_global_assignment -name DEVICE EP2C5T144C8
set_global_assignment -name PROJECT_CREATION_TIME_DATE "11:17:07 MAY 17, 2018"
set_global_assignment -name ORIGINAL_QUARTUS_VERSION "13.0 SP1"
set_global_assignment -name LAST_QUARTUS_VERSION "13.0 SP1"
set_global_assignment -name MIN_CORE_JUNCTION_TEMP 0
set_global_assignment -name MAX_CORE_JUNCTION_TEMP 85
set_global_assignment -name TOP_LEVEL_ENTITY hello
set_global_assignment -name SYSTEMVERILOG_FILE hello.sv
set_location_assignment PIN_3 -to LED[0]
set_location_assignment PIN_7 -to LED[1]
set_location_assignment PIN_9 -to LED[2]
set_location_assignment PIN_17 -to clk50
set_location_assignment PIN_144 -to KEY
set_instance_assignment -name WEAK_PULL_UP_RESISTOR ON -to KEY
```

```
# hello.sdc
create_clock -name "clk50" -period "50 MHz" [get_ports {clk50}]
derive_pll_clocks -create_base_clocks
derive_clock_uncertainty
```

```
/*
 * "Hello World" for the EP2C5T144 minimum development board
 *
 * Count in binary on the three LEDs; press the button to make it count faster
 */


module hello(input clk50,
              input KEY,
              output [2:0] LED);

    logic [26:0] count;
    always_ff @(posedge clk50)
        count <= count + (KEY ? 27'd1 : 27'd4); // KEY = 0 when pressed

    assign LED = ~count[26:24];

endmodule
```

# The KIM-1

 

MOS Technology, 1976

1 MHz MCS6502 processor

2 MCS6530 "RIOT" chips:  
1K ROM + 64B RAM + GPIO +  
timer

1K Static RAM ( $8 \times 6102$ )

24-key hexadecimal keyboard

6 7-segment LEDs

Serial port:  
20 mA current loop

Cassette interface

**MOS**  
**MOS**  
**MOS**

**MOS**

**MICROCOMPUTERS**

**MICROCOMPUTERS**

**MICROCOMPUTERS**

**MICROCOMPUTERS**

**PROGRAMMING MANUAL**


**MICROCOMPUTERS**

**MICROCOMPUTERS**

**MICROCOMPUTERS**

**KIM-1 USER MANUAL**

**HARDWARE MANUAL**

 

Need SystemVerilog for  
these blocks

---

6502	steal
1K RAM	write
6530	write
Keyboard	build
Display	build
TTY	emulate
Audio	ignore

---

Source: KIM-1 User Manual

## Which 6502 Module To Use?

Coding and verifying even an 8-bit processor is not trivial

Fortunately, others have done this. I found four in Verilog:


- ▶ Thomas Skibo  
<http://www.thomasskibo.com/projects/pet2001fpga/>
- ▶ Arlet Ottens  
<https://github.com/Arlet/verilog-6502>
- ▶ Oleg Odintsov  
[http://opencores.org/project,ag\\_6502](http://opencores.org/project,ag_6502)
- ▶ Rob Finch  
[http://finitron.ca/Projects/Prj6502/bc6502\\_page.html](http://finitron.ca/Projects/Prj6502/bc6502_page.html)

I selected Arlet Ottens': simple and designed for FPGAs.  
OpenCores core complicated & modeled the 6502's  
two-phase clock.
 
# Instantiating the 6502 Module

```
module KIM_1(input          clk,
              input          reset,
              input          NMI,
              output [15:0] AB,
              output [7:0]  DO,
              output [7:0]  DI,
              output         WE,
              output         RDY,
              // ....
            );

mcs6502 U1(.clk( clk ),
            .reset( reset ),
            .AB( AB ),
            .DI( DI ),
            .DO( DO ),
            .WE( WE ),
            .IRQ( 1'b0 ),
            .NMI( NMI ),
            .RDY( RDY ) );
```



Debounced RS (reset)  
and ST (stop/NMI) keys

Take from environment;  
assume good signals

Address decoder

Easily coded

1 MHz crystal


Derive from 50 MHz

Single-step (SST) switch  
and logic

6502 module doesn't  
have sync; omitted

Source: KIM-1 User Manual

# 74LS145 BCD-to-Decimal Decoder

 

```
module SN74145(input [3:0] select,
                output [9:0] out);
    always_comb
        case (select)
            4'd0:   out = 10'b11_1111_1110;
            4'd1:   out = 10'b11_1111_1101;
            4'd2:   out = 10'b11_1111_1011;
            4'd3:   out = 10'b11_1111_0111;
            4'd4:   out = 10'b11_1110_1111;
            4'd5:   out = 10'b11_1101_1111;
            4'd6:   out = 10'b11_1011_1111;
            4'd7:   out = 10'b11_0111_1111;
            4'd8:   out = 10'b10_1111_1111;
            4'd9:   out = 10'b01_1111_1111;
        default: out = 10'b11_1111_1111;
    endcase
endmodule
```

```
output [7:0] K // Active-low address decoder output
logic [9:0] u4out;
SN74145 U4( .select ( {DECODE_ENABLE, AB[12:10]} ),
            .out ( u4out ) );
assign K = u4out[7:0]; // outputs 8,9 are not connected
```

# The Clock

Oscillators have to come from outside an FPGA

EP2C5T144 includes a 50 MHz crystal oscillator on pin 17

The KIM-1 runs at 1 MHz

Solution: Divide-by-50 counter:

```
logic [4:0] clkcount = 5'h0;
logic      clk = 1'b0;           // 1 MHz clock
always @(posedge clk50) begin    // 50 MHz clock
    if (clkcount == 5'd24) begin // Every 25 cycles,
        clkcount <= 5'd0;       // Reset the counter
        clk <= ~clk;           // And toggle the clock
    end
    else
        clkcount <= clkcount + 5'd1;
end
```

FPGAs also have programmable PLLs; EP2C5's could only divide down to 10 MHz

# 1K RAM

Originally 8 6102 SRAM chips. Easy to model:

```
// U5-U14: 1K Static RAM

logic [7:0] RAM1K [0:1023];
logic [7:0] RAM1K_D0;           // Read data from 1K RAM
logic      RAM1K_OE;          // Data from the 1K RAM

always_ff @(posedge clk) begin
{RAM1K_OE, RAM1K_D0} <= {1'b0, 8'bx};
if (!K[0])
  if (WE) RAM1K[ AB[9:0] ] <= D0;
  else {RAM1K_OE, RAM1K_D0} <= { 1'b1, RAM1K[ AB[9:0] ] };
end
```

```
// Emulate the tri-state data bus being driven by the peripherals
always_comb
  if      (RAM1K_OE)   DI = RAM1K_D0;
  else if (RAM128_OE)  DI = RAM128_D0;
  else if (ROM2K_OE)   DI = ROM2K_D0;
  else if (RIOT002_OE) DI = RIOT002_D0;
  else if (RIOT003_OE) DI = RIOT003_D0;
  else                 DI = 8'bx;
```

## 2K ROM

6530s each have 1K ROM; easier to model a 2K ROM

```
// 2K ROM within the two 6530s

logic [7:0] ROM2K [0:2047];
initial $readmemh("ROM.hex", ROM2K); // Load the ROM from a file
logic [7:0] ROM2K_D0; // Data from the 2K ROM
logic ROM2K_OE; // 2K ROM selected


always_ff @(posedge clk) begin
    {ROM2K_OE, ROM2K_D0} <= {1'b0, 8'bx};
    if (!K[6] || !K[7])
        {ROM2K_OE, ROM2K_D0} <= {1'b1, ROM2K[ AB[10:0] ] };
end
```

Creating the .hex file:


```
# cat 6530-003.bin 6530-002.bin | \
od -v -t x1 -An > ROM.hex
```

```
a9 ad 8d ec 17 20 32 19 a9 27 8d 42 17 a9 bf 8d
43 17 a2 64 a9 16 20 7a 19 ca d0 f8 a9 2a 20 7a
```

# The 6530 RIOT

 

```
logic IOT_SELECT;
assign IOT_SELECT = !CS1 && (A[9:6] == IOT_BASE[9:6]);
always_ff @(posedge clk)
  if (reset) begin
    PA0 <= 8'd0;      PAOE <= 8'd0;
    PBO <= 8'd0;      PBOE <= 8'd0;
  end else begin
    {OE, DO} <= {1'b0, 8'bx};
    if (IOT_SELECT)
      case ({RW, A[2:0]})
        4'b0_000 : PA0 <= DI;                      // Write port A
        4'b1_000 : {OE, DO} <= {1'b1, PAI_int};    // Read port A
        4'b0_001 : PAOE <= DI;                     // Write DDRA
        4'b1_001 : {OE, DO} <= {1'b1, PAOE};       // Read DDRA
        4'b0_010 : PBO <= DI;                      // Write port B
        4'b1_010 : {OE, DO} <= {1'b1, PBI_int};    // Read port B
        4'b0_011 : PBOE <= DI;                     // Write DDRB
        4'b1_011 : {OE, DO} <= {1'b1, PBOE};       // Read DDRB
      default : ;
    endcase
  end
```

 


Multiplexed 6 common-anode LEDs

Anodes driven by a PNP transistor

'145 selects one of the digits or one of the three keyboard rows. Open-collector output.

 Cathodes with current-limiting resistors driven by keyboard columns through inverters



We have enough pins; use them:

**Emulated '145:**


**LED\_DIG[9:4]** Anode outputs  
(Active low)

**KB\_ROW[2:0]** Row outputs  
(Open Collector)

 **Inputs and outputs separated**

**LED\_SEG[6:0]** Segment drivers  
(Active low)

**KB\_COL[6:0]** Column inputs  
(Weak pullup resistor)



# Creating Constraints Algorithmically

Use the Quartus GUI or program in Tcl (run quartus\_sh):

```
project_new KIM_EP2C5 -overwrite

foreach svfile {
    KIM_1.sv
    mcs6530.sv
    KIM_EP2C5.sv
} { set_global_assignment -name SYSTEMVERILOG_FILE $svfile }

foreach {signal pin} {
    clk50 PIN_17
    LED[0] PIN_3
    LED[1] PIN_7
    LED[2] PIN_9
    KEY    PIN_144

    LED_DIG[4] PIN_65
    LED_DIG[5] PIN_67
    LED_DIG[6] PIN_69
    LED_DIG[7] PIN_70
    LED_DIG[8] PIN_71
    LED_DIG[9] PIN_72

} {
    set_location_assignment $pin -to $signal
    set_instance_assignment -name OUTPUT_PIN_LOAD 20 -to $signal
}
```

# Top-Level File

Separate KIM-1-specific from board/chip-specific:

```
module KIM_EP2C5(input          clk50,
                   inout [7:0]  PA,
                   inout [7:0]  PB,
                   output [3:0] KB_ROW,
                   input [6:0]  KB_COL,
                   output [9:4] LED_DIG, // Active low: 4 is leftmost
                   output [6:0] LED_SEG, // Active low: 0 is segment A
                   // ...
                   );
  KIM_1 TOP( .PAI ( PA ),
             .PBI ( PB ),
             .DECODE_ENABLE ( 1'b0 ),
             .RDY (),
             .K ( K ),
             // ...
             );
  /* Emulate open-collector outputs on the KB_ROW signals */
  logic [3:0] KB_ROW_int;
  generate
    for (i = 0 ; i < 4 ; i++ ) begin: KB_ROW_pins
      assign KB_ROW[i] = KB_ROW_int[i] ? 1'bz : 1'b0;
    end
  endgenerate
```

# Fitter Summary Report

Fitter Status : Successful - Thu May 17 23:19:56 2018  
Quartus II 64-Bit Version : 13.0.1 Build 232 06/12/2013 SP  
Revision Name : KIM\_EP2C5  
Top-level Entity Name : KIM\_EP2C5  
Family : Cyclone II  
Device : EP2C5T144C8  
Timing Models : Final  
Total logic elements : 607 / 4,608 ( 13 % )  
    Total combinational functions : 575 / 4,608 ( 12 % )  
    Dedicated logic registers : 259 / 4,608 ( 6 % )  
Total registers : 259  
Total pins : 52 / 89 ( 58 % )  
Total virtual pins : 0  
Total memory bits : 28,160 / 119,808 ( 24 % )  
Embedded Multiplier 9-bit elements : 0 / 26 ( 0 % )  
Total PLLs : 0 / 2 ( 0 % )

# Other FPGA Retro Sites

<http://www.fpgaarcade.com>



Featured Cores

**AMIGA**

The Amiga was based on the Motorola 68000 CPU and was sold by Commodore between 1985 and 1994. Its advanced graphics and sound made it popular for gaming and video production.

[READ MORE](#)

**commodore 64**


The Commodore 64 is a computer that was manufactured by Commodore between 1982 and 1994. It was very popular during the 80's and early 90's.

[READ MORE](#)



Grant Searle
 
<http://searle.hostei.com/grant/Multicomp/>



MiSTer FPGA board

[https://github.com/MiSTER-devel/Main\\_MiSTER/wiki](https://github.com/MiSTER-devel/Main_MiSTER/wiki)

