# W4281 - Introduction to Quantum Computing

# **Homework 2**

due date: Thursday 6/16/2005

#### Exercise 1 (10 points):

The swap gate is defined as


$$Q|a\rangle |b\rangle = |b\rangle |a\rangle$$
 for  $a, b \in \{0, 1\}$ ,

and its circuit representation is



1. Find the matrix representation of Q (and prove its correctness).

2. Prove that

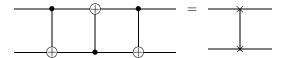

3. The controlled-swap (Fredkin gate) is defined as



Find the matrix representation of this gate (and prove its correctness).

### Exercise 2 (10 points):

Let  $|\psi\rangle = H^{\otimes n} |0\rangle$ , and let


$$A=I-2\left|\psi\right\rangle \left\langle \psi\right|.$$

Prove that

$$e^{i\pi A} = -I.$$
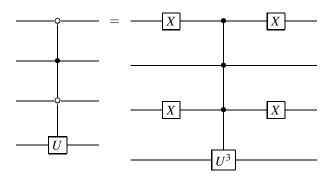
## Exercise 3 (10 points):

Write a program which verifies whether the following circuits are equivalent:



The first circuit applies U if the first three qubits are  $|0\rangle |1\rangle |0\rangle$  (the first and third dots should be empty).

*Input:* A  $2 \times 2$  unitary matrix *U*:

$$U = \left[ \begin{array}{cc} u_{11} & u_{12} \\ u_{21} & u_{22} \end{array} \right]$$

*Output:* YES or NO depending on whether the circuits are (approximately) equivalent. If you are using a symbolic program like Mathematica it should be easy to check whether they actually are equivalent. If you are using a numerical package like Matlab, check that the circuits  $C_1$  and  $C_2$  are *approximately* equivalent, which means that for all  $|\psi\rangle \in \mathbb{C}^{2^4}$ ,  $|||\psi\rangle|| = 1$ 

$$\left\|C_1 \left|\psi\right\rangle - C_2 \left|\psi\right\rangle\right\| < \varepsilon.$$

A good choice for  $\varepsilon$  would be proportional to the rounding unit.

Test your program for  $U \in \{X, Y, Z, H, S, T\}$  and document these test runs.