

# An Introduction to Hazard-Free Logic Synthesis (Fundamental Mode)

Steven M. Nowick

Columbia University

*(nowick@cs.columbia.edu)*

*July 15, 2002*

# Goal

**Given:** a Boolean function


**Design:** a *hazard-free* circuit implementation


 
# Goal

**Given:** a Boolean function

**Design:** a hazard-free circuit implementation



# Outline

Basics: Hazards

**Part I.** 2-Level Logic

**Part II.** Multi-Level Logic and  
Technology Mapping


Conclusions

# Basics
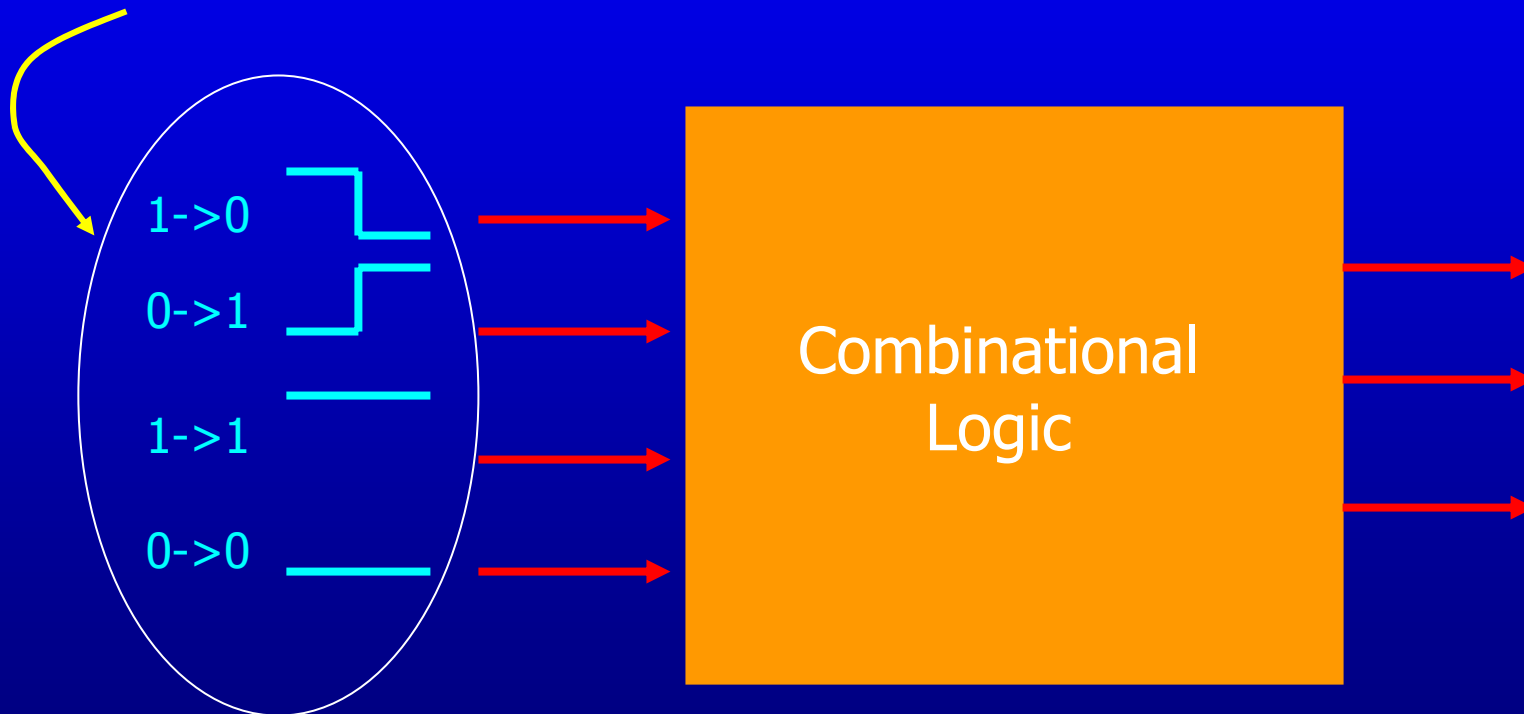
## 1) "Input Transition"

= "multiple-input transition", "multiple-input change" [*MIC*]

= a change from one input vector to another




Assume: "clean" input transitions => no glitches!

# Basics
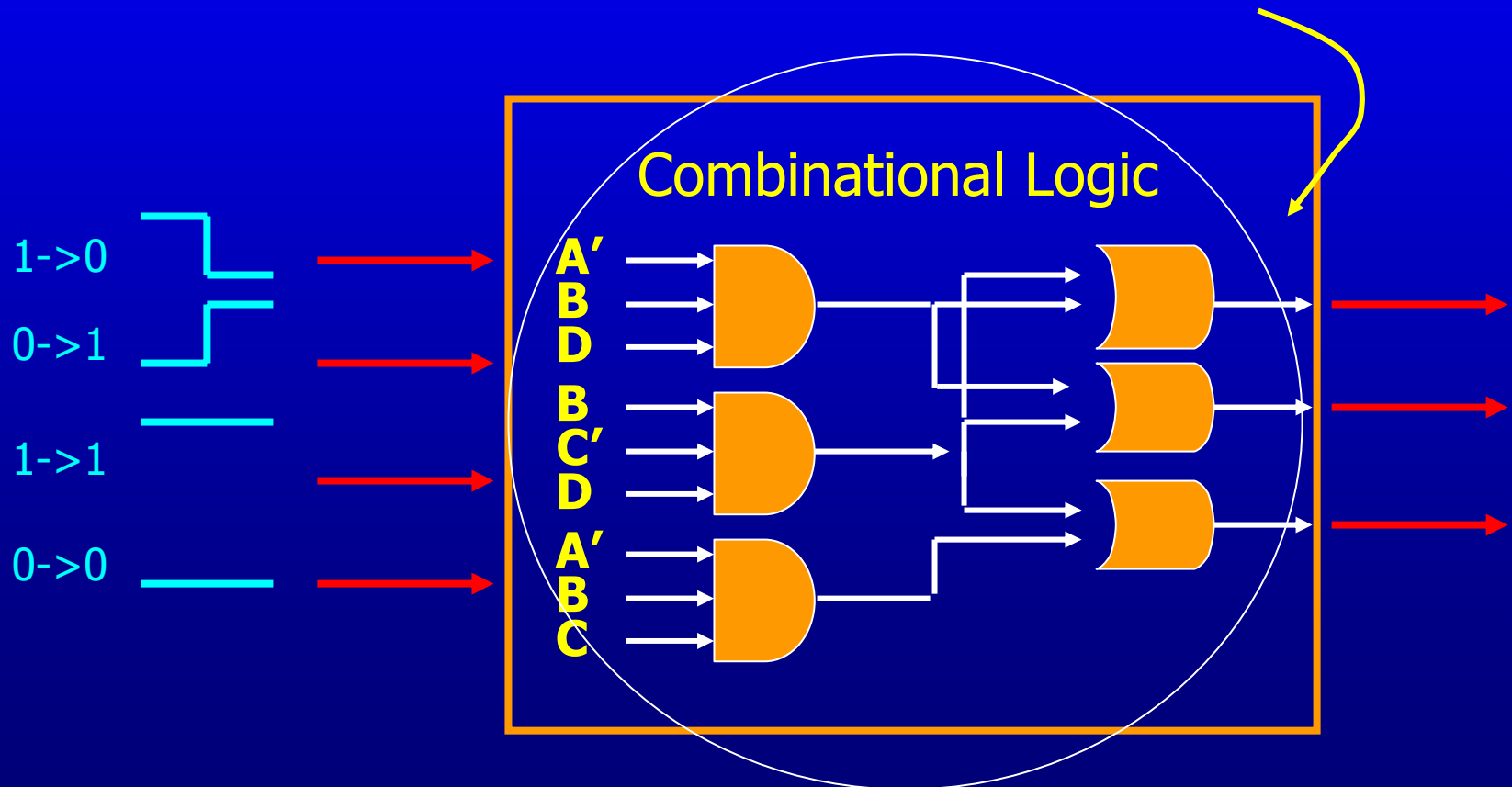
## 2) Circuit Model


Assume an *"unbounded wire delay"* model

... gates and wires may have arbitrary (finite) delays!


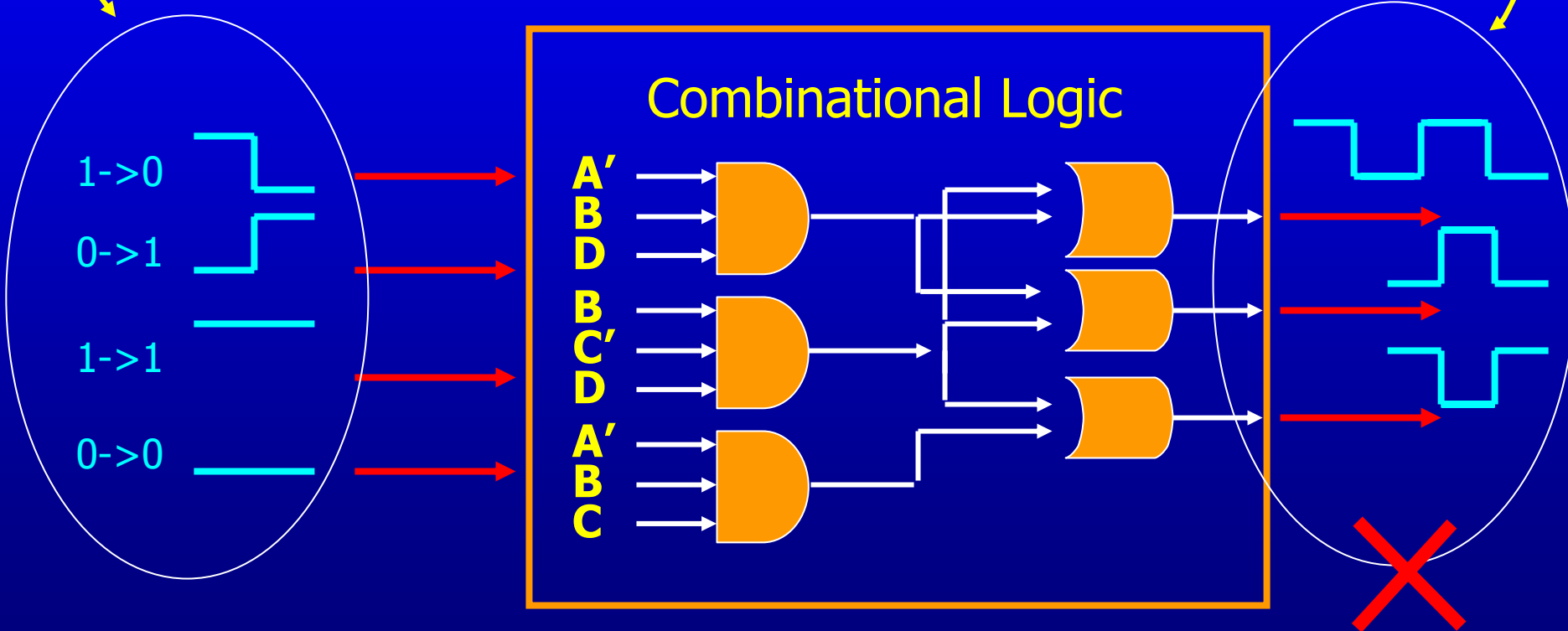
# The Goal

Given a *specified input transition*, synthesize a circuit impltn. with *no "combinational hazards"* for this transition (i.e. no possible glitch on outputs!)




... assuming above *circuit & environmental models*...

Hazardous
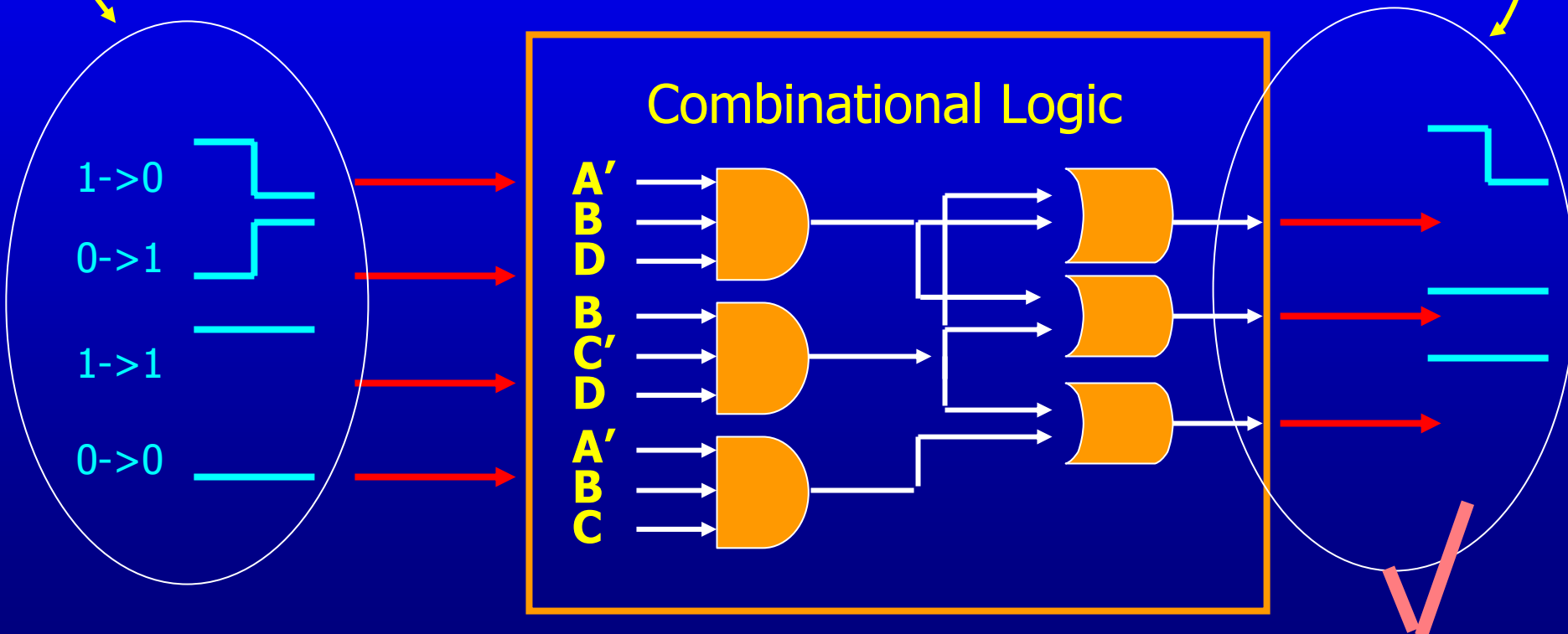
# The Goal

Given a *specified input transition*, synthesize a circuit impltn. with *no "combinational hazard"* for this transition (i.e. no possible glitch on outputs!)



... assuming above *circuit & environmental models...*

Hazard-Free




# Basics
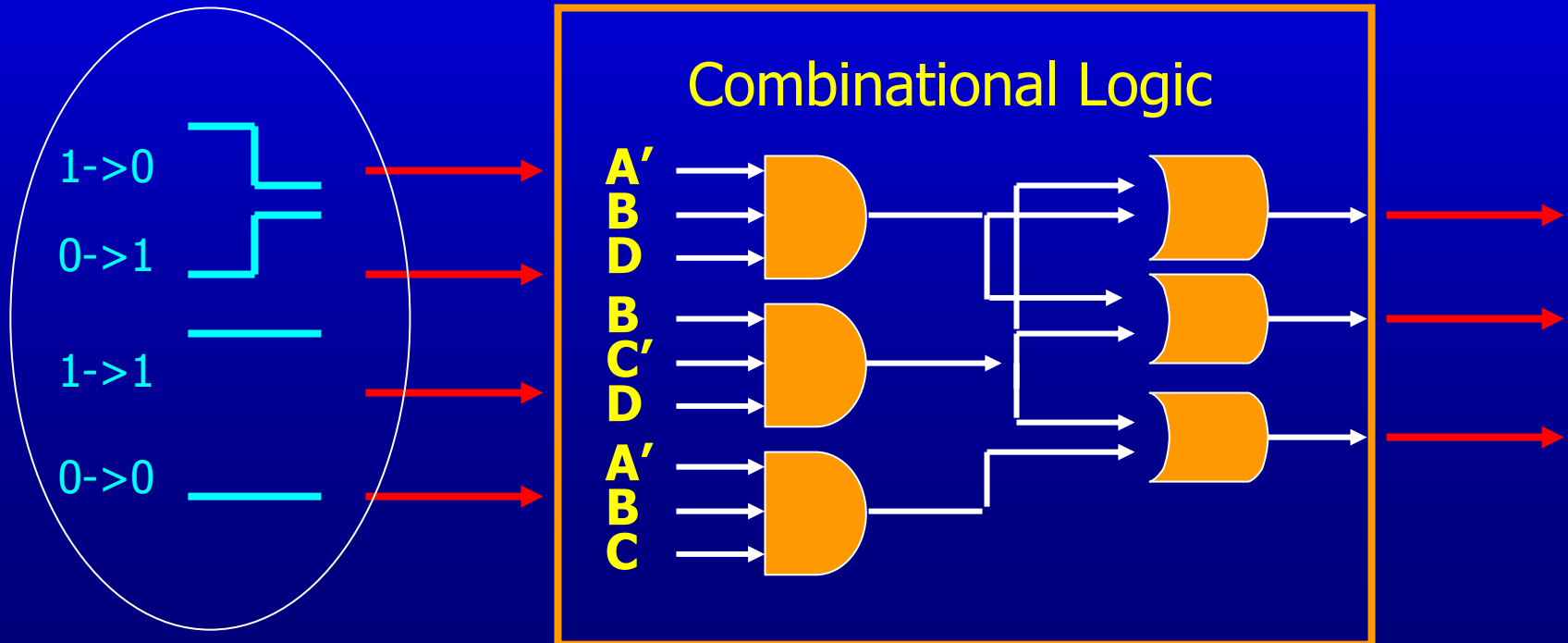
## 3) Environmental Model

Assume "*generalized fundamental mode*"

... after an input transition, *no new inputs may arrive until the circuit has stabilized!*



# Key Differences from “QDI” Hazard-Free Design

1. Combinational Circuit Model: *now more robust!*
  - *circuits correct for arbitrary gate + wire delays*
  - ... vs. QDI: *uses “isochronic fork” assumption*
2. Environmental Model: *“generalized fundamental mode”*
  - now, *timing assumptions on environment (1-sided)*
  - ... vs. QDI: *“input/output mode” (= none)*

# Basics: Combinational Hazards

Two types of combinational hazards:

## 1. Function Hazard:


- *inherent in combinational function*

## 2. Logic Hazard:

- *inherent in circuit implementation*
 
# Function Hazards


Non-monotonic changes  
on output function  
during an input transition  
(i.e., >1 change on output!)



Function + 4 input transitions
 
# Function Hazards

Non-monotonic changes  
on output function  
during an input transition  
(>1 change on output!)



function hazards

function hazard-free

# Function Hazards: Summary

Function hazards: cannot be removed

- inherent in function itself
- cannot guarantee glitch-free logic implementation [Unger]

Therefore, only consider function hazard-free transitions:

- most “specified behaviors” = naturally monotonic (not glitchy)

Sequential synthesis methods:

- must not introduce function hazards

**Burst-mode:** uses ...

- constrained ‘state minimization’ + ‘state assignment’ steps
- always succeeds: no undesired function hazards introduced...

# Logic Hazards

Now, assume function hazard-free input transitions....

**Logic Hazard** = property of a given circuit implementation

**Def. Logic Hazard:** Given combinational function  $f$ , circuit implementation  $C$ , and an input transition  $t$ .


If  $f$  is function hazard-free for input transition  $t$ ,  
but implementation  $C$  may glitch during transition  $t$ ,  
then circuit  $C$  has a logic hazard for transition  $t$ .

Otherwise, circuit  $C$  is logic hazard-free for transition  $t$ .

# Logic Hazards

		AB			
		00	01	11	10
CD	00	0	0	0	0
	01	0	1	0	0
	11	0	1	0	0
	10	0	1	-	0

Function hazard-free  
input transition

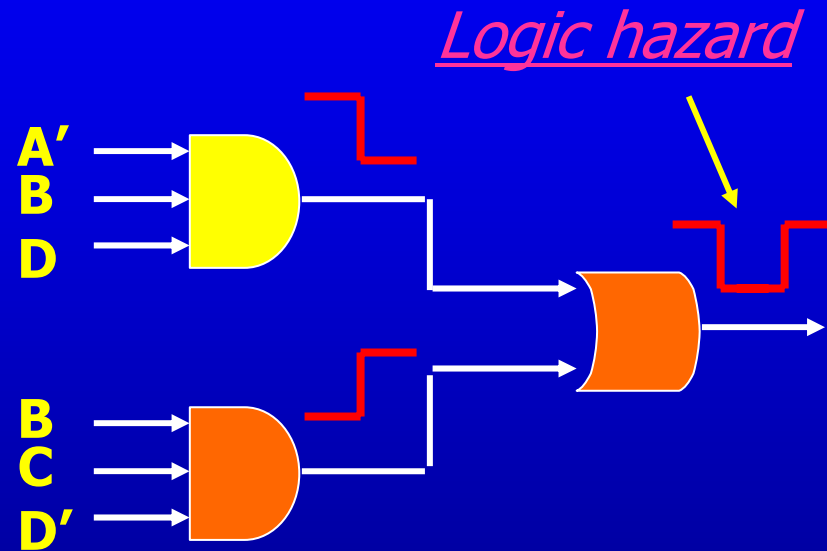


"input change":  $D: 1 \rightarrow 0$   
( $ABC=011$ )



# Logic Hazards

		AB			
		00	01	11	10
CD	00	0	0	0	0
	01	0	1	0	0
	11	0	1	0	0
	10	0	1	—	0

*A Different Implementation*

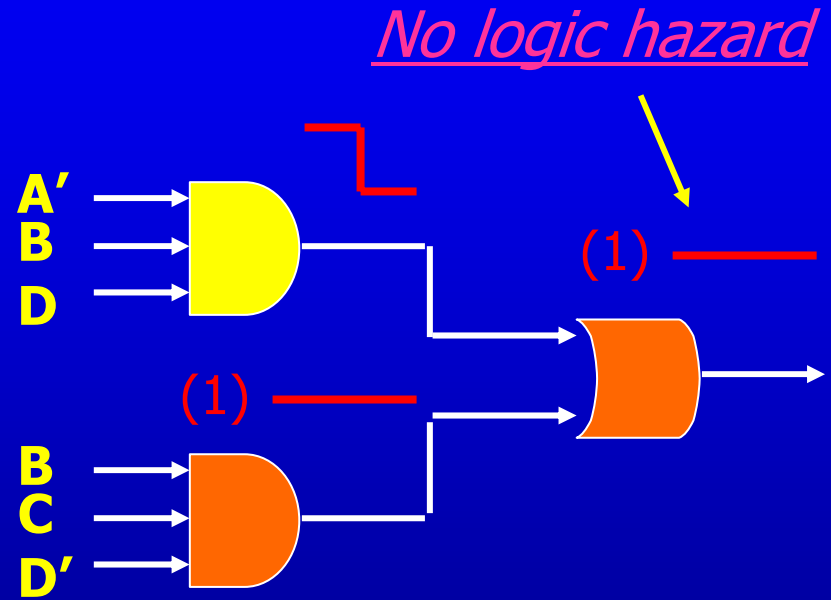

“input change”:  $D: 1 \rightarrow 0$   
( $ABC=011$ )

# Part I

## Two-Level Logic

# Part I: Outline

- **Problem #1:** Eliminating Logic Hazards for *One* Input Transition
- **Problem #2:** Eliminating Logic Hazards for *Several* Input Transitions
- **2-Level Hazard-Free Logic Minimization:** *a Complete Example*
- **Existence of a Hazard-Free Solution**
- **An Alternative Approach:** *Using GC-Elements*

# PROBLEM #1: Eliminating Logic Hazards for One Input Transition

**Given:** a combinational function  $f$ ,  
and a function hazard-free input transition  $t$ .

**Goal:** find a 2-level (AND-OR) implementation of  $f$   
which is logic hazard-free for input transition  $t$ .

# SUMMARY:


## Eliminating Logic Hazards for One Input Transition

transition type	hazard-free requirements
0 --> 0	?
1 --> 1	?
1 --> 0, 0 --> 1	?

# Eliminating Hazards: "Static Transition" (0->0)

		AB			
		00	01	11	10
CD	00	0	0	0	0
	01	0	1	0	0
	11	0	1	0	0
	10	0	1	-	0

 "input change":  $BC: 10 \rightarrow 01$   
( $AD=11$ )




**Example Circuit**

# Eliminating Hazards: 0->0 Transition

		AB			
		00	01	11	10
CD	00	0	0	0	0
	01	0	1	0	0
	11	0	1	0	0
	10	0	1	-	0

**No Requirement!**

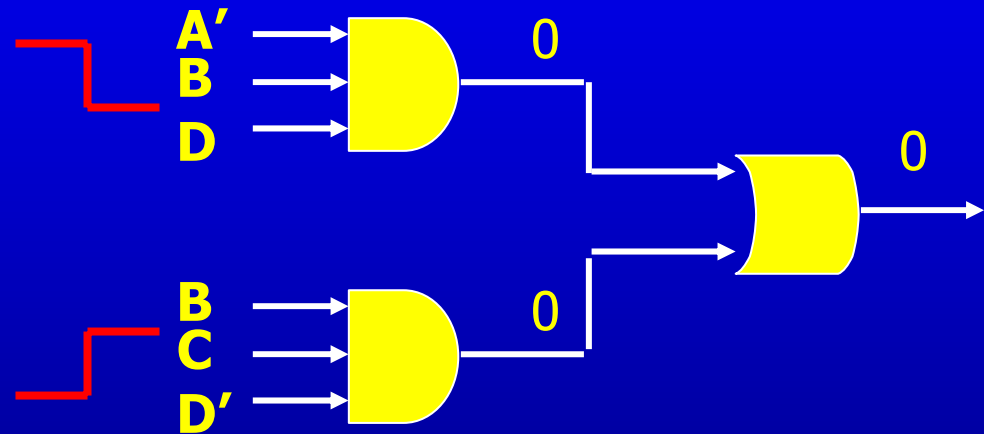


If no function hazard,  
then every 2-level implementation  
is free of logic hazards [Unger]

# Eliminating Hazards: "Static Transition" (1->1)

		AB			
		00	01	11	10
CD	00	0	0	0	0
	01	0	1	0	0
	11	0	1	0	0
	10	0	1	-	0

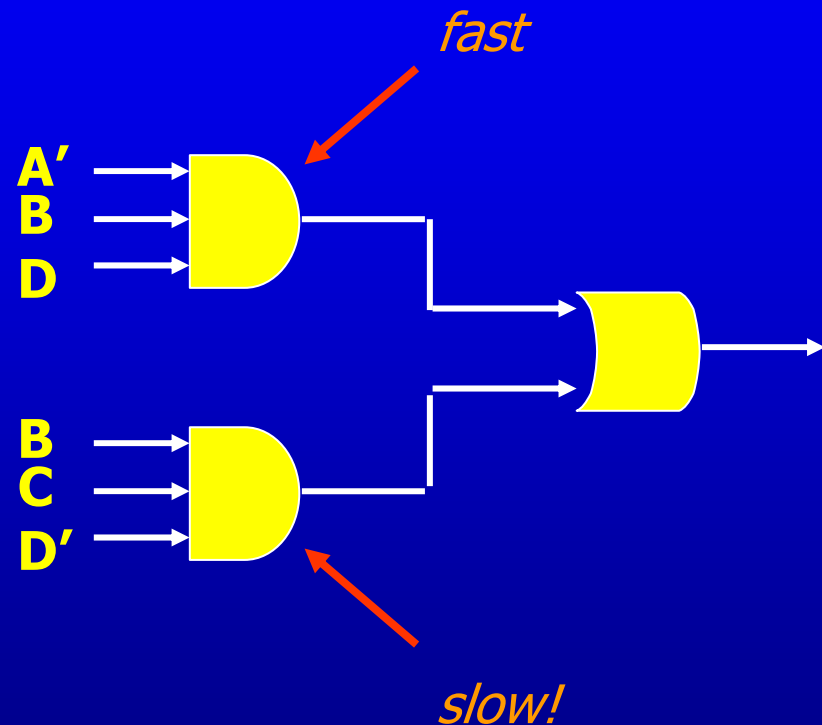"input change":  $D: 1 \rightarrow 0$   
( $ABC=011$ )




**Example Circuit**




# Eliminating Hazards: 1- $\rightarrow$ 1 Transition

		AB			
		00	01	11	10
CD	00	0	0	0	0
	01	0	1	0	0
	11	0	1	0	0
	10	0	1	-	0

 


# Eliminating Hazards: 1- $\rightarrow$ 1 Transition

		AB			
		00	01	11	10
CD	00	0	0	0	0
	01	0	1	0	0
	11	0	1	0	0
	10	0	1	-	0

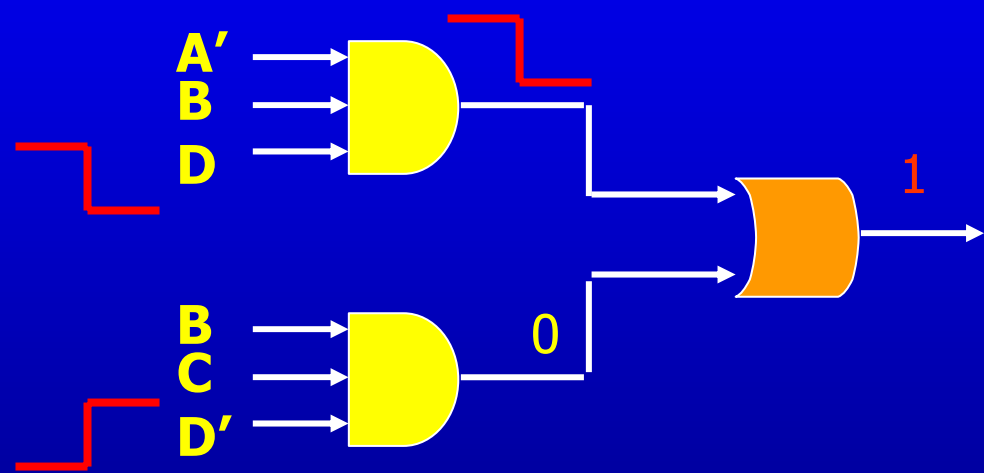


# Eliminating Hazards: 1- $\rightarrow$ 1 Transition

		AB			
		00	01	11	10
CD	00	0	0	0	0
	01	0	1	0	0
	11	0	1	0	0
	10	0	1	-	0

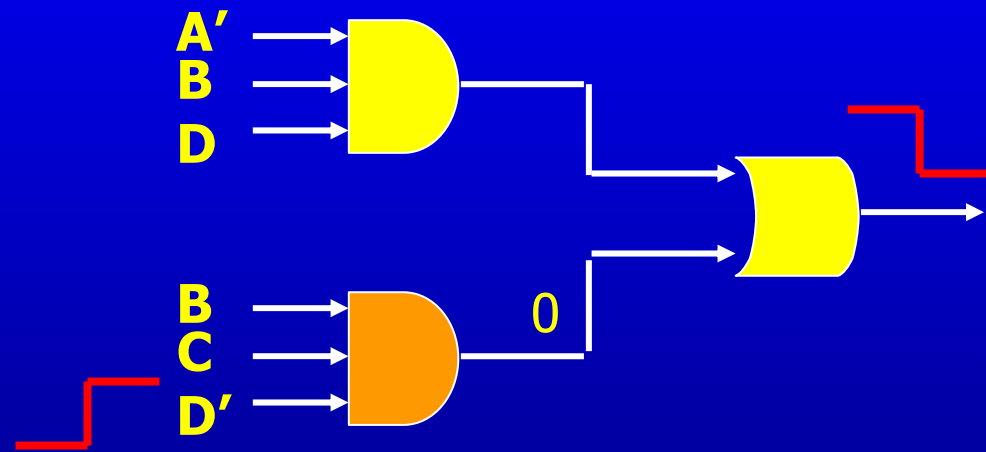


# Eliminating Hazards: 1- $\rightarrow$ 1 Transition

		AB			
		00	01	11	10
CD	00	0	0	0	0
	01	0	1	0	0
	11	0	1	0	0
	10	0	1	—	0

 


# Eliminating Hazards: 1- $\rightarrow$ 1 Transition

		AB			
		00	01	11	10
CD	00	0	0	0	0
	01	0	1	0	0
	11	0	1	0	0
	10	0	1	—	0

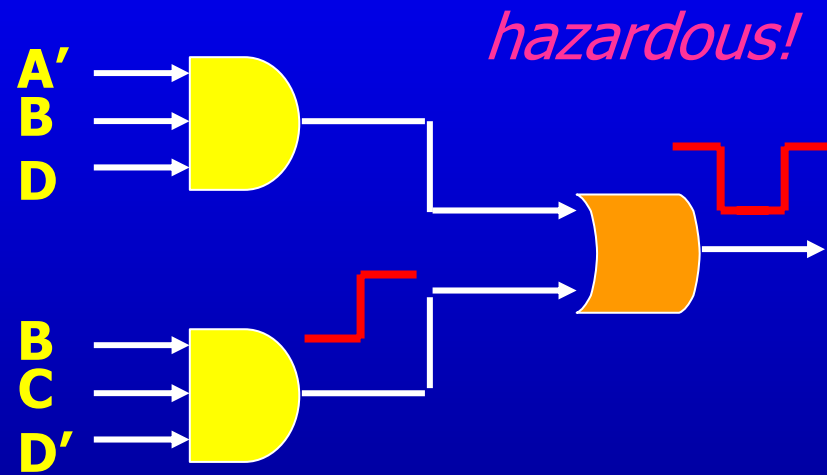

# Eliminating Hazards: 1->1 Transition

		AB			
		00	01	11	10
CD	00	0	0	0	0
	01	0	1	0	0
	11	0	1	0	0
	10	0	1	—	0

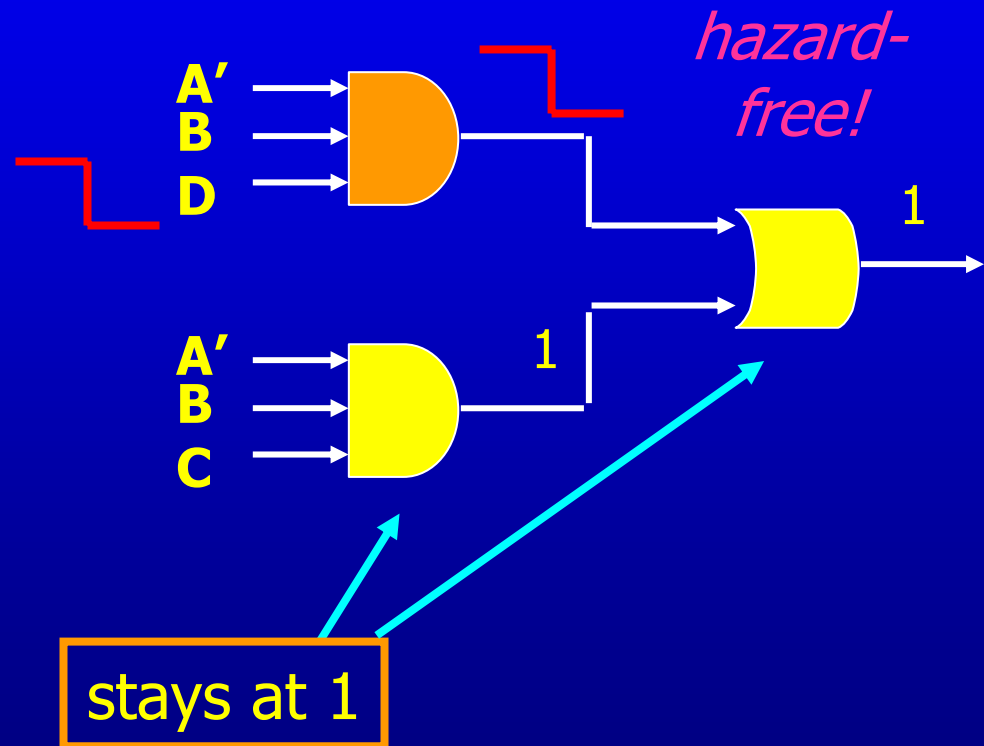

**Alternative Circuit**

# Eliminating 1->1 Hazard: Summary

hazardous

0	0	0	0
0	1	0	0
0	1	0	0
0	1	-	0

NO

hazard-free

0	0	0	0
0	1	0	0
0	1	0	0
0	1	-	0

YES

**Requirement**


"required cube": must be completely contained in some product

# Eliminating Hazards:

“Dynamic Transition” (1- $\rightarrow$ 0 or 0- $\rightarrow$ 1)

		AB			
		00	01	11	10
CD	00	0	0	0	0
	01	0	1	1	0
	11	0	1	0	0
	10	0	1	0	0

 “input change”:  $AC: 00 \rightarrow 11$   
( $BD=11$ )




**Example Circuit**



# Eliminating Hazards: 1->0 Transition

		AB			
		00	01	11	10
CD	00	0	0	0	0
	01	0	1	1	0
	11	0	1	0	0
	10	0	1	0	0

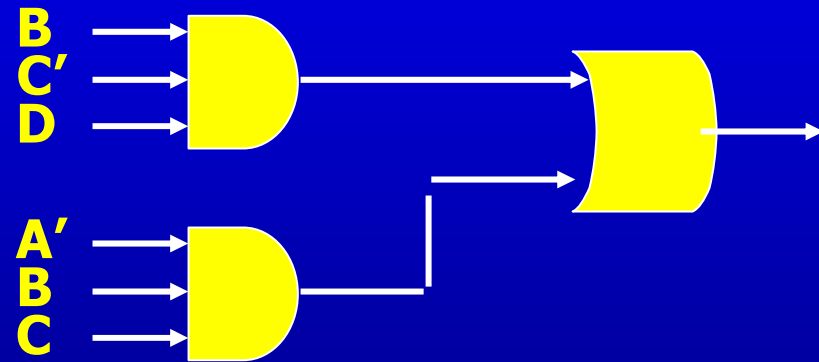


**Problem #1:** 1-to-1 "partial transition" is *hazardous*:  
- violates 1->1 covering requirement

# Eliminating Hazards: 1->0 Transition



		AB			
		00	01	11	10
CD	00	0	0	0	0
	01	0	1	1	0
	11	0	1	0	0
	10	0	1	0	0

 A Karnaugh map for a 4-variable function with variables A, B, C, and D. The map shows a transition from 1 to 0. A dashed blue cube highlights the transition from (01, 01) to (01, 11). A solid yellow oval highlights the transition from (01, 01) to (11, 01). A red arrow points from the 1 at (01, 01) to the 0 at (11, 01).



**Problem #1:** "required cube" for partial transition  
- ... not covered by any product!

# Eliminating Hazards: 1->0 Transition

 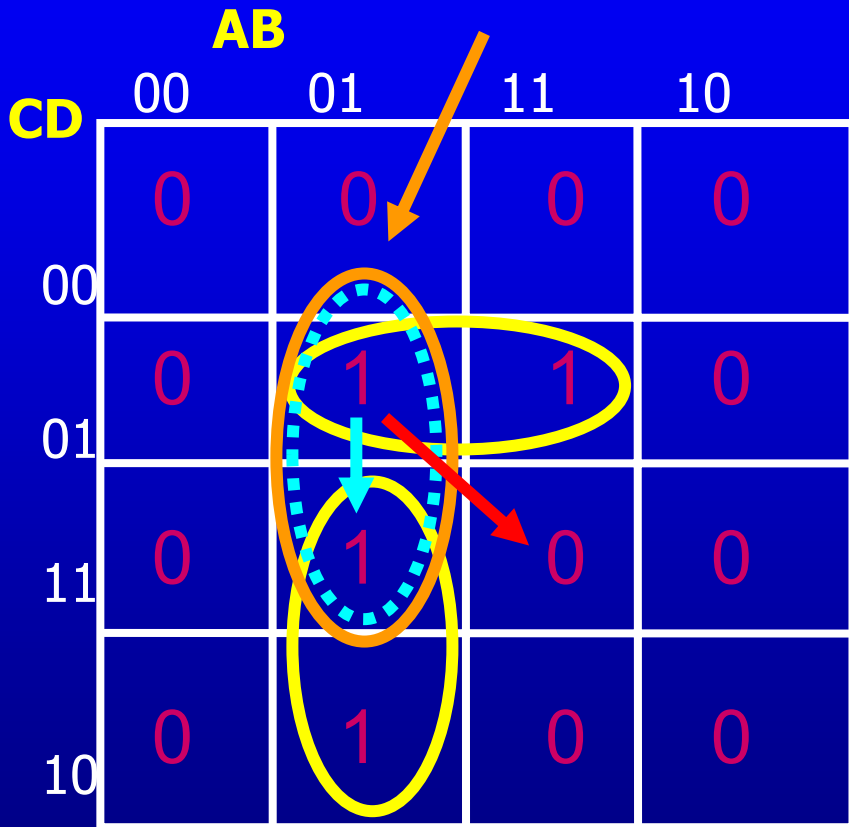


**Requirement #1**

**Solution:** cover the "required cube" for each partial transition  
 - ... by some product

# Eliminating Hazards: 1->0 Transition


		AB			
		00	01	11	10
CD	00	0	0	0	0
	01	0	1	1	0
	11	0	1	0	0
	10	0	1	0	0

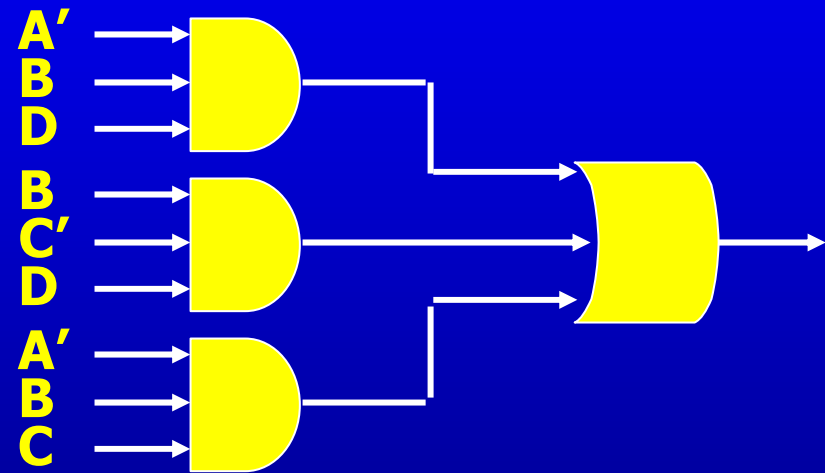

**Problem #2:** *entire dynamic 1-to-0 transition still hazardous!*


# Eliminating Hazards: 1->0 Transition

		AB			
		00	01	11	10
CD	00	0	0	0	0
	01	0	1	1	0
	11	0	1	0	0
	10	0	1	0	0

 


# Eliminating Hazards: 1->0 Transition

		AB			
		00	01	11	10
CD	00	0	0	0	0
	01	0	1	1	0
	11	0	1	0	0
	10	0	1	0	0

 


# Eliminating Hazards: 1->0 Transition

		AB			
		00	01	11	10
CD	00	0	0	0	0
	01	0	1	1	0
	11	0	1	0	0
	10	0	1	0	0

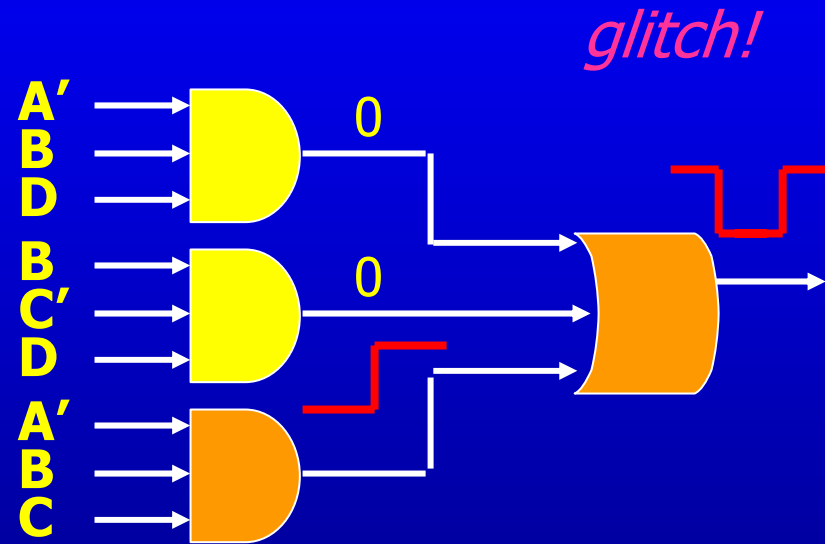



# Eliminating Hazards: 1->0 Transition

		AB			
		00	01	11	10
CD	00	0	0	0	0
	01	0	1	1	0
	11	0	1	0	0
	10	0	1	0	0

 



# Eliminating 1->0 Hazard: Summary

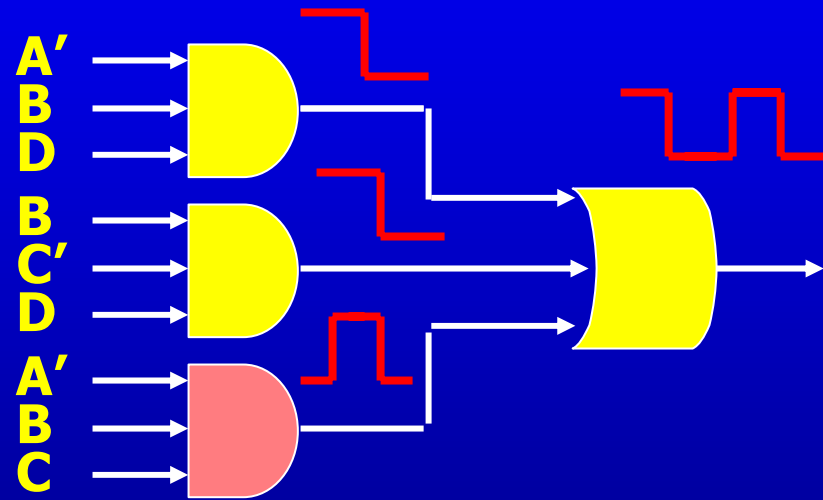 


*"illegal intersection"*

# Eliminating 1->0 Hazard: Summary

0	0	0	0
0	1	1	0
0	1	0	0
0	1	0	0

*no "illegal intersection"*

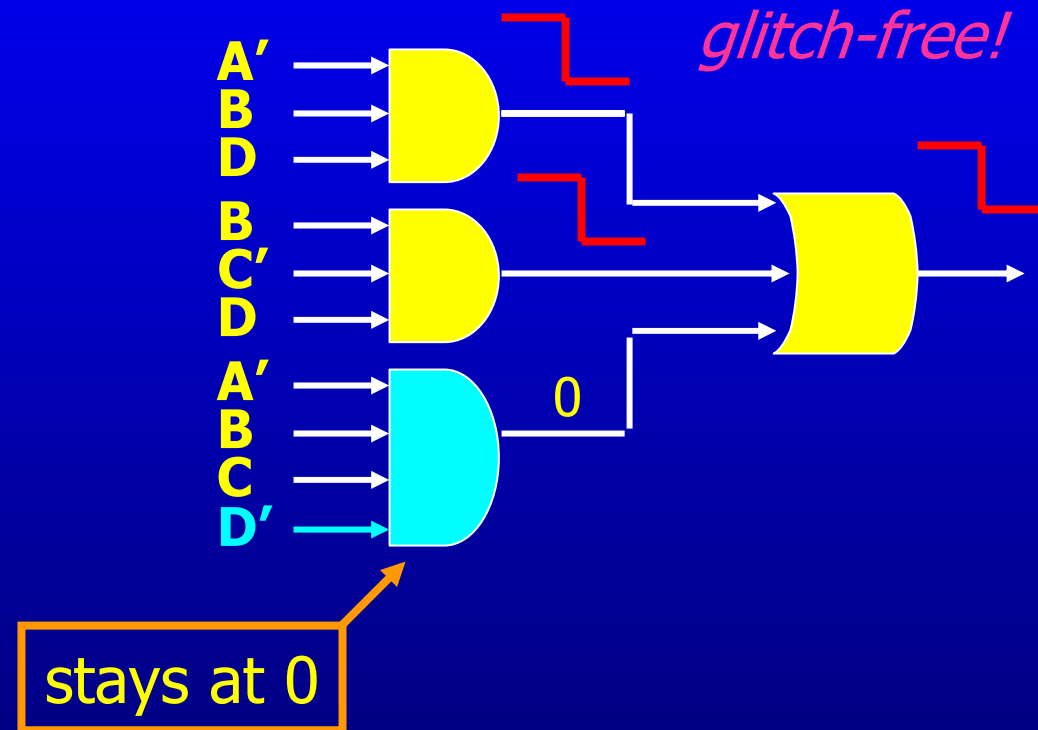

**Alternative Circuit:**  
**Hazard-Free**

# Eliminating 1->0 Hazard: "Privileged Cubes"

"start point" (function is 1)

0	0	0	0
0	1	1	0
0	1	0	0
0	1	0	0


"privileged cube"

- The entire dynamic transition is called a "***privileged cube***"

- No implicant can intersect any "***privileged cube***" unless it also contains its "***start point***"


# Eliminating 1->0 Hazard: Summary

*hazardous*

 

illegal intersection

*hazard-free*

 

legal intersection

**Requirement #2**

*"privileged cube": must not be illegally intersected by any product*

# FINAL SUMMARY: Eliminating Logic Hazards for One Input Transition

transition type	hazard-free requirements
0 --> 0	- [none]
1 --> 1	- required cube: must be covered by some implicant
1 --> 0, 0 --> 1	- required cubes: each must be covered by some implicant - privileged cube: must not be illegally intersected

# PROBLEM #2: Eliminating Logic Hazards for Several Input Transitions

## "2-Level Hazard-Free Logic Minimization Problem"

### Given:

- a Boolean function
- a specified set of input transitions

### Find:

- a minimum-cost 2-level implementation which is hazard-free for each specified input transition (i.e, guaranteed not to glitch)

### Goals and Assumptions:

- produce hazard-free combinational circuit:
  - guaranteed glitch-free, regardless of gate+wire delays
- inputs: assumed to be glitch-free

# 2-Level Hazard-Free Logic Minimization Problem

## Equivalent Goal

Find a 2-level circuit implementation, where:

- no privileged cube is "illegally intersected" by a product; and
- each required cube is completely contained in some product.

# "Dynamic Hazard-Free (DHF) Prime Implicants"

0	0
0	1
1	1
1	0

Prime Implicant

0	0
0	1
1	1
1	0

**NOT DHF-Prime:**  
has illegal  
intersection

**DHF-Prime Implicant =**

a maximal implicant which  
has no "illegal intersections"  
with any privileged cubes

0	0
0	1
1	1
1	0

**DHF-Prime**  
**Implicant:**  
no illegal  
intersections



# 2-Level Hazard-Free Logic Minimization Problem (cont.)

## Revised Goal (version #2):

Find a 2-level circuit implementation:

- ... using only DHF-prime implicants,
- ... where **each required cube** is completely covered by some product.

# 2-Level Logic Minimization: a Comparison (Classic vs. Hazard-Free)

In each case, solve a "*covering problem*":

<"objects to be covered", "covering objects">

■ **Classic** (Quine-McCluskey method, espresso-exact, ...):

<on-set minterms, prime implicants>

■ **Hazard-Free** (Nowick/Dill [92]):

<required cubes, DHF-prime implicants>

# 2-Level Logic Minimization: a Comparison

## Classic Method: *Non-Hazard-Free*

**Step 1:** Generate All Prime Implicants

**Step 2:** Generate Prime Implicant Table

**Step 3:** Solve Covering Problem

## New Method: *Hazard-Free* [Nowick/Dill '92]

**Step 1:** Generate All DHF-Prime Implicants

**Step 2:** Generate DHF-Prime Implicant Table

**Step 3:** Solve Covering Problem

# 2-Level Hazard-Free Logic Minimization: a Complete Example

		<i>ab</i>			
		<i>00</i>	<i>01</i>	<i>11</i>	<i>10</i>
<i>cd</i>	<i>00</i>	1	1	1	1
	<i>01</i>	0	1	1	1
	<i>11</i>	1	1	1	0
	<i>10</i>	1	1	0	0


The Karnaugh map shows four hazard-free transitions highlighted with orange arrows and dashed boxes:

- Transition 1: From  $ab=00, cd=00$  to  $ab=01, cd=00$ .
- Transition 2: From  $ab=11, cd=00$  to  $ab=10, cd=00$ .
- Transition 3: From  $ab=01, cd=11$  to  $ab=10, cd=10$ .
- Transition 4: From  $ab=11, cd=11$  to  $ab=11, cd=10$ .

[from: Nowick/Dill, ICCAD'92;  
IEEE Trans. On CAD Aug.'95]

Boolean Function +  
4 (function hazard-free) input transitions

 
# 2-Level Hazard-Free Logic Minimization: a Complete Example



## Required Cubes:

Each required cube must be completely contained in some product
 
# 2-Level Hazard-Free Logic Minimization: a Complete Example




**Privileged Cubes:**  
If any product intersects a  
*privileged cube*,  
it must also intersect its *start point*

# 2-Level Hazard-Free Logic Minimization: a Complete Example

## Step 1: Generate All DHF-Prime Implicants
 
### Approach: 2 steps

- Generate All Prime Implicants
- Reduce to DHF-Prime Implicants



# 2-Level Hazard-Free Logic Minimization: a Complete Example

## Step 1: Generate All DHF-Prime Implicants

1	1	1	1
0	1	1	1
1	1	1	0
1	1	0	0

### Approach: 2 steps

- Generate All Prime Implicants
- Reduce to DHF-Prime Implicants

**Total: 7 Prime Implicants**





# 2-Level Hazard-Free Logic Minimization: a Complete Example

## Step 1: Generate All DHF-Prime Implicants

### Approach: 2 steps

- Generate All Prime Implicants


→ Reduce to DHF-Prime Implicants

  

= privileged cube

# 2-Level Hazard-Free Logic Minimization: a Complete Example
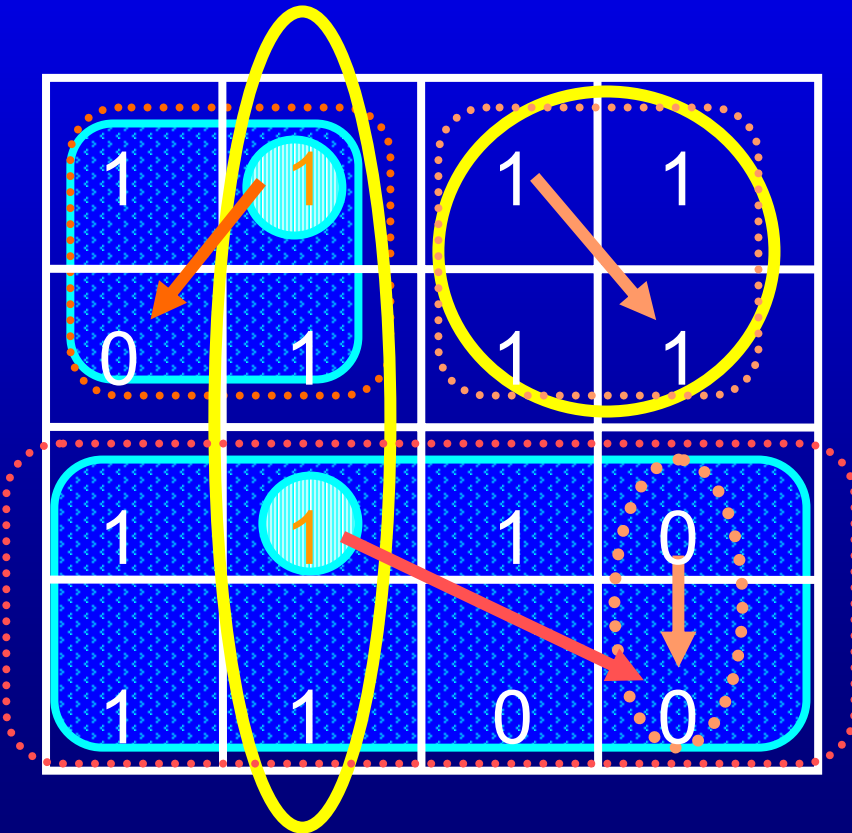
## Step 1: Generate All DHF-Prime Implicants




### Approach: 2 steps

- Generate All Prime Implicants
- ➔ Reduce to DHF-Prime Implicants

**Some primes have  
no illegal intersections  
=> they are DHF-primes**

# 2-Level Hazard-Free Logic Minimization: a Complete Example
 
## Step 1: Generate All DHF-Prime Implicants



### Approach: 2 steps


- Generate All Prime Implicants
- Reduce to DHF-Prime Implicants

**Some primes have  
no illegal intersections  
=> they are DHF-primes**

# 2-Level Hazard-Free Logic Minimization: a Complete Example

## Step 1: Generate All DHF-Prime Implicants

*illegal intersection!*

 

### Approach: 2 steps


- Generate All Prime Implicants
- ➔ Reduce to DHF-Prime Implicants

Other primes have  
illegal intersections  
=> they must be **reduced**

# 2-Level Hazard-Free Logic Minimization: a Complete Example

## Step 1: Generate All DHF-Prime Implicants

### First reduction of prime implicant

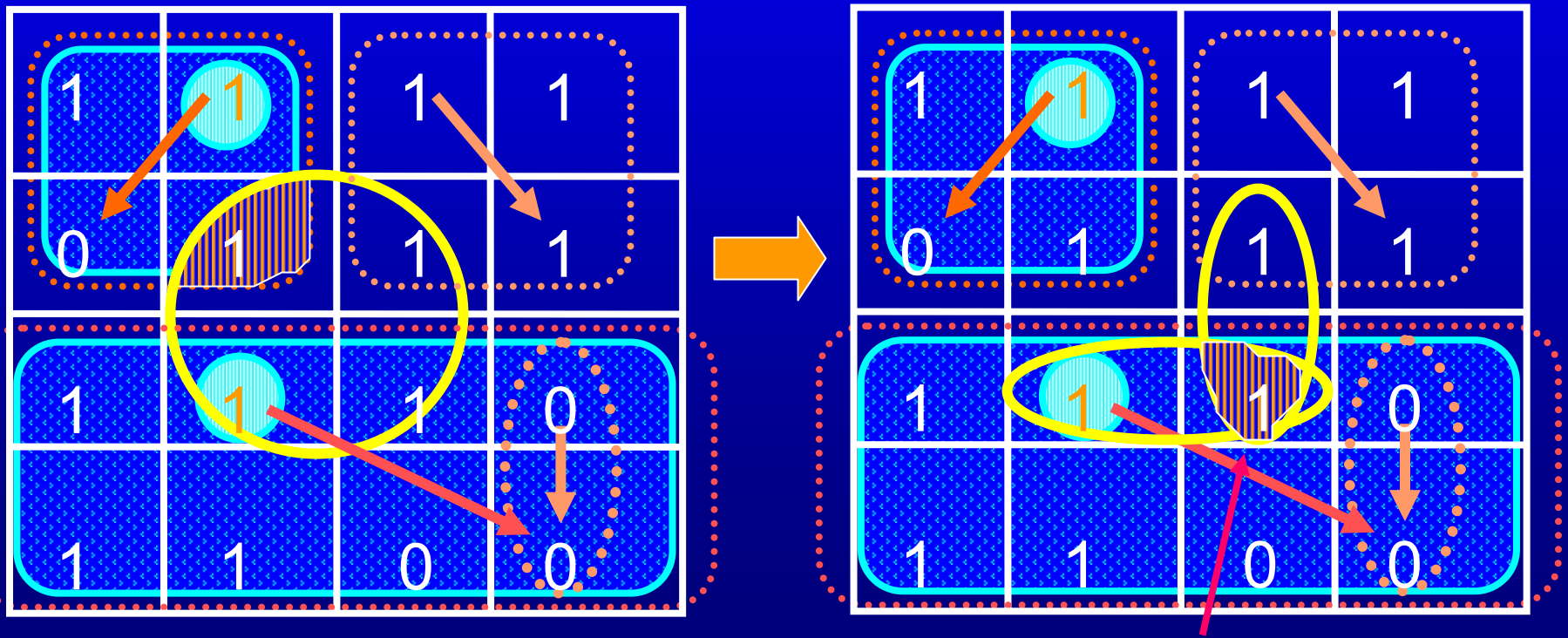


*new illegal intersection!*

# 2-Level Hazard-Free Logic Minimization: a Complete Example

## Step 1: Generate All DHF-Prime Implicants

### Second reduction of prime implicant

*DISCARD: contained  
in a DHF-Prime*

 


*All illegal intersections eliminated*

*KEEP: new DHF-Prime*

# 2-Level Hazard-Free Logic Minimization: a Complete Example
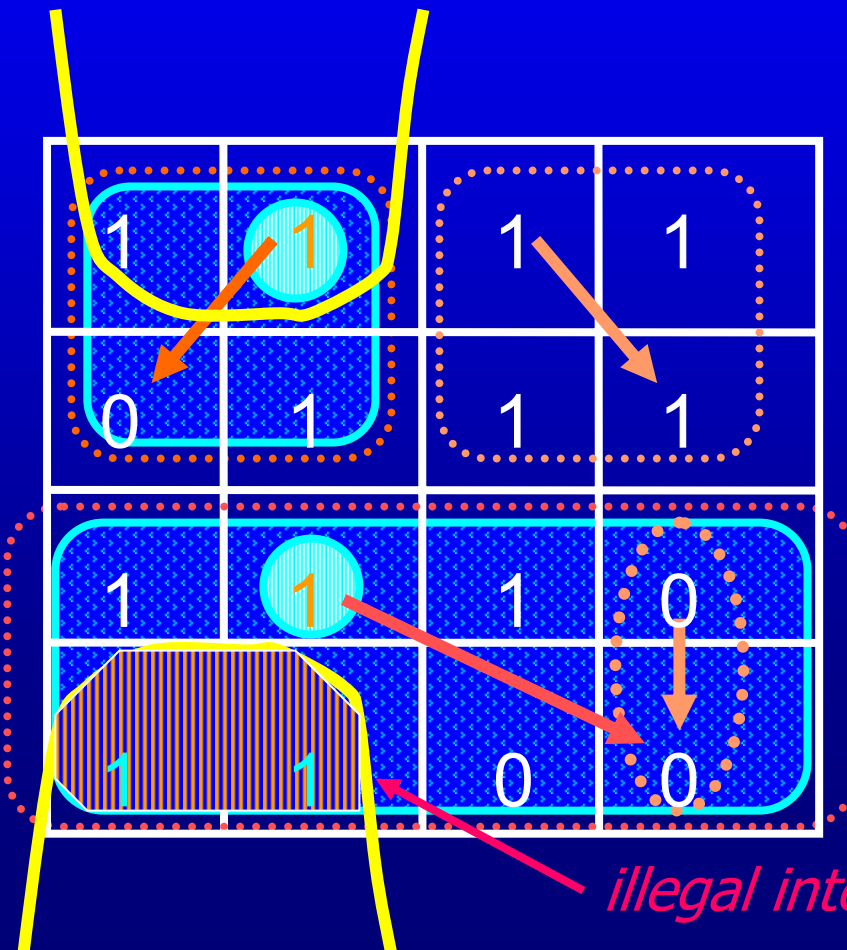
## Step 1: Generate All DHF-Prime Implicants



### Approach: 2 steps

- Generate All Prime Implicants
- ➔ Reduce to DHF-Prime Implicants

**Other primes have illegal intersections**  
=> they must be **reduced**



*illegal intersection!*

# 2-Level Hazard-Free Logic Minimization: a Complete Example

## Step 1: Generate All DHF-Prime Implicants

**First reduction of prime implicant**

*DISCARD: contained  
in a DHF-Prime*

  


*All illegal intersections eliminated*



# 2-Level Hazard-Free Logic Minimization: a Complete Example
 
## Step 1: Generate All DHF-Prime Implicants



**Final Result:**  
**6 DHF-Prime Implicants**

# 2-Level Hazard-Free Logic Minimization: a Complete Example

## Step 2: Generate DHF-Prime Implicant Table

		<u>DHF-Prime Implicants</u>					
		<i>P1</i>	<i>P2</i>	<i>P3</i>	<i>P4</i>	<i>P5</i>	<i>P6</i>
<u>Required Cubes</u>	<i>ac'</i>				X		
	<i>a'c'd'</i>	X					
	<i>a'bc'</i>		X	X			
	<i>a'c</i>					X	
	<i>bcd</i>						X

# 2-Level Hazard-Free Logic Minimization: a Complete Example

## Step 3: Solve Covering Problem

pick either DHF-prime

○ = pick all essential  
DHF-primes

DHF-Prime Implicants



P1 P2 P3 P4 P5 P6

Required Cubes

$ac'$				X		
$a'c'd'$	X					
$a'bc'$		X	X			
$a'c$					X	
$bcd$						X

# 2-Level Hazard-Free Logic Minimization: a Complete Example

  
## Final Hazard-Free Circuit (minimum-cost):




**5 DHF-Prime Implicants**

# 2-Level Hazard-Free Logic Minimization: a Complete Example
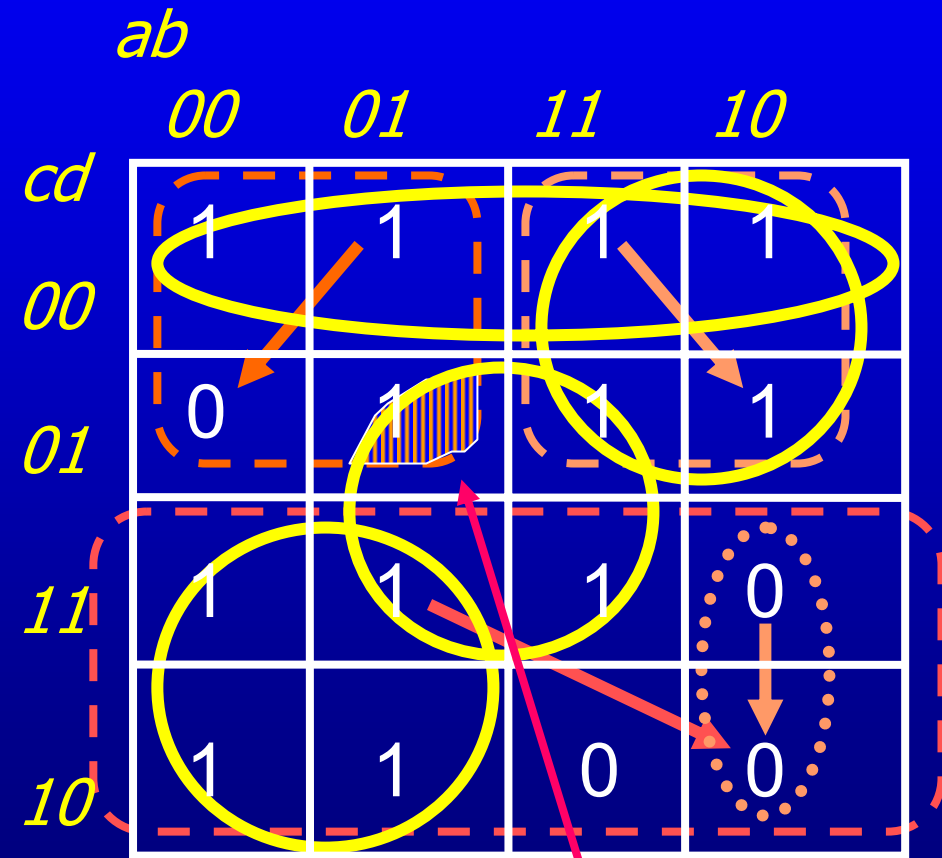
## Final *Non-Hazard-Free* Circuit (minimum-cost):



*illegal intersection => logic hazard*

 


*1 fewer product*

**4 Prime Implicants**

# 2-Level Hazard-Free Logic Minimization: Another Example

*same # of products*

 


**Non-hazard-free:**  
min cost = 3 products

**Hazard-free:**  
min cost = 3 products
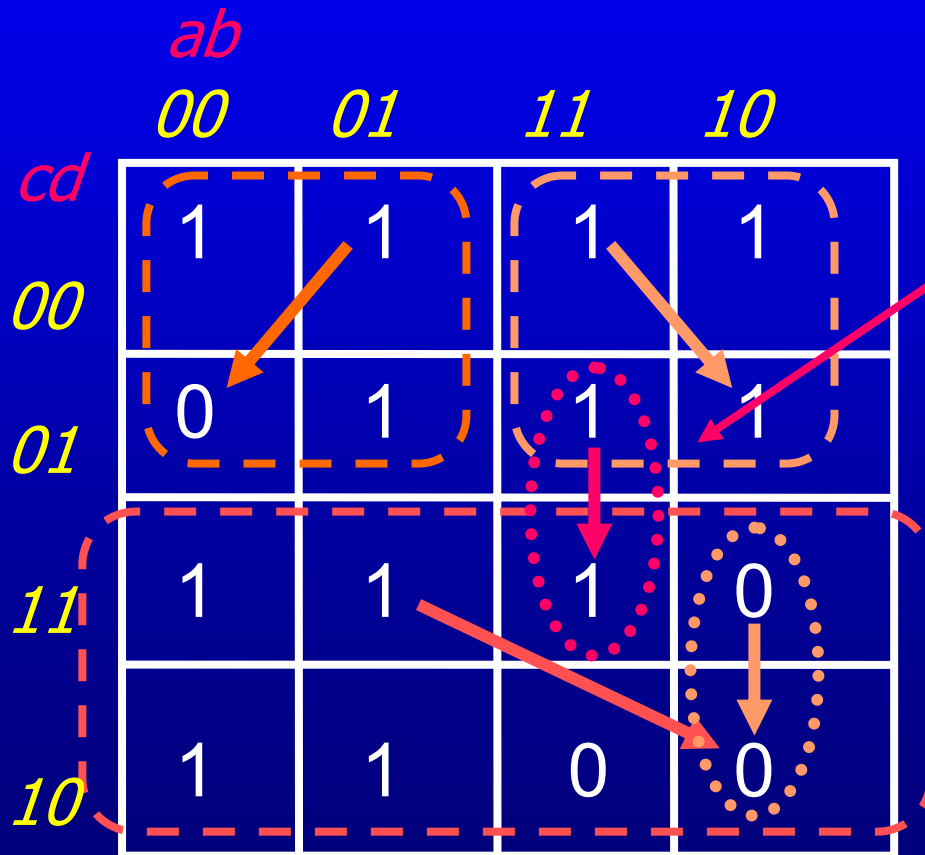
# Existence of a Hazard-Free Solution


**Challenge:** a hazard-free 2-level implementation does not always exist!



**New Example:** add 1 more input transition
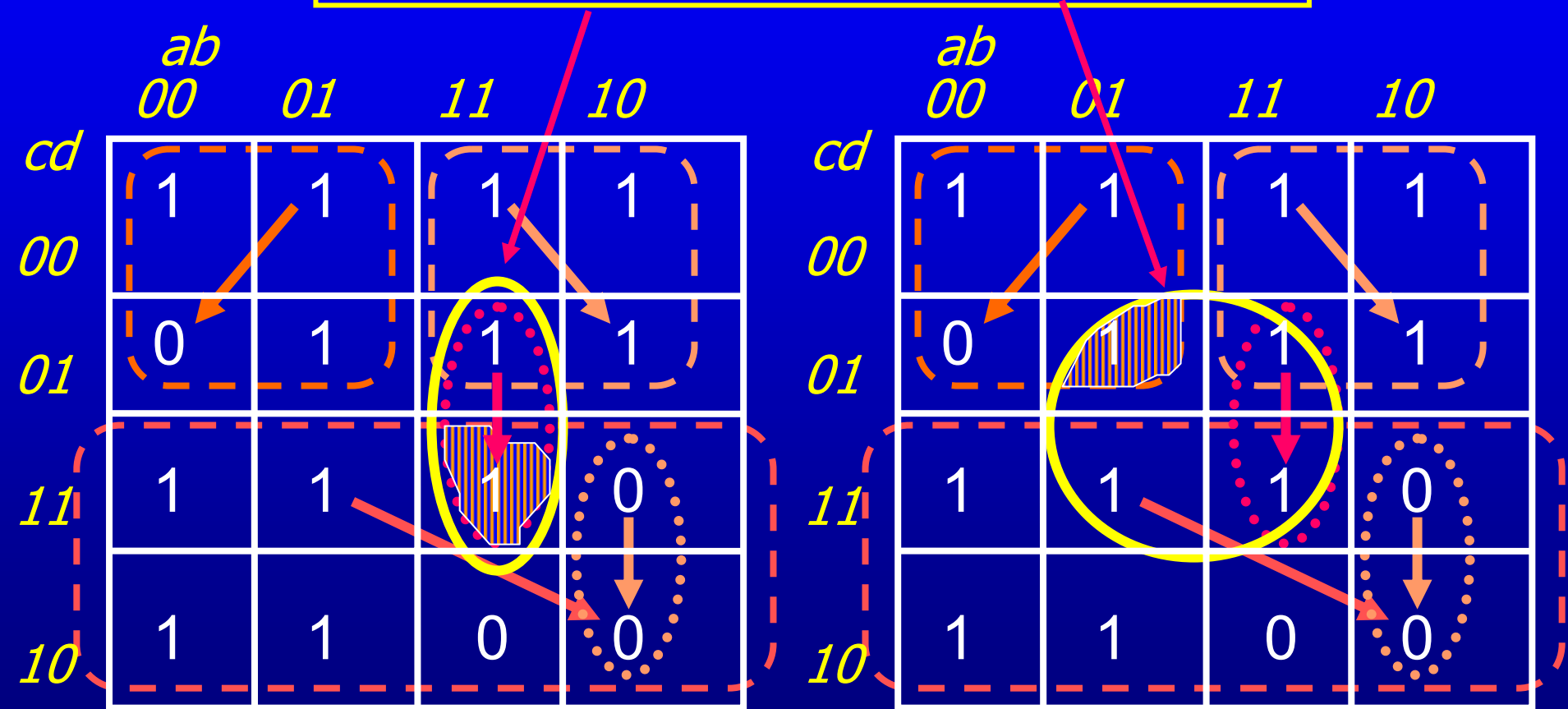
# Existence of a Hazard-Free Solution

Every implicant containing the new required cube also has an *illegal intersection*!



No hazard-free 2-level implementation exists



# Existence of a Hazard-Free Solution

## DHF-Prime Implicant Table

### DHF-Prime Implicants

	<i>P1</i>	<i>P2</i>	<i>P3</i>	<i>P4</i>	<i>P5</i>	<i>P6</i>
<i>ac'</i>				X		
<i>a'c'd'</i>	X					
<i>a'bc'</i>		X	X			
<i>a'c</i>					X	
<i>bcd</i>						X
<i>abd</i>						

Required Cubes

*new*



*abd*

*not covered!*



# Existence of a Hazard-Free Solution

## Conclusion:

- asynchronous sequential synthesis methods:  
must produce functions for which hazard-free implementations exist!

**Burst-Mode Synthesis Methods:** impose constraints on

- state minimization
- state assignment


... to generate Boolean functions where all logic hazards can *always* be eliminated

Always guarantee a hazard-free solution exists

# An Alternative Approach: using "Generalized C-Elements"

## Alternative to 2-Level Logic

Target = "Generalized C-element (*GC*)":


 


# Hazard-Free Logic Using GC-Elements

## gC-Based Mapping: an Example

AB		CD			
		00	01	11	10
CD	00	1	1	1	0
	01	1	1	—	—
	11	1	0	0	—
	10	1	1	1	1

Function

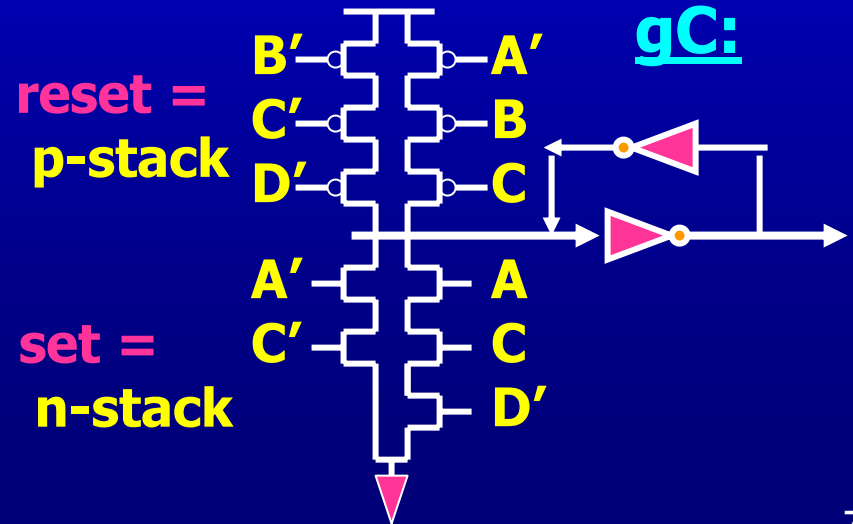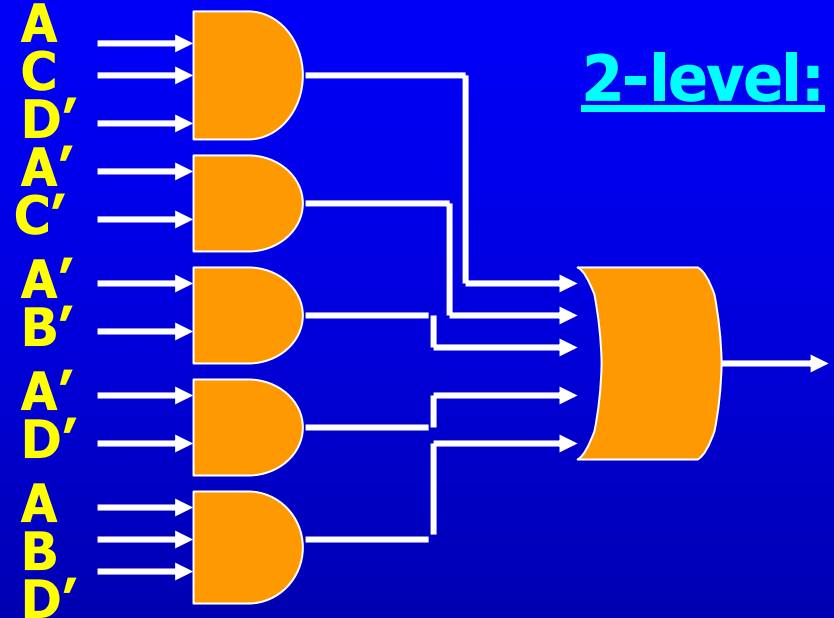

# A Reading List

## Hazard Basics:

- S. Unger, *Asynchronous Sequential Switching Circuits*, Wiley Interscience, 1969
- J. Beister, "A Unified Approach to Combinational Hazards", IEEE Transactions on Computers, vol C-23, no. 6, 1974
- S.M. Nowick, *Automatic Synthesis of Burst-Mode Asynchronous Controllers*, PhD Thesis, Stanford University, March 1993 (revised technical report, Stanford Computer Systems Lab CSL-TR-95-686, Dec. 1995).
- S.M. Nowick and D.L. Dill, "Exact Two-Level Minimization of Hazard-Free Logic with Multiple-Input Changes", IEEE Transactions on Computer-Aided Design, vol. 14, pp. 986-997, August 1995

## Two-Level Hazard-Free Logic Minimization:

Basic Method: (first complete solution) exact hazard-free minimization

- S.M. Nowick and D.L. Dill, "Exact Two-Level Minimization of Hazard-Free Logic with Multiple-Input Changes", IEEE Transactions on Computer-Aided Design, vol. 14, pp. 986-997, August 1995

# A Reading List (cont.)

## Two-Level Hazard-Free Logic Minimization (cont.):

HFMIN: binary & symbolic (exact) hazard-free minimization

- R.M. Fuhrer and S.M. Nowick, *Sequential Optimization of Asynchronous and Synchronous Finite-State Machines: Algorithms and Tools*. Kluwer Academic, 2001.

### Recent Methods: Exact Solutions

- **"IMPYMIN"**: M. Theobald and S.M. Nowick, "Fast Heuristic and Exact Algorithms for Two-Level Hazard-Free Logic Minimization", IEEE Transactions on Computer-Aided Design, vol. 17, pp. 1130-1147, November 1998
- C. Myers and H. Jacobson, "Efficient Exact Two-Level Hazard-Free Logic Minimization", Async-01 Symposium (IEEE Int. Symp. On Advanced Rsrch. In Asynchronous Circuits and Systems), pp. 64-73, March 2001
- J. Rutten, M. Berkelaar, et al., "An Efficient Divide and Conquer Algorithm for Exact Hazard-Free Logic Minimization", Design, Automation and Test in Europe Conference (DATE), pp. 749-754, February 1998.

### Recent Methods: Heuristic Solutions

- **"ESPRESSO-HF"**: M. Theobald and S.M. Nowick, "Fast Heuristic and Exact Algorithms for Two-Level Hazard-Free Logic Minimization", IEEE Transactions on Computer-Aided Design, vol. 17, pp. 1130-1147, November 1998

## Part II


# Multi-Level Logic and Technology Mapping

# Goal: Hazard-Free Multi-Level Logic
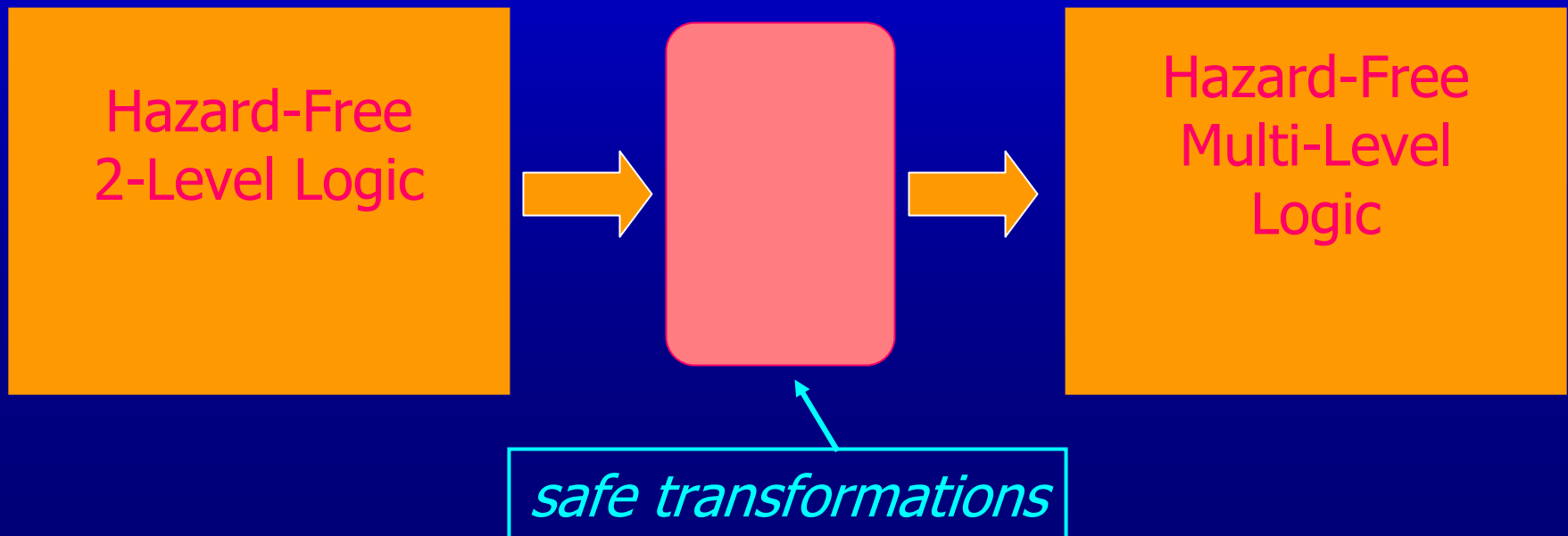
## Strategy

Start with: hazard-free 2-level logic

Apply: *hazard-non-increasing* multi-level transformations






# Hazard-Non-Increasing Multi-Level Transforms

A Large Menu of “Safe Transforms”: [Unger, Kung]

- Associative Law
- Factoring
- DeMorgan’s Law
- ... Many others:
  - Kernel & Cube Factoring
  - Dual Global Flow
  - Double Inversion
  - Tree Decomposition of a Gate

# Associative Law (1)

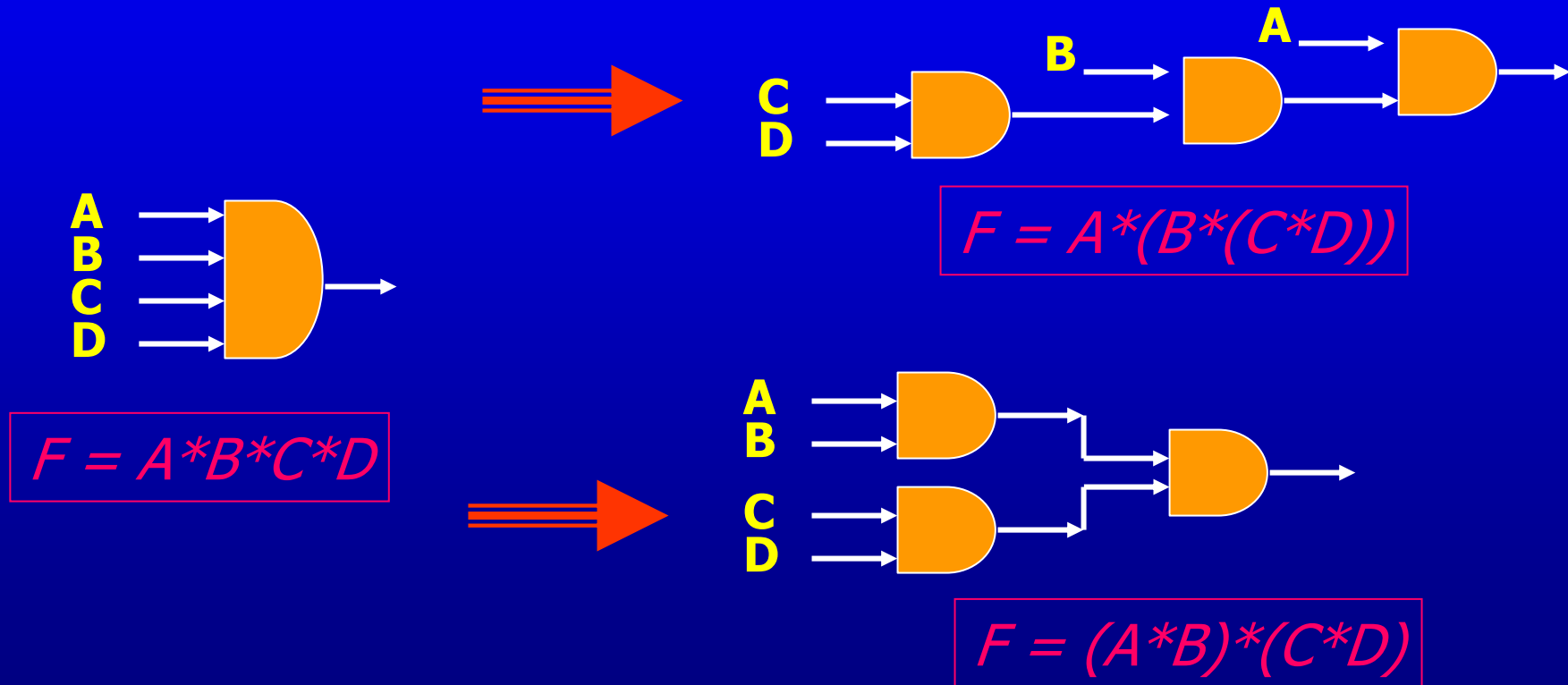
**Example:** *decomposing large fan-in gates*



This transform may introduce hazards in 'speed-independent' or 'QDI' circuits.

# Associative Law (2)

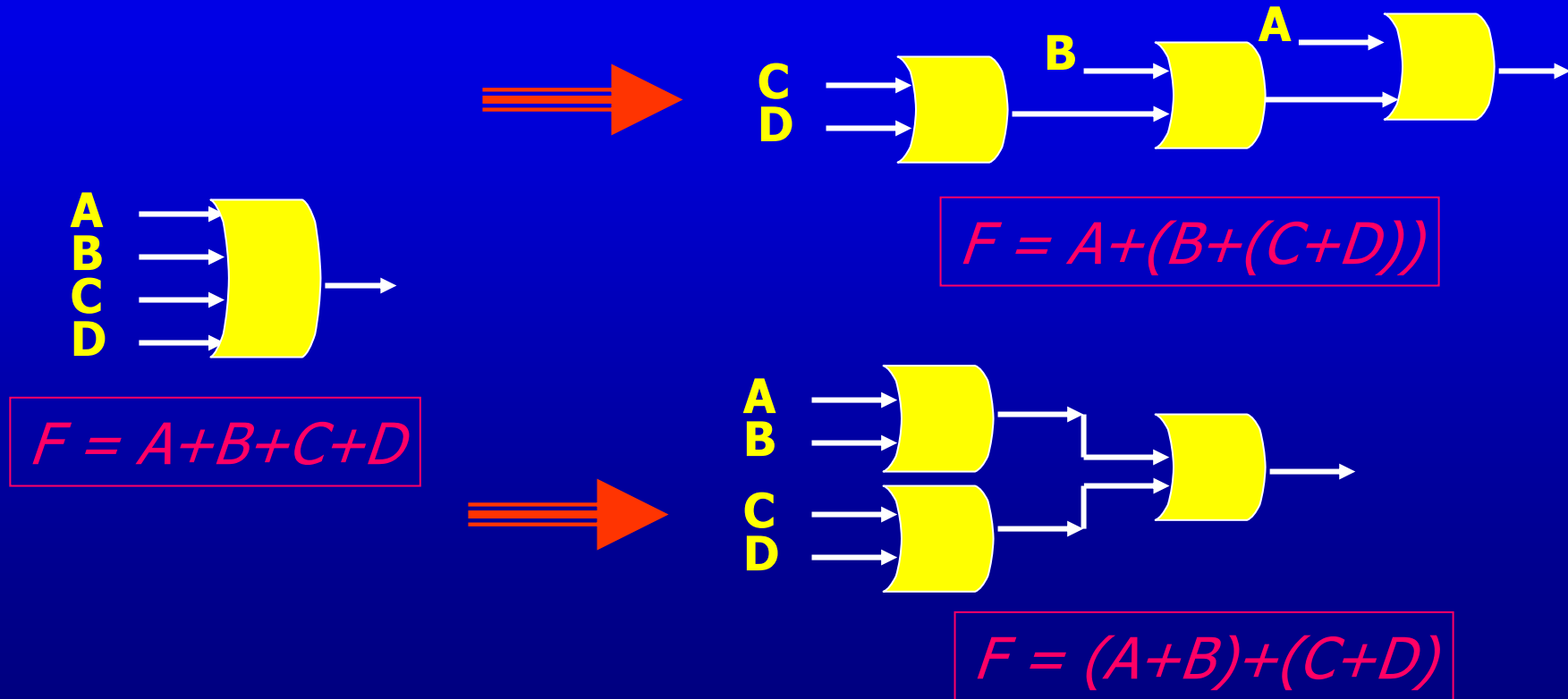
**Example:** *decomposing large fan-in gates*



This transform may introduce hazards in 'speed-independent' or 'QDI' circuits.

# Factoring


Example:

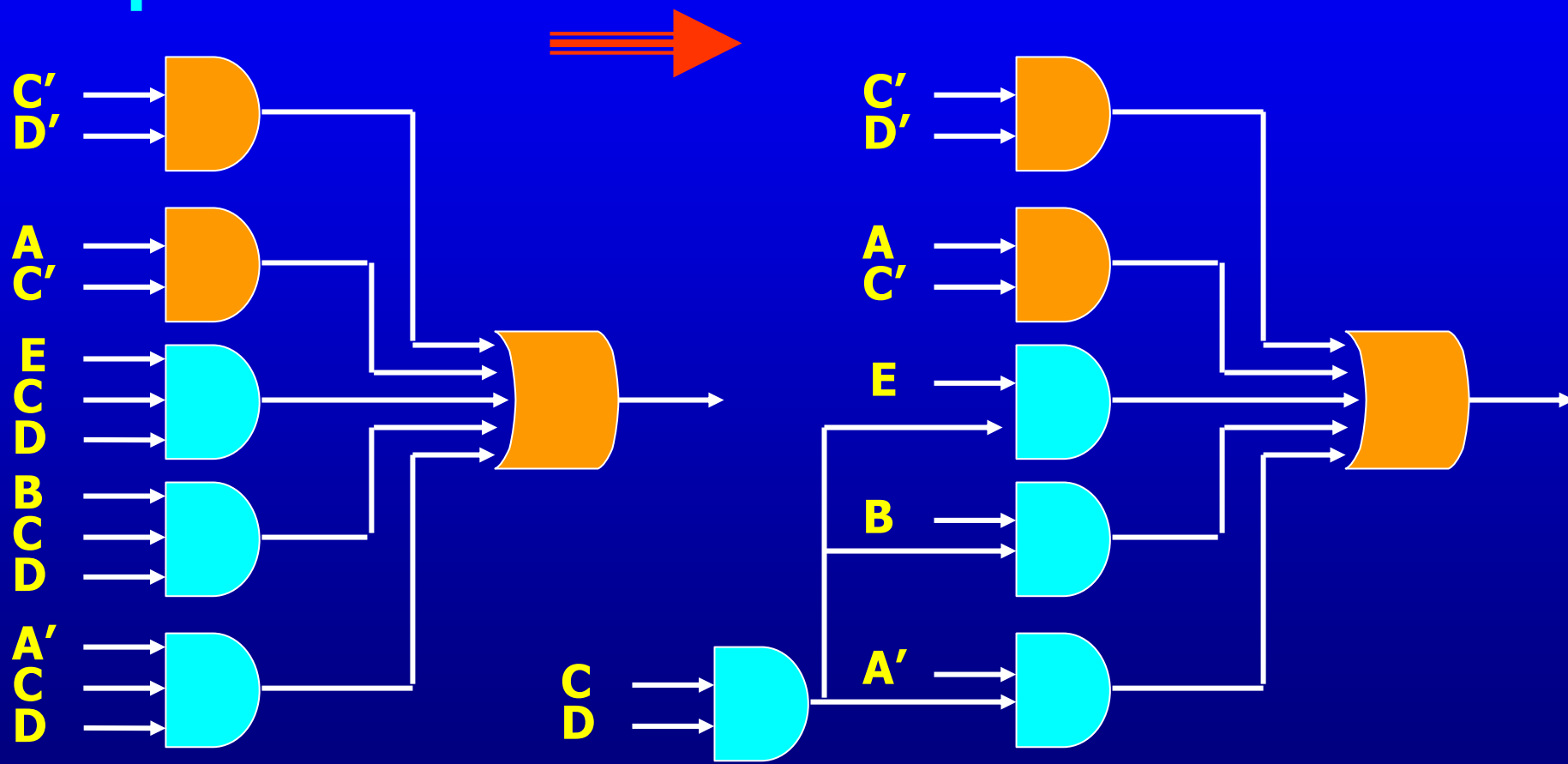


# DeMorgan's Law

## Example:

$$(A+B+C+D)' = A'*B'*C'*D'$$

 


$$(A*B*C*D)' = A'+B'+C'+D'$$

 

*Allows replacement of AND/OR gates by NAND (NOR) gates*

# Example: 2-Level Circuit (cont.)

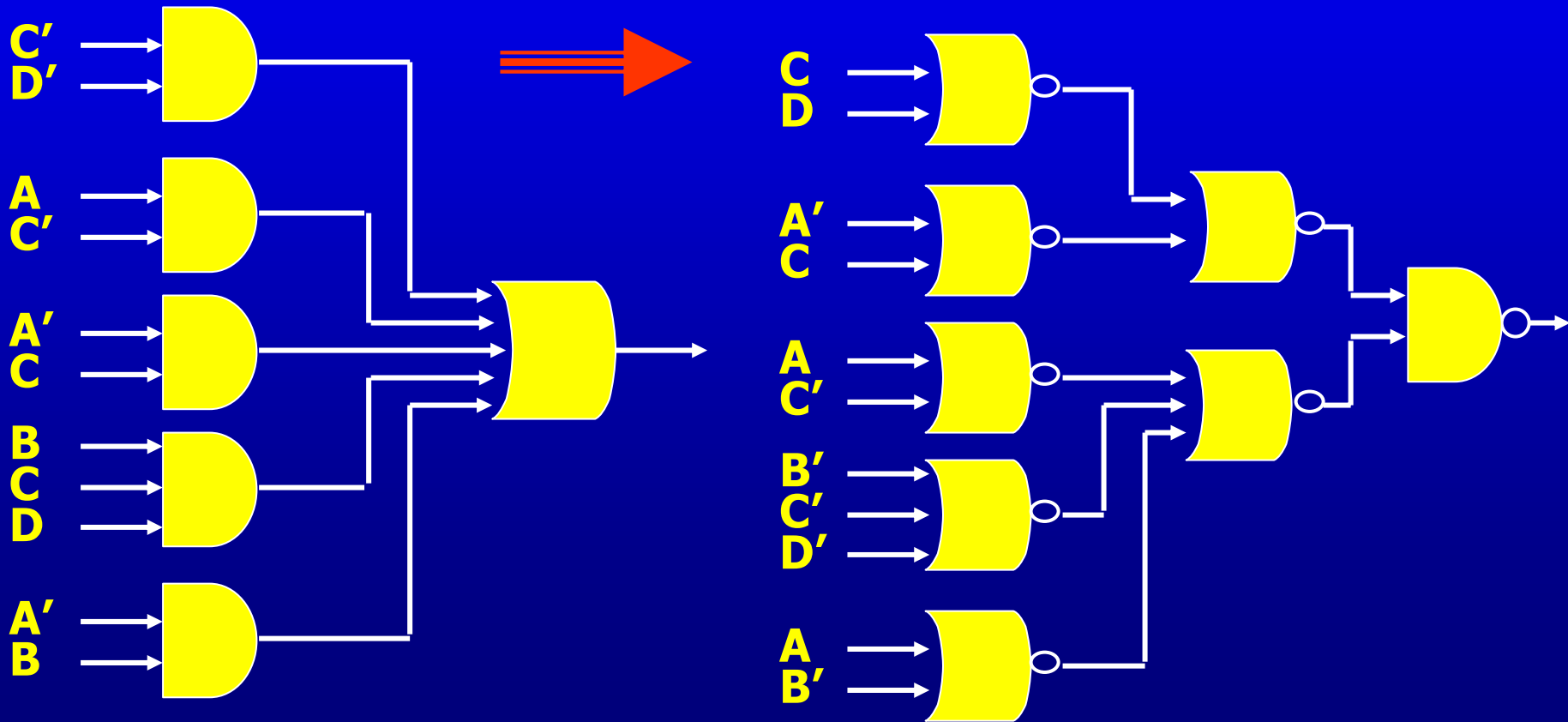

# Summary

## Hazard-Non-Increasing Transforms:

- Allow hazard-free decomposition into simple gates (*always!*)
- Wide & flexible range of safe transforms:
  - much overlap with 'scripts' of Synopsys Design Compiler
- Less restrictive than QDI or speed-independent transforms:
  - many safe "fundamental mode" multi-level transforms fail with QDI [e.g. associative law]

# Hazard-Free Technology Mapping

## 1. Basic approach:

- Siegel, De Micheli [DAC'93]

## 2. For improved “average-case performance”:

- basic: Beerel et al. [Async'96]
- transistor-level optimization: James, Yun [Async'98]

## 3. For complex CMOS gates:

- Kudva et al. [DAC'96]



# A Reading List

## Hazard-Free Multi-Level Logic:

- S. Unger, *Asynchronous Sequential Switching Circuits*, Wiley Interscience, 1969
- D. Kung, "Hazard-non-increasing gate-level optimization algorithms", IEEE International Conference on CAD (ICCAD), pp. 631-634, Nov. 1992
- B. Lin and S. Devadas, "Synthesis of Hazard-Free Multi-Level Logic Under Multiple-Input Changes from Binary Decision Diagrams", IEEE Transactions on Computer-Aided Design, vol. 14:8, pp. 974-985, August 1995

## Hazard-Free Technology Mapping:

- P. Siegel, G. De Micheli, and D. Dill, "Automatic Technology Mapping for Generalized Fundamental Mode Asynchronous Designs," IEEE Design Automation Conference (DAC), pp. 61-67, June 1993
- P.A. Beerel, K.Y. Yun, and W.C. Chou, "Optimizing Average-Case Delay in Technology Mapping of Burst-Mode Circuits", Async Symposium (IEEE Intl. Symposium on Advanced Research in Async. Circuits and Systems), PP. 244-259, March 1996.

# A Reading List (cont.)

## Hazard-Free Technology Mapping (cont.):

- K. James and K.Y. Yun, "Average-case optimized transistor-level technology mapping of extended burst-mode circuits", Async Symposium (IEEE Intl. Symposium on Advanced Research in Async. Circuits and Systems), PP. 70-79, April 1998.
- P. Kudva, G. Gopalakrishnan, H. Jacobson, and S. Nowick, "Synthesis of Hazard-Free Customized CMOS Complex-Gate Networks Under Multiple-Input Changes", IEEE Design Automation Conference (DAC), pp. 77-82, June 1996