

CSEE 6861
Prof. Nowick

Kernels, Co-Kernels
& Extraction Examples

This handout covers kernels/co-kernels, Brayton/McMillen's theorem,
& multi-cube + single-cube extraction.

(these examples were presented in class in a previous lecture.)

we'll start with multi-cube extraction, then later do single-cube extraction.

multi-cube extraction


Ex.#1

we are given 2 local functions:

$$f_1 = abcd + abce + abf + ag + hi$$


$$f_2 = cdhk + cehk + hkji + an$$

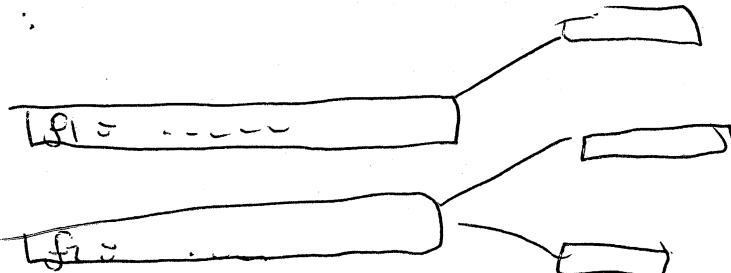In our multi-level representation, these are 2 separate nodes
in a given logic network:



Our goal:

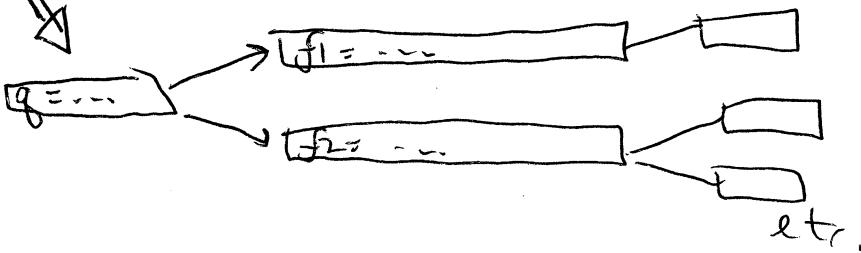extract a multi-cube divisor g, allowing us to
simplify nodes $f_1 + f_2$ et.



Kernels, Co-kernels
& extraction (cont.)

multi-cube extraction (cont.)

Compute kernels/co-kernels of $f_1 + f_2$:

$$f_1 = abcd + abce + abf + ag + hi$$

Co-kernels/Kernels(f_1):

$$\text{trivial co-kernel}$$

$$\text{trivial kernel} = f$$

$$f_1 - 1) \quad 1. (abcd + abce + abf + ag + hi)$$

$$f_1 - 2) \quad a \cdot (bcd + bce + bf + g)$$

co-kernel

kernel

(level-3)

$$f_1 - 3) \quad ab \cdot (cd + ce + f)$$

co-kernel

kernel

(level-1)

$$f_1 - 4) \quad abc \cdot (d + e)$$

co-kernel

kernel

(level-0)

$$f_2 = cdhk + cehk + hkji + an$$

trivial co-kernel

trivial kernel = f

Co-kernels/Kernels(f_2):

$$f_2 - 1) \quad 1. (cdhk + cehk + hkji + an)$$

$$f_2 - 2) \quad hk \cdot (cd + ce + ji)$$

co-kernel

kernel

(level-1)

$$f_2 - 3) \quad chk \cdot (d + e)$$

co-kernel

kernel

(level-0)

Now use Brayton/Mcmullen's Theorem to find candidate multi-cube extracted
drives.

Method: Kernel intersection = find all non-trivial multi-cube
kernel intersections (between f_1 and f_2):

- Examples:
- Kernel $f_1 - 3 \cap$ Kernel $f_2 - 2 = \{cd, ce\} = [cd + ce]$
 - Kernel $f_1 - 4 \cap$ Kernel $f_3 - 3 = \{d, e\} = [d + e]$

Kernels, Co-Kernels & extraction (cont.)



multi-cube extraction (cont.)

as our multi-cube divisor.


Let's pick $[g = cd + ce]$ (To be legitimate, this must contain 2 or more cubes — it does, & contributes to 2 or more local functions — it does $[f_1, f_2]$).

Note the circuit structure before & after multi-cube extraction:


Before multi-cube extraction:

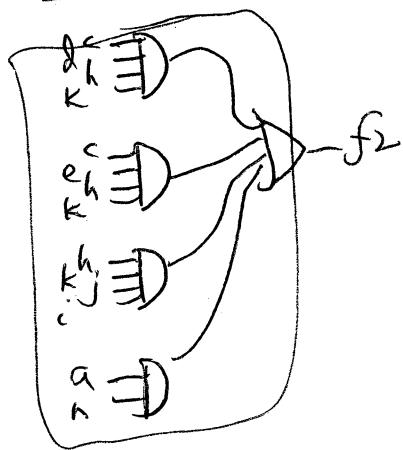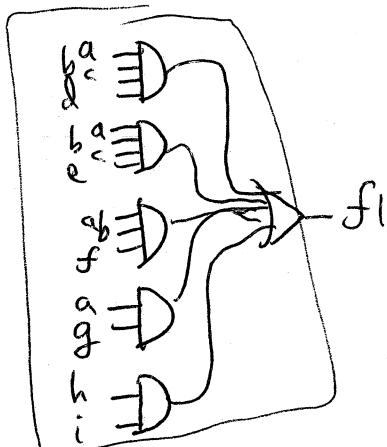

After multi-cube extraction:

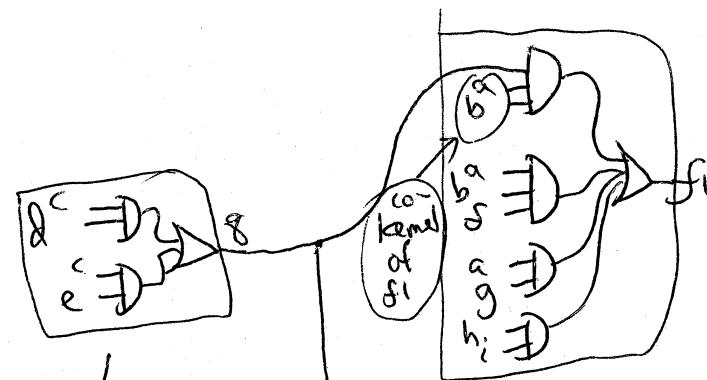

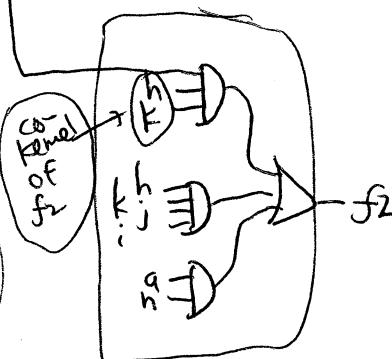extracted multi-cube expression
= kernel intersection
(of kernel
 $f_1 \rightarrow$ of f_1
and kernel
 $f_2 \rightarrow$ of f_2)



Next, we'll do a single-cube extraction example, re-using local functions but also with a new local function f_3 .


single-cube extraction

Ex.#2 We are given 2 local functions:

(same
as before)


$$\begin{aligned} f_2 &= cdhk + cehk + hkji + an \\ f_3 &= abchi + cdhi + gchi + j \end{aligned}$$

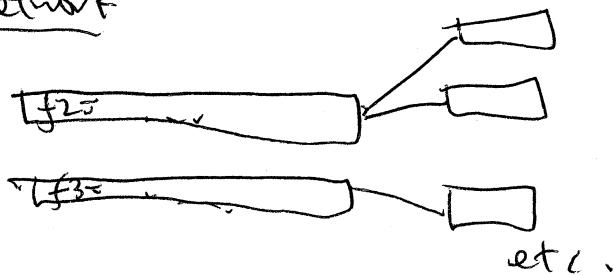In our multi-level representation, these are 2 separate nodes in a given logic network:



Our goal:

extract a single-cube divisor of, allowing us to simplify nodes f_2 & f_3

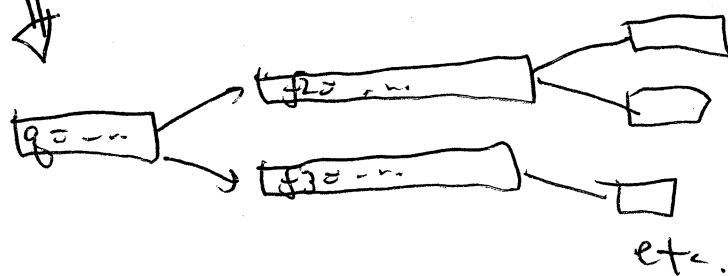

CSEE 6861
Prof. Nowick

Kernels, co-kernels,
+ extraction (cont.)

Single-cube extraction (cont.)

Compute kernels/co-kernels of $f_2 + f_3$:

Co-kernels / Kernels (f_2): <see p. 2>

	<u>co-kernel</u>	<u>kernel</u>
$f_{2-1})$	$\overbrace{1 \cdot}$	$\overbrace{(cdhk + cehk + hkji + an)}$
$f_{2-2})$	$\overbrace{hk \cdot}$	$\overbrace{(cd + ce + ji)}$
$f_{2-3})$	$\overbrace{chk \cdot}$	$\overbrace{(d + e)}$

Co-kernels / Kernels (f_3):

	<u>co-kernel</u>	<u>kernel</u>
$f_{3-1})$	$\overbrace{i \cdot}$	$\overbrace{(abchi + cdhi + gchi + j)}$
$f_{3-2})$	$\overbrace{chi \cdot}$	$\overbrace{(ab + d + g)}$

Now use a variant of Brzozowski/McMillen's theorem to find all candidate single-cube extracted divisors.

(Method): co-kernel intersection = find all non-trivial (single-cube) co-kernel intersections (between f_1 and f_2):

Example: only one! =


$$\begin{aligned} \text{Co-kernel } f_{2-3} \cap \text{co-kernel } f_{3-2} \\ = \text{ chk } \cap \text{ chi } = \boxed{\text{ch}} \end{aligned}$$

Kernels, co-kernels,
+ extraction (cont.)

Single-ake extraction (cont.)

Note the circuit structure before after single-ake extraction.
(In this case, the intersected co-kernel is extracted, while for multi-ake extraction on p.3 the intersected kernel is extracted!)

Before single-ake extraction:

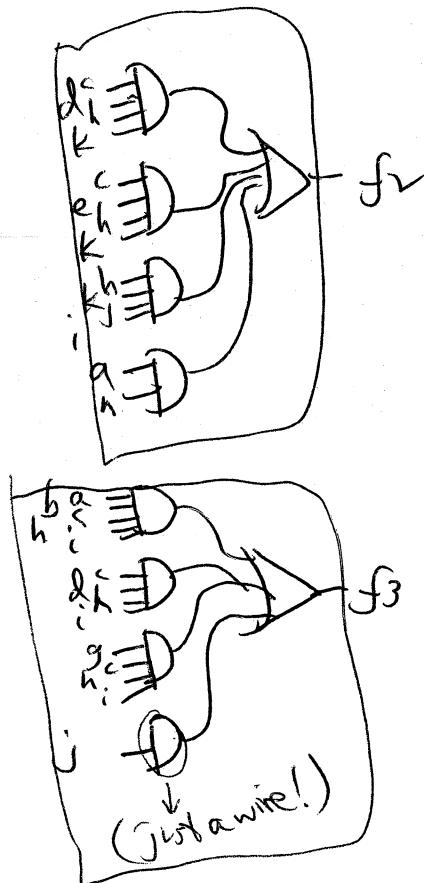

After single-ake extraction:

