

CSEE 6861 CAD of Digital Systems
Handout: Lecture #1
1/21/16

Prof. Steven M. Nowick
nowick@cs.columbia.edu

Department of Computer Science (and Elect. Eng.)
Columbia University
New York, NY, USA

Overview of Design Flow

Key Synthesis/Optimization Steps: at 3 Levels

1. Architectural Synthesis (also, "High-Level Synthesis" [HLS])

Starting point: behavioral system specification

Steps: *scheduling, resource allocation (sharing) and binding*

Outcome: register-transfer level (RTL) optimized design
for block-level datapath + FSM controller specification

2. Logic Synthesis

Steps:

sequential synthesis: FSM optimization

combinational synthesis: (i) 2-level logic minimization, (ii) multi-level logic optimization

technology mapping: optimal mapping of gates to VLSI "library" cells

Outcome: mapped gate-level circuit

3. Physical Design

Steps: *circuit partitioning, chip floorplanning, place-and-route ("P&R")*
... + late timing correction/optimizations, etc.

Outcome: complete chip layout → ready for fabrication

#3

Architectural Synthesis

High-Level Specification: Differential Equation Solver (diff-eq) Custom Unit

```
diffeq {
  read ( x, y, u, dx, a );
  repeat {
    x1 = x + dx;
    u1 = u - ( 3 * x * u * dx ) - ( 3 * y * dx );
    y1 = y + u * dx;
    c = x1 < a;
    x = x1 ; u = u1 ; y = y1;
  }
  until ( c );
  write ( y );
}
```

Figures courtesy of: G. De Micheli, *Synthesis and Optimization of Digital Circuits*, McGraw-Hill (1994)

#4

Architectural Synthesis

Target Micro-Architecture: Register-Transfer Level

 


FIGURE 1.12
Example of structural view at the architectural level.

#5

Architectural Synthesis

Detailed Target Micro-Architecture:

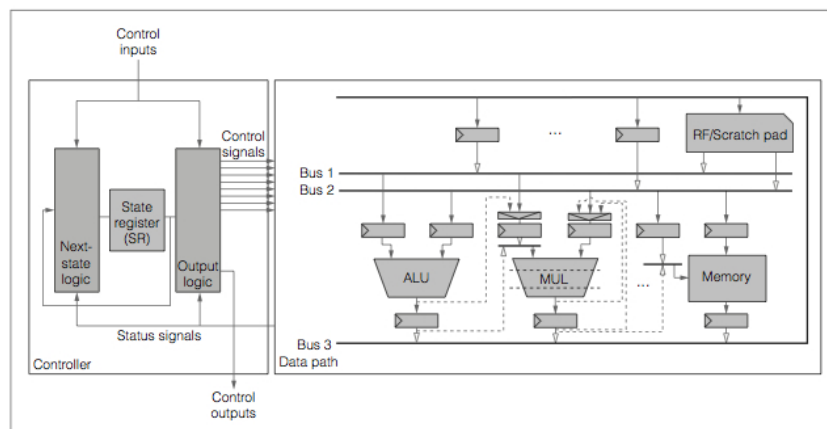



Figure 2. Typical architecture.

Courtesy of: P. Coussy, D.D. Gajski, M. Meredith and A. Takach,
"An Introduction to High-Level Synthesis", IEEE Design & Test of Computers (July/Aug. 2009)
 
#6

Architectural Synthesis


Unscheduled Control-Dataflow Graph (CDFG): *diff-eq*



#7

Architectural Synthesis


Scheduled CDFG: **minimum-latency**

 
 
#8

Architectural Synthesis


Scheduled CDFG: **min-area**
= resource-constrained (RC)



#9

Architectural Synthesis


Resource Allocation/Sharing

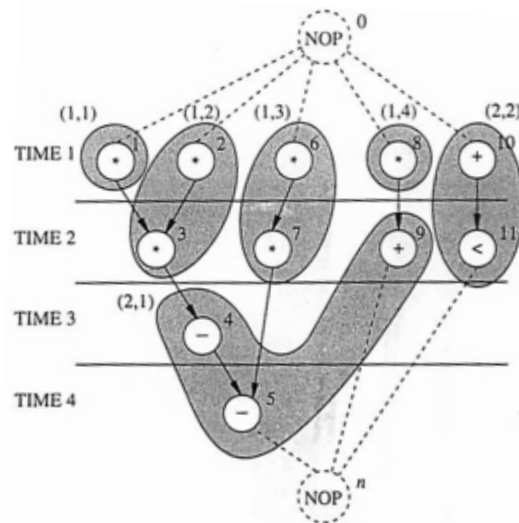
 
#10

Logic Synthesis

Result of Multi-Level Optimization: "opa"
2119 gate inputs (literals) down to 430 gate inputs



#13

Logic Synthesis

Technology Mapping =
binding to VLSI cells

 


FIGURE 10.6
Covering of a subject graph.

#14

Physical Design

Optimal Circuit Partitioning: Kernighan-Lin Algorithm

 


Fig. 1. Partitioning of 412-cell circuit into groups of size ≤ 8 .

Figure courtesy of: A.E. Dunlop and B.W. Kernighan, "A Procedure for Placement of Standard-Cell VLSI Circuits", IEEE Trans. On Computer-Aided Design (Jan. 1985)

#15

Physical Design

Optimal Place-and-Route

 


Fig. 4. Automatically generated layout for circuit with 453 signals and 412 cells.

Figure courtesy of: A.E. Dunlop and B.W. Kernighan, "A Procedure for Placement of Standard-Cell VLSI Circuits", IEEE Trans. On Computer-Aided Design (Jan. 1985)

#16

Physical Design

Final Chip Layout

 


FIGURE 1.3
One of AT&T's Application Specific Standard Product chips. The chip was designed and laid out using AT&T CAD tools, with a standard cell design style. (Courtesy of AT&T.)

17

Review: Basic Definitions (2-Level Logic Minimization)

Review: Basic Definitions

Literal: a variable (x) or its complement (x')

Product: an "AND" of literals (e.g. $xy'z$, $a'bcd'$)

Cube: a product (another equivalent name)

Implicant: a cube/product which contains no OFF-set minterm (i.e. 0 value)

• *Note:* implicants do not need to contain any ON-set minterms (i.e. 1 values), but they usually do

Prime Implicant (PI, prime): a maximal implicant (i.e. not contained in any larger implicant)

Essential Prime Implicant (essential): a prime which contains at least one ON-set minterm (i.e. 1 value) not contained in any other prime

Sum-of-products (SOP, disjunctive normal form):

a sum of products ("AND-OR" 2-level circuit)

Cover: a set of primes (SOP) which together contain all ON-set minterms (i.e. 1 values) of a function

Complete Sum: a cover containing all possible prime implicants of the function

#19

Review: Basic Definitions

The 2-Level Logic Minimization Problem: given Boolean function f ,

(i) Find a **minimum-cost set of prime implicants which "covers"** (i.e. contains) **all ON-set minterms of function f** (and possibly some DC-set minterms)

or (...equivalently):

(ii) Find a **minimum-cost cover F of function f**

#20

2-Level Logic Minimization: Definitions + Design Space Exploration

2-Level Logic Minimization: Example


		AB			
		00	01	11	10
CD	00	1	1	0	0
	01	0	1	1	0
	11	0	0	1	1
	10	0	0	0	0

#22

2-Level Logic Minimization: Example

Solution #1: All Primes = 5 Products (AND gates)

		AB			
		00	01	11	10
CD	00	1	1	0	0
	01	0	1	1	0
	11	0	0	1	1
	10	0	0	0	0

 

"Complete Sum":
cover containing all prime implicants

corresponding 2-level implementation


#23

2-Level Logic Minimization: Example

Solution #2: Subset of Primes = 4 Products (AND gates)

		AB			
		00	01	11	10
CD	00	1	1	0	0
	01	0	1	1	0
	11	0	0	1	1
	10	0	0	0	0

Locally sub-optimal solution

 

"Redundant Cover":
can remove a product and still have legal cover

corresponding 2-level implementation


#24

2-Level Logic Minimization: Example

Solution #3: Subset of Primes = 4 Products (AND gates)

		AB			
		00	01	11	10
CD	00	1	1	0	0
	01	0	1	1	0
	11	0	0	1	1
	10	0	0	0	0

 Locally optimal solution:
... but globally sub-optimal = "LOCAL MINIMUM"



"Irredundant Cover" (but globally sub-optimal):
cannot remove any product and still have legal cover

corresponding 2-level implementation


#25

2-Level Logic Minimization: Example

Solution #4: Subset of Primes = 3 Products (AND gates)

		AB			
		00	01	11	10
CD	00	1	1	0	0
	01	0	1	1	0
	11	0	0	1	1
	10	0	0	0	0

Globally-optimal solution

 

OPTIMAL SOLUTION (also irredundant)

corresponding 2-level implementation

#26

Exact 2-Level Logic Minimization: Quine-McCluskey (QM) Method

Quine-McCluskey Method: Examples

Example #1: $f(A,B,C,D) = m(0,4,5,11,15) + d(2,6,9)$

[m = ON-set minterms, d = DC-set minterms]

		AB			
		00	01	11	10
CD	00	1	1	0	0
	01	0	1	0	-
	11	0	0	1	1
	10	-	-	0	0

#28

Quine-McCluskey Method: Examples

Example #1 (cont.)

		AB			
		00	01	11	10
CD	00	1	1	0	0
	01	0	1	0	-
	11	0	0	1	1
	10	-	-	0	0

P1
P2
P4
P3

Generate all prime implicants

#29

Quine-McCluskey Method: Examples

Example #1 (cont.)

		AB			
		00	01	11	10
CD	00	1 ⊕	1	0	0
	01	0	1 ⊕	0	-
	11	0	0	1 ⊕	1
	10	-	-	0	0

P1
P2
P4
P3

⊕ = distinguished minterm

Prime Implicant Table

		prime implicants			
		(P1)	(P2)	(P3)	P4
ON-set minterms	⊕ 0	X			
	4	X	X		
	⊕ 5		X		
	11			X	X
	⊕ 15			X	

○ = essential prime

Approach: **remove & save essentials** {p1, p2, p3}, and **delete intersecting rows** ... **empty table: nothing left to cover.** #30

Quine-McCluskey Method: Examples

Example #2: $f(A,B,C) = m(0,1,2,6) + d(5)$

[m = ON-set minterms, d = DC-set minterms]

		A	
		0	1
BC	00	1	0
	01	1	-
	11	0	0
	10	1	1

More complex example: illustrates "table reduction step" using column dominance

#31

Quine-McCluskey Method: Examples

Example #2: $f(A,B,C) = m(0,1,2,6) + d(5)$

[m = ON-set minterms, d = DC-set minterms]

		A	
		0	1
BC	00	1	0
	01	1	-
	11	0	0
	10	1	1

⊗ = distinguished minterm

Prime Implicant Table

		prime implicants			
		P1	P2	P3	P4
ON-set minterms	0	X		X	
	1	X			X
	2		X	X	
	⊗ 6		X		
	5				

○ = essential prime

Initial PI Table

#32

Quine-McCluskey Method: Examples

Example #2: $f(A,B,C) = m(0,1,2,6) + d(5)$

[m = ON-set minterms, d = DC-set minterms]

		prime implicants			
		P1	P2	P3	P4
ON-set minterms	0	X		X	
	1	X			X
	2		X	X	
	6		X		

○ = essential prime

Initial PI Table

		prime implicants		
		P1	P3	P4
ON-set minterms	0	X	X	
	1	X		X

Reduced PI Table (a)

Approach: remove & save essential p2, and delete intersecting rows.

#33

Quine-McCluskey Method: Examples

Example #2: $f(A,B,C) = m(0,1,2,6) + d(5)$

[m = ON-set minterms, d = DC-set minterms]

		prime implicants		
		P1	P3	P4
ON-set minterms	0	X	X	
	1	X		X

Reduced PI Table (a)

		prime implicants
		P1
ON-set minterms	0	X
	1	X

Reduced PI Table (b)

"Column Dominance":

- column p1 'column-dominates' column p3
- column p1 'column-dominates' column p4

...delete dominated columns {p3,p4}

#34

Quine-McCluskey Method: Examples

Example #2: $f(A,B,C) = m(0,1,2,6) + d(5)$

[m = ON-set minterms, d = DC-set minterms]

prime implicants

	(P1)
0	X
1	X

⊙ = secondary essential prime

“Secondary Essential Primes”:
- column p1 has now become ‘essential’

Approach: remove & save secondary essential p1,
and delete intersecting rows.
... empty table: nothing left to cover.

Reduced PI Table (b)

Final solution: {p1,p2}

#35

Quine-McCluskey Method: Examples

Example #3: $f(A,B,C) = m(0,2,3,4,5,7)$

[m = ON-set minterms, d = DC-set minterms]

	A	
	0	1
BC	P1	P2
00	1	1
01	0	1
11	1	1
P5		
10	1	0

P6 is indicated by a bracket on the left side of the table, covering rows 00, 01, 11, and 10.

More complex example: illustrates (i) no reduction possible,
and (ii) resulting “cyclic core”

FOR EXACT SOLUTION: can use Petrick's Method (or more advanced techniques)
SEE QUINE-MCCLUSKEY HANDOUT


#36

Heuristic 2-Level Logic Minimization: the “Espresso” Method

Introduction to ESPRESSO: Examples

Example #1: Basic “Expand” Step

Function $f(x,y,z)$:

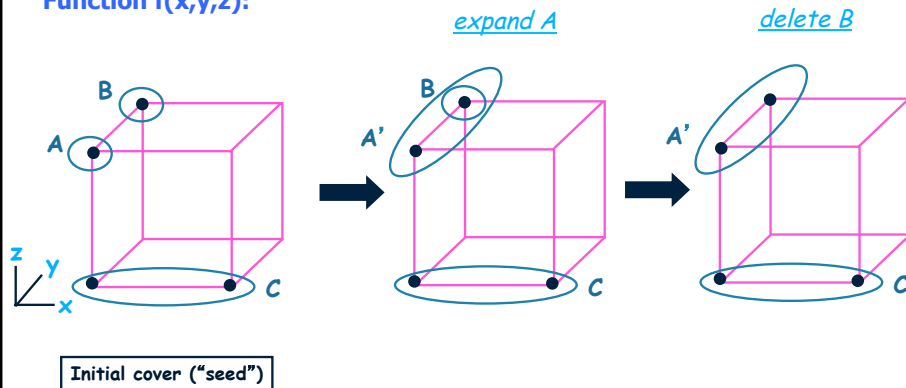


#38

Introduction to ESPRESSO: Examples

Example #2: Basic "Expand" + "Irredundant" Steps

Function $f(x,y,z)$:

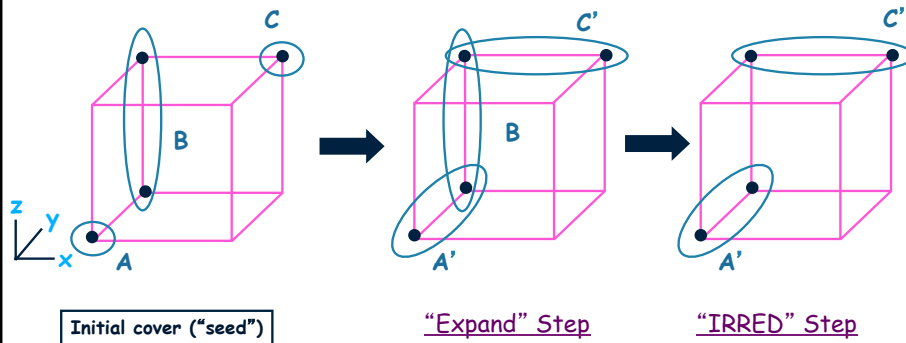


#39

Introduction to ESPRESSO: Examples

Example #3: "Expand"/"Irredundant"/"Reduce" Iteration


Function $f(x,y,z)$:

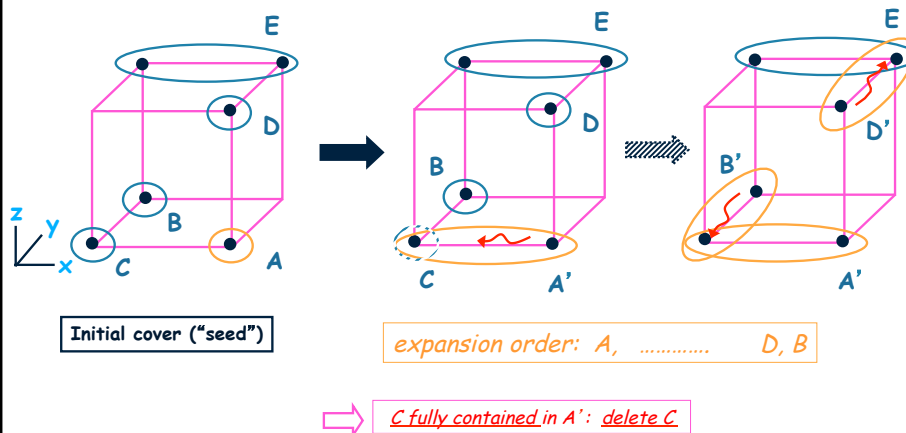

#40

Introduction to ESPRESSO: Examples

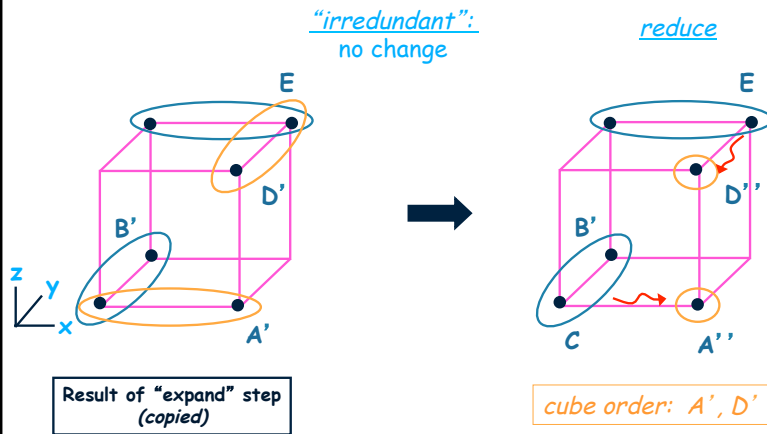
Example #3 (cont.): "Expand"/"Irredundant"/"Reduce" Iteration



#41

Introduction to ESPRESSO: Examples

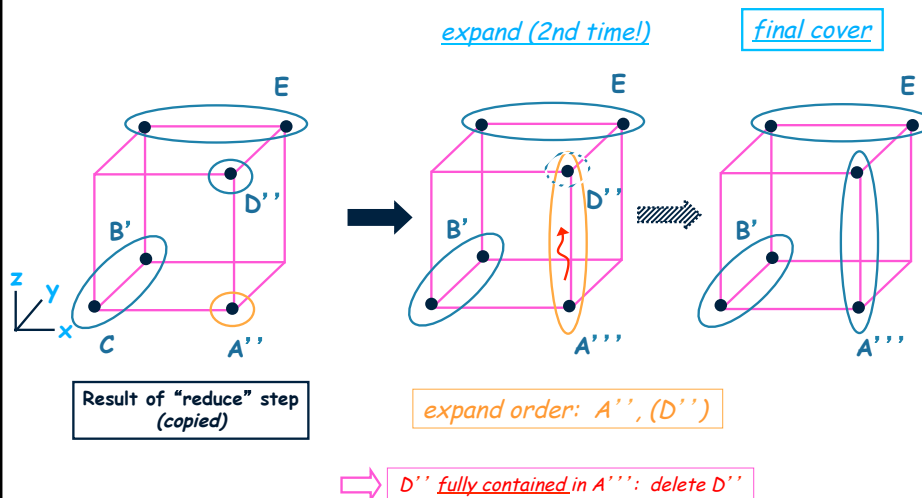Example #3 (cont.): "Expand"/"Irredundant"/"Reduce" Iteration



#42