


Combinational circuits

- Combinational circuits are stateless
- The outputs are functions only of the inputs




Enabler Circuit (High-level view)

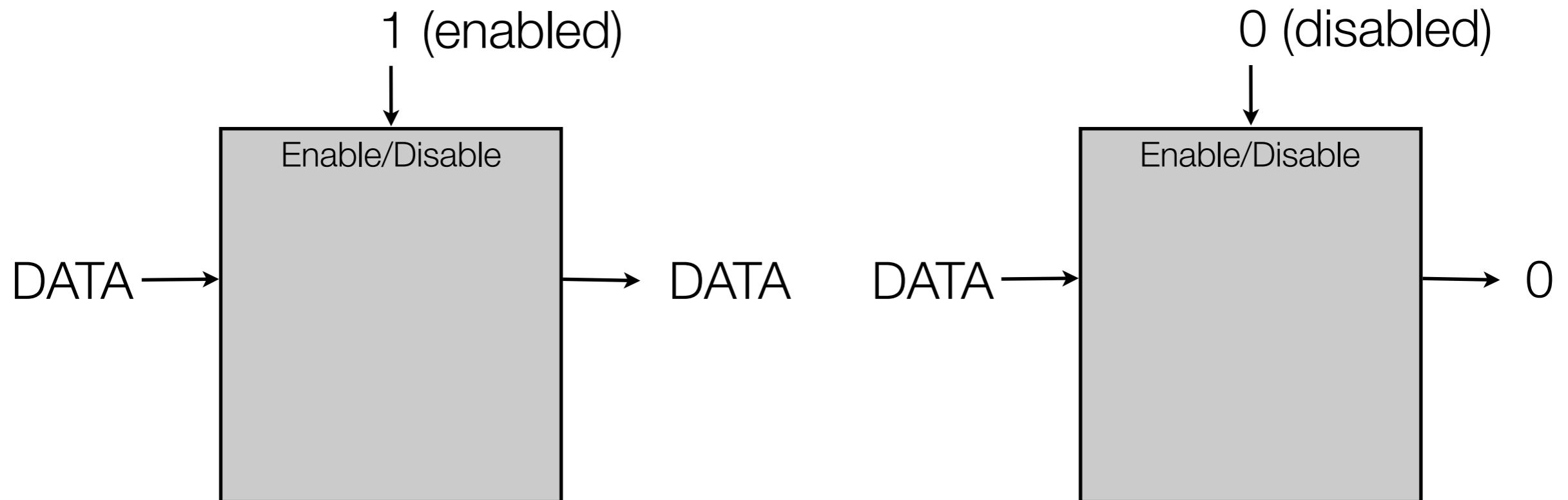- Enabler circuit has 2 inputs
 - data (can be several bits, but 1 bit examples for now)
 - enable/disable (i.e., on/off)
- Enable circuit “on”: output = data, Enable circuit “off”: output is “zeroed” (e.g., output signal is all 0’s)




MUX Circuit (High-level)

 - k Data values enter as input
- Selector chooses which one comes out



Decoder Circuit (high-level view)

 
- No DATA inputs
- 2^k 1-bit outputs
- Selector input chooses which output = 1, all other outputs = 0



Building “big” circuits: Hierarchical design

3-4


“Big” Circuit

 


(a)

Design small circuits to be used in a bigger circuit

Smaller Circuits

 


(b)

 

(c)

© 2008 Pearson Education, Inc.
M. Morris Mano & Charles R. Kime
LOGIC AND COMPUTER DESIGN FUNDAMENTALS, 4e

 Notation: Emulating a k-input gate via 2-input





- Each stage in the circuit cuts # of gates by half
- k input gate emulated with $\log_2 k$ depth 2-input gate circuits
- Same process works for OR, XOR as well

Enabler circuits: 1 bit Data input “A”

3-15

  Abbreviated truth table (input listed in the output)




EN	F
0	0
1	A

EN	F
0	1
1	A

For both enabler circuits above, output is “enabled” ($F=X$) only when input ‘ENABLE’ signal is asserted ($EN=1$). Note the different output when DISABLED

Decoder-based circuits

 Converts n -bit input to m -bit output, where $n \leq m \leq 2^n$




“Standard” Decoder: i^{th} output = 1, all others = 0,
where i is the binary representation of the input (ABC)

Decoder-based circuits

Converts n-bit input to m-bit output, where $n \leq m \leq 2^n$

e.g., $ABC = 101$ ($i=5$)

 


“Standard” Decoder: i^{th} output = 1, all others = 0,
where i is the binary representation of the input (ABC)

Decoder (1:2) Internal Design

3-17

A	D₀	D₁
0	1	0
1	0	1

(a)

 


(b)

Decoder (2:4)

3-18

A_1	A_0	D_0	D_1	D_2	D_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1


(a)

 

(b)

“Standard” Decoder: i^{th} output = 1, all others = 0,
where i is the binary representation of the input

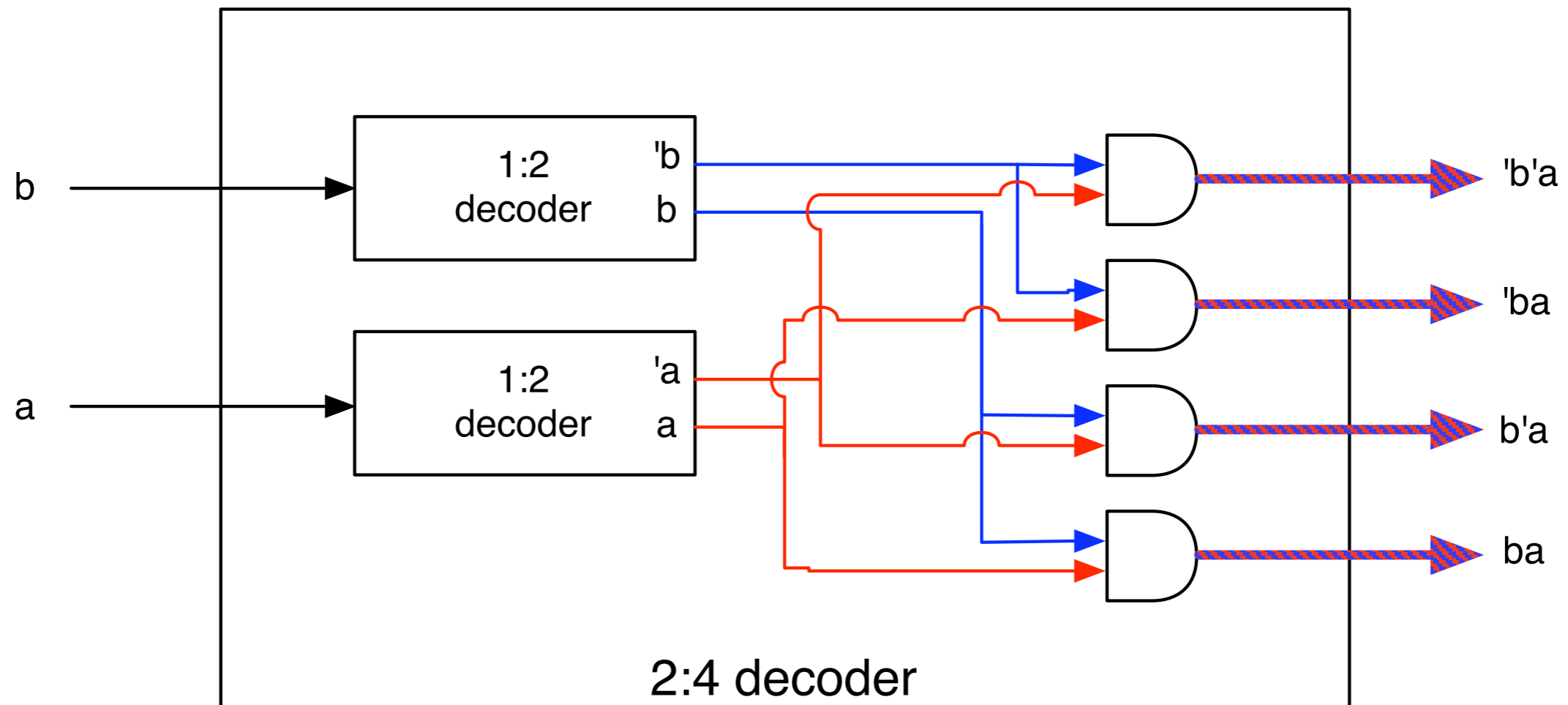Hierarchical design of decoder (2:4 decoder)




Can build 2:4 decoder out of two 1:2 decoders (and some additional circuitry)

Decoder (3:8)

Hierarchical design: use small decoders to build bigger decoder

3-19

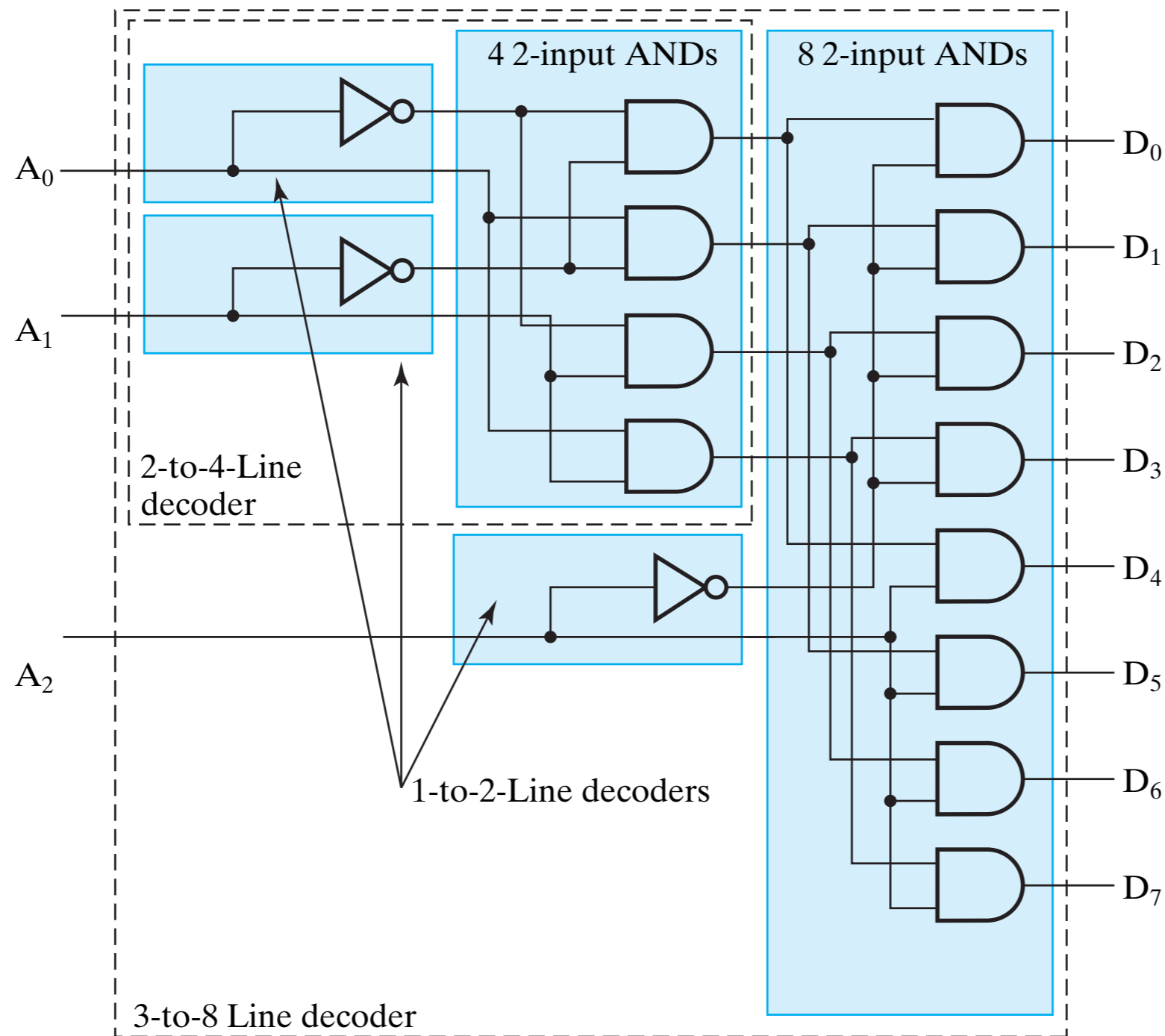

Note: A_2 "selects" whether the 2-to-4 line decoder is active in the top half ($A_2=0$) or the bottom ($A_2=1$)

Encoders

Inverse of a decoder: converts m-bit input to n-bit output, where $n \leq m \leq 2^n$

□ **TABLE 3-7**
Truth Table for Octal-to-Binary Encoder

Inputs								Outputs		
D_7	D_6	D_5	D_4	D_3	D_2	D_1	D_0	A_2	A_1	A_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

Decoders and encoders



BCD values			One-hot encoding								
0	0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0	0
0	1	1	0	0	0	0	1	0	0	0	0
1	0	0	0	0	0	1	0	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0	0



Note: for Encoders - input is assumed to be just one 1, the rest 0's

Priority Encoder

T 3-8


- Designed for any combination of inputs

□ **TABLE 3-8**
Truth Table of Priority Encoder

Inputs				Outputs		
D_3	D_2	D_1	D_0	A_1	A_0	V
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

General code conversion: a circuit that converts some inputs to outputs

3-3

 


(a) Segment designation



(b) Numeric designation for display

Code conversion

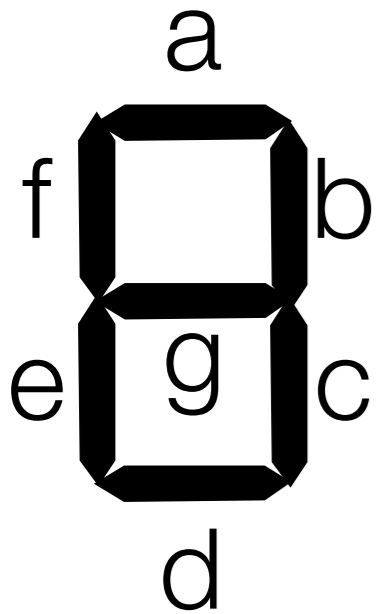


Input

Output

Va	W	X	Y	Z	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1
X	1	0	1	0	X	X	X	X	X	X	X
X	1	0	1	1	X	X	X	X	X	X	X
X	1	1	0	0	X	X	X	X	X	X	X
X	1	1	0	1	X	X	X	X	X	X	X
X	1	1	1	0	X	X	X	X	X	X	X
X	1	1	1	1	X	X	X	X	X	X	X


Code conversion

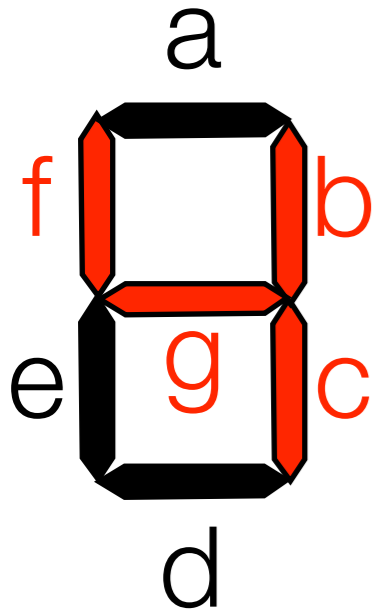


e.g., what outputs
“lights up” when input
 $V=4$?

Input					Output						
Va	W	X	Y	Z	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1
X	1	0	1	0	X	X	X	X	X	X	X
X	1	0	1	1	X	X	X	X	X	X	X
X	1	1	0	0	X	X	X	X	X	X	X
X	1	1	0	1	X	X	X	X	X	X	X
X	1	1	1	0	X	X	X	X	X	X	X
X	1	1	1	1	X	X	X	X	X	X	X

Code conversion

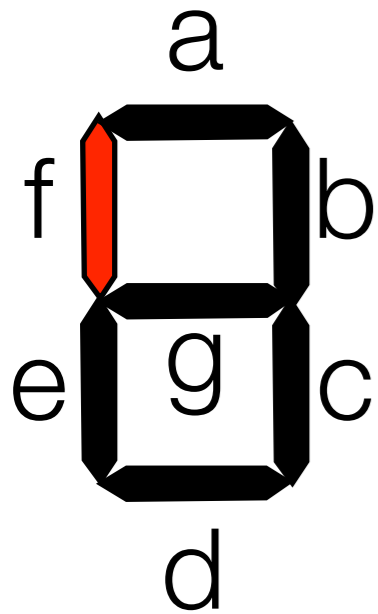


 For what values does output f "light up" for?




Input					Output						
Va	W	X	Y	Z	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1
X	1	0	1	0	X	X	X	X	X	X	X
X	1	0	1	1	X	X	X	X	X	X	X
X	1	1	0	0	X	X	X	X	X	X	X
X	1	1	0	1	X	X	X	X	X	X	X
X	1	1	1	0	X	X	X	X	X	X	X
X	1	1	1	1	X	X	X	X	X	X	X

Algebra and Circuit for "f"

 

 
$$f = W + \bar{Y}\bar{Z} + X\bar{Z} + \bar{X}\bar{Y} = W + (X + \bar{Y})\bar{Z} + \bar{X}\bar{Y}$$




Multiplexers

 - Combinational circuit that **selects** binary information from one of many input lines and directs it to one output line




n selection bits
indicate (in binary) which input feeds to the output

Multiplexer example

 


Multiplexers & Demultiplexers

 


2 ⁿ inputs									n-bit BCD value			1 output
a	x	x	x	x	x	x	x	x	0	0	0	a
x	b	x	x	x	x	x	x	x	0	0	1	b
x	x	c	x	x	x	x	x	x	0	1	0	c
x	x	x	d	x	x	x	x	x	0	1	1	d
x	x	x	x	e	x	x	x	x	1	0	0	e
x	x	x	x	x	f	x	x	x	1	0	1	f
x	x	x	x	x	x	x	g	x	1	1	0	g
x	x	x	x	x	x	x	x	h	1	1	1	h

 Muxes and demuxes called “steering logic”




“merge”

 

“fork”

Demultiplexers

 


1 input	n-bit BCD value			2^n outputs									
a	0	0	0	a	0	0	0	0	0	0	0	0	0
b	0	0	1	0	b	0	0	0	0	0	0	0	0
c	0	1	0	0	0	c	0	0	0	0	0	0	0
d	0	1	1	0	0	0	d	0	0	0	0	0	0
e	1	0	0	0	0	0	0	e	0	0	0	0	0
f	1	0	1	0	0	0	0	0	f	0	0	0	0
g	1	1	0	0	0	0	0	0	0	g	0	0	0
h	1	1	1	0	0	0	0	0	0	0	h	0	0

Internal mux organization


3-26

 Selector Logic (selects which input "flows through")



Only 1 AND gate passes "1" through

Enabler logic (takes inputs)

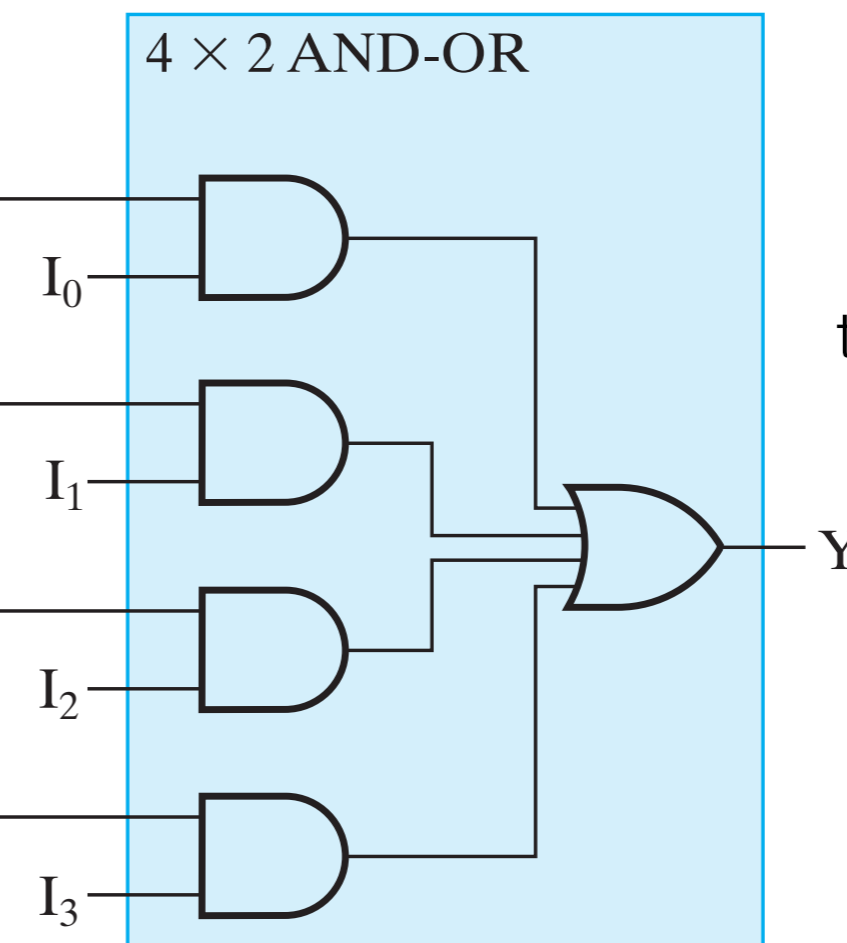



Or gate "passes through" the non-zeroed out I_i

AND gates "zero out" unselected I_i

Representing Functions with Decoders and MUXes

- e.g., $F = A\bar{C} + BC$


A	B	C	minterm	F
0	0	0	$\bar{A}\bar{B}\bar{C}$	0
0	0	1	$\bar{A}\bar{B}C$	0
0	1	0	$\bar{A}B\bar{C}$	0
0	1	1	$\bar{A}BC$	1
1	0	0	$A\bar{B}\bar{C}$	1
1	0	1	$A\bar{B}C$	0
1	1	0	$AB\bar{C}$	1
1	1	1	ABC	1

  

- Decoder: OR minterms for which F should evaluate to 1
- MUX: Feed in the value of F for each minterm

A Slick MUX trick

 - Can use a smaller MUX with a little trick e.g., $F = AC + B\bar{C}$
- Note for rows paired below, A&B have same values, C iterates between 0&1
- For the pair of rows, F either equals 0, 1, C or \bar{C}



Slick MUX trick: Example

- e.g., $F = \bar{A}C + \bar{B}\bar{C} + A\bar{C}$

