

Fundamentals of Computer Systems

Combinational Logic

Martha A. Kim

Columbia University

Fall 2014

Combinational Circuits

Combinational circuits are stateless.

Their output is a function *only* of the current input.



Basic Combinational Circuits

Enabler

Encoders and Decoders

Multiplexers

Shifters

Circuit Timing

Critical and Shortest Paths

Glitches

Arithmetic Circuits

Ripple Carry Adder

Adder/Subtractor

Carry Lookahead Adder


Enablers

Overview: Enabler

An enabler has two inputs:

- ▶ data: can be several bits, but 1 bit examples for now
- ▶ enable/disable: 1 bit on/off switch

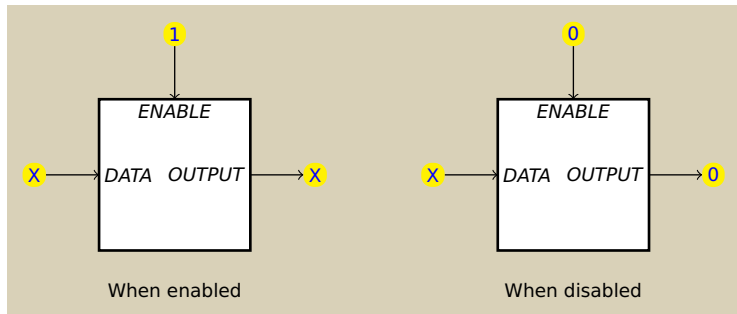When enabled, the circuit's output is its input data.
When disabled, the output is 0.





Enabler Implementation

Note abbreviated truth table: input, A, listed in output column

EN	F
0	0
1	A

EN	F
0	1
1	A

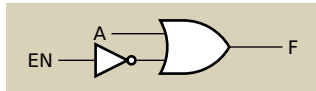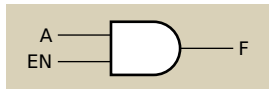


In both cases, output is enabled when $EN = 1$, but they handle the disabled ($EN = 0$) cases differently.

Encoders and Decoders

Overview: Decoder


A decoder takes a k – bit input and produces 2^k single-bit outputs.

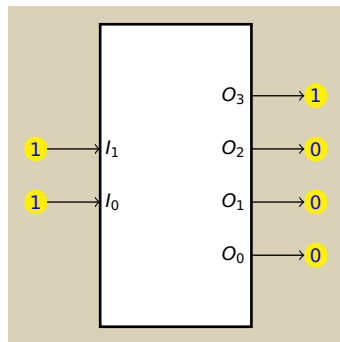The input determines which output will be 1, all others 0. This representation is called *one-hot encoding*.



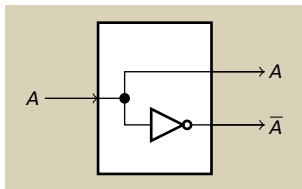
1:2 Decoder

The smallest decoder: one bit input, two bit outputs



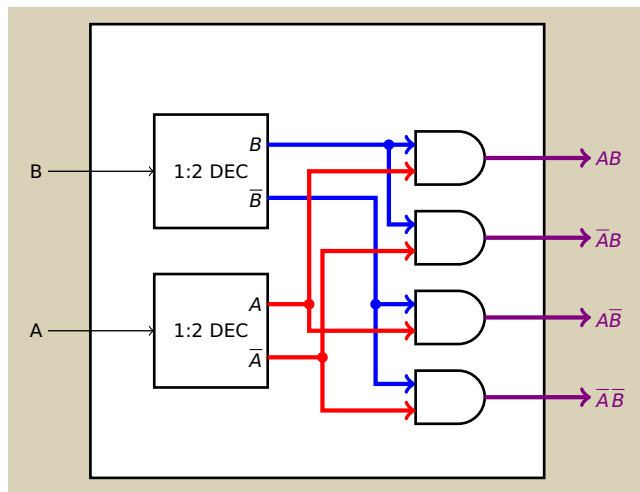
2:4 Decoder

Decoder outputs are simply minterms. Those values can be constructed as a flat schematic (manageable at small sizes) or hierarchically, as below.



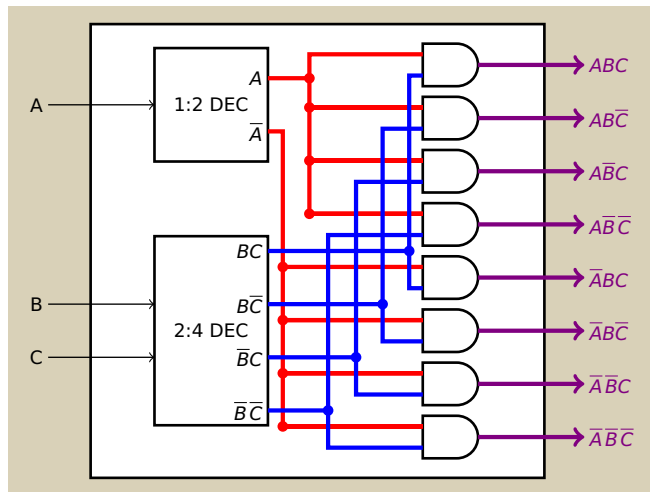3:8 Decoder


Applying *hierarchical design* again, the 2:4 DEC helps construct a 3:8 DEC.



Implementing a function with a decoder


E.g., $F = A\bar{C} + BC$

C	B	A	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

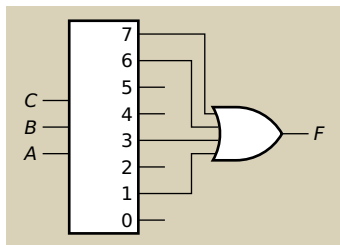


Warning: Easy, but not a minimal circuit.

Encoders and Decoders

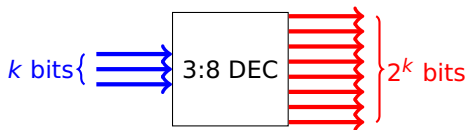

BCD			One-Hot								
0	0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0	0
0	1	1	0	0	0	0	1	0	0	0	0
1	0	0	0	0	0	1	0	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0	0

 

Priority Encoder

An encoder designed to accept any input bit pattern.

I_3	I_2	I_1	I_0	V	O_1	O_0
0	0	0	0	0	X	X
0	0	0	1	1	0	0
0	0	1	X	1	0	1
0	1	X	X	1	1	0
1	X	X	X	1	1	1

$$V = I_3 + I_2 + I_1 + I_0$$

$$O_1 = I_3 + \overline{I_3}I_2$$


$$O_0 = I_3 + \overline{I_3}\overline{I_2}I_1$$

Multiplexers

Overview: Multiplexer (or Mux)

A mux has a k – bit selector input and 2^k data inputs (multi or single bit).

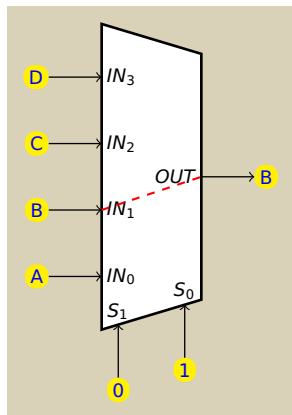It outputs a single data output, which has the value of one of the data inputs, according to the selector.



2:1 Mux Circuit

There are a handful of implementation strategies.

E.g., a truth table and k-map are feasible for a design of this size.


S	I_1	I_0	O
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

2:1 Mux Circuit

There are a handful of implementation strategies.

E.g., a truth table and k-map are feasible for a design of this size.

S	I_1	I_0	O
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

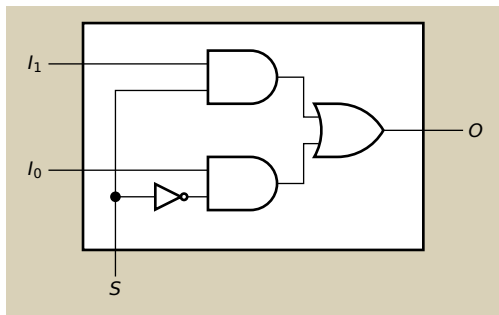


2:1 Mux Circuit


There are a handful of implementation strategies.

E.g., a truth table and k-map are feasible for a design of this size.


S	I_1	I_0	O
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

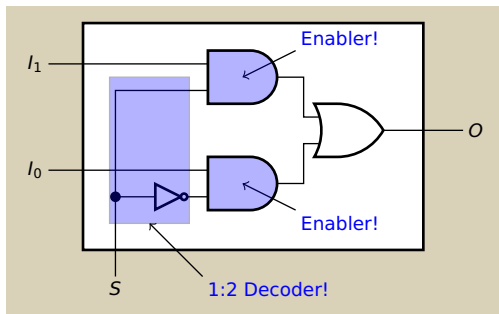


4:1 Mux Circuit

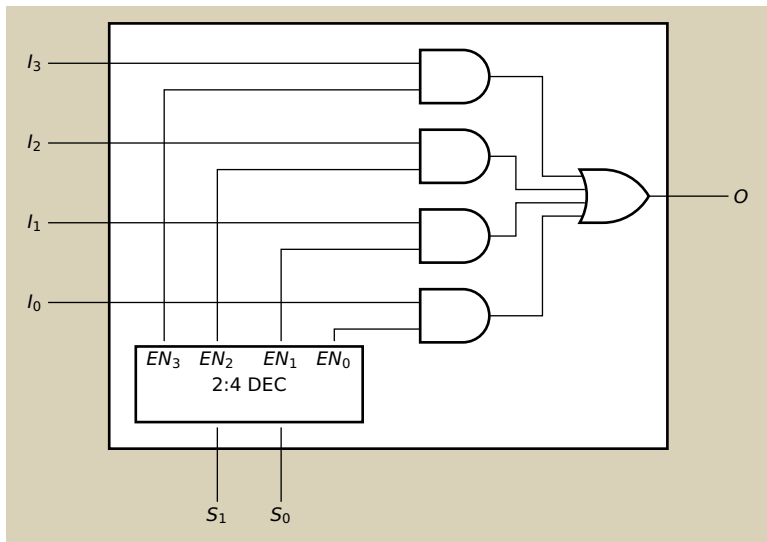

Muxing Wider Values (Overview)

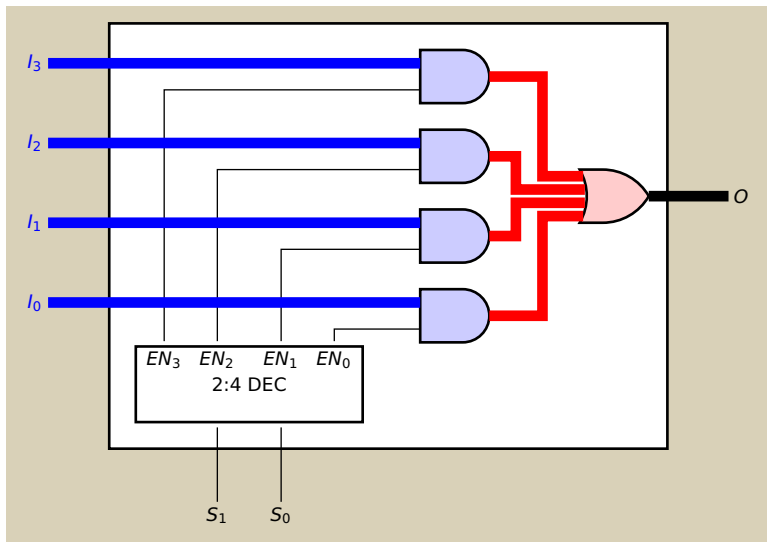

Muxing Wider Values (Components)

 


Using a Mux to Implement an Arbitrary Function Version 1

Think of a function as using k input bits to choose from 2^k outputs.

E.g., $F = BC + A\bar{C}$


A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

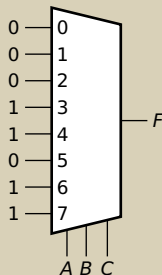

Using a Mux to Implement an Arbitrary Function Version 1

Think of a function as using k input bits to choose from 2^k outputs.

E.g., $F = BC + A\bar{C}$

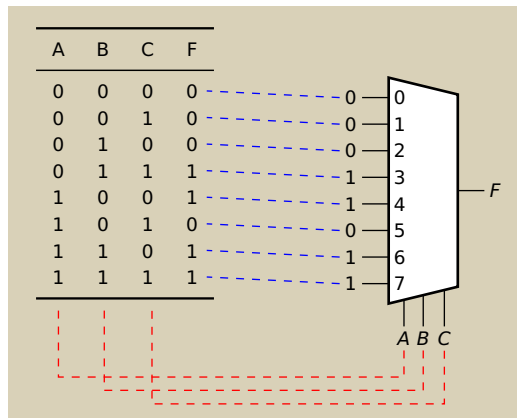

Using a Mux to Implement an Arbitrary Function Version 2

Can we use a smaller MUX?

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Using a Mux to Implement an Arbitrary Function Version 2

Can we use a smaller MUX?

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Using a Mux to Implement an Arbitrary Function Version 2

Can we use a smaller MUX?

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Using a Mux to Implement an Arbitrary Function Version 2


Can we use a smaller MUX?

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

A	B	F
0	0	0
0	1	C
1	0	\bar{C}
1	1	1

Using a Mux to Implement an Arbitrary Function Version 2

Can we use a smaller MUX?

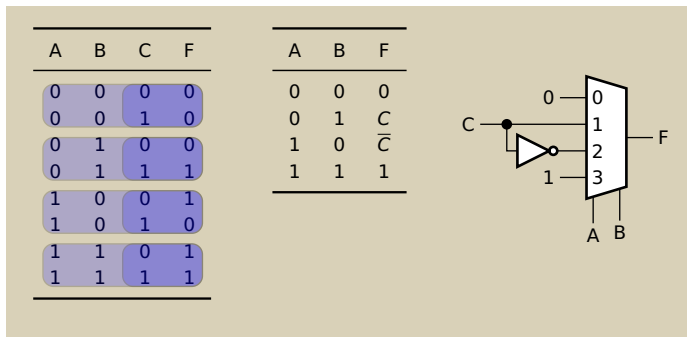


Instead of feeding just 0 or 1 into the mux, as in Version 1, one can remove a bit from the select, and feed it into the data ports along with the constant.

Shifters

Overview: Shifters

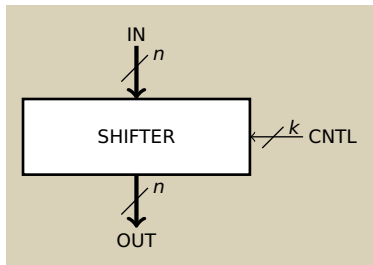A shifter shifts the inputs bits to the left or to the right.




There are various types of shifters.

- ▶ Barrel: Selector bits indicate (in binary) how far to the left to shift the input.
- ▶ L/R with enable: Two control bits (upper enables, lower indicates direction).


In either case, bits may “roll out” or “wraparound”

Example: Barrel Shifter with Wraparound

 


Implementation of Barrel Shifter with Wraparound (Part 2)

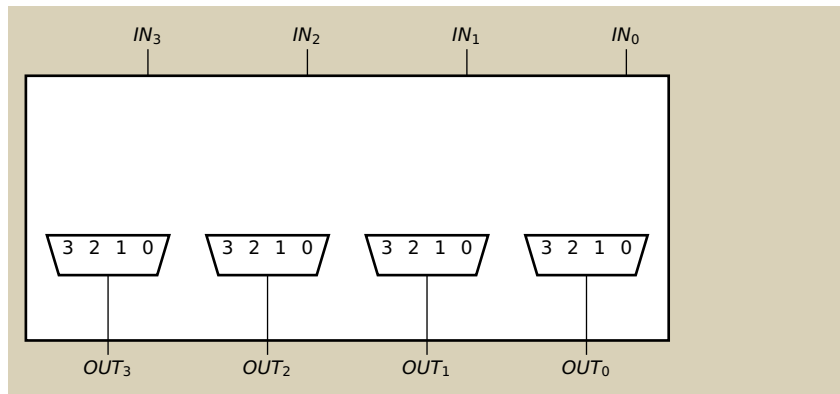Main idea: wire up all possible shift amounts and use muxes to select correct one.




Implementation of Barrel Shifter with Wraparound (Part 2)

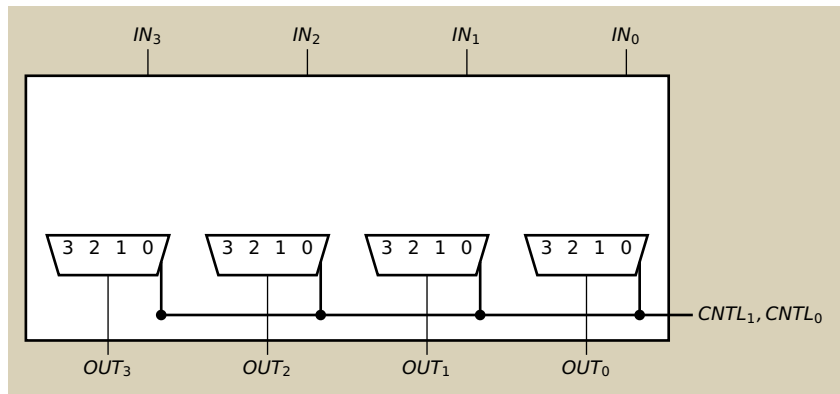Main idea: wire up all possible shift amounts and use muxes to select correct one.




Implementation of Barrel Shifter with Wraparound (Part 2)

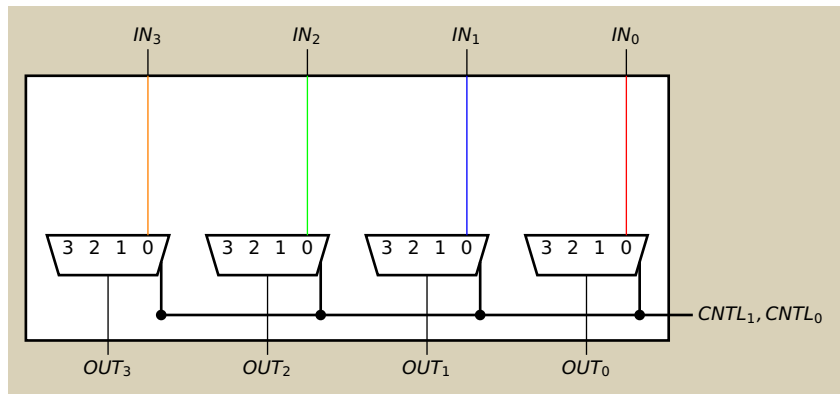Main idea: wire up all possible shift amounts and use muxes to select correct one.




Implementation of Barrel Shifter with Wraparound (Part 2)

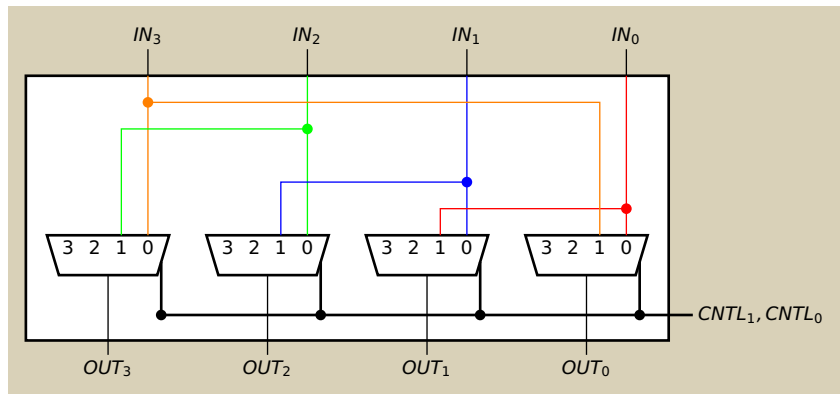Main idea: wire up all possible shift amounts and use muxes to select correct one.




Implementation of Barrel Shifter with Wraparound (Part 2)

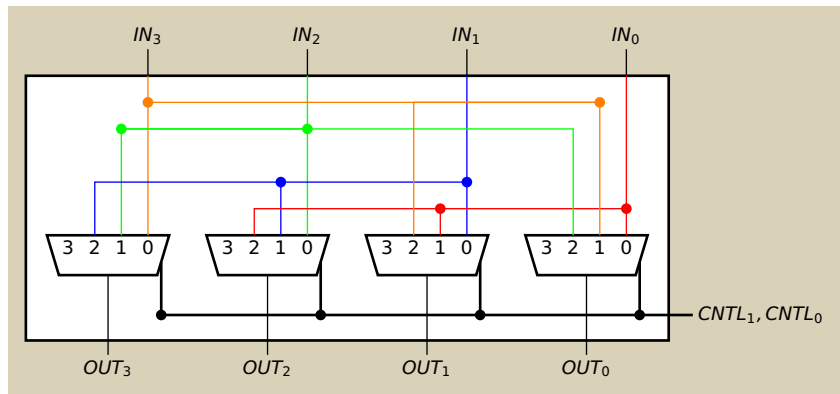Main idea: wire up all possible shift amounts and use muxes to select correct one.




Implementation of Barrel Shifter with Wraparound (Part 2)

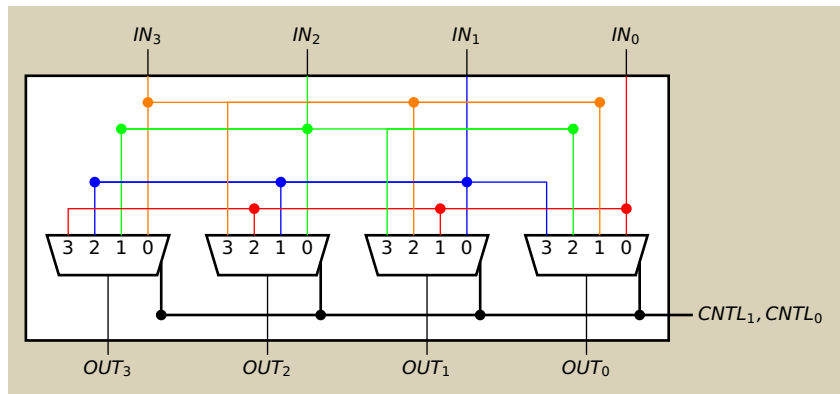Main idea: wire up all possible shift amounts and use muxes to select correct one.




Circuit Timing

Computation Always Takes Time

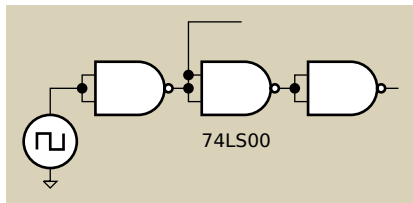


There is a delay between inputs and outputs, due to:

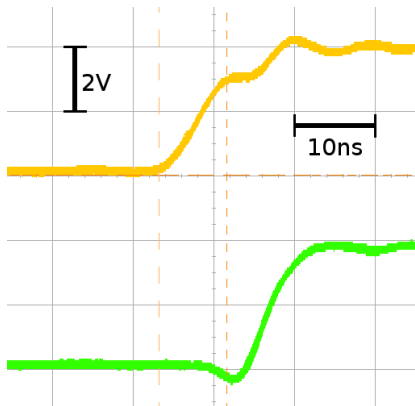- Limited currents charging capacitance
- The speed of light




The Simplest Timing Model

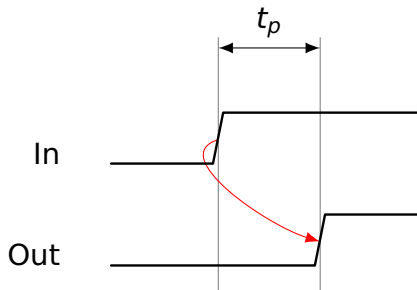

- ▶ Each gate has its own propagation delay t_p .
- ▶ When an input changes, any changing outputs do so after t_p .
- ▶ Wire delay is zero.


A More Realistic Timing Model

 

It is difficult to manufacture two gates with the same delay; better to treat delay as a range.


- ▶ Each gate has a minimum and maximum propagation delay $t_{p(\min)}$ and $t_{p(\max)}$.
- ▶ Outputs may start changing after $t_{p(\min)}$ and stabilize no later than $t_{p(\max)}$.

Critical Paths and Short Paths

 

How slow can this be?

Critical Paths and Short Paths

 


How slow can this be?

The **critical path** has the longest possible delay.

$$t_{p(\max)} = t_{p(\max, \text{AND})} + t_{p(\max, \text{OR})} + t_{p(\max, \text{AND})}$$

Critical Paths and Short Paths

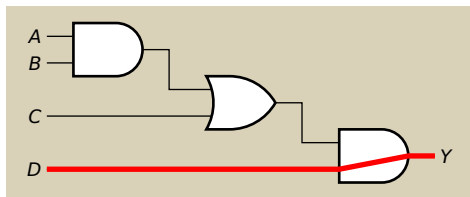


How fast can this be?

The **shortest path** has the least possible delay.

$$t_{p(\min)} = t_{p(\min, \text{AND})}$$

Glitches

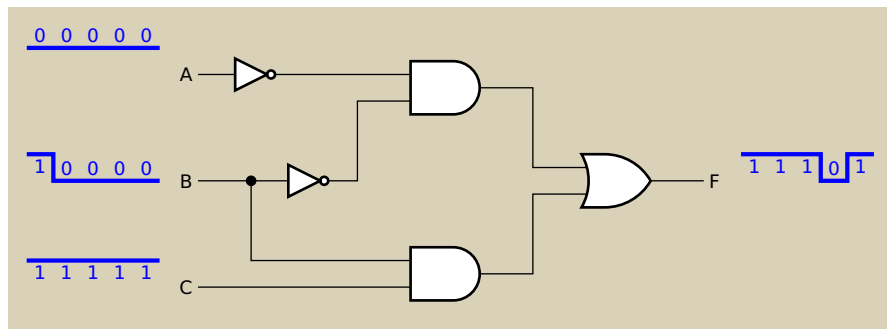
A glitch is when a single change in input values can cause multiple output changes.



Glitches *may* occur when there are multiple paths of different length from input I to output O .

Glitches

 
A glitch is when a single change in input values can cause multiple output changes.



Glitches *may* occur when there are multiple paths of different length from input *I* to output *O*.

Glitches

 
A glitch is when a single change in input values can cause multiple output changes.



Glitches *may* occur when there are multiple paths of different length from input *I* to output *O*.

Glitches

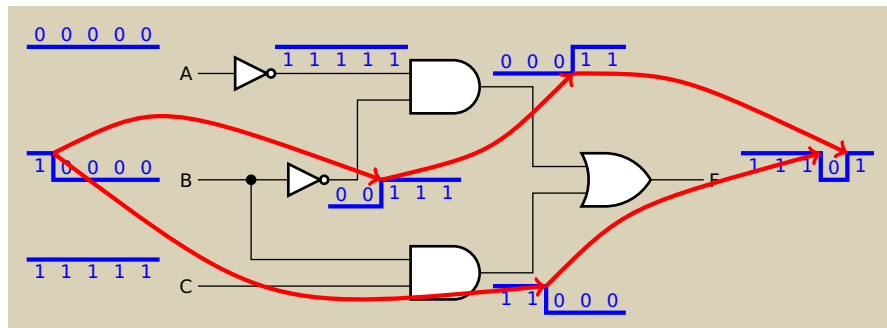A glitch is when a single change in input values can cause multiple output changes.




Glitches *may* occur when there are multiple paths of different length from input I to output O .

Preventing Single Input Glitches

Additional terms can prevent single input glitches (at a cost of a few extra gates).


	<i>B</i>			
	┌───┴───┐			
	1	0	0	0
<i>C</i>	1	1	1	0
	└───┬───┘			
	<i>A</i>			

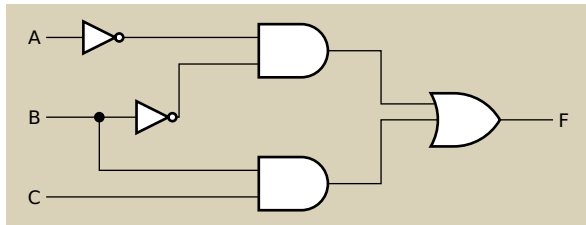

Preventing Single Input Glitches

Additional terms can prevent single input glitches (at a cost of a few extra gates).

	<i>B</i>				
	┌───┴───┐				
	1	0	0	0	
C	1	1	1	0	
	└───┬───┘				
	<i>A</i>				

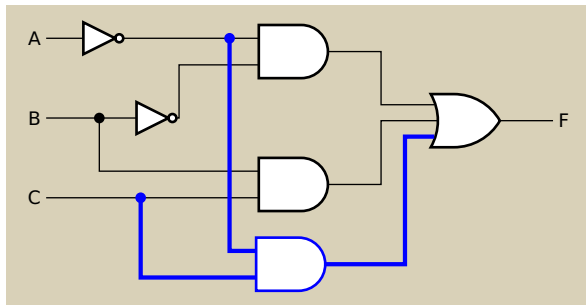


Arithmetic Circuits

Arithmetic: Addition

Adding two one-bit numbers: A and B

Produces a two-bit result: C and S (carry and sum)

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


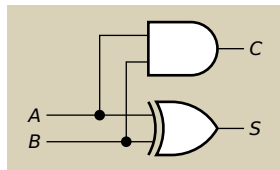


Half Adder



Full Adder

In general, due to a possible carry in, you need to add *three bits*:

$C_i A B$	$C_o S$
0 0 0	0 0
0 0 1	0 1
0 1 0	0 1
0 1 1	1 0
1 0 0	0 1
1 0 1	1 0
1 1 0	1 0
1 1 1	1 1

  


A Four-Bit Ripple-Carry Adder

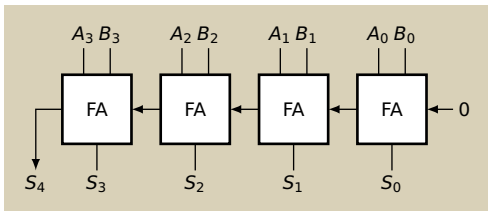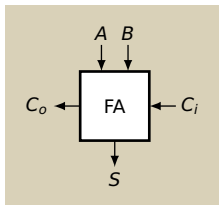

A Two's Complement Adder/Subtractor

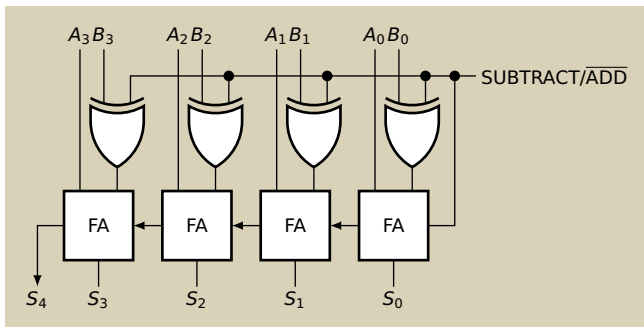To subtract B from A , add A and $-B$.
Neat trick: carry in takes care of the $+1$ operation.



Overflow in Two's-Complement Representation

When is the result too positive or too negative?


+	-2	-1	0	1
-2	$\begin{array}{r} 10 \\ 10 \\ +10 \\ \hline 00 \end{array}$			
-1	$\begin{array}{r} 10 \\ 10 \\ +11 \\ \hline 01 \end{array}$	$\begin{array}{r} 11 \\ 11 \\ +11 \\ \hline 10 \end{array}$		
0	$\begin{array}{r} 00 \\ 10 \\ +00 \\ \hline 10 \end{array}$	$\begin{array}{r} 00 \\ 11 \\ +00 \\ \hline 11 \end{array}$	$\begin{array}{r} 00 \\ 00 \\ +00 \\ \hline 00 \end{array}$	
1	$\begin{array}{r} 00 \\ 10 \\ +01 \\ \hline 11 \end{array}$	$\begin{array}{r} 11 \\ 11 \\ +01 \\ \hline 00 \end{array}$	$\begin{array}{r} 00 \\ 00 \\ +01 \\ \hline 01 \end{array}$	$\begin{array}{r} 01 \\ 01 \\ +01 \\ \hline 10 \end{array}$

Overflow in Two's-Complement Representation


When is the result too positive or too negative?

	+	-2	-1	0	1
-2		$\begin{array}{r} 10 \\ 10 \\ +10 \\ \hline 00 \end{array} \text{X}$			
-1		$\begin{array}{r} 10 \\ 10 \\ +11 \\ \hline 01 \end{array} \text{X}$	$\begin{array}{r} 11 \\ 11 \\ +11 \\ \hline 10 \end{array}$		
0		$\begin{array}{r} 00 \\ 10 \\ +00 \\ \hline 10 \end{array}$	$\begin{array}{r} 00 \\ 11 \\ +00 \\ \hline 11 \end{array}$	$\begin{array}{r} 00 \\ 00 \\ +00 \\ \hline 00 \end{array}$	
1		$\begin{array}{r} 00 \\ 10 \\ +01 \\ \hline 11 \end{array}$	$\begin{array}{r} 11 \\ 11 \\ +01 \\ \hline 00 \end{array}$	$\begin{array}{r} 00 \\ 00 \\ +01 \\ \hline 01 \end{array}$	$\begin{array}{r} 01 \\ 01 \\ +01 \\ \hline 10 \end{array} \text{X}$

 The result does not fit when the top two carry bits differ.



Ripple-Carry Adders are Slow

 


The *depth* of a circuit is the number of gates on a critical path.

This four-bit adder has a depth of 8.

n -bit ripple-carry adders have a depth of $2n$.

Carry Generate and Propagate

 The carry chain is the slow part of an adder; carry-lookahead adders reduce its depth using the following trick:



For bit i ,

$$\begin{aligned}C_{i+1} &= A_i B_i + A_i C_i + B_i C_i \\ &= A_i B_i + C_i (A_i + B_i) \\ &= G_i + C_i P_i\end{aligned}$$

K-map for the carry-out function of a full adder

Generate $G_i = A_i B_i$ sets carry-out regardless of carry-in.

Propagate $P_i = A_i + B_i$ copies carry-in to carry-out.

Carry Lookahead Adder

Expand the carry functions into sum-of-products form:

$$C_{i+1} = G_i + C_i P_i$$

$$C_1 = G_0 + C_0 P_0$$

$$C_2 = G_1 + C_1 P_1$$

$$= G_1 + (G_0 + C_0 P_0) P_1$$

$$= G_1 + G_0 P_1 + C_0 P_0 P_1$$

$$C_3 = G_2 + C_2 P_2$$

$$= G_2 + (G_1 + G_0 P_1 + C_0 P_0 P_1) P_2$$


$$= G_2 + G_1 P_2 + G_0 P_1 P_2 + C_0 P_0 P_1 P_2$$

$$C_4 = G_3 + C_3 P_3$$

$$= G_3 + (G_2 + G_1 P_2 + G_0 P_1 P_2 + C_0 P_0 P_1 P_2) P_3$$

$$= G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3 + C_0 P_0 P_1 P_2 P_3$$

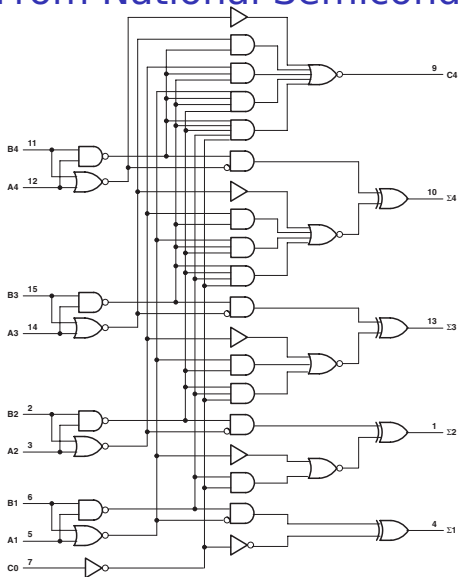The 74283 Binary Carry-Lookahead Adder (From National Semiconductor)



Carry out i has $i + 1$ product terms, largest of which has $i + 1$ literals.

If wide gates don't slow down, delay is independent of number of bits.

More realistic: if limited to two-input gates, depth is $O(\log_2 n)$.