

CSEE W3827
Fundamentals of Computer Systems
Homework Assignment 2

Prof. Martha A. Kim
Columbia University

Due September 25, 2014 at 10:10 AM

Write your name **and UNI** on your solutions

Show your work for each problem; we are more interested in how you get the answer than whether you get the right answer.




1. (15 points) Show how to build a half adder using only two 4:1 muxes.

2. (15 points) Show how to build a full adder using only two 3:8 decoders and two OR4 gates (OR4 = 4 input OR).

3. (15 points) Show how to build a full adder using two 4:1 muxes and an inverter.

4. (10 points) Show how to build a 4-bit “multiplier by negative one”. This multiplier takes a 4-bit input A (A_3, A_2, A_1, A_0) and produces a 5-bit output N (N_4, N_3, N_2, N_1, N_0) that has the negative of the two's complement value of A .

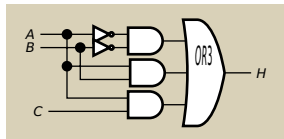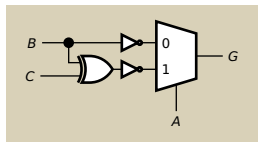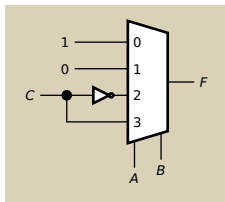5. (45 points) For this problem, you will analyze the three functions, F, G, and H, implemented below.



- (a) (10 points) Do the three schematics above compute the same or different functions? (In other words, is $F == G$? $G == H$?) Provide support for your answer.

(b) (10 points) Given the component area and critical paths in the table below, complete the table for F, G, and H.

	Area	Critical Path
4:1 MUX	10	4
2:1 MUX	5	2
XOR2	4	3
OR3	3	1
AND3	3	1
OR2	2	1
AND2	2	1
INV	1	0.5
F		
G		
H		

(c) (10 points) Give a function J that computes the same function as F , but has a shorter critical path than F . Provide J 's schematic, area, and critical path.

(d) (15 points) Does H have a glitch? If yes, provide the input transition that triggers it. If no, argue why not.