

CSEE W3827
Fundamentals of Computer Systems
Homework Assignment 3

Prof. Martha A. Kim
Columbia University

Due October 7, 2014 at 10:10 AM


Write your name **and UNI** on your solutions

Show your work for each problem; we are more interested in how you get the answer than whether you get the right answer.

1. (10 points) With a schematic, show how a positive edge triggered D flip-flop can be augmented to implement a positive edge triggered T (“toggle”) flip-flop.

A T flip-flop has one input, T, and when $T=1$, the contents of the flip-flop will toggle from 0 to 1 or 1 to 0. When $T=0$ there is no change in the flip-flop state.

 2. (35 points) Examine the state transition diagram below for a simple network send interface FSM. Upon receipt of the *SEND* input, the interface will attempt to send data for two cycles or until it receives back an *ACK*, whichever comes first. After each successful or attempted send it returns to an idle state where it awaits the next *SEND*. If a *SEND* arrives while the interface is already sending, the machine enters an error state from which the only exit is *RST*.





- (a) (15 points) Using the state encoding given below, give expressions for this machine's output logic (*READY* and *ERROR*) and next state logic (*D1*, *D0*).

State	<i>Q1</i>	<i>Q0</i>
<i>IDLE</i>	0	0
<i>SEND1</i>	0	1
<i>SEND2</i>	1	0
<i>ERROR</i>	1	1


- (b) (15 points) Using the state encoding given below, give expressions for this machine's output logic (*READY* and *ERROR*) and next state logic (D_{IDLE} , D_{SEND1} , D_{SEND2} , D_{ERROR}).

State	Q_{IDLE}	Q_{SEND1}	Q_{SEND2}	Q_{ERROR}
<i>IDLE</i>	1	0	0	0
<i>SEND1</i>	0	1	0	0
<i>SEND2</i>	0	0	1	0
<i>ERROR</i>	0	0	0	1

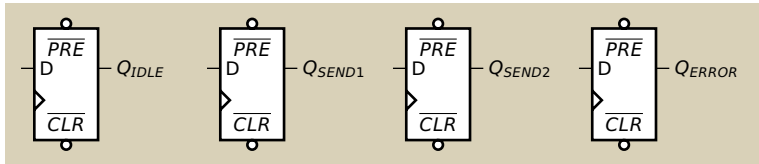 (c) (5 points) On the diagrams below, show how to wire up the \overline{RST} signal for each of the two machines above.



 
3. (35 points) Examine the sequential circuit below.



(a) (5 points) Is this a Mealy or a Moore machine?

- (b) (20 points) Draw the state transition diagram for this machine.
- (c) (10 points) Describe, in English, what this machine is doing.

 4. (20 points) If the the up/down counter shown below is constructed using D flip-flops with a 2ns setup time, 2 ns hold time, a minimum propagation delay of 1ns, and a maximum propagation delay of 3ns, answer the following questions about the 32-bit adder used in the design.



- (a) What is the smallest safe propagation delay through the adder?
- (b) Assuming a 10ns clock period, what is the longest safe propagation delay through the adder?