

Fundamentals of Computer Systems


Finite State Machines

Martha A. Kim


Columbia University

Fall 2015

Finite State Machine Components

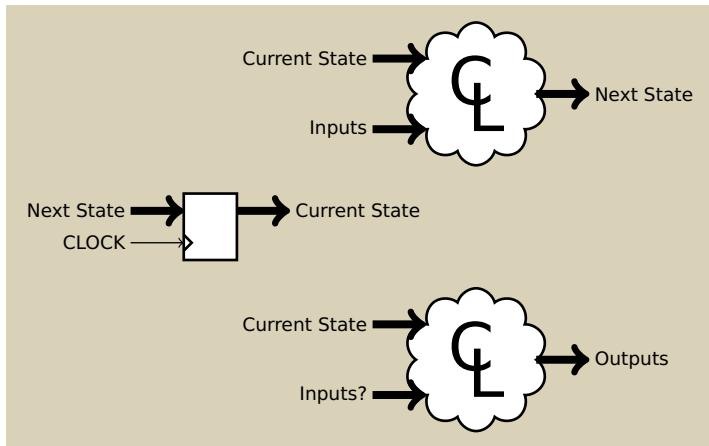


Moore and Mealy Machines

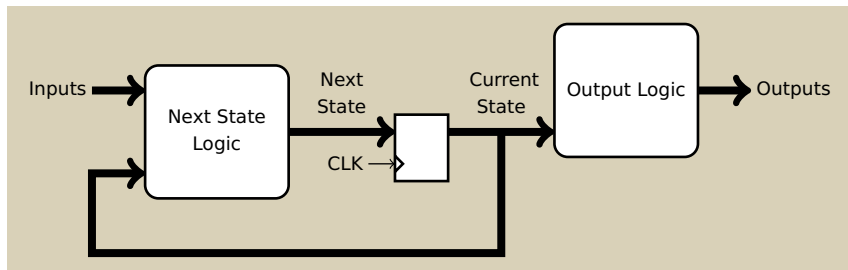

The Moore Form:

Outputs are a function of *only* the current state.

Moore and Mealy Machines

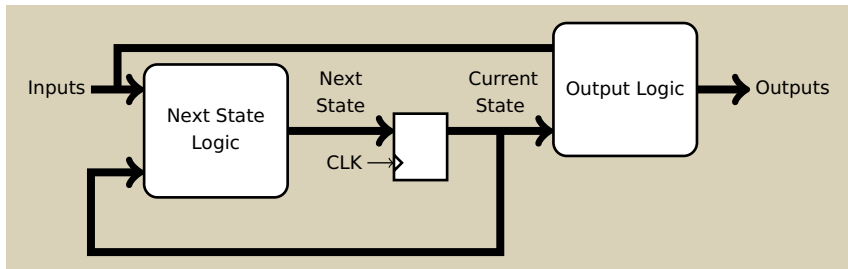


The Mealy Form:

Outputs may be a function of *both* the current state and the inputs.

A mnemonic: *Moore* machines often have *more* states.


Mealy Machines are the Most General

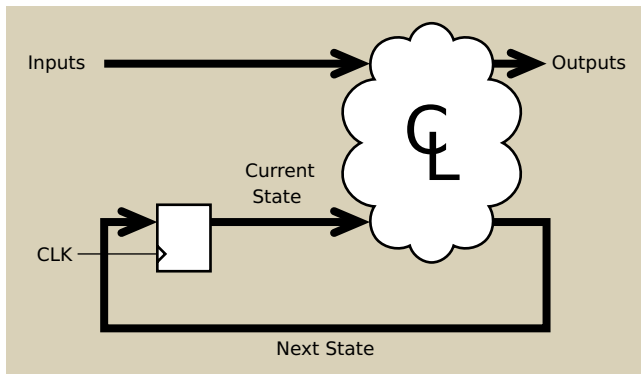

Another, equivalent way of drawing Mealy Machines


This is exactly the synchronous digital logic paradigm

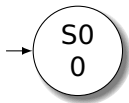State Transition Diagrams: Looking for “1101”




Moore Machine: States indicate output

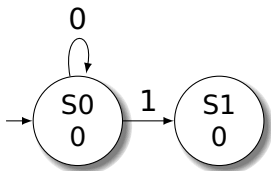State Transition Diagrams: Looking for “1101”




Moore Machine: States indicate output

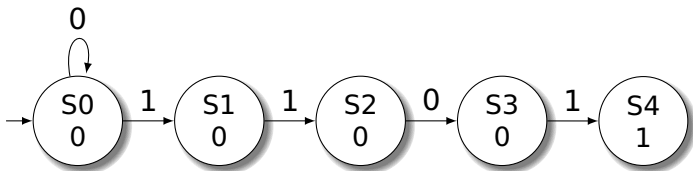State Transition Diagrams: Looking for "1101"




Moore Machine: States indicate output

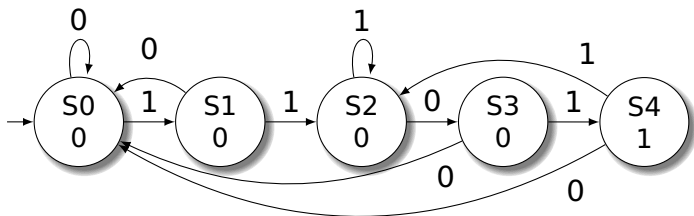State Transition Diagrams: Looking for "1101"




Moore Machine: States indicate output

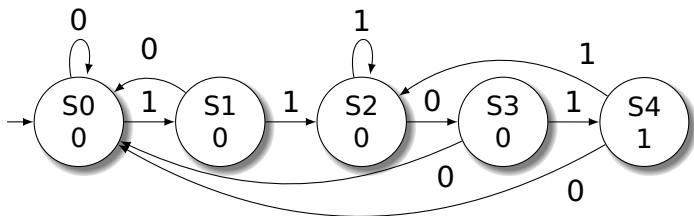State Transition Diagrams: Looking for “1101”




Moore Machine: States indicate output

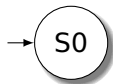


Mealy Machine: Arcs indicate input/output

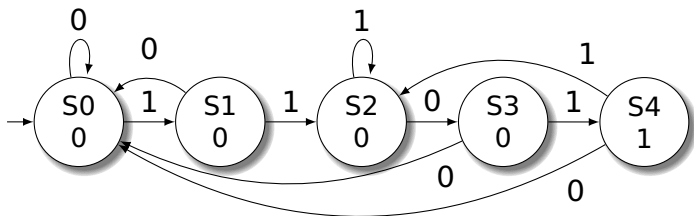State Transition Diagrams: Looking for “1101”




Moore Machine: States indicate output

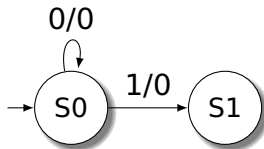


Mealy Machine: Arcs indicate input/output

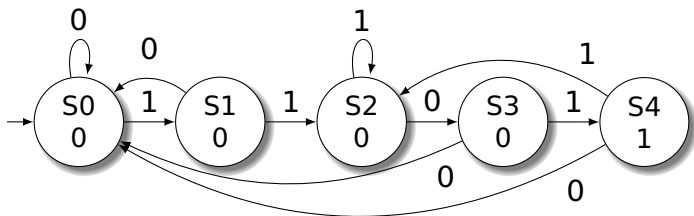State Transition Diagrams: Looking for "1101"




Moore Machine: States indicate output

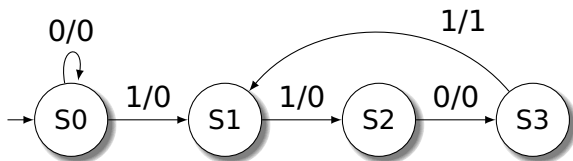


Mealy Machine: Arcs indicate input/output

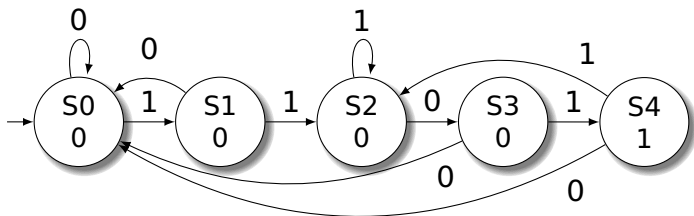State Transition Diagrams: Looking for "1101"



Moore Machine: States indicate output

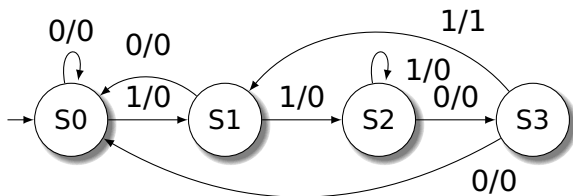


Mealy Machine: Arcs indicate input/output

Moore Machine

Next State			Output	
S	A	S'	S	Y
S0	0	S0	S0	0
S0	1	S1	S1	0
S1	0	S0	S2	0
S1	1	S2	S3	0
S2	0	S3	S4	1
S2	1	S2		
S3	0	S0		
S3	1	S4		
S4	0	S0		
S4	1	S2		

Moore Machine

Next State			Output	
S	A	S'	S	Y
000	0	000	000	0
000	1	001	001	0
001	0	000	010	0
001	1	010	011	0
010	0	011	100	1
010	1	010		
011	0	000		
011	1	100		
100	0	000		
100	1	010		

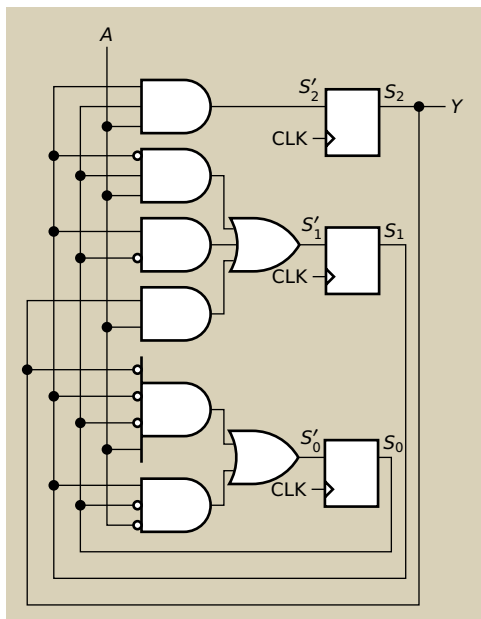


Mealy Machine


S	A	S'	Y
S0	0	S0	0
S0	1	S1	0
S1	0	S0	0
S1	1	S2	0
S2	0	S3	0
S2	1	S2	0
S3	0	S0	0
S3	1	S1	1

Mealy Machine


S	A	S'	Y
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	11	0
10	1	10	0
11	0	00	0
11	1	01	1

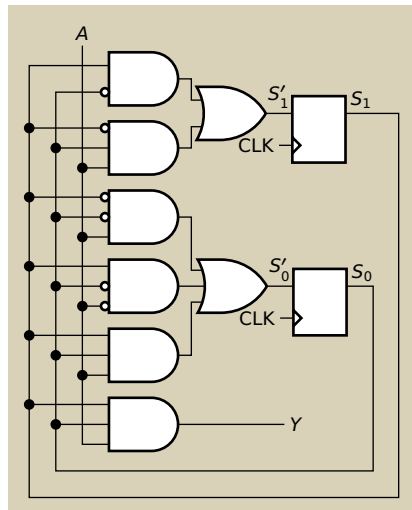

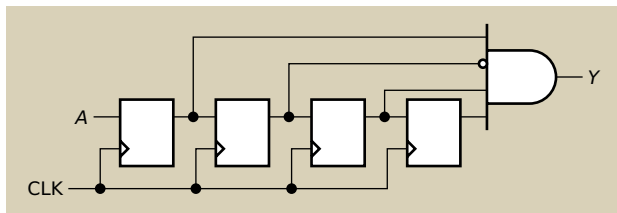More Intuitive Solutions using Shift Registers




Moore Form: Output Depends Only on State

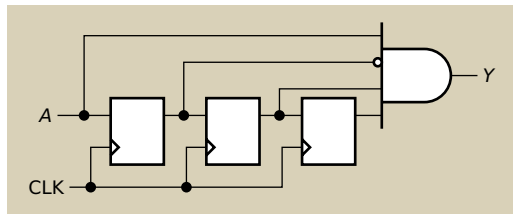

Mealy Form: Output Depends on Input Immediately


FSM Example: A Traffic Light Controller

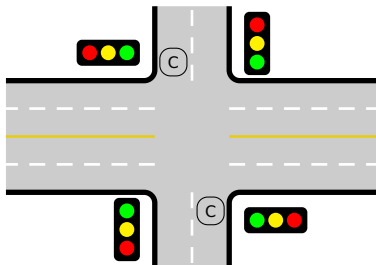

This controls a traffic light at the intersection of a busy highway and a farm road. Normally, the highway light is green but if a sensor detects a car on the farm road, the highway light turns yellow then red. The farm road light then turns green until there are no cars or after a long timeout. Then, the farm road light turns yellow then red, and the highway light returns to green and cannot be interrupted by a car before a long timer has elapsed.

Source: Mead and Conway, *Introduction to VLSI Systems*, 1980, p. 85.


FSM Example: A Traffic Light Controller

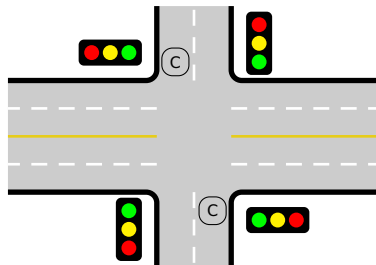

The inputs to the machine are the car sensor, a short timeout signal, and a long timeout signal. The outputs are a timer start signal and the colors of the highway and farm road lights.

Source: Mead and Conway, *Introduction to VLSI Systems*, 1980, p. 85.

State Transition Diagram for the TLC

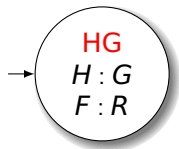

Inputs

C = Car sensor

S = Short Timeout

L = Long Timeout


Outputs

T = Timer Reset

H = Highway color

F = Farm road color

State Transition Diagram for the TLC

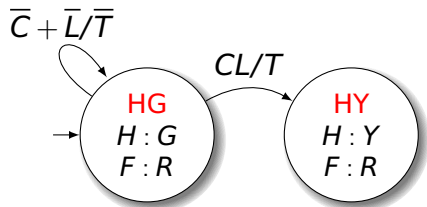

Inputs

C = Car sensor

S = Short Timeout

L = Long Timeout


Outputs

T = Timer Reset

H = Highway color

F = Farm road color

State Transition Diagram for the TLC

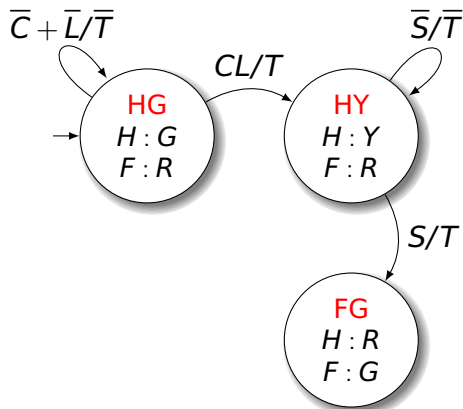

Inputs

C = Car sensor

S = Short Timeout

L = Long Timeout


Outputs

T = Timer Reset

H = Highway color

F = Farm road color

State Transition Diagram for the TLC

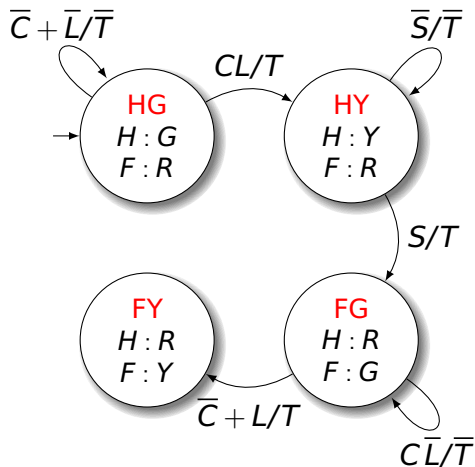

Inputs

C = Car sensor

S = Short Timeout

L = Long Timeout


Outputs

T = Timer Reset

H = Highway color

F = Farm road color

State Transition Diagram for the TLC

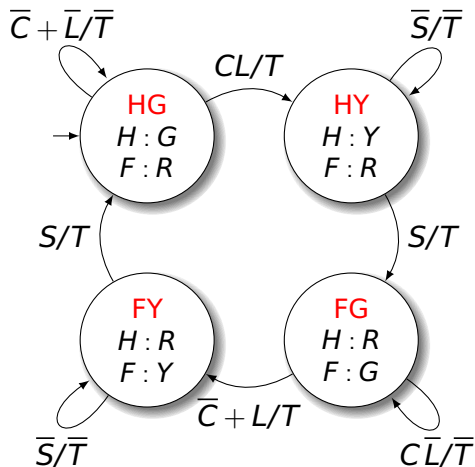

Inputs

C = Car sensor

S = Short Timeout

L = Long Timeout


Outputs

T = Timer Reset

H = Highway color

F = Farm road color

State Transition Diagram for the TLC

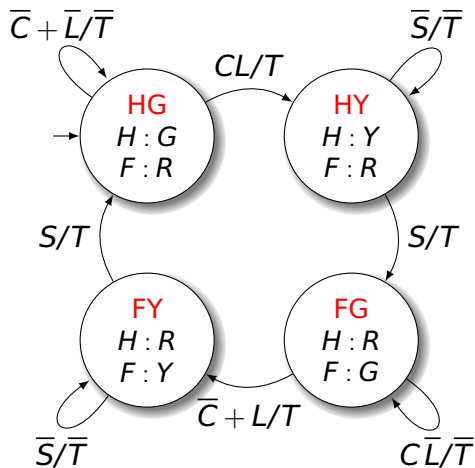

Q	C	S	L	T	D
HG	0	X	X	0	HG
HG	X	X	0	0	HG
HG	1	X	1	1	HY
HY	X	0	X	0	HY
HY	X	1	X	1	FG
FG	1	X	0	0	FG
FG	0	X	X	1	FY
FG	X	X	1	1	FY
FY	X	0	X	0	FY
FY	X	1	X	1	HG

Q	H	F
HG	G	R
HY	Y	R
FG	R	G
FY	R	Y

State and Output Encoding 1: Binary

States	
HG	00
HY	01
FG	10
FY	11

Outputs	
G	00
Y	01
R	10

State and Output Encoding 1: Binary

Q	C	S	L	T	D
00	0	X	X	0	00
00	X	X	0	0	00
00	1	X	1	1	01
01	X	0	X	0	01
01	X	1	X	1	10
10	1	X	0	0	10
10	0	X	X	1	11
10	X	X	1	1	11
11	X	0	X	0	11
11	X	1	X	1	00

Q	H	F
00	00	10
01	01	10
10	10	00
11	10	01

$$T = \overline{Q_1} \overline{Q_0} C L + \overline{Q_1} Q_0 S + Q_1 \overline{Q_0} (\overline{C} + L) + Q_1 Q_0 S$$

$$D_1 = \overline{Q_1} Q_0 S + Q_1 \overline{Q_0} + Q_1 Q_0 S$$

$$D_0 = \overline{Q_1} \overline{Q_0} C L + \overline{Q_1} Q_0 \overline{S} + Q_1 \overline{Q_0} (\overline{C} + L) + Q_1 Q_0 \overline{S}$$

$$H_1 = Q_1$$

$$H_0 = \overline{Q_1} Q_0$$

$$F_1 = \overline{Q_1}$$

$$F_0 = Q_1 Q_0$$

State and Output Encoding 1: Binary

Q	C	S	L	T	D
00	0	X	X	0	00
00	X	X	0	0	00
00	1	X	1	1	01
01	X	0	X	0	01
01	X	1	X	1	10
10	1	X	0	0	10
10	0	X	X	1	11
10	X	X	1	1	11
11	X	0	X	0	11
11	X	1	X	1	00

Q	H	F
00	00	10
01	01	10
10	10	00
11	10	01

$$T = \overline{Q_1} \overline{Q_0} CL + Q_0 S + Q_1 \overline{Q_0} (\overline{C} + L)$$

$$D_1 = Q_0 S + Q_1 \overline{Q_0}$$

$$D_0 = \overline{Q_1} \overline{Q_0} CL + Q_0 \overline{S} + Q_1 \overline{Q_0} (\overline{C} + L)$$

$$H_1 = Q_1$$

$$H_0 = \overline{Q_1} Q_0$$

$$F_1 = \overline{Q_1}$$

$$F_0 = Q_1 Q_0$$

State and Output Encoding 1: Binary

Q	C	S	L	T	D
00	0	X	X	0	00
00	X	X	0	0	00
00	1	X	1	1	01
01	X	0	X	0	01
01	X	1	X	1	10
10	1	X	0	0	10
10	0	X	X	1	11
10	X	X	1	1	11
11	X	0	X	0	11
11	X	1	X	1	00

Q	H	F
00	00	10
01	01	10
10	10	00
11	10	01

$$T = \overline{Q_0}(\overline{Q_1}CL + Q_1(\overline{C} + L)) + Q_0S$$

$$D_1 = Q_0S + Q_1\overline{Q_0}$$

$$D_0 = \overline{Q_0}(\overline{Q_1}CL + Q_1(\overline{C} + L)) + Q_0\overline{S}$$


$$H_1 = Q_1$$

$$H_0 = \overline{Q_1}Q_0$$

$$F_1 = \overline{Q_1}$$

$$F_0 = Q_1Q_0$$

State and Output Encoding 1: Binary

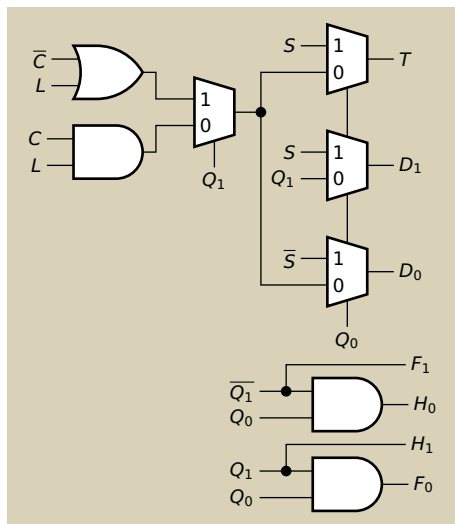

$$T = \bar{Q}_0(\bar{Q}_1 CL + Q_1(\bar{C} + L)) + Q_0 S$$

$$D_1 = Q_0 S + Q_1 \bar{Q}_0$$

$$D_0 = \bar{Q}_0(\bar{Q}_1 CL + Q_1(\bar{C} + L)) + Q_0 \bar{S}$$

$$H_1 = Q_1$$

$$H_0 = \bar{Q}_1 Q_0$$

$$F_1 = \bar{Q}_1$$

$$F_0 = Q_1 Q_0$$

State and Output Encoding 2: One-Hot

States	
HG	0001
HY	0010
FG	0100
FY	1000

Outputs	
G	001
Y	010
R	100

State and Output Encoding 2: One-Hot

Q	C	S	L	T	D
HG	0	X	X	0	HG
HG	X	X	0	0	HG
HG	1	X	1	1	HY
HY	X	0	X	0	HY
HY	X	1	X	1	FG
FG	1	X	0	0	FG
FG	0	X	X	1	FY
FG	X	X	1	1	FY
FY	X	0	X	0	FY
FY	X	1	X	1	HG

Q	H	F
HG	G	R
HY	Y	R
FG	R	G
FY	R	Y

State and Output Encoding 2: One-Hot

Q	C	S	L	T	D
0001	0	X	X	0	0001
0001	X	X	0	0	0001
0001	1	X	1	1	0010
0010	X	0	X	0	0010
0010	X	1	X	1	0100
0100	1	X	0	0	0100
0100	0	X	X	1	1000
0100	X	X	1	1	1000
1000	X	0	X	0	1000
1000	X	1	X	1	0001

Q	H	F
0001	001	100
0010	010	100
0100	100	001
1000	100	010

State and Output Encoding 2: One-Hot

Q	C	S	L	T	D
0001	0	X	X	0	0001
0001	X	X	0	0	0001
0001	1	X	1	1	0010
0010	X	0	X	0	0010
0010	X	1	X	1	0100
0100	1	X	0	0	0100
0100	0	X	X	1	1000
0100	X	X	1	1	1000
1000	X	0	X	0	1000
1000	X	1	X	1	0001

Q	H	F
0001	001	100
0010	010	100
0100	100	001
1000	100	010

$$T = Q_0CL + Q_1S + Q_2(\bar{C} + L) + Q_3S$$

$$D_3 = Q_2(\bar{C} + L) + Q_3\bar{S}$$

$$D_2 = Q_1S + Q_2(\bar{C} + L)$$

$$D_1 = Q_0CL + Q_1\bar{S}$$

$$D_0 = Q_0(\bar{C}L) + Q_3S$$

$$H_R = Q_2 + Q_3$$

$$H_Y = Q_1$$


$$H_G = Q_0$$

$$F_R = Q_0 + Q_1$$

$$F_Y = Q_3$$

$$F_G = Q_2$$

State and Output Encoding 2: One-Hot

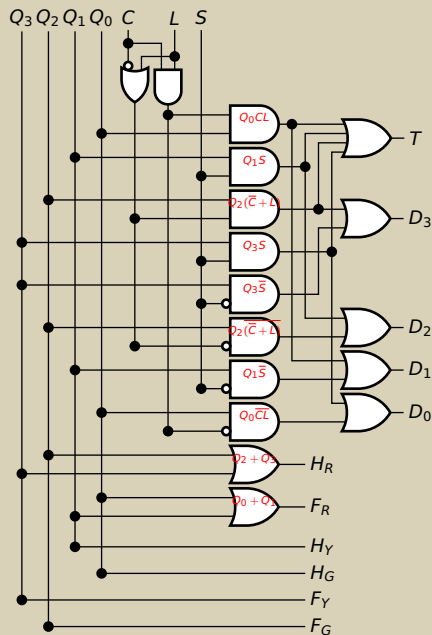

$$T = Q_0CL + Q_1S + Q_2(\bar{C} + L) + Q_3S$$

$$D_3 = Q_2(\bar{C} + L) + Q_3\bar{S}$$

$$D_2 = Q_1S + Q_2(\bar{C} + L)$$

$$D_1 = Q_0CL + Q_1\bar{S}$$

$$D_0 = Q_0(\bar{C}\bar{L}) + Q_3S$$

$$H_R = Q_2 + Q_3$$

$$H_Y = Q_1$$

$$H_G = Q_0$$

$$F_R = Q_0 + Q_1$$

$$F_Y = Q_3$$

$$F_G = Q_2$$