

Fundamentals of Computer Systems



Sequential Logic

Martha A. Kim

Columbia University



Fall 2015

Bistable Elements

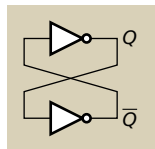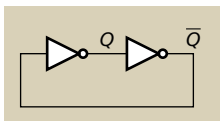


Equivalent circuits; right is more traditional.

Two stable states:

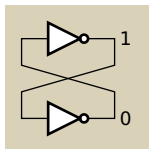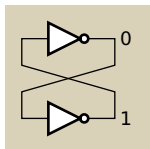


RS Latch

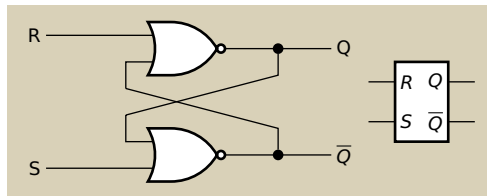


R	S	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		

RS Latch

 


R	S	Q	\bar{Q}	
0	0			
0	1	1	0	Set ($Q = 1$)
1	0			
1	1			

RS Latch

 


R	S	Q	\bar{Q}	
0	0			
0	1	1	0	Set ($Q = 1$)
1	0	0	1	Reset ($Q = 0$)
1	1			

RS Latch

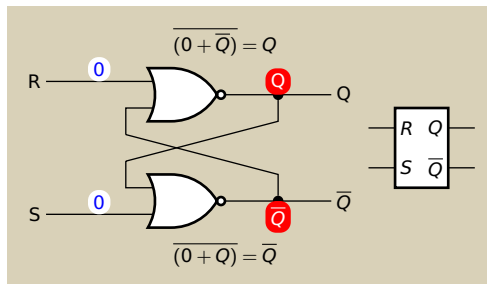


R	S	Q	\bar{Q}	
0	0	Q	\bar{Q}	Hold previous value
0	1	1	0	Set ($Q = 1$)
1	0	0	1	Reset ($Q = 0$)
1	1			

RS Latch

 


R	S	Q	\bar{Q}	
0	0	Q	\bar{Q}	Hold previous value
0	1	1	0	Set ($Q = 1$)
1	0	0	1	Reset ($Q = 0$)
1	1	0	0	Bad. Do not use.

$\overline{R}\overline{S}$ Latch

 

R	S	Q	\overline{Q}	
0	0	1	1	Bad. Do not use.
0	1	0	1	Reset ($Q = 0$)
1	0	1	0	Set ($Q = 1$)
1	1	Q	\overline{Q}	Hold previous value


D Latch

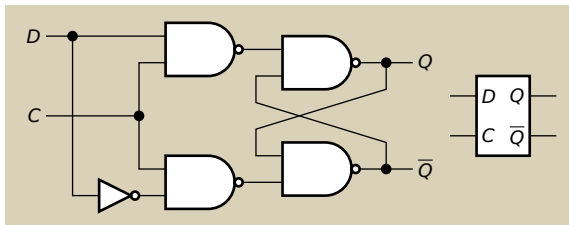

C	D	Q	\bar{Q}
0	X	Q	\bar{Q}
1	0	0	1
1	1	1	0

A Challenge: Build a traffic light controller

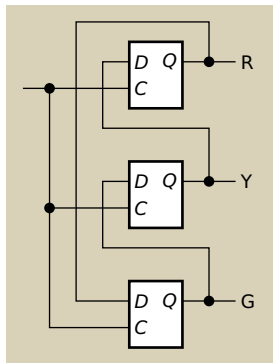Want the lights to cycle green-yellow-red.




Does this work?








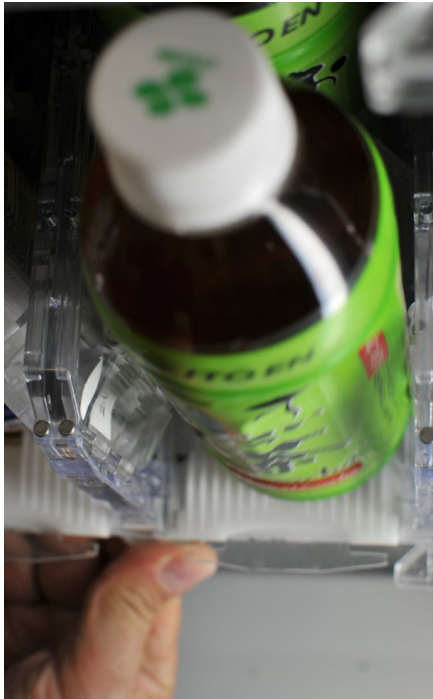











 


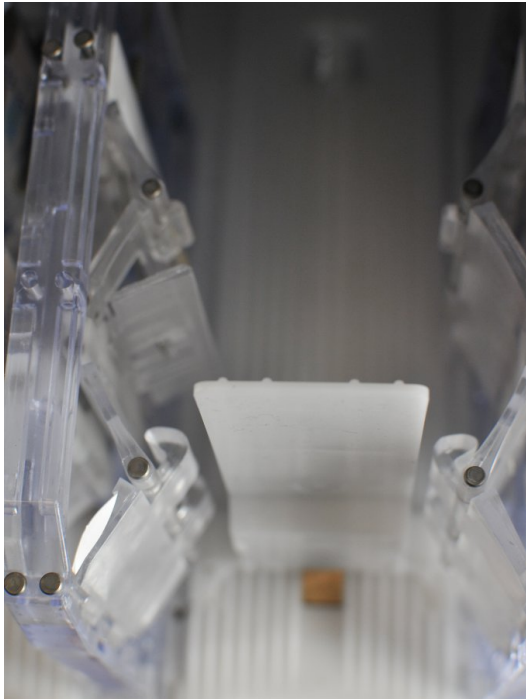


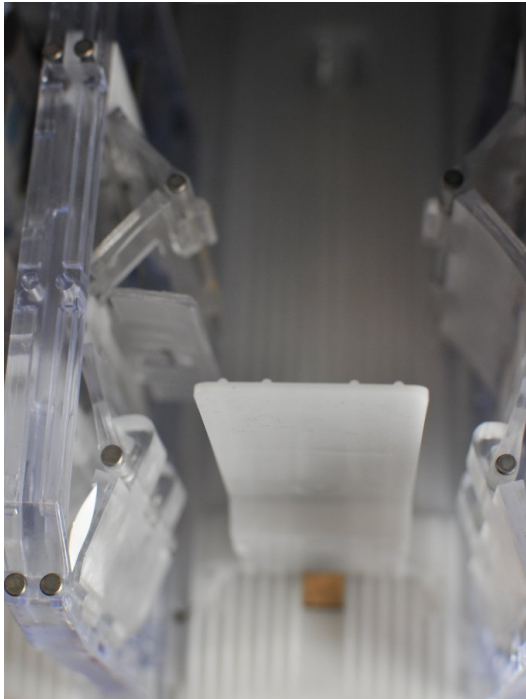


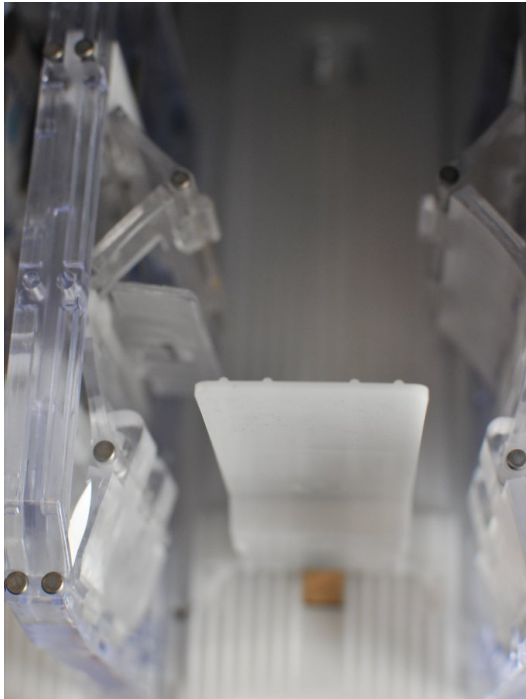


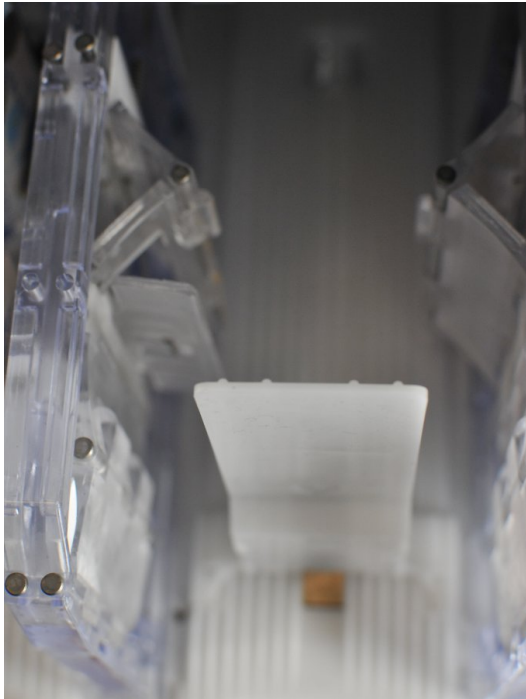



Positive-Edge-Triggered D Flip-Flop

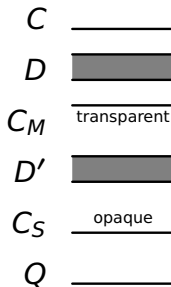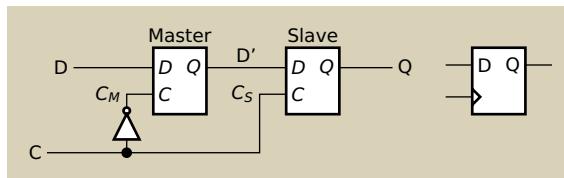


Positive-Edge-Triggered D Flip-Flop

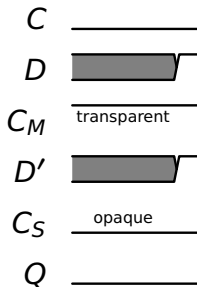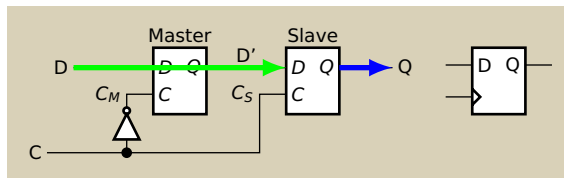



Positive-Edge-Triggered D Flip-Flop

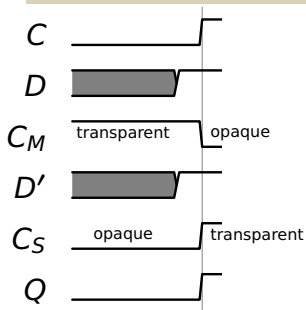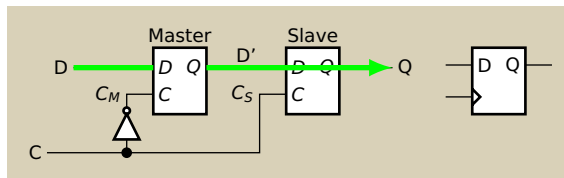


Positive-Edge-Triggered D Flip-Flop

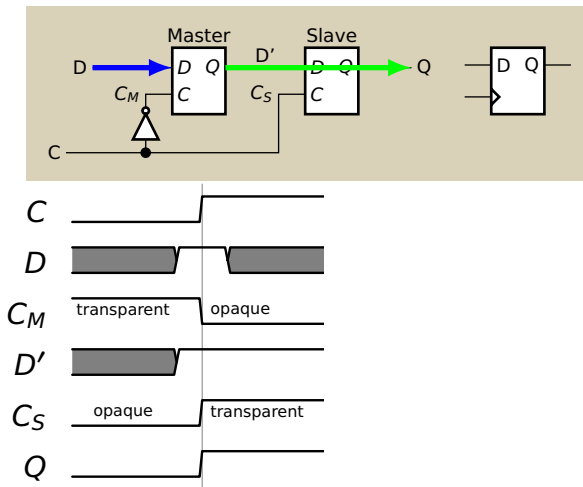

Positive-Edge-Triggered D Flip-Flop

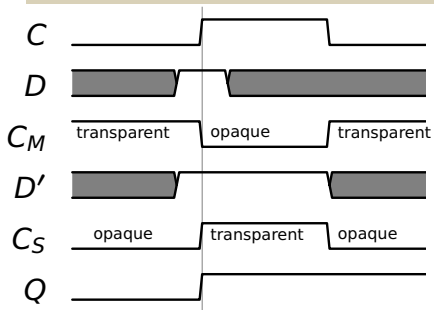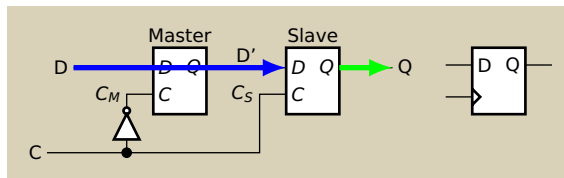


Positive-Edge-Triggered D Flip-Flop

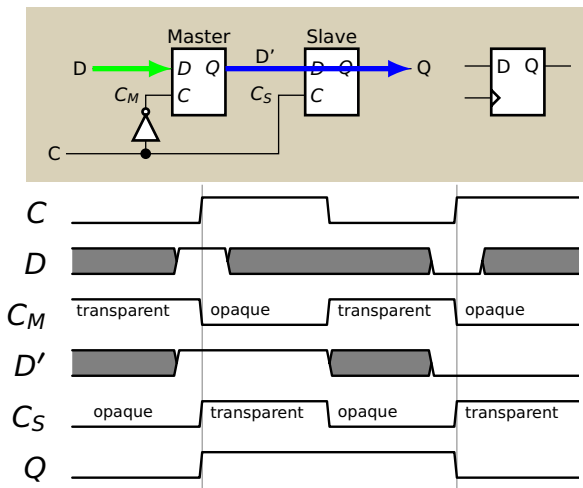

The Traffic Light Controller: A second try

Let's try this again with D flip-flops.

 

CLK ___



R ___

Y ___

G ___



The Traffic Light Controller: A second try

Let's try this again with D flip-flops.

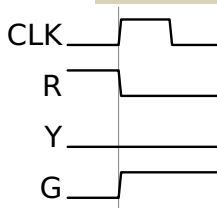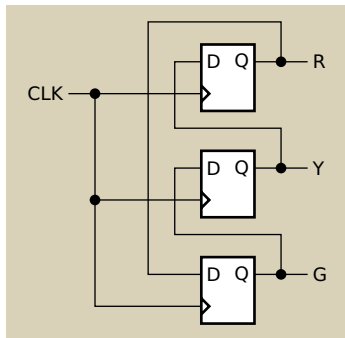



The Traffic Light Controller: A second try

Let's try this again with D flip-flops.

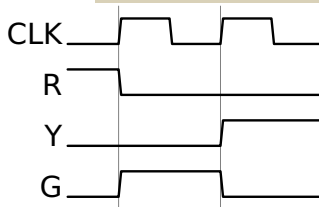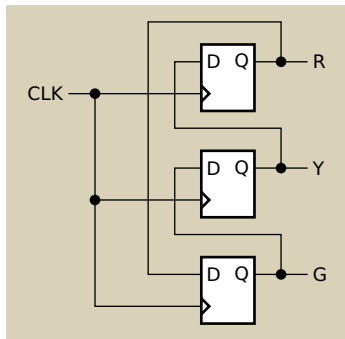



The Traffic Light Controller: A second try

Let's try this again with D flip-flops.

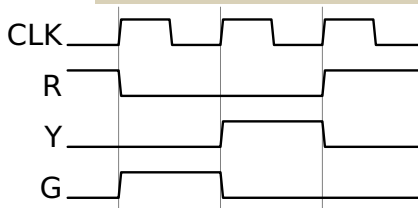
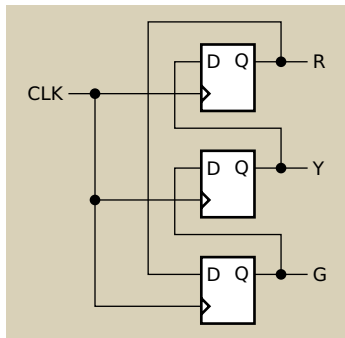


The Traffic Light Controller: A second try



Let's try this again with D flip-flops.

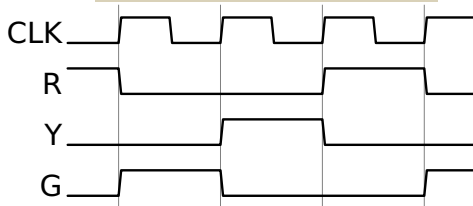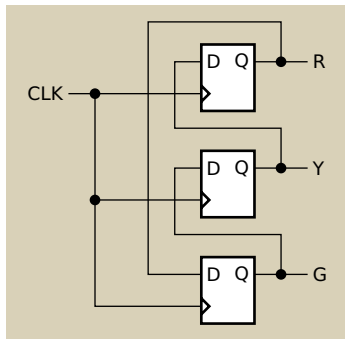



The Traffic Light Controller with Reset

 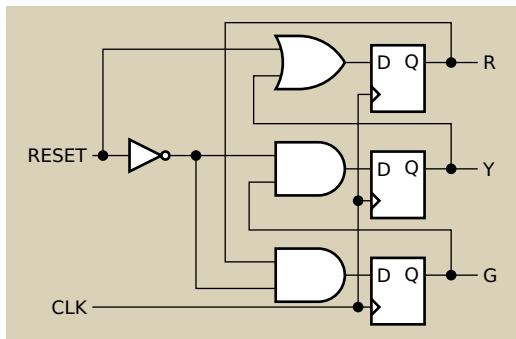



The Traffic Light Controller with Reset

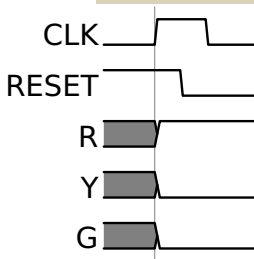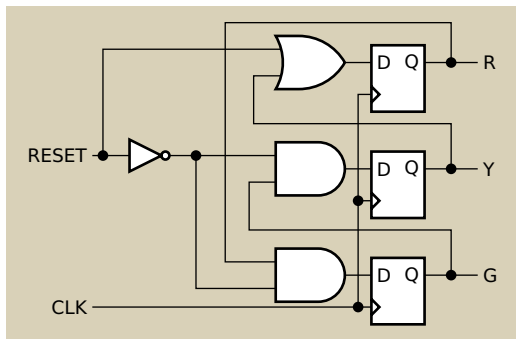



The Traffic Light Controller with Reset

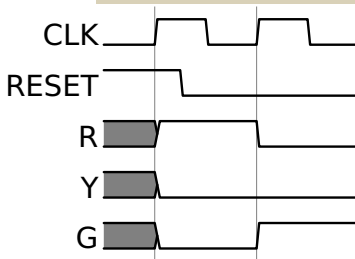 



The Traffic Light Controller with Reset

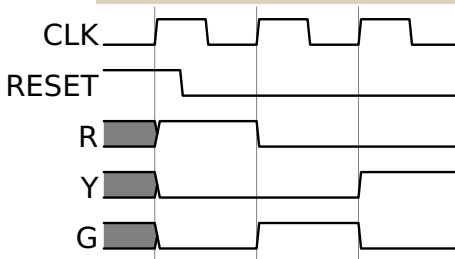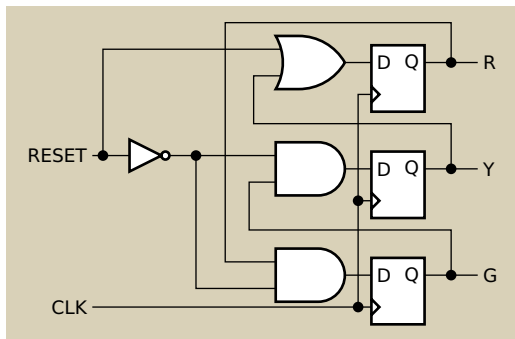


The Traffic Light Controller with Reset

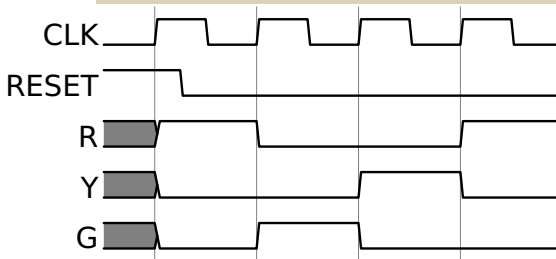 


The Traffic Light Controller with Reset

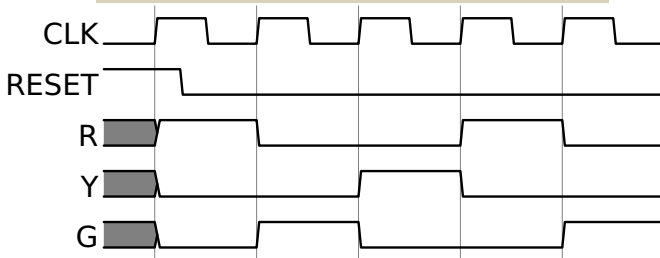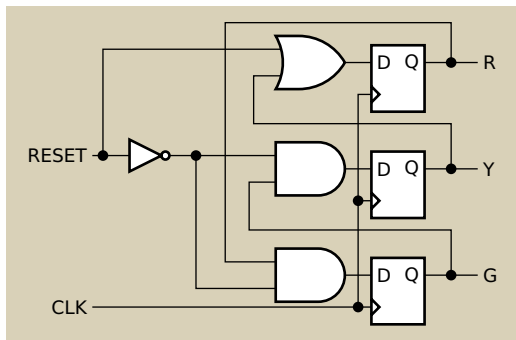

D Flip-Flop with Enable


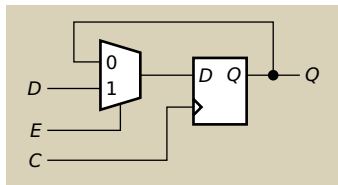


C	E	D	Q
\uparrow	0	X	Q
\uparrow	1	0	0
\uparrow	1	1	1
0	X	X	Q
1	X	X	Q

 


What's wrong with this solution?

Asynchronous Preset/Clear

 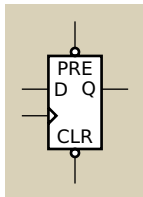

 The Traffic Light Controller w/ Async. Reset




The Synchronous Digital Logic Paradigm


Gates and D
flip-flops only

Each flip-flop
driven by the
same clock

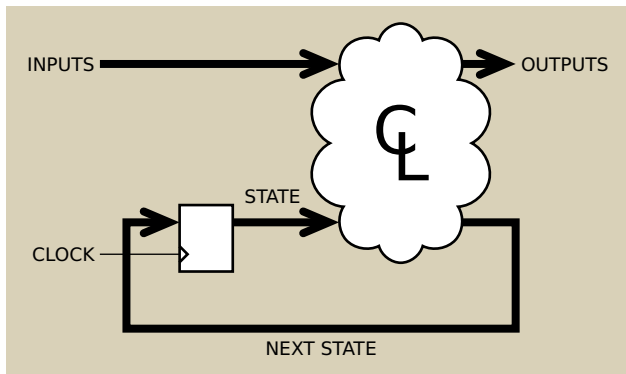Every cyclic
path contains
at least one
flip-flop




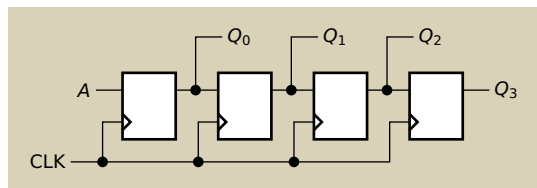Cool Sequential Circuits: Shift Registers



A	Q_0	Q_1	Q_2	Q_3
0	X	X	X	X
1	0	X	X	X
1	1	0	X	X
0	1	1	0	X
1	0	1	1	0
0	1	0	1	1
0	0	1	0	1
0	0	0	1	0
1	0	0	0	1
0	1	0	0	0

Universal Shift Register

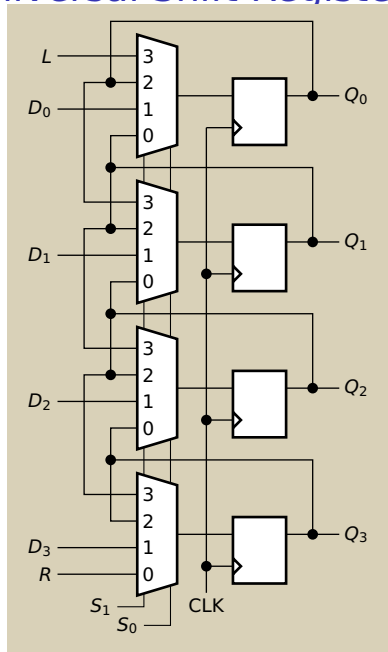


S_1	S_0	Q_3	Q_2	Q_1	Q_0
0	0	R	Q_3	Q_2	Q_1
0	1	D_3	D_2	D_1	D_0
1	0	Q_3	Q_2	Q_1	Q_0
1	1	Q_2	Q_1	Q_0	L

S_1	S_0	Operation
0	0	Shift right
0	1	Load
1	0	Hold
1	1	Shift left


Cool Sequential Circuits: Counters

 Cycle through sequences of numbers, e.g.,



Flip-Flop Timing

 
Setup Time: Time before the clock edge after which the data may not change



Flip-Flop Timing

Setup Time: Time before the clock edge after which the data may not change

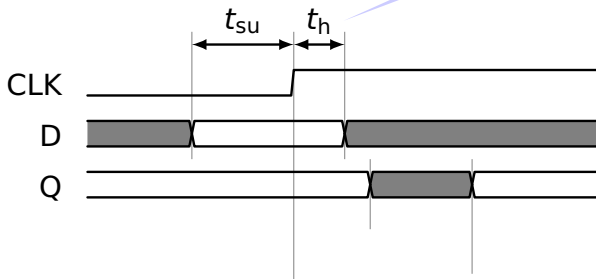
Hold Time: Time after the clock edge after which the data may change



Flip-Flop Timing

Setup Time: Time before the clock edge after which the data may not change

 Hold Time: Time after the clock edge after which the data may change




Minimum Propagation Delay: Time from clock edge to when Q might start changing

Flip-Flop Timing

Setup Time: Time before the clock edge after which the data may not change


 
Hold Time: Time after the clock edge after which the data may change



Minimum Propagation Delay: Time from clock edge to when Q might start changing


Maximum Propagation Delay: Time from clock edge to when Q guaranteed stable

Timing in Synchronous Circuits

 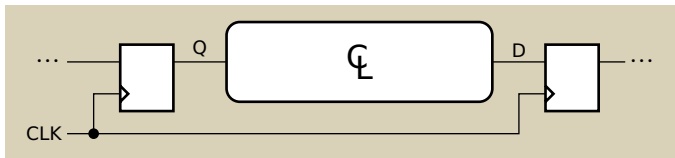


t_c : Clock period. E.g., 10 ns for a 100 MHz clock

Timing in Synchronous Circuits


 


Sufficient Hold Time?

 


Hold time constraint: how soon after the clock edge is
D liable to start changing?
Min. FF delay + min. logic delay

Timing in Synchronous Circuits

  


Setup time constraint: when before the clock edge is D guaranteed to have stabilized?
Max. FF delay + max. logic delay

Clock Skew: What Really Happens

 


Sufficient Hold Time?

 


CLK_2 arrives late, creating potential hold time violation

Clock Skew: What Really Happens

 

Sufficient Setup Time?

 

CLK_2 arrives early, creating potential setup time violation