



CSEE 3827: Fundamentals of Computer Systems

Lecture 9

February 18, 2009

Martha Kim
martha@cs.columbia.edu

Combinational v. sequential logic

  


Asynchronous v. synchronous circuits

- **asynchronous sequential circuits:** behavior depends on input signals at *any instant of time*



 - **synchronous sequential circuits:** behavior defined by signal values at *discrete times*




Latches (asynchronous storage elements)

Simple logic for information storage

5-2

 
Can build basic storage out of any gate that has delay (t_G)




However, these storage circuits are not writable. . .

SR latch

 
- Latch constructed of cross-coupled NOR gates



SR latch state diagram

 


SR latch characteristic table

 

S	R	next state
0	0	no change
0	1	reset ($Q=0$)
1	0	set ($Q=1$)
1	1	invalid


'S'R latch

 - Latch constructed of cross-coupled NAND gates




- This latch holds its state when both inputs are 1. $'S = 0$ makes $Q = 1$, $'R = 0$ makes $Q = 0$.

'S'R latch characteristic table

 


'S	'R	next state
0	0	invalid
0	1	set ($Q=1$)
1	0	reset ($Q=0$)
1	1	no change

SR latch with control input

 


 SR latch with control input characteristic table



C	S	R	\bar{S}	\bar{R}	next state
0	x	x	1	1	no change
1	0	0	1	1	no change
1	0	1	1	0	reset ($Q=0$)
1	1	0	0	1	set ($Q=1$)
1	1	1	0	0	invalid

 D latch with control input characteristic table




C	D	'S	'R	next state
0	x	1	1	no change
1	0	1	0	reset (Q=0)
1	1	0	1	set (Q=1)

Flip-flops (synchronous storage elements)

Why we need flip flops

 
- This circuit is not safely (predictably) synchronous




- The problem is transparency of latches: as soon as the input changes, at some time later the output will change
- Flip flops are designed so that outputs will **not** change within a single clock pulse

SR master-slave flip-flop


 
*Internal state (Y) updated
when $CLK=1$*




 
*External state (Q)
updated when $CLK=0$*





Negative-edge-triggered D flip-flop

  


Positive-edge-triggered D flip-flop

  


D latch v. D flip-flop

  

Some notes on notation

 


(a) Latches

 


(c) Edge-Triggered Flip-Flops

Adding reset signals

 

(a) Asynchronous Reset







(resets immediately)

 

(b) Synchronous Reset

(resets at clock edge only)

Two more flip-flops: JK and T flip-flops

      Type	Symbol	Logic Diagrams		Characteristic Table			Characteristic Equation			Excitation Table				
D		See Figure 5-12		D	Q(t+1)	Operation	$Q(t + 1) = D(t)$			Q(t+1)	D	Operation		
				0	0	Reset				0	0	Reset		
SR		See Figure 5-9		S	R	Q(t+1)	Operation	$Q(t + 1) = S(t) + \bar{R}(t) Q(t)$			Q(t)	Q(t+1)	S R Operation	
				0	0	$Q(t)$	No change				0	0	0 X	No change
				0	1	0	Reset				0	1	1 0	Set
				1	0	1	Set				1	0	0 1	Reset
JK				J	K	Q(t+1)	Operation	$Q(t + 1) = J(t) \bar{Q}(t) + \bar{K}(t) Q(t)$			Q(t)	Q(t+1)	J K Operation	
				0	0	$Q(t)$	No change				0	0	0 X	No change
				0	1	0	Reset				0	1	1 X	Set
				1	0	1	Set				1	0	X 1	Reset
				1	1	$\bar{Q}(t)$	Complement				1	1	X 0	No Change
T				T	Q(t+1)	Operation	$Q(t + 1) = T(t) \oplus Q(t)$			Q(t+1)	T	Operation		
				0	$Q(t)$	No change				$Q(t)$	0	No change		
				1	$\bar{Q}(t)$	Complement				$\bar{Q}(t)$	1	Complement		