

Complete the following problems. Be sure to show your work for partial credit.

- Determine the base of the numbers in each equation for the following operations to be correct:
 - $14 / 2 = 5$
 - $54 / 4 = 13$
 - $24 + 17 = 40$
- Demonstrate by means of truth tables the validity of the following identities:
 - DeMorgan's theorem for three variables:
 - $\overline{x + y + z} = \bar{x} \cdot \bar{y} \cdot \bar{z}$; and
 - $\overline{x \cdot y \cdot z} = \bar{x} + \bar{y} + \bar{z}$
 - The distributive law: $x + y \cdot z = (x + y) \cdot (x + z)$
- Given the Boolean functions F_1 and F_2 .
 - Show that the Boolean function $E = F_1 + F_2$ contains the sum of the minterms of F_1 and F_2 .
 - Show that the Boolean function $G = F_1 F_2$ contains only the minterms that are common to F_1 and F_2 .

Hint: start by identifying a general expression for minterm i (m_i) of F_1 , F_2 , E , and G .
- Given the Boolean function: $F = x \cdot y + \bar{x} \cdot \bar{y} + \bar{y} \cdot z$
 - implement it with OR and inverter gates.
 - implement it with AND and inverter gates.
- Show that the dual of the XOR is equal to its complement.
- Give an example of a truth table requiring between 3 billion and 5 billion rows that can be constructed using fewer than 40 (but at least 1) two-input gates.
- Convert the following expressions into sum of products and product of sums, and simplify as much as possible:
 - $(AB + C)(B + \bar{C}D)$
 - $\bar{x} + x(x + \bar{y})(y + \bar{z})$
- Simplify the following Boolean equations using Boolean theorems. Check for correctness using a K-map.
 - $Y = A \cdot C + \bar{A} \cdot \bar{B} \cdot C$
 - $Y = \bar{A} \cdot \bar{B} + \bar{A} \cdot B \cdot \bar{C} + \overline{(A + \bar{C})}$
 - $Y = \bar{A} \cdot \bar{B} \cdot \bar{C} \cdot \bar{D} + A \cdot \bar{B} \cdot \bar{C} + A \cdot \bar{B} \cdot C \cdot \bar{D} + A \cdot B \cdot D + \bar{A} \cdot \bar{B} \cdot C \cdot \bar{D} + B \cdot \bar{C} \cdot D + \bar{A}$
- Simplify the following functions using K-maps, and implement them with two-level NOR gate circuits:
 - $F = w \cdot \bar{x} + \bar{y} \cdot \bar{z} + \bar{w} \cdot y \cdot \bar{z}$
 - $F(w, x, y, z) = \Sigma(5, 6, 9, 10)$