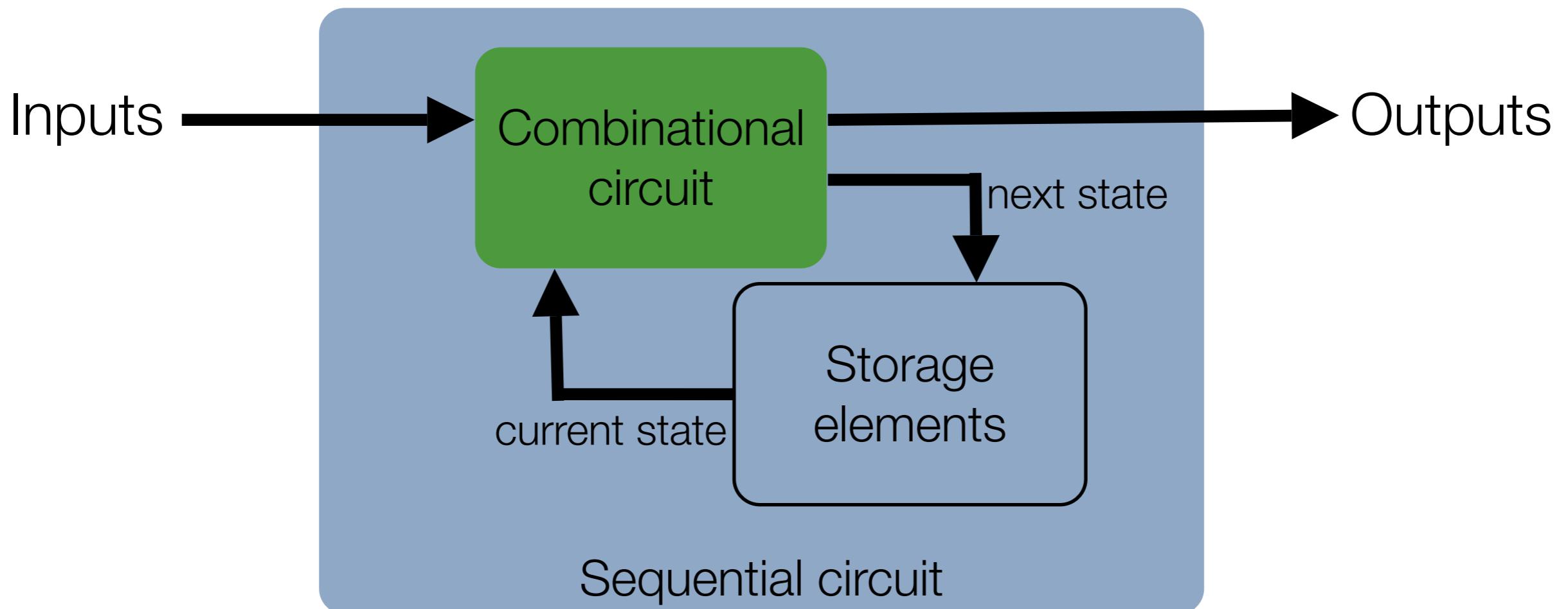


CSEE 3827: Fundamentals of Computer Systems


Finite State Machine Design

Recall: Sequential circuit




Example sequential circuit (schematic)

5-15

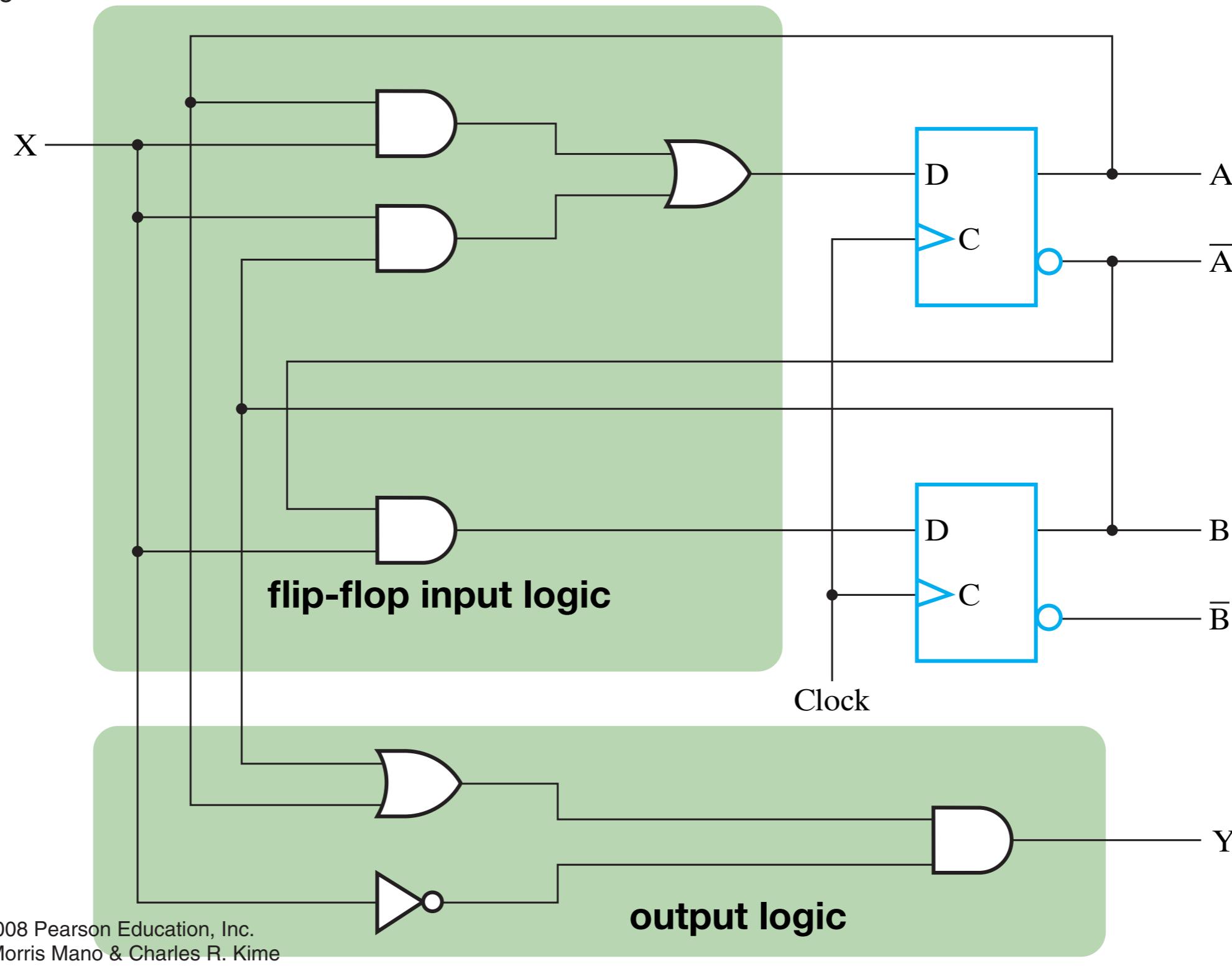

Reverse engineering a sequential circuit

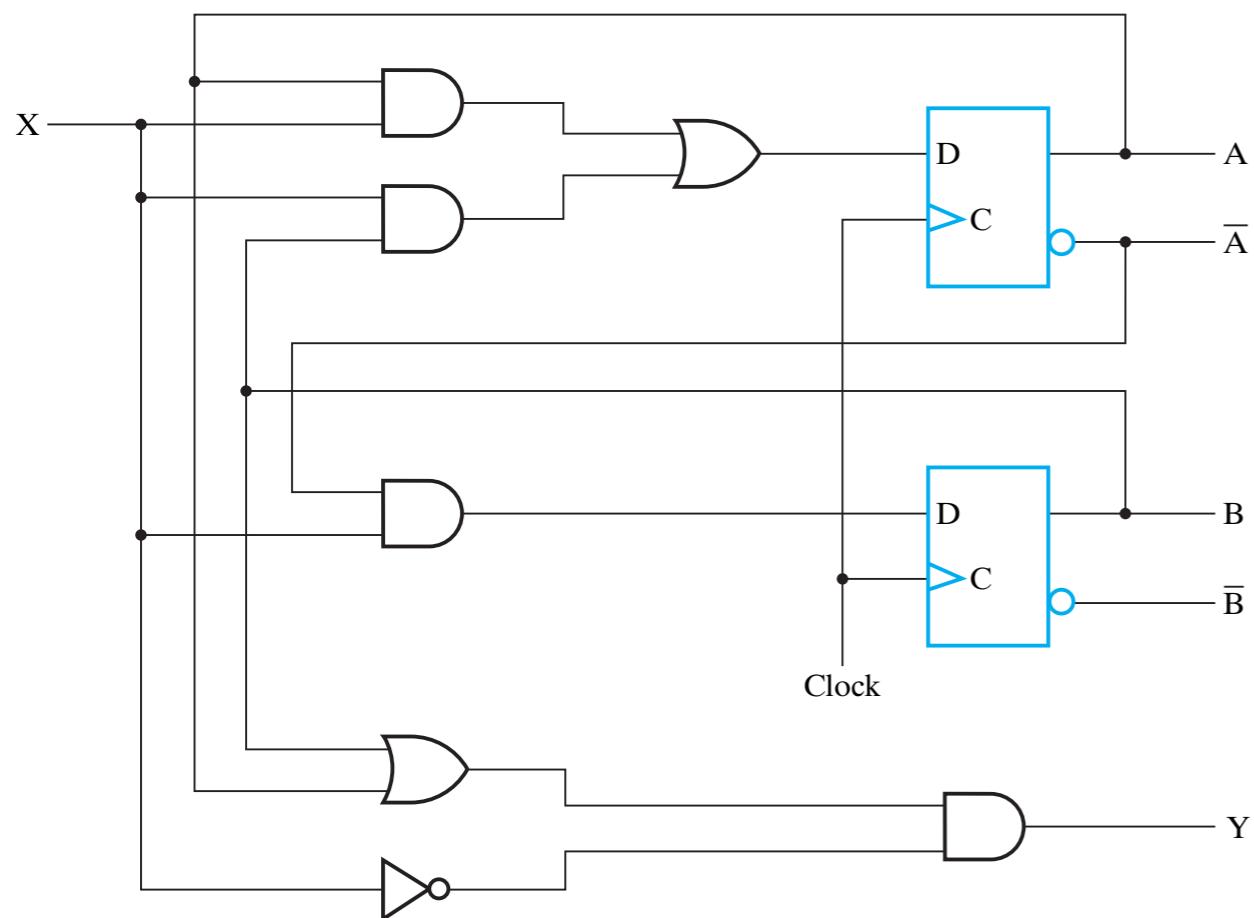


State machine

*A state machine model of a system's behavior in terms of **states** and **transitions** between those states that are triggered by **actions**.*

State diagrams represent state machines

one or more states, indicated by nodes

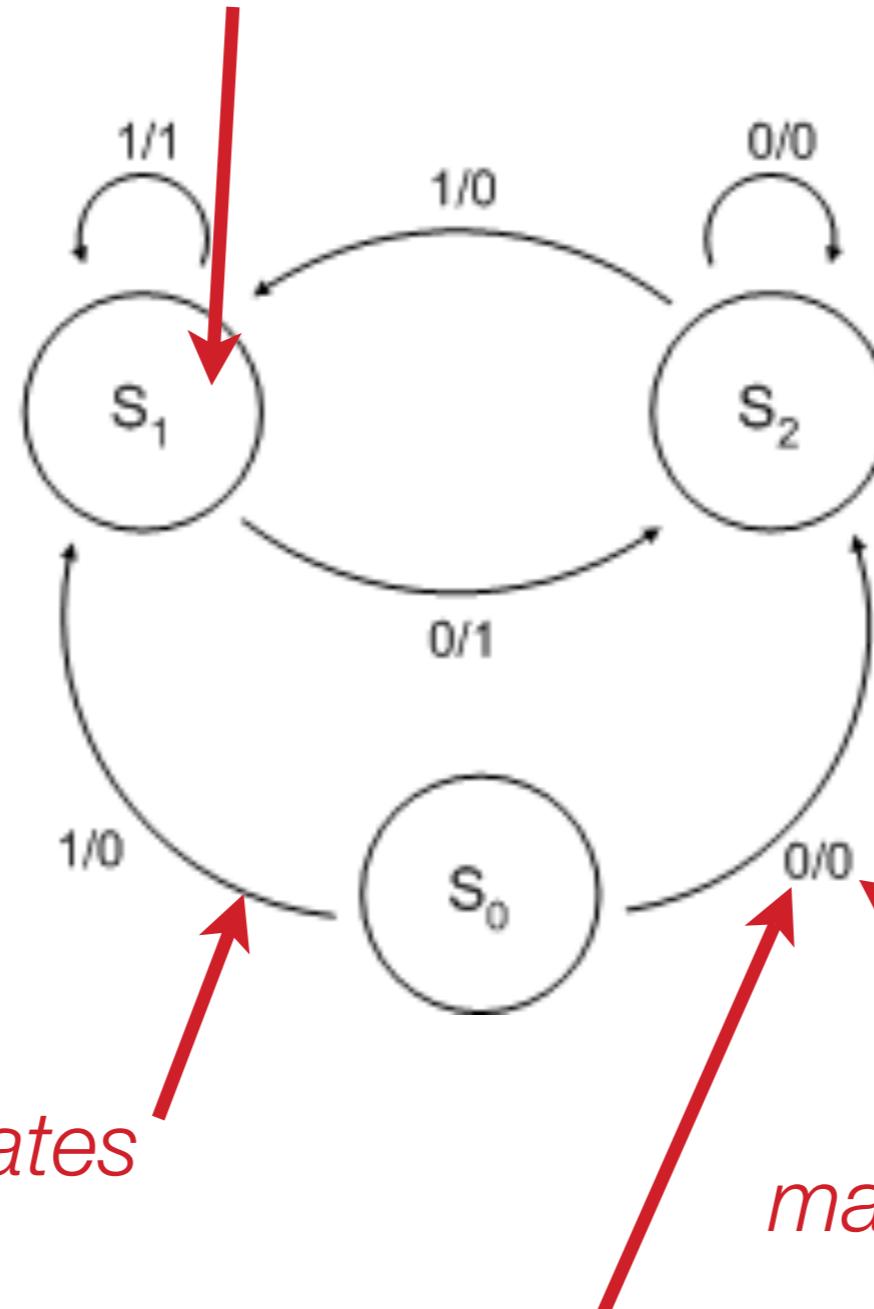

edges between states

machine output at transition

input value that triggers transition on edge


Finite state machine (FSM)

A state machine that has a finite number of states

- * *Any finite state machine can be implemented with sequential logic*
- * *All sequential circuits implement finite state machines*

Implementing a finite state machine

1. describe operation

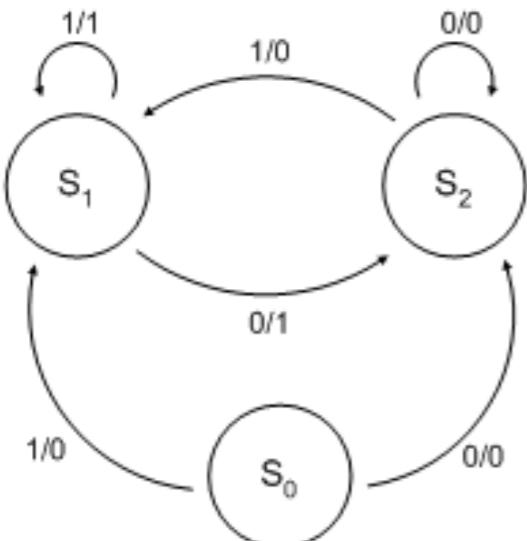

2. convert to truth table

S	in	S+	out
00	0	10	0
00	1	01	0
01	0	10	1
01	1	01	1
10	0	10	0
10	1	01	0

3. choose type of flip-flop

4. annotate table with flip-flop inputs for next state

S	in	S+	out	T1	T2
00	0	10	0	1	0
00	1	01	0	0	1
01	0	10	1	1	1
01	1	01	1	0	0
10	0	10	0	0	0
10	1	01	0	1	1

5. derive “next state” and “output” logic


6. wire circuit and flip-flops together together

From State Machine to Sequential Circuit


- Specify behavior of state machine (including input and output values)
- Encode states
 - *figure out how many bits needed to store state (one FF per bit)*
 - *assign state values to states*
- Select FF type (i.e., D, T, JK, etc.)
- Compute combinational logic functions
 - “*next state*” logic: $S+ = F(S, \text{inputs})$
 - “*output*” logic:
 - Mealy machine: $\text{output} = G(S, \text{inputs})$
 - Moore machine: $\text{output} = H(S)$

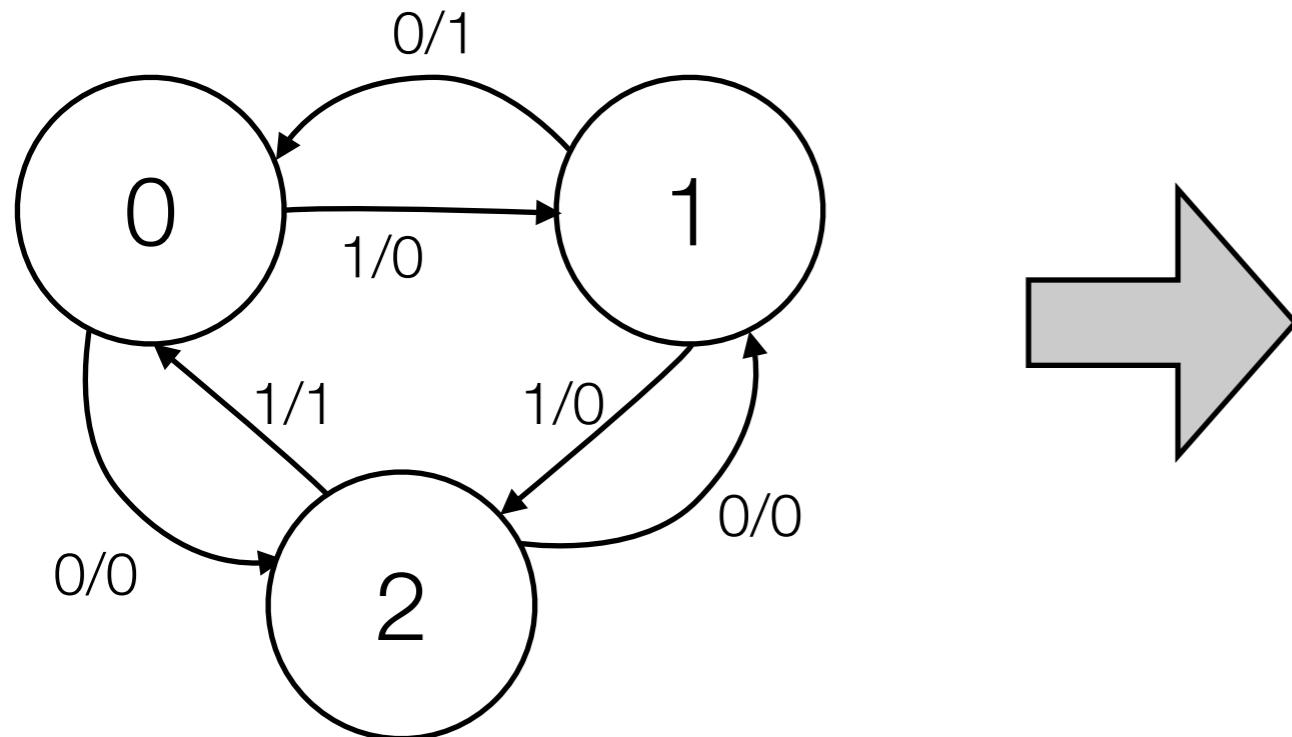Example State Machine

- 1 input, 1 output
- Let $X = \#$ of 1's input so far, $Y = \#$ of 0's input so far.
- Output 1 whenever $X-Y = 0 \pmod{3}$



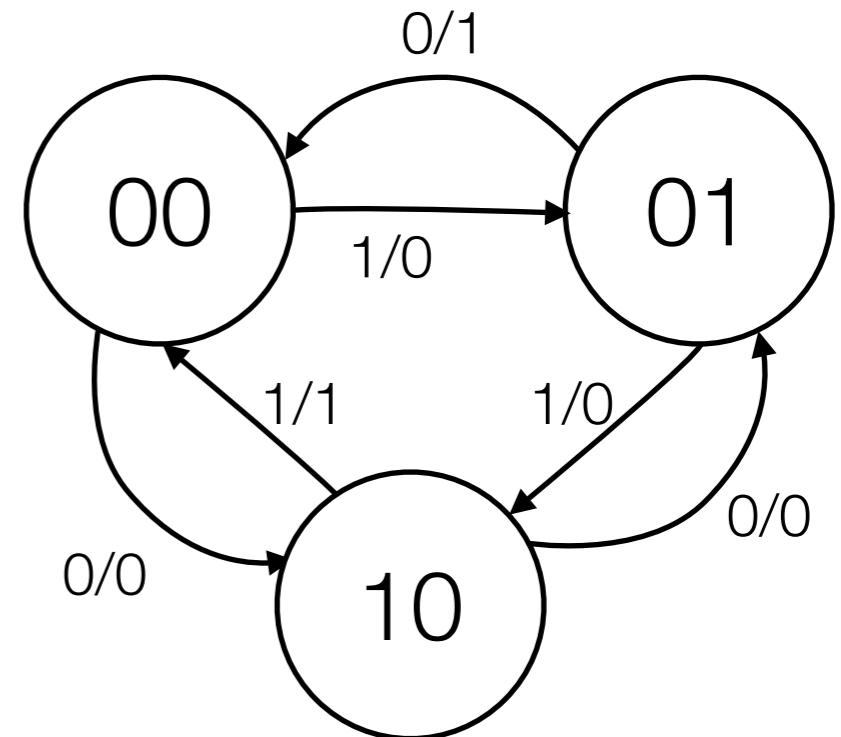State label is current value of $X-Y \bmod 3$




Binary Labeling

Design with D Flip-Flops

- D FF's are easy: we input the value to the FF that we want it set to

A _{cur}	B _{cur}	In	A _{next}	B _{next}	Out
0	0	0	1	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	0	1
1	1	0	X	X	X
1	1	1	X	X	X

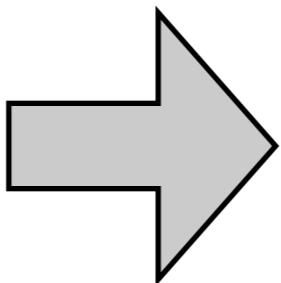

A _{cur}	B _{cur}	In	A _{next}	D _A	B _{next}	D _B	Out
0	0	0	1	1	0	0	0
0	0	1	0	0	1	1	0
0	1	0	0	0	0	0	1
0	1	1	1	1	0	0	0
1	0	0	0	0	1	1	0
1	0	1	0	0	0	0	1
1	1	0	X	X	X	X	X
1	1	1	X	X	X	X	X

New columns indicate what values feed into D FF (mimic “next” values for that FF)

Design with D Flip-Flops Cont'd

- Build K-Maps, get equations for output and FF input vals (in terms of inputs and previous F vals)

A _{cur}	B _{cur}	In	A _{next}	D _A	B _{next}	D _B	Out
0	0	0	1	1	0	0	0
0	0	1	0	0	1	1	0
0	1	0	0	0	0	0	1
0	1	1	1	1	0	0	0
1	0	0	0	0	1	1	0
1	0	1	0	0	0	0	1
1	1	0	X	X	X	X	X
1	1	1	X	X	X	X	X

$$D_A = \bar{A}\bar{B}\bar{I} + BI$$

$$D_B = A\bar{B}\bar{I} + \bar{A}\bar{B}I$$

$$Out = AI + B\bar{I}$$

D_A:

		In			
		1	0	1	0
		0	0	X	X
A _{cur}	B _{cur}				

D_B:

		In			
		0	1	0	0
		1	0	X	X
A _{cur}	B _{cur}				

Out:


		In			
		0	0	0	1
		0	1	X	X
A _{cur}	B _{cur}				

Design with D FF's cont'd

$$D_A = \bar{A}\bar{B}\bar{I} + BI$$

$$D_B = A\bar{B}\bar{I} + \bar{A}\bar{B}I$$


$$\text{Out} = AI + B\bar{I}$$

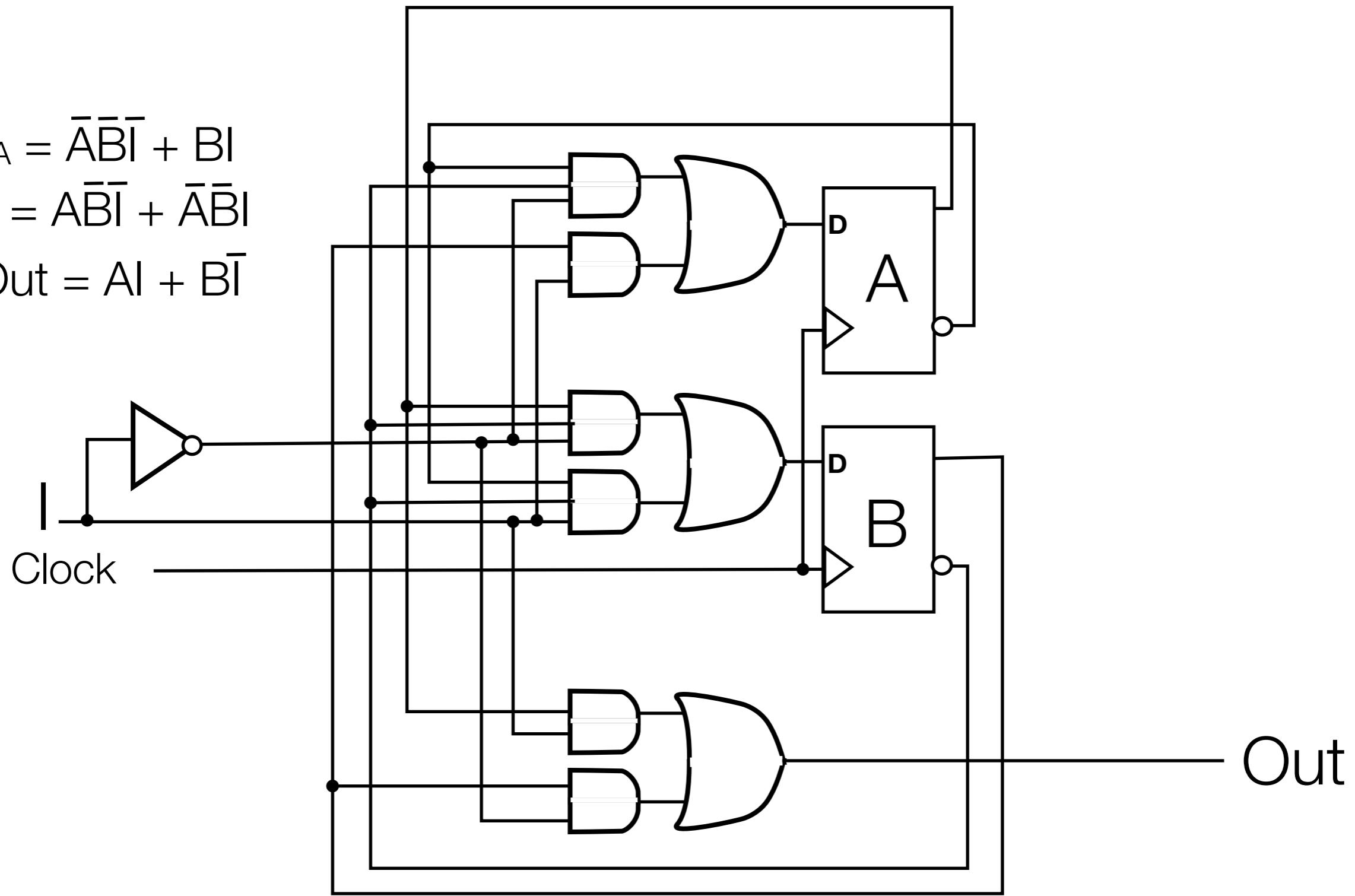

Design with T Flip Flops

- Value fed into T FF is 0 if FF should maintain value, 1 if it should flop

A _{cur}	B _{cur}	In	A _{next}	B _{next}	Out
0	0	0	1	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	0	1
1	1	0	X	X	X
1	1	1	X	X	X

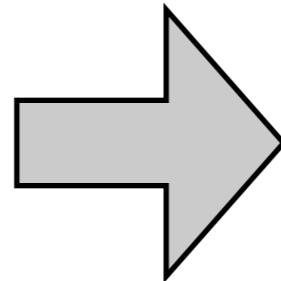

A _{cur}	B _{cur}	In	A _{next}	T _A	B _{next}	T _B	Out
0	0	0	1	1	0		0
0	0	1	0	0	1		0
0	1	0	0	0	0		1
0	1	1	1	1	0		0
1	0	0	0	1	1		0
1	0	1	0	0	1		1
1	1	0	X	X	X		X
1	1	1	X	X	X		X

In

1	0	1	0
1	1	X	X

B_{cur}

T_A:


A_{cur}

$$T_A = A + BI + \bar{B}\bar{I}$$

Design with T Flip Flops

- Value fed into T FF is 0 if FF should maintain value, 1 if it should flop

A _{cur}	B _{cur}	In	A _{next}	B _{next}	Out
0	0	0	1	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	0	1
1	1	0	X	X	X
1	1	1	X	X	X

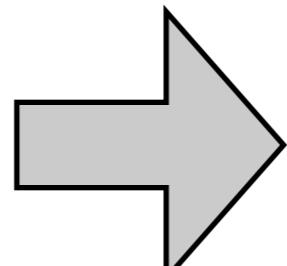

In

A _{cur}	B _{cur}	In	A _{next}	T _A	B _{next}	T _B	Out
0	0	0	1	1	0	0	0
0	0	1	0	0	1	1	0
0	1	0	0	0	0	1	1
0	1	1	1	1	0	1	0
1	0	0	0	1	1	1	0
1	0	1	0	0	1	1	0
1	0	1	0	1	0	0	1
1	1	0	X	X	X	X	X
1	1	1	X	X	X	X	X

T_B:

A_{cur}

0	1	0	0
1	0	X	X

B_{cur}

$$T_B = A\bar{B}\bar{I} + \bar{A}\bar{B}I$$

Design with JK Flip-Flops

- Note: to change A_{cur} to the correct A_{next} value, two possible input pairs can be fed into the J,K inputs of a JK Flip-Flop


J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\overline{Q(t)}$

A_{cur}	A_{next}	J,K
0	0	0,0 or 0,1 (0,X)
0	1	1,0 or 1,1 (1,X)
1	0	0,1 or 1,1 (X,1)
1	1	0,0 or 1,0 (X,0)

Design with JK Flip-Flop

A_{cur}	A_{next}	J,K
0	0	0,0 or 0,1 (0,X)
0	1	1,0 or 1,1 (1,X)
1	0	0,1 or 1,1 (X,1)
1	1	0,0 or 1,0 (X,0)

A _{cur}	B _{cur}	In	A _{next}	B _{next}	Out
0	0	0	1	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	0	1
1	1	0	X	X	X
1	1	1	X	X	X

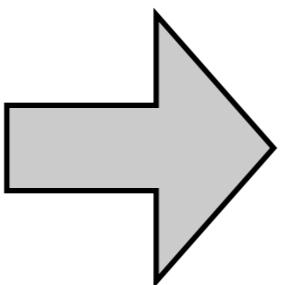


A _{cur}	B _{cur}	In	A _{next}	J _A	K _A	B _{next}	J _B	K _B	Out
0	0	0	1	1	X	0			0
0	0	1	0	0	X	1			0
0	1	0	0	0	X	0			1
0	1	1	1	1	X	0			0
1	0	0	0	X	1	1			0
1	0	1	0	X	1	0			1
1	1	0	X	X	X	X			X
1	1	1	X	X	X	X			X

Design with JK Flip-Flop

A_{cur}	A_{next}	J,K
0	0	0,0 or 0,1 (0,X)
0	1	1,0 or 1,1 (1,X)
1	0	0,1 or 1,1 (X,1)
1	1	0,0 or 1,0 (X,0)

A _{cur}	B _{cur}	In	A _{next}	B _{next}	Out
0	0	0	1	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	0	1
1	1	0	X	X	X
1	1	1	X	X	X

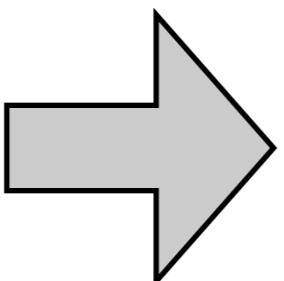

A _{cur}	B _{cur}	In	A _{next}	J _A	K _A	B _{next}	J _B	K _B	Out
0	0	0	1	1	X	0	0	X	0
0	0	1	0	0	X	1	1	X	0
0	1	0	0	0	X	0	X	1	1
0	1	1	1	1	X	0	X	1	0
1	0	0	0	X	1	1	1	X	0
1	0	1	0	X	1	0	0	X	1
1	1	0	X	X	X	X	X	X	X
1	1	1	X	X	X	X	X	X	X

Design with JK Flip-Flop

A _{cur}	B _{cur}	In	A _{next}	J _A	K _A	B _{next}	J _B	K _B	Out
0	0	0	1	1	X	0	0	X	0
0	0	1	0	0	X	1	1	X	0
0	1	0	0	0	X	0	X	1	1
0	1	1	1	1	X	0	X	1	0
1	0	0	0	X	1	1	1	X	0
1	0	1	0	X	1	0	0	X	1
1	1	0	X	X	X	X	X	X	X
1	1	1	X	X	X	X	X	X	X

J_A:

In			
1	0	1	0
X	X	X	X
A _{cur}			
B _{cur}			

K_A:

In			
X	X	X	X
1	1	X	X
A _{cur}			
B _{cur}			

J_B:

In			
0	1	X	X
1	0	X	X
A _{cur}			
B _{cur}			

K_B:

In			
X	X	1	1
X	X	X	X
A _{cur}			
B _{cur}			

$$J_A = BI + \bar{B}\bar{I}$$

$$K_A = 1$$

$$J_B = \bar{A}I + A\bar{I}$$

$$K_B = 1$$


Design with JK FF's cont'd

$$J_A = BI + \bar{B}\bar{I}$$

$$K_A = 1$$


$$J_B = \bar{A}I + A\bar{I}$$

$$K_B = 1$$

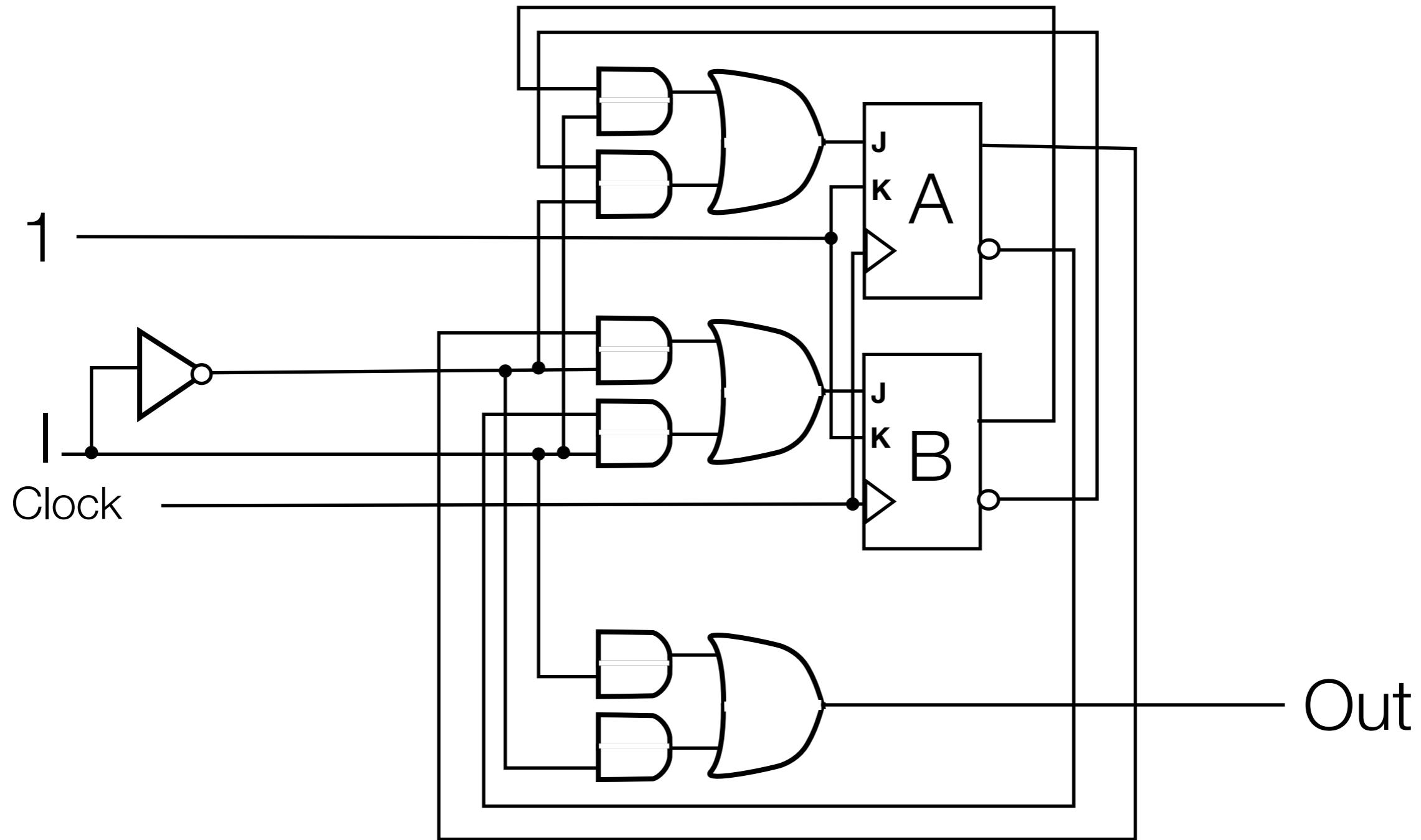


In class exercise: design a 3-bit counter

Moore machine

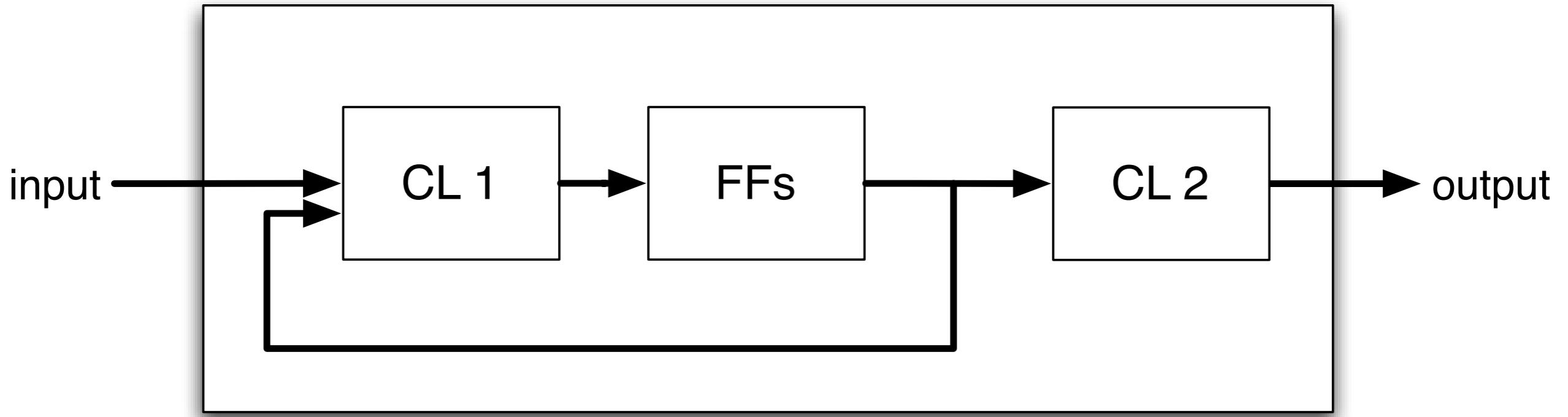


a circuit in which the output depends only on the current state

Mealy machine

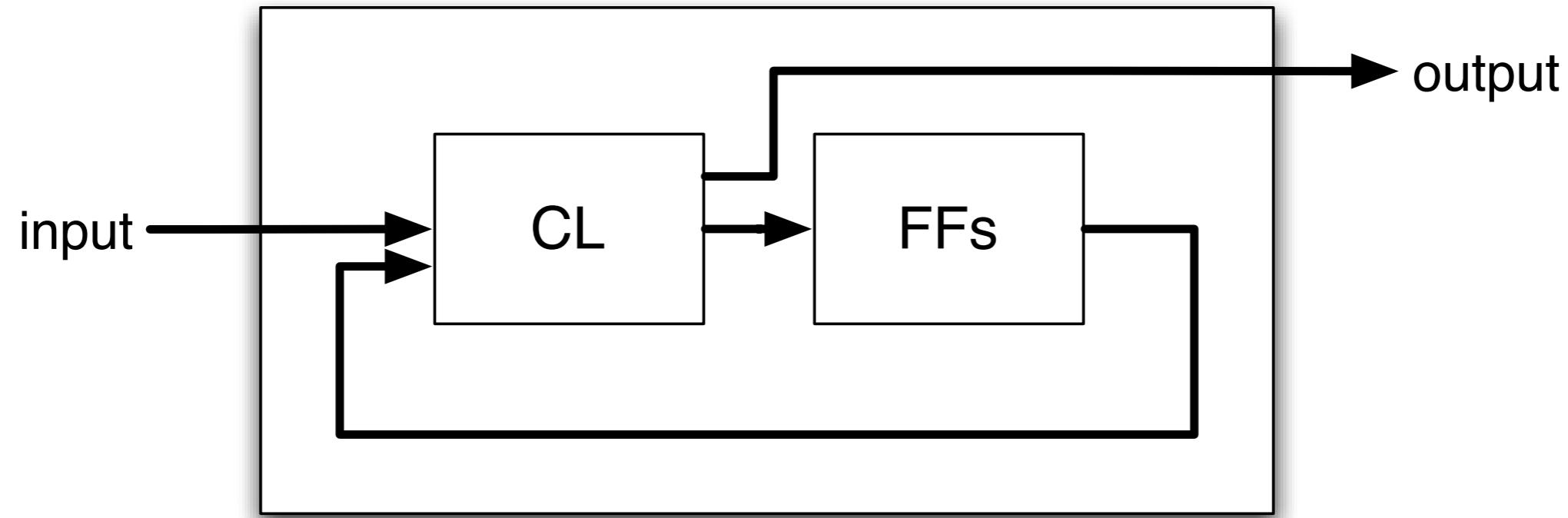


a circuit in which the outputs depend on the inputs as well as the current state

A Mealy or Moore circuit?

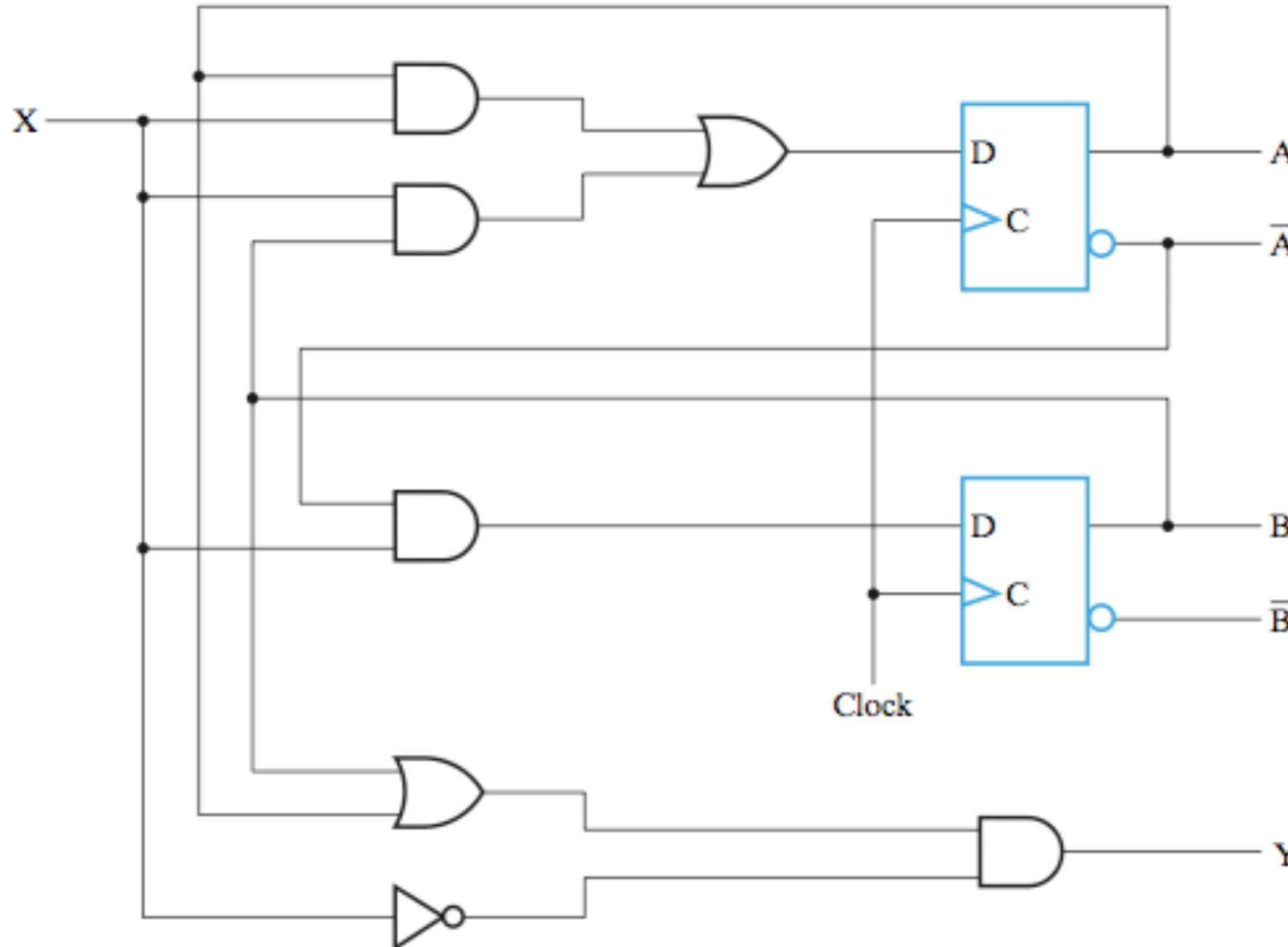

An example Moore circuit

5-16

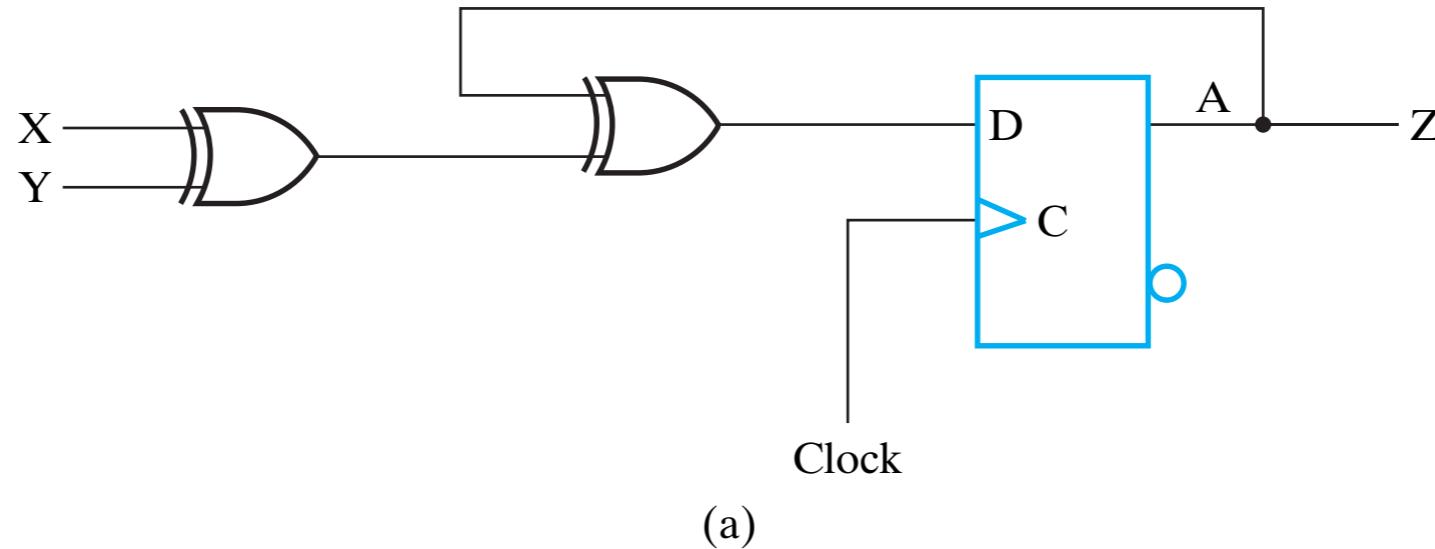


Present state		Next state		Output
A	X Y	A	Z	
0	0 0	0	0	0
0	0 1	1	1	0
0	1 0	1	0	0
0	1 1	0	0	0
1	0 0	1	1	1
1	0 1	0	1	1
1	1 0	0	1	1
1	1 1	1	1	1


(b) State table

FSM timing characteristics

MEALY

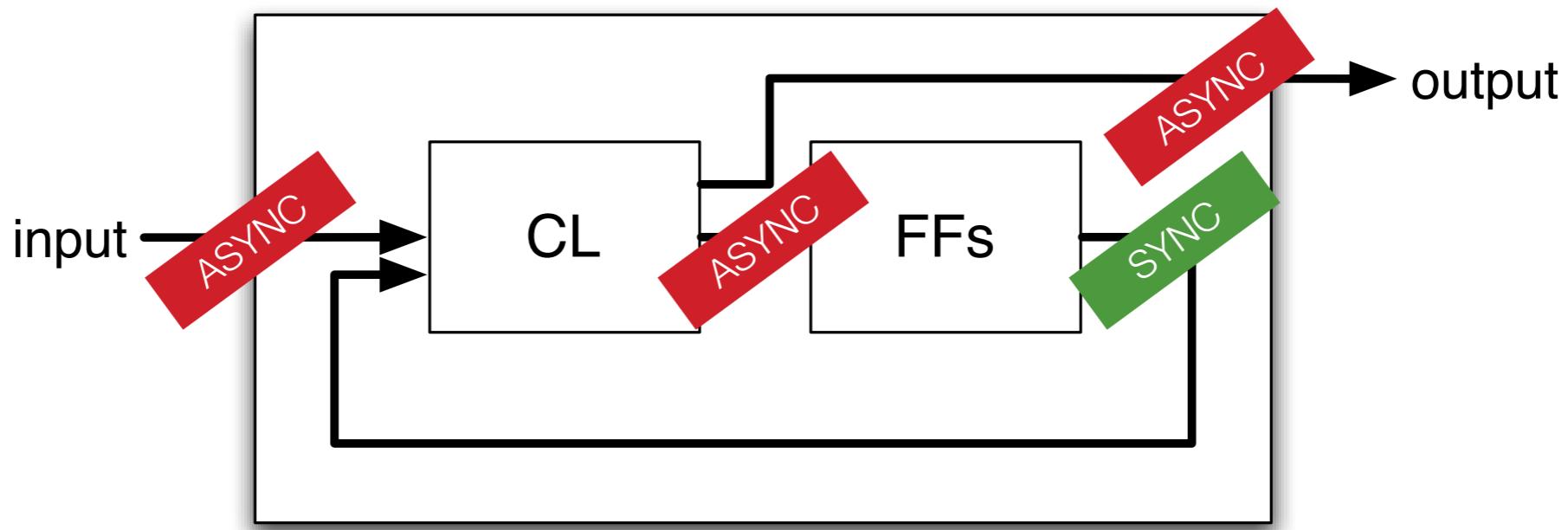

MOORE

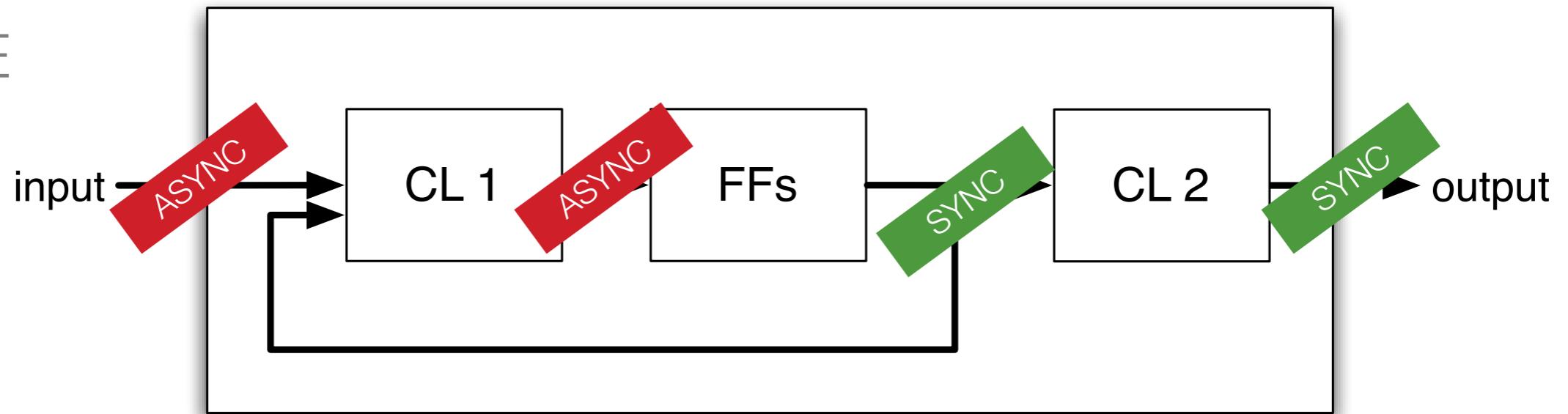

Advanced FSM design and implementation

Unused states: extra state encodings (e.g., using 3 FFs to represent 6 states leaves 2 unused states) can be treated as “don’t care” values and used to simplify the combinational logic

State minimization: two states are equivalent if they transition to the same or equivalent states on the same inputs (while producing the same outputs in the case of a Mealy machine)