

# CSEE 3827: Fundamentals of Computer Systems

---

Boolean Logic & Boolean Algebra

# Agenda (M&K 2.1-2.2, 2.8-2.9)

---

- Terminology
- Boolean algebra
- Logic gates
- Circuit fabrication
  - NAND, NOR
- DUAL
- XOR

# Terminology

---

- **Digital / Binary / Boolean**: 0 = False, 1 = True
- Binary **Variable**: a symbolic representation of a value that might be 0 or 1, e.g., X, Y, A, B
- **Complement** (e.g., of a variable X): written  $\bar{X}$ : the opposite value of X

X	$\bar{X}$
0	1
1	0

- **Literal**: a boolean variable or its complement (e.g., X,  $\bar{X}$ ,  $\bar{Y}$ )

# Boolean Logic

---

- All logical functions can be implemented in terms of three logical operations:

NOT

x	$\bar{x}$
0	1
1	0

AND

can omit the "."

x	y	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

OR

x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

# Boolean Logic 2

---

- Precedence rules just like decimal system
- Implied precedence: NOT > AND > OR
- Use parentheses as necessary

$$AB + C = (AB) + C$$

$$(\overline{A} + B)C = ((\overline{A} + B)C)$$

# Terminology cont'd

---

- **Expression**: a set of literals (possibly with repeats) combined with logic operations (and possibly ordered by parentheses)

- e.g., 4 expressions:  $AB + C$ ,  $(AB) + C$ ,  $(\overline{A} + B)C$ ,  $((\overline{A}) + B)C$

- Note: can compliment expressions, too, e.g.,  $\overline{((\overline{A}) + B)C}$

- **Equation**: expression1 = expression2

- e.g.,  $\overline{(\overline{A} + B)C} = ((\overline{A}) + B)C$

- **Function** of (possibly several) variables: an equation where the lefthand side is defined by the righthand side

$$F(A,B,C) = ((\overline{A}) + B)C$$

# Boolean Logic: Example

---

*Truth Table: all combinations of input variables*

*k variables  $\rightarrow 2^k$  input combinations*

D	X	A	$\overline{DX} + A$
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

# Boolean Logic: Example 2

---

X	Y	$XY + \overline{\overline{X}}\overline{\overline{Y}}$
0	0	
0	1	
1	0	
1	1	



# Boolean Algebra: Identities and Theorems

OR	AND	NOT	
$X+0 = X$	$X1 = X$		(identity)
$X+1 = 1$	$X0 = 0$		(null)
$X+X = X$	$XX = X$		(idempotent)
$X+\overline{X} = 1$	$X\overline{X} = 0$		(complementarity)
		$\overline{\overline{X}} = X$	(involution)
$X+Y = Y+X$	$XY = YX$		(commutativity)
$X+(Y+Z) = (X+Y)+Z$	$X(YZ) = (XY)Z$		(associativity)
$X(Y+Z) = XY + XZ$	$X+YZ = (X+Y)(X+Z)$		(distributive)
$\overline{X+Y} = \overline{X}\overline{Y}$	$\overline{XY} = \overline{X} + \overline{Y}$		(DeMorgan's theorem)

# Boolean Algebra: Example

---

*Simplify this equation using algebraic manipulation.*

$$F = \bar{X}YZ + \bar{X}Y\bar{Z} + XZ$$

# Boolean Algebra: Example 2

---

*Find the complement of F.*

$$F = A\bar{B} + \bar{A}B$$

$$\bar{F} =$$

# DeMorgan's Theorem

---

- Procedure for complementing expressions
- Remove the “big bar” over AND or OR of 2 (or more) functions (e.g., F & G) and replace...
  - AND with OR, OR with AND
  - 1 with 0, 0 with 1
  - function F with  $\bar{F}$ ,  $\bar{F}$  with F

$$\overline{FG} = \bar{F} + \bar{G}$$

$$\overline{F + G} = \bar{F}\bar{G}$$







# DeMorgan's Practice

---

$$\overline{\overline{ABC} + \overline{ACD} + B\overline{C}}$$
      
# Circuit Representation

- Information flows from left to right
- Input(s) all the way on the left, output(s) on the right



These circuits consume area, power, and time

Goal: minimize the amount of circuitry to compute the desired function

We simplify to reduce required circuitry...

---

$$F = \bar{X}YZ + \bar{X}Y\bar{Z} + XZ$$


$$\bar{X}Y(Z + \bar{Z}) + XZ \quad (\text{by reverse distribution})$$

$$\bar{X}Y1 + XZ \quad (\text{by complementarity})$$


$$\bar{X}Y + XZ \quad (\text{by identity})$$
 
# Circuit view

wire connector: black dot signifies wires are connected



 (a)  $F = \bar{X}YZ + \bar{X}Y\bar{Z} + XZ$



(b)  $F = \bar{X}Y + XZ$



# Universal gates: NAND, NOR


---

x	y	$z = \overline{xy}$
0	0	1
0	1	1
1	0	1
1	1	0



Note: the “o” in a circuit represents a NOT (inverter)

x	y	$z = \overline{x+y}$
0	0	1
0	1	0
1	0	0
1	1	0

 

Different from “●” which represents wire connector

# NAND and NOR universal because...

---

- NOT, AND, OR can each be implemented using only NAND gates
- NOT, AND, OR can each be implemented using only NOR gates

$\bar{A} = A \text{ NAND } A$	$\bar{A} = A \text{ NOR } A$
$AB = \overline{A \text{ NAND } B}$	$A+B = \overline{A \text{ NOR } B}$
$A+B = \bar{A} \text{ NAND } \bar{B}$	$AB = \bar{A} \text{ NOR } \bar{B}$

# Duals

---

# Duals

---

- All boolean expressions have duals
- Any theorem you can prove, you can also prove for its dual
- To form a dual...
  - replace AND with OR, OR with AND
  - replace 1 with 0, 0 with 1


What is the dual of this theorem?

---

$$\overline{X} + \overline{Y} = \overline{XY}$$

# Duals and Complements

---

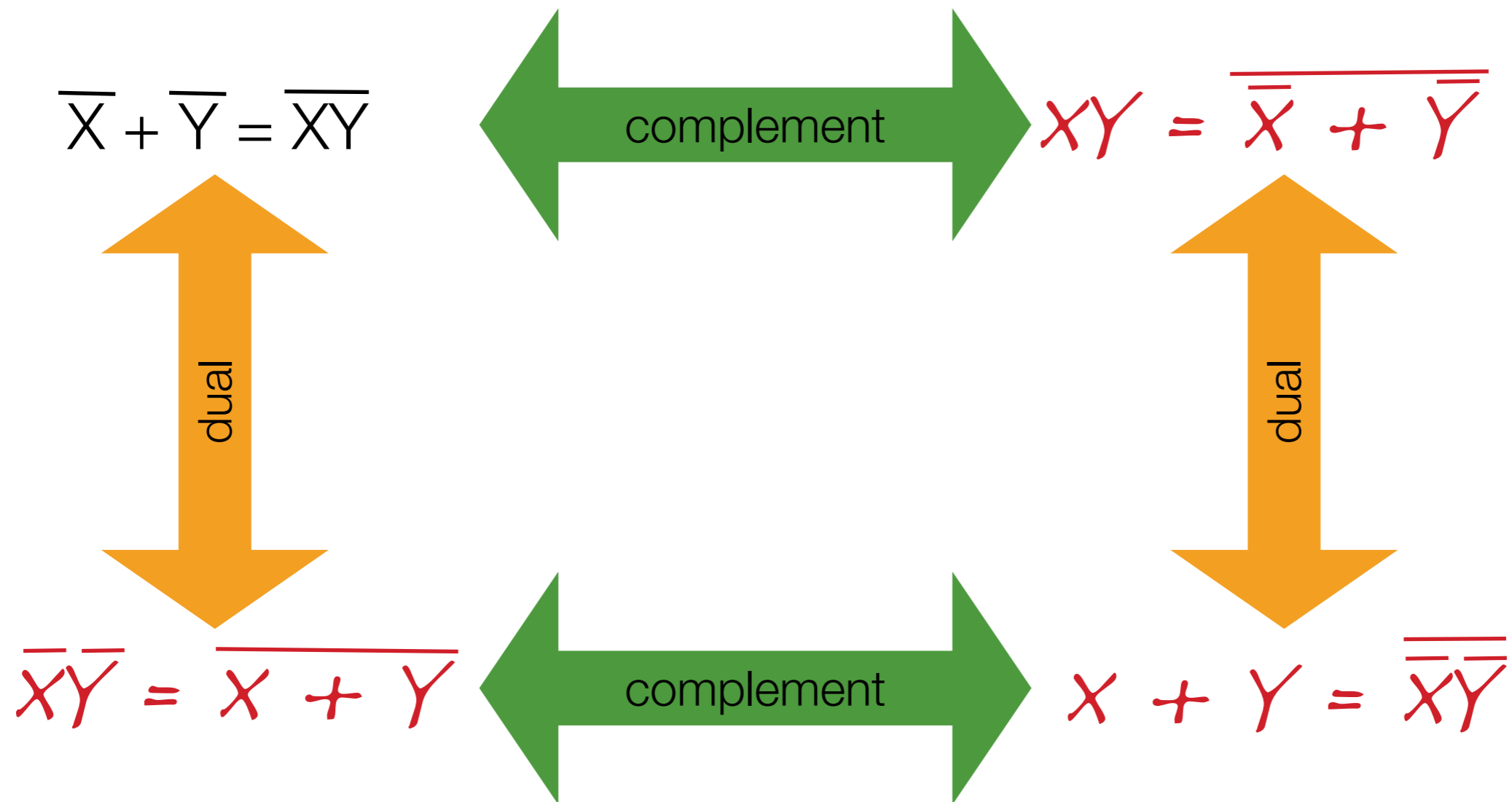

*Note: to complement a function, compute its dual and complement literals*

# “Complement using Dual” example


---

$$F = X + A (Z + \bar{X} (Y + W) + \bar{Y} (Z + W))$$


Can be used for gate manipulation.

---

 
$$\overline{X} + \overline{Y} = \overline{XY}$$



 
$$XY = \overline{\overline{X} + \overline{Y}}$$


 
$$\overline{\overline{X} \overline{Y}} = \overline{X + Y}$$


 
$$X + Y = \overline{\overline{X} \overline{Y}}$$








    
# Converting circuits to all-NAND (or all-NOR)


---

- Work from right to left
- When manipulating an (AND or OR) gate, stick in pairs of NOT gates to get it in “appropriate” form
- Isolated NOT gates are easily implemented as a NAND (NOR) gate
- example manipulations (for NAND gates)





# Convert-to-all-NAND example

---

 

# Convert-to-all-NAND example

---

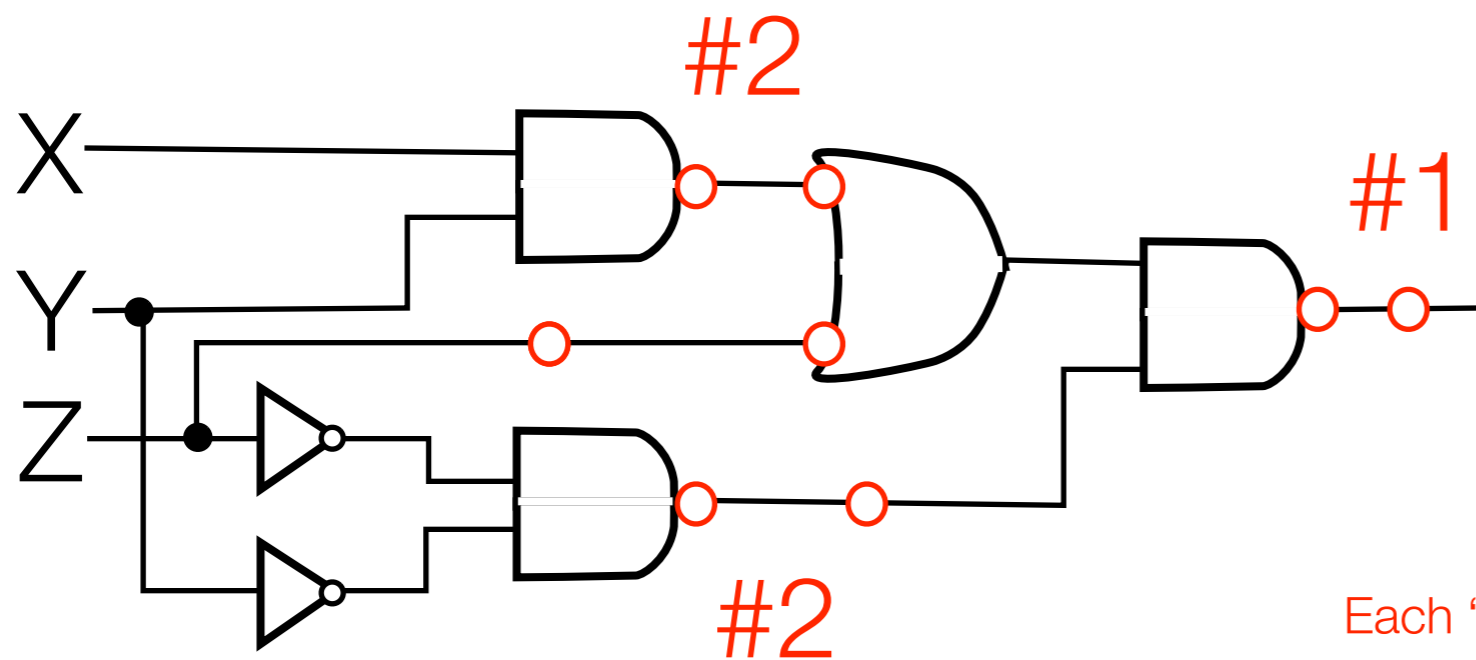 

Each "o" by itself represents a NOT gate

# XOR: the parity operation

---

- $X \oplus Y = X\bar{Y} + \bar{X}Y$

X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

- In general, represents parity, i.e.,

- $X_1 \oplus X_2 \oplus X_3 \oplus \dots \oplus X_k = 1$  when an odd number of  $X_i = 1$