

Complete the following problems. Be sure to show your work for partial credit.

1. A two-bit wide, 2:1 mux selects between two inputs, A and B, each of which is two bits wide, placing one of the inputs onto the two bit output C. Given this interface (IN: A_1, A_0, B_1, B_0, S , OUT: C_1, C_0), draw a circuit implementing such a mux.
2. Show how $F(ABC) = \Sigma m(0, 2, 6, 7)$ can be implemented using
 - (a) an 8:1 mux
 - (b) a 4:1 mux
3. In this problem you are going to design an RNA translation circuit. In biology, RNA translation is the process through which trios of nucleotides (also called codons) from a strand of RNA are translated into the corresponding amino acid. We have decomposed the translation into three component steps, followed by a final assembly of each of the component modules. To implement each module, you may either draw a circuit or give the boolean expressions for the circuitry. For our and your sakes, please pick reasonably natural notations.
 - (a) **BP_DEC (Base Pair Decoder)**: The BP_DEC module has a two bit input I_1, I_0 and four bits of output A, C, G, U . The two bits encode one of four possible base pairs, according to the following code:

I_1	I_0	A	C	G	U
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Give an implementation for BP_DEC. You may use any of the modules we've discussed in class in your design.

- (b) Trios of base pairs (or codons) can be interpreted as codewords for particular amino acids. The table below shows the codon to amino acid mappings. Note that (1) the code is redundant, i.e., there are 4^3 possible codons, but only 20 amino acids, meaning multiple codons code for the same amino acid, and (2) in addition to the amino acids, there are special Stop codons which terminate the string of amino acids that forms a protein.

Next implement the **CODON_CODE (Codon Code)** module which takes in a trio of base pairs as twelve bits of input ($First_A, First_C, First_G, First_U, Second_A, Second_C, Second_G, Second_U, Third_A, Third_C, Third_G, Third_U$) and produces twenty one bits of output ($Phe, Leu, Ile, Met, Val, Ser, Pro, Thr, Ala, Tyr, Stop, His, Gln, Asn, Lys, Asp, Glu, Cys, Trp, Arg, Gly$). As above, implement CODON_CODE. Please do not give a minterm expansion, but instead simplify where possible. The structure of the table below that shows the mapping from codon to amino acid should provide some hints.

- (c) **AA_ENC (Amino acid encoder)**: This module takes twenty one bits in with one bit per amino acid plus one for the *Stop* (the same twenty one signals that are generated by the CODON_CODE module) and produces five bits of encoded output (A_4, A_3, A_2, A_1, A_0), where $Phe = 00000, Leu = 00001, Ile = 00010, Met = 00011, \dots, Arg = 10011, Gly = 10100$.

		Second Position				
		U	C	A	G	
First Position	U	UUU } Phe	UCU } Ser	UAU } Tyr	UGU } Cys	U
		UUC } Phe	UCC } Ser	UAC } Tyr	UGC } Cys	C
		UUA } Leu	UCA } Ser	UAA } Stop	UGA } Stop	A
		UUG } Leu	UCG } Ser	UAG } Stop	UGG } Trp	G
	C	CUU } Leu	CCU } Pro	CAU } His	CGU } Arg	U
		CUC } Leu	CCC } Pro	CAC } His	CGC } Arg	C
		CUA } Leu	CCA } Pro	CAA } Gln	CGA } Arg	A
		CUG } Leu	CCG } Pro	CAG } Gln	CGG } Arg	G
	A	AUU } Ile	ACU } Thr	AAU } Asn	AGU } Ser	U
		AUC } Ile	ACC } Thr	AAC } Asn	AGC } Ser	C
		AUA } Ile	ACA } Thr	AAA } Lys	AGA } Arg	A
		AUG } Met	ACG } Thr	AAG } Lys	AGG } Arg	G
	G	GUU } Val	GCU } Ala	GAU } Asp	GGU } Gly	U
		GUC } Val	GCC } Ala	GAC } Asp	GGC } Gly	C
		GUA } Val	GCA } Ala	GAA } Glu	GGA } Gly	A
		GUG } Val	GCG } Ala	GAG } Glu	GGG } Gly	G

- (d) Finally, show how BP_DEC, CODON_CODE, and AA_ENC can be used to implement RNA_TRANSLATE, which translates six bits of input describing a codon (i.e., the two bit code for each of three base pairs: $I_1, I_0, J_1, J_0, K_1, K_0$) into five bits indicating the corresponding amino acid or stop code.