

# CSEE 3827: Fundamentals of Computer Systems

Midterm Exam

March 9, 2011

## SOLUTIONS

**Read all of the following information before starting the exam:**

- Be sure to write your name on each page of the exam.
- Use the exam itself for your solutions (no blue books or spare sheets of paper). You may use the backside of pages if you need more space.
- Show your work in order to earn partial credit.
- You may use your textbook and class notes, but *absolutely no electronic devices (laptops, cell phones, etc.)*
- Good luck!

Problem	Point Value	Points Earned
1	12	
2	10	
3	8	
4	10	
5	10	
<b>Total</b>	50	

1. (12 points) Salt and pepper.

(a) (2 points) Prove algebraically that  $BC + AB + \overline{A}B = B$ .

- $BC + AB + \overline{A}B$
- $B(C + A + \overline{A})$
- $B(C + 1)$
- $B(1)$
- $B$

(b) (4 points) Draw a schematic for a *minimal* circuit that uses only *and*, *or*, and *not* gates that performs the two's complement operation on a four bit input value. Let the input be  $X_{3:0}$  and the output be  $Y_{3:0}$ .




$X_3$	$X_2$	$X_1$	$X_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	0	0	0
0	0	0	1	1	1	1	1
0	0	1	0	1	1	1	0
0	0	1	1	1	1	0	1
0	1	0	0	1	1	0	0
0	1	0	1	1	0	1	1
0	1	1	0	1	0	1	0
0	1	1	1	1	0	0	1
1	0	0	0	1	0	0	0
1	0	0	1	1	1	1	1
1	0	1	0	0	1	1	0
1	0	1	1	0	1	0	1
1	1	0	0	0	1	0	0
1	1	0	1	0	0	1	1
1	1	1	0	0	0	1	0
1	1	1	1	0	0	0	1

$$Y_3 = \overline{X_3} \cdot X_2 + \overline{X_3} \cdot X_0 + \overline{X_3} \cdot X_1 + X_3 \cdot \overline{X_2} \cdot \overline{X_1} \cdot \overline{X_0}$$

$$Y_2 = X_2 \cdot \overline{X_1} \cdot \overline{X_0} + X_0 \cdot \overline{X_2} + X_1 \cdot \overline{X_2}$$

$$Y_1 = \overline{X_1} \cdot X_0 + X_1 \cdot \overline{X_0}$$

$$Y_0 = X_0$$

   




2. (10 points) Design a 32-bit ALU (arithmetic logic unit) which computes either  $+$ ,  $-$ ,  $\times$ ,  $\div$  of two 32-bit values  $A$  and  $B$  putting the result on 32-bit output  $C$ . You may assume the presence of existing a 32-bit adder, subtractor, multiplier, and divider, and you may incorporate them in your design as black boxes. The particular operation is controlled by an additional two bit input  $S$ , where

*NB: In addition to the arithmetic modules, you may incorporate muxes, decoders, and other standard components as you find helpful.*

- if  $S = 00$ ,  $C = A + B$
- if  $S = 01$ ,  $C = A - B$
- if  $S = 10$ ,  $C = A \times B$
- if  $S = 11$ ,  $C = A \div B$

 
- (a) Draw a schematic for your ALU design.
- (b) Give an expression for the propagation delay ( $TP_{ALU}$ ) and contamination delay ( $TC_{ALU}$ ) of your ALU, in terms of the propagation and contamination delays of the sub-modules. For example,  $TP_+$  is the propagation delay of the adder, and  $TC_{MUX}$  is the contamination delay of a mux.




$$TP_{ALU} = \max(TP_+, TP_-, TP_\times, TP_\div) + TP_{MUX}$$

$$TC_{ALU} = \min(TC_+, TC_-, TC_\times, TC_\div) + TC_{MUX}$$

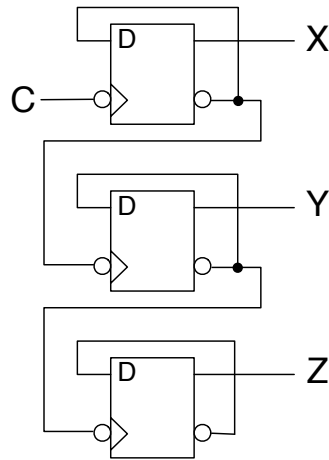3. (8 points) Examine the circuit below. Note that these D flip-flops are negative, or falling, edge triggered.



 - (a) Complete the following timing diagram. You may assume wires and gates have zero delay (i.e., all transitions are instantaneous), and that at the start  $X = Y = Z = 0$ .




- (b) Describe conceptually what this circuit does.  
This is a 3-bit up-counter.

4. (10 points) Use D flip-flops and basic combinational gates (AND, OR, NOT) to design the following counter/pseudorandom number generator. The circuit has a CLK and RST and one control input  $x$ . It provides a three bit output indicating the numeric output  $N_{2:0}$ . When  $x = 0$ , the circuit should operate a binary up-counter. Otherwise, it should operate as a pseudorandom number generator according to the following function table.

NB: While your design must use only the primitive elements listed above, it need not be minimal.

Present State	Next State	
	Binary Up-Counter ( $x = 0$ )	Pseudorandom No. Gen. ( $x = 1$ )
0	1	5
1	2	6
2	3	4
3	4	0
4	5	3
5	6	1
6	7	7
7	0	2

 

(unlabeled edges transition on  $x$ )


- Use 8 D flipflops, with a one hot state encoding (i.e., state  $i \Leftrightarrow Q_i$ )
- Next state logic
  - $D_0 = \bar{x}Q_7 + xQ_3 + RST$
  - $D_1 = \bar{x}Q_0 + xQ_5$
  - $D_2 = \bar{x}Q_1 + xQ_7$
  - $D_3 = \bar{x}Q_2 + xQ_4$
  - $D_4 = \bar{x}Q_3 + xQ_2$
  - $D_5 = \bar{x}Q_4 + xQ_0$
  - $D_6 = \bar{x}Q_5 + xQ_1$
  - $D_7 = \bar{x}Q_6 + xQ_6$
- Output logic
  - $N_2 = Q_4 + Q_5 + Q_6 + Q_7$
  - $N_1 = Q_2 + Q_3 + Q_6 + Q_7$
  - $N_0 = Q_1 + Q_3 + Q_5 + Q_7$

5. (10 points) Give a state transition diagram for a *Message Transmission Controller* Mealy Machine. Messages are broken into four packets for transmission, so sending a message amounts to sending packet 0, packet 1, packet 2, and packet 3. The sender must receive an acknowledgement of packet  $i$  before transmitting packet  $i + 1$ .

*NB: You need only provide the state transition diagram, no implementation necessary.*

The Message Transmission controller has the following interface:

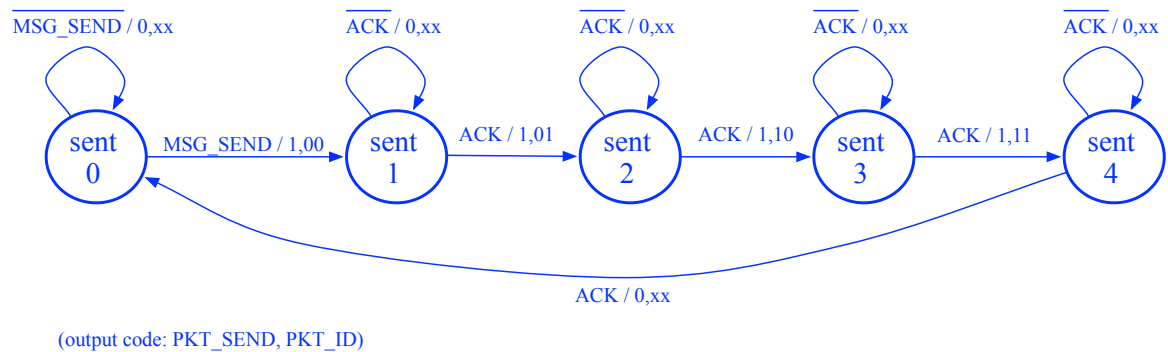- Inputs:
  - **MSG\_SEND**: 1 bit signal that initiates the transmission of the four packets that comprise the message
  - **PKT\_ACK**: 1 bit signal acknowledging receipt of the previous packet
- Outputs:
  - **PKT\_SEND**: 1 bit signal that initiates the transmission of a packet
  - **PKT\_ID**: 2 bits indicating which packet is to be sent



(Scratch space.)