

CSEE 3827: Fundamentals of Computer Systems, Spring 2011

3. Combinational Circuit Design

Prof. Martha Kim (martha@cs.columbia.edu)

Web: <http://www.cs.columbia.edu/~martha/courses/3827/sp11/>

Outline (H&H 2.8, 5.2)

- Standard combinational circuits
 - Decoder
 - Encoder / priority encoder (bonus, not in text)
 - Code converter (bonus, not in text)
 - Multiplexer
- Addition
 - Half and full adders
 - Ripple carry adder
 - Carry lookahead adder
- Subtraction
- Comparator (“!=” in lecture, “<” in text)
- ALU (in text, not covering yet)
- Shifter

Combinational circuits


- Combinational circuits are stateless
- The outputs are functions only of the inputs




Hierarchical design

3-4

"Big" Circuit

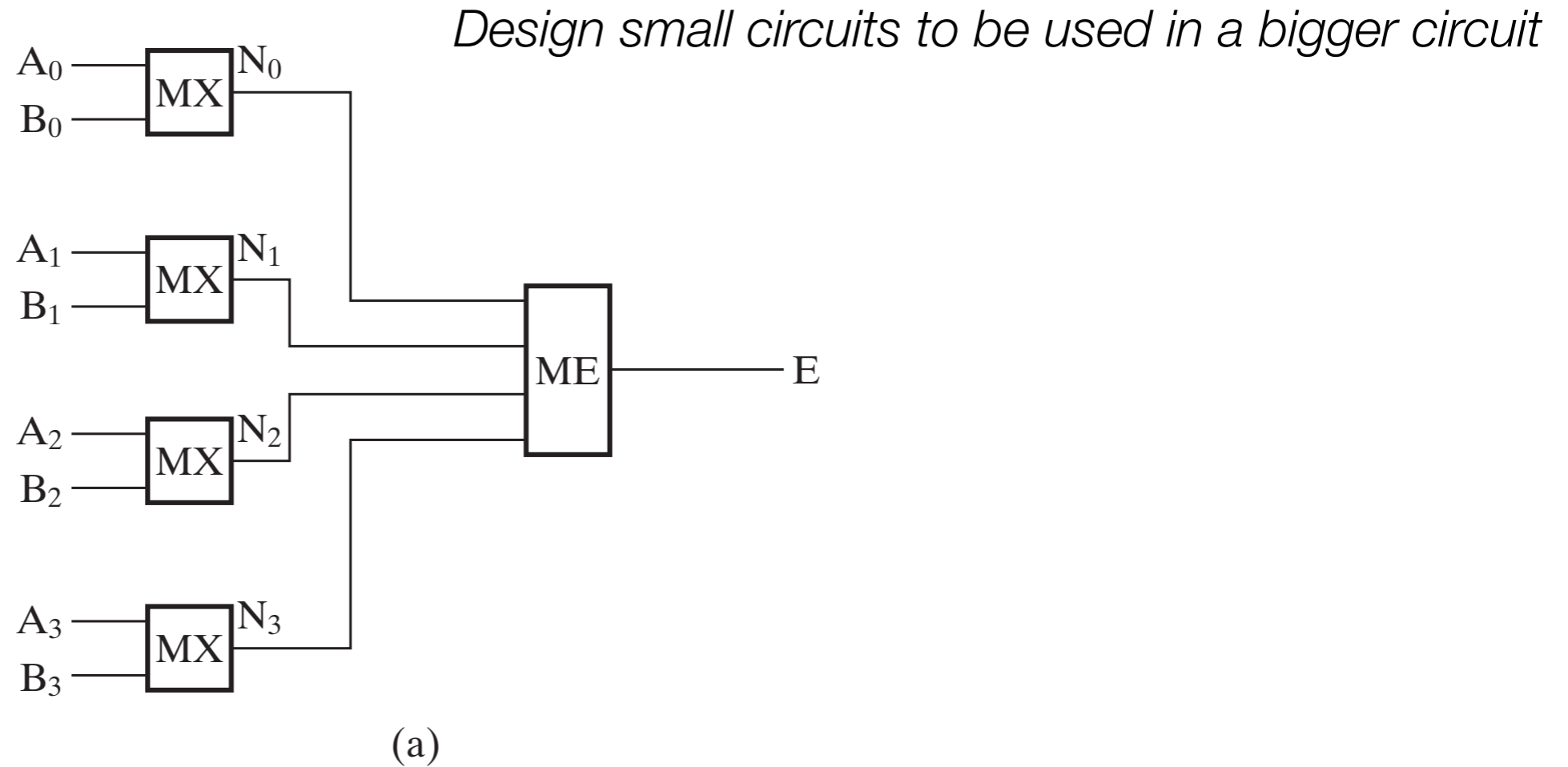


Smaller Circuits

 


Hierarchical design (It's a comparator!)

3-4

(4-bit equality comparator)

 

(a)

 


(b)

(c)

Enabler circuits


3-15

 Output is “enabled” ($F=A$) only when input ‘ENABLE’ signal is asserted ($EN=1$)



(a)

| EN | F |
|----|---|
| 0 | 0 |
| 1 | A |

 


(b)

| EN | F |
|----|---|
| 0 | 1 |
| 1 | A |

Decoder-based circuits

 
Converts n -bit input to m -bit output, where $n \leq m \leq 2^n$



*“Standard” Decoder: i^{th} output = 1, all others = 0,
where i is the binary representation of the input (ABC)*

Decoder-based circuits

 Converts n -bit input to m -bit output, where $n \leq m \leq 2^n$



e.g., $ABC = 101$ ($i=5$)


“Standard” Decoder: i^{th} output = 1, all others = 0,
where i is the binary representation of the input (ABC)

Internal design of 1:2 decoder

3-17

| A | D₀ | D₁ |
|----------|----------------------|----------------------|
| 0 | 1 | 0 |
| 1 | 0 | 1 |

(a)

 


(b)

Internal design of 2:4 decoder

3-18


| A_1 | A_0 | D_0 | D_1 | D_2 | D_3 |
|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |

(a)

 


(b)

Hierarchical design of 2:4 decoder

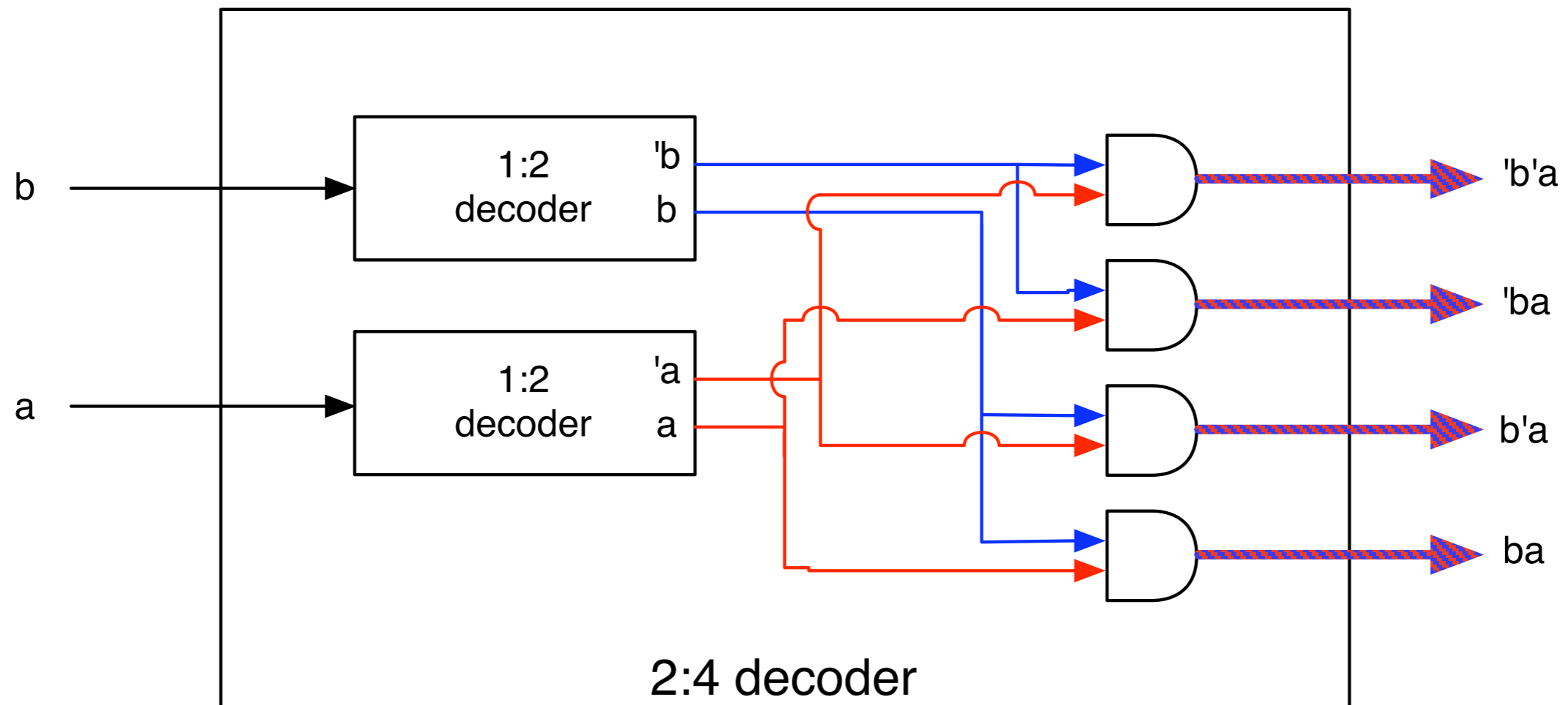

*Can build 2:4 decoder out of two 1:2 decoders
(and some additional circuitry)*

Hierarchical design of 3:8 decoder

 

Encoders

T 3-7

Inverse of a decoder: converts m -bit input to n -bit output, where $n \leq m \leq 2^n$


TABLE 3-7
Truth Table for Octal-to-Binary Encoder

| Inputs | | | | | | | | Outputs | | |
|--------|-------|-------|-------|-------|-------|-------|-------|---------|-------|-------|
| D_7 | D_6 | D_5 | D_4 | D_3 | D_2 | D_1 | D_0 | A_2 | A_1 | A_0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 |

Decoder and encoder summary




| BCD values | | | One-hot encoding | | | | | | | | |
|------------|---|---|------------------|---|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |

 


Note: for Encoders - input is assumed to have just one 1, the rest 0's

In class design: priority encoder

 A priority encoder takes **2^n bit input (I)** and produces **n bits of output (K)** indicating in BCD the position of the most significant 1 on the input.




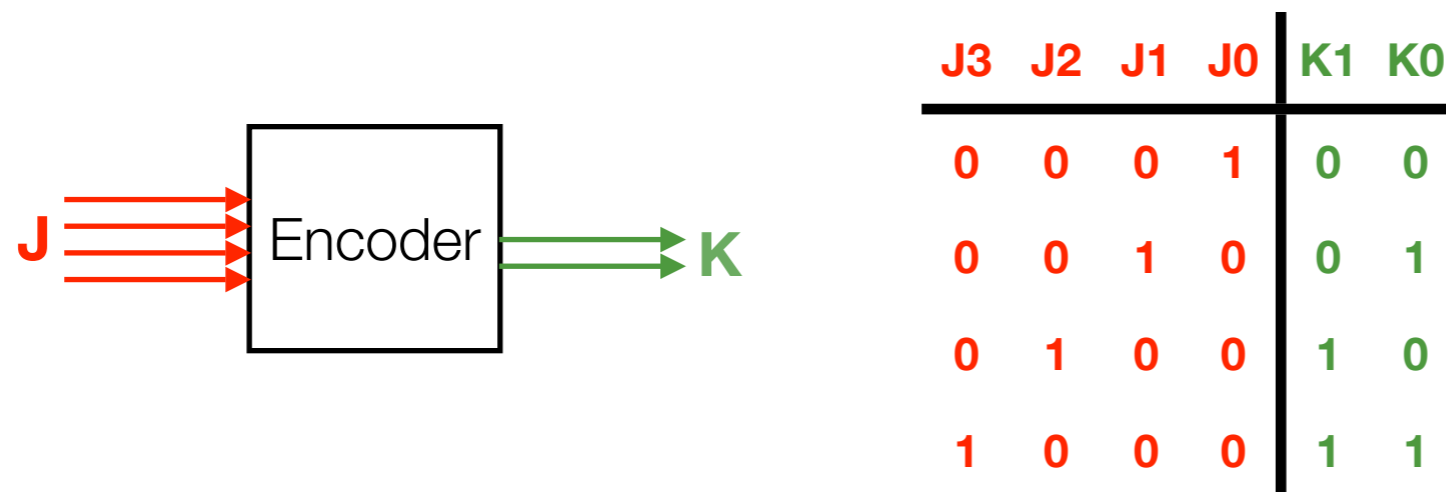We will leverage a regular encoder which takes **2^n bit one-hot encoded input (J)** and produces **n bits of output (K)** indicating in BCD the position of the 1 on the input.



In class design: priority encoder (2)

 This gets us part of the way there, leaving us with a simpler problem of translating **I** into **J**:



| I ₃ | I ₂ | I ₁ | I ₀ | J ₃ | J ₂ | J ₁ | J ₀ |
|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | x | 0 | 0 | 1 | 0 |
| 0 | 1 | x | x | 0 | 1 | 0 | 0 |
| 1 | x | x | x | 1 | 0 | 0 | 0 |

NB: An input $i = x$ is still a don't care, it means "for all possible values of i ". So here input $1xxx$ means any 4-bit input starting with a 1, i.e., 1000, 1001, 1010, 1011, 1100, ...

From inspection of the truth table we can see the following definitions of J_x . Could also have used k -maps.

$$J_3 = I_3$$


$$J_2 = I_2 \bar{I}_3$$

$$J_1 = I_1 \bar{I}_2 \bar{I}_3$$

$$J_0 = I_0 \bar{I}_1 \bar{I}_2 \bar{I}_3$$

General code conversion

3-3

 


(a) Segment designation



(b) Numeric designation for display


Code conversion

 

Input Output

| Va | W | X | Y | Z | a | b | c | d | e | f | g |
|----|---|---|---|---|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 2 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| 3 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 1 |
| 4 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 5 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |
| 6 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 7 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |
| 8 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 9 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 1 |
| X | 1 | 0 | 1 | 0 | X | X | X | X | X | X | X |
| X | 1 | 0 | 1 | 1 | X | X | X | X | X | X | X |
| X | 1 | 1 | 0 | 0 | X | X | X | X | X | X | X |
| X | 1 | 1 | 0 | 1 | X | X | X | X | X | X | X |
| X | 1 | 1 | 1 | 0 | X | X | X | X | X | X | X |
| X | 1 | 1 | 1 | 1 | X | X | X | X | X | X | X |


Code conversion

 


e.g., what outputs
“lights up” when input
 $V=4$?

| Input | | | | | Output | | | | | | |
|-------|---|---|---|---|--------|---|---|---|---|---|---|
| Va | W | X | Y | Z | a | b | c | d | e | f | g |
| 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 2 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| 3 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 1 |
| 4 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 5 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |
| 6 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 7 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |
| 8 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 9 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 1 |
| X | 1 | 0 | 1 | 0 | X | X | X | X | X | X | X |
| X | 1 | 0 | 1 | 1 | X | X | X | X | X | X | X |
| X | 1 | 1 | 0 | 0 | X | X | X | X | X | X | X |
| X | 1 | 1 | 0 | 1 | X | X | X | X | X | X | X |
| X | 1 | 1 | 1 | 0 | X | X | X | X | X | X | X |
| X | 1 | 1 | 1 | 1 | X | X | X | X | X | X | X |

Code conversion

 


 For what values does output f "light up" for?




| Input | | | | | Output | | | | | | |
|-------|---|---|---|---|--------|---|---|---|---|---|---|
| Va | W | X | Y | Z | a | b | c | d | e | f | g |
| 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 2 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| 3 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 1 |
| 4 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 5 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |
| 6 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 7 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |
| 8 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 9 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 1 |
| X | 1 | 0 | 1 | 0 | X | X | X | X | X | X | X |
| X | 1 | 0 | 1 | 1 | X | X | X | X | X | X | X |
| X | 1 | 1 | 0 | 0 | X | X | X | X | X | X | X |
| X | 1 | 1 | 0 | 1 | X | X | X | X | X | X | X |
| X | 1 | 1 | 1 | 0 | X | X | X | X | X | X | X |
| X | 1 | 1 | 1 | 1 | X | X | X | X | X | X | X |

Algebra and Circuit for "f"

 

 
$$f = W + \bar{Y}\bar{Z} + X\bar{Z} + \bar{X}\bar{Y} = W + (X+\bar{Y})\bar{Z} + \bar{X}\bar{Y}$$



Multiplexers (or Muxes)

 - Combinational circuit that **selects** binary information from one of many input lines and directs it to one output line




n selection bits
indicate (in binary) which input feeds to the output

Multiplexers (or Muxes)


- Combinational circuit that **selects** binary information lines and directs it to one output line

2^n inputs

 

n selection bits

 indicate (in binary) which input feeds to the output




1 output

Internal mux organization


3-26

Selector Logic

 

Only 1 AND gate passes "1" through

Enabler logic

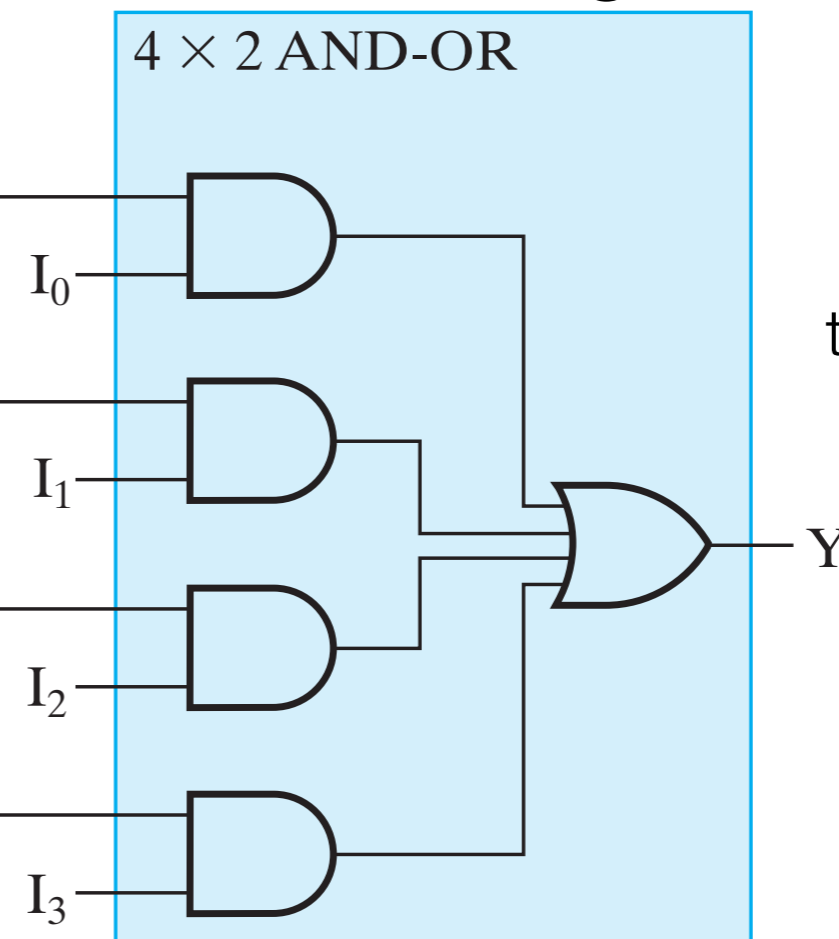


Or gate "passes through" the non-zeroed out I_i

AND gates "zero out" unselected I_i

In class exercise


How would you implement an 8:1 mux using two 4:1 muxes?

Multiplexer truth table

 


| 2^n inputs | | | | | | | | | n-bit BCD value | | | 1 output |
|--------------|---|---|---|---|---|---|---|---|-----------------|---|---|----------|
| a | x | x | x | x | x | x | x | x | 0 | 0 | 0 | a |
| x | b | x | x | x | x | x | x | x | 0 | 0 | 1 | b |
| x | x | c | x | x | x | x | x | x | 0 | 1 | 0 | c |
| x | x | x | d | x | x | x | x | x | 0 | 1 | 1 | d |
| x | x | x | x | e | x | x | x | x | 1 | 0 | 0 | e |
| x | x | x | x | x | f | x | x | x | 1 | 0 | 1 | f |
| x | x | x | x | x | x | x | g | x | 1 | 1 | 0 | g |
| x | x | x | x | x | x | x | x | h | 1 | 1 | 1 | h |

Demultiplexers (Demuxes)

 


| 1 input | n-bit BCD value | | | 2^n outputs | | | | | | | | | |
|----------|-----------------|---|---|---------------|----------|----------|----------|----------|----------|----------|----------|---|---|
| a | 0 | 0 | 0 | a | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| b | 0 | 0 | 1 | 0 | b | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| c | 0 | 1 | 0 | 0 | 0 | c | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| d | 0 | 1 | 1 | 0 | 0 | 0 | d | 0 | 0 | 0 | 0 | 0 | 0 |
| e | 1 | 0 | 0 | 0 | 0 | 0 | 0 | e | 0 | 0 | 0 | 0 | 0 |
| f | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | f | 0 | 0 | 0 | 0 |
| g | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | g | 0 | 0 | 0 |
| h | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | h | 0 | 0 |

 Muxes and demuxes called “steering logic”



“merge”


 


“fork”

Representing Functions with Decoders and MUXes

- e.g., $F = A\bar{C} + BC$


| A | B | C | minterm | F |
|---|---|---|-------------------------|---|
| 0 | 0 | 0 | $\bar{A}\bar{B}\bar{C}$ | 0 |
| 0 | 0 | 1 | $\bar{A}\bar{B}C$ | 0 |
| 0 | 1 | 0 | $\bar{A}B\bar{C}$ | 0 |
| 0 | 1 | 1 | $\bar{A}BC$ | 1 |
| 1 | 0 | 0 | $A\bar{B}\bar{C}$ | 1 |
| 1 | 0 | 1 | $A\bar{B}C$ | 0 |
| 1 | 1 | 0 | $AB\bar{C}$ | 1 |
| 1 | 1 | 1 | ABC | 1 |

  

- Decoder: OR minterms for which F should evaluate to 1
- MUX: Feed in the value of F for each minterm


A Slick MUX trick

 - Can use a smaller MUX with a little trick e.g., $F = AC + B\bar{C}$
- Note for rows paired below, A&B have same values, C iterates between 0&1
- For the pair of rows, F either equals 0, 1, C or \bar{C}



Slick MUX trick: Example 2

 - e.g., $F = \bar{A}C + \bar{B}\bar{C} + A\bar{C}$




Addition: The Half-Adder

- Addition of 2 bits: A & B produces a summand (S) and carry (C)

| A | B | S | C |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

$$S = A \oplus B$$

$$C = AB$$

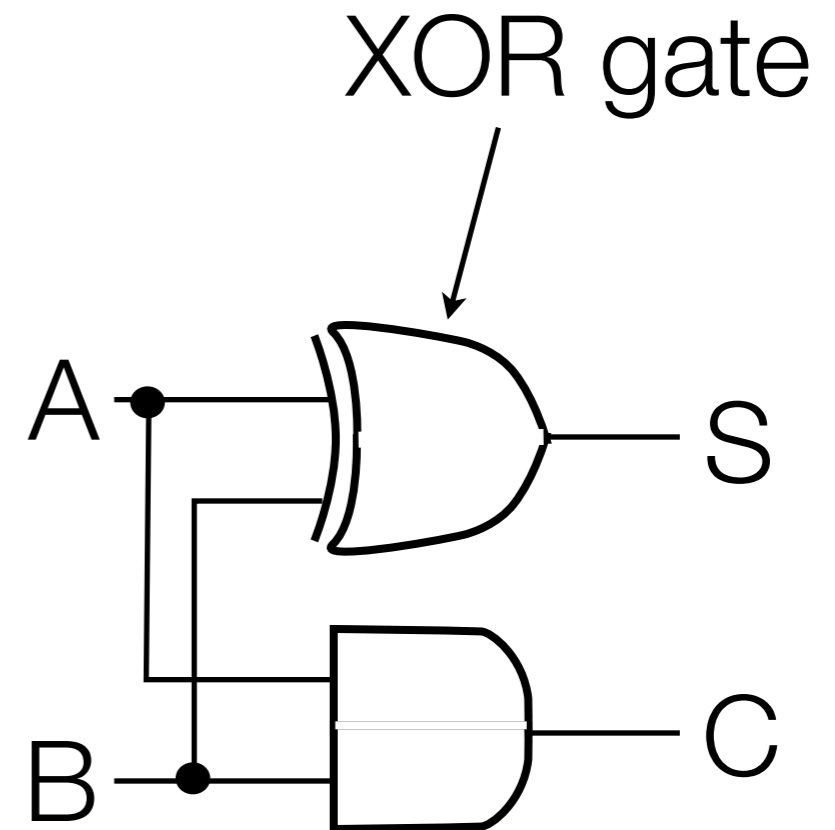

- But to do addition, we really need to add 3 bits at a time (to account for carries), e.g.,

$$\begin{array}{r} 011 \leftarrow \text{carry bits} \\ + 1011 \\ \underline{1001} \\ 10101 \end{array}$$

The Full Adder

- Takes as input 2 digits (A&B) and a previous carry (P)

| P | A | B | C | S |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

S:




| | B | | | |
|---|---|---|---|---|
| | 0 | 1 | 0 | 1 |
| P | 1 | 0 | 1 | 0 |
| | A | | | |

C:

| | B | | | |
|---|---|---|---|---|
| | 0 | 0 | 1 | 0 |
| P | 0 | 1 | 1 | 1 |
| | A | | | |


$$S = A \oplus B \oplus P$$

$$C = AB + AP + BP$$

   


5-bit ripple carry adder

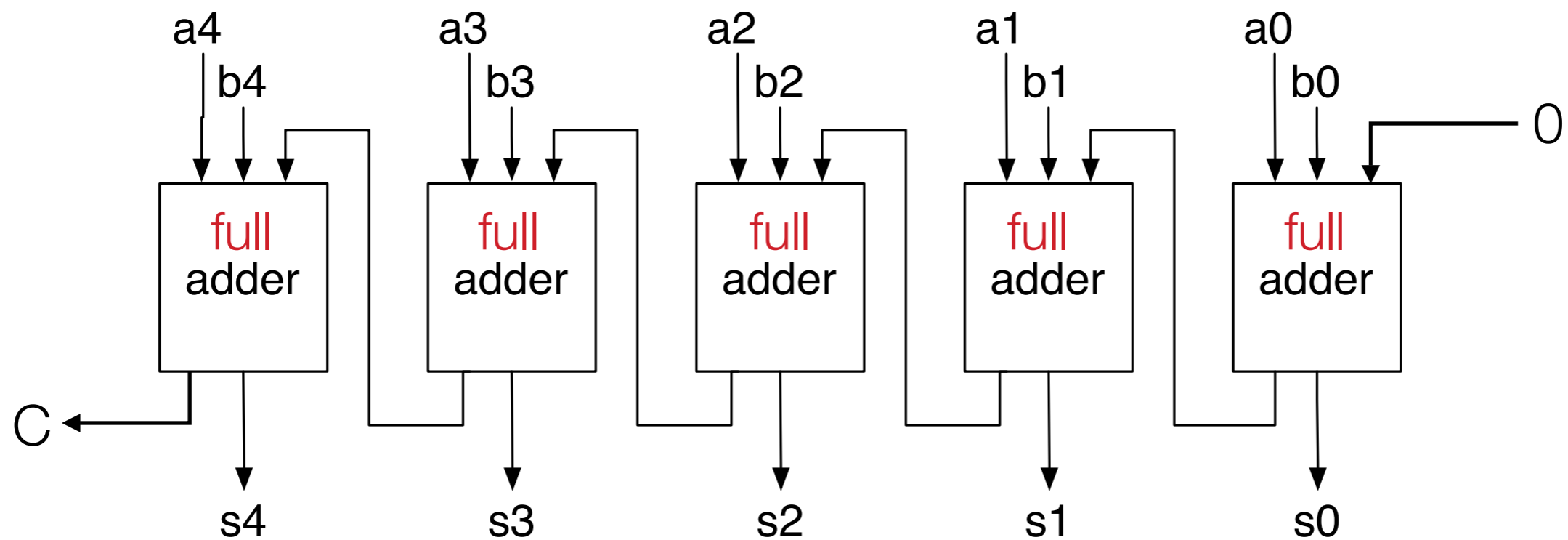Computes $a_4a_3a_2a_1a_0 + b_4b_3b_2b_1b_0$



- Note how computation “ripples” through adders from left to right
 - Each full adder’s has depth 2 (inputs pass through 2 gates to reach output)
 - Full adder that computes s_i cannot “start” its computation until previous full adder computes carry
 - The longest depth in a k-bit ripple carry adder is 2k

Handling overflow

 

~~$$\begin{array}{r}
 0111 \\
 (-5) \ 0101 \\
 (-3) \ 0011 \\
 \hline
 1000 \quad (-8)
 \end{array}$$~~

$$\begin{array}{r}
 1111 \\
 (-5) \ 1011 \\
 (-3) \ 1101 \\
 \hline
 1000 \quad (-8)
 \end{array}$$

~~$$\begin{array}{r}
 1000 \\
 (-6) \ 1010 \\
 (-3) \ 1101 \\
 \hline
 0111 \quad (7)
 \end{array}$$~~

$$\begin{array}{r}
 0010 \\
 (-6) \ 1010 \\
 (3) \ 0011 \\
 \hline
 1101 \quad (-3)
 \end{array}$$

Handling overflow

| | | | | |
|----|----|----|----|----|
| c4 | c3 | c2 | c1 | c0 |
| | a3 | a2 | a1 | a0 |
| | b3 | b2 | b1 | b0 |
| | s3 | s2 | s1 | s0 |

| a3 | b3 | c3 | c4 | s3 | overflow |
|----|----|----|----|----|----------|
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 | 0 |


sum of
two pos
is pos

sum of
two negs
is neg

n bit two's comp: -2^n
 $\langle \text{---} \rangle 2^n - 1$
 split into pos and neg
 ranges and find smallest
 and largest possible
 results. show that they're
 in range for twos comp.

Overflow computation in adder/subtractor

 For 2's complement, overflow if 2 most significant carries differ




= 0 then no overflow,

= 1 then overflow

Ripple-Carry adder circuit depth

$$A_3A_2A_1A_0 + B_3B_2B_1B_0 = S_3S_2S_1S_0$$

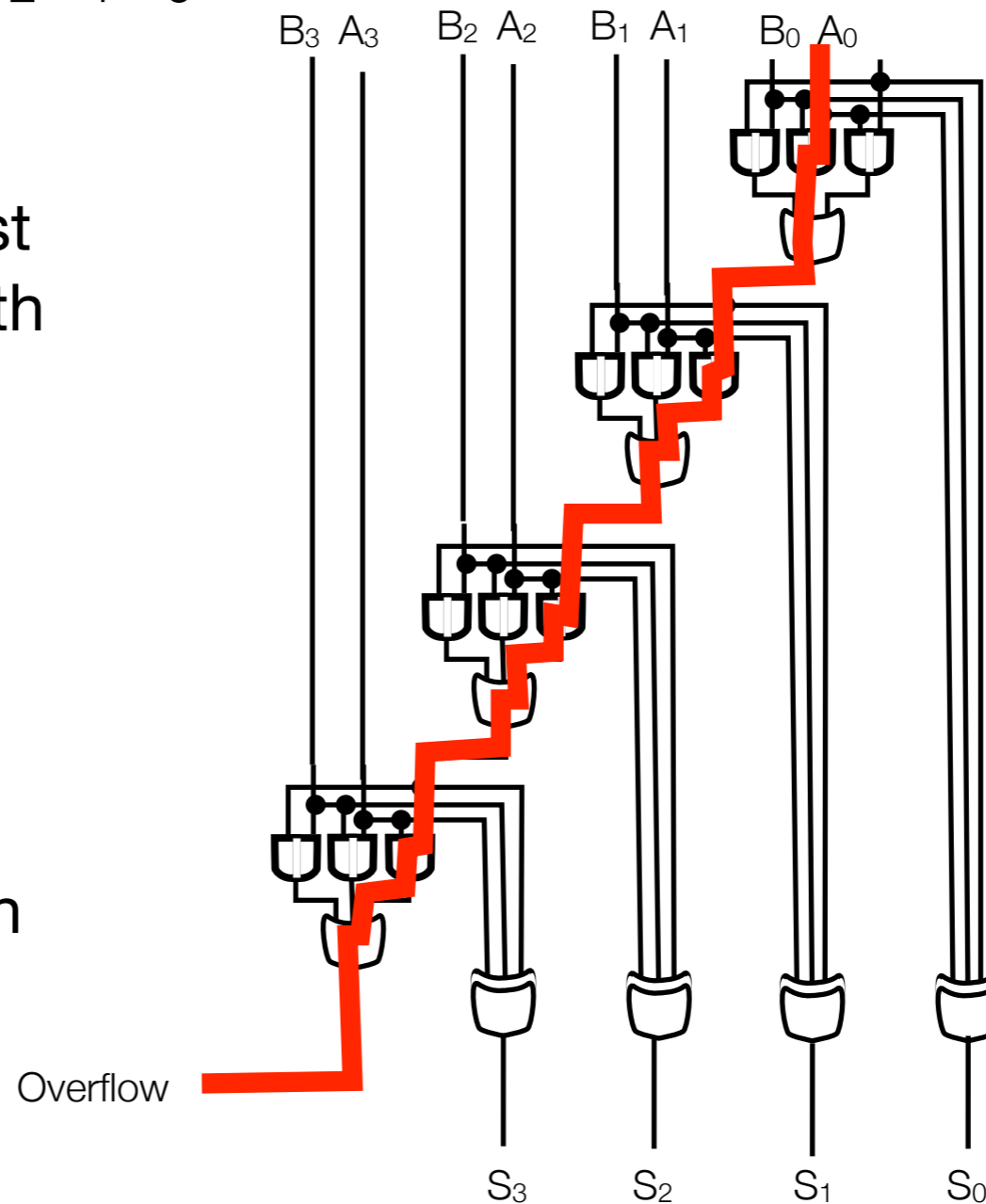- Depth of a circuit is the longest (most gates to go through) path
- Overflow has depth 8
- S_3 has depth 7
- In general, S_i has depth $2i+1$ in Ripple-Carry Adder



Carry lookahead adder (CLA)

- Goal: produce an adder of shorter circuit depth
- Start by rewriting the carry function

$$C_{i+1} = a_i b_i + a_i c_i + b_i c_i$$

$$C_{i+1} = a_i b_i + c_i (a_i + b_i)$$

$$C_{i+1} = g_i + c_i (p_i)$$

carry generate

$$g_i = a_i b_i$$

carry propagate

$$p_i = a_i + b_i$$

Carry lookahead adder (CLA) (2)

- Can recursively define carries in terms of propagate and generate signals

$$C_1 = g_0 + C_0p_0$$

$$C_2 = g_1 + C_1p_1$$

$$= g_1 + (g_0 + C_0p_0)p_1$$

$$= g_1 + g_0p_1 + C_0p_0p_1$$

$$C_3 = g_2 + C_2p_2$$

$$= g_2 + (g_1 + g_0p_1 + C_0p_0p_1)p_2$$

$$= g_2 + g_1p_2 + g_0p_1p_2 + C_0p_0p_1p_2$$

- i th carry has $i+1$ product terms, the largest of which has $i+1$ literals
- If AND, OR gates can take unbounded inputs: total circuit depth is 2 (SoP form)
- If gates take 2 inputs, total circuit depth is $1 + \log_2 k$ for k -bit addition

Carry lookahead adder (CLA) (3)

$$C_0 = 0$$

$$C_1 = g_0 + C_0 p_0$$

$$C_2 = g_1 + g_0 p_1 + C_0 p_0 p_1$$

$$C_3 = g_2 + g_1 p_2 + g_0 p_1 p_2 + C_0 p_0 p_1 p_2$$

$$C_4 = g_3 + g_2 p_3 + g_1 p_2 p_3 + g_0 p_1 p_2 p_3 + C_0 p_0 p_1 p_2 p_3$$


$$S_0 = a_0 \oplus b_0 \oplus C_0$$

$$S_1 = a_1 \oplus b_1 \oplus C_1$$

$$S_2 = a_2 \oplus b_2 \oplus C_2$$

$$S_3 = a_3 \oplus b_3 \oplus C_3$$

$$S_4 = a_4 \oplus b_4 \oplus C_4$$

 

Depth of 3 for all c_i

Depth of 4 for all $s_i, i > 0$


Note: gates take only 2 inputs: depth increases by a \log_2 factor: still much less than linear of ripple-carry adder

Contraction

Contraction is the simplification of a circuit through constant input values.

Contraction example: adder to incrementer

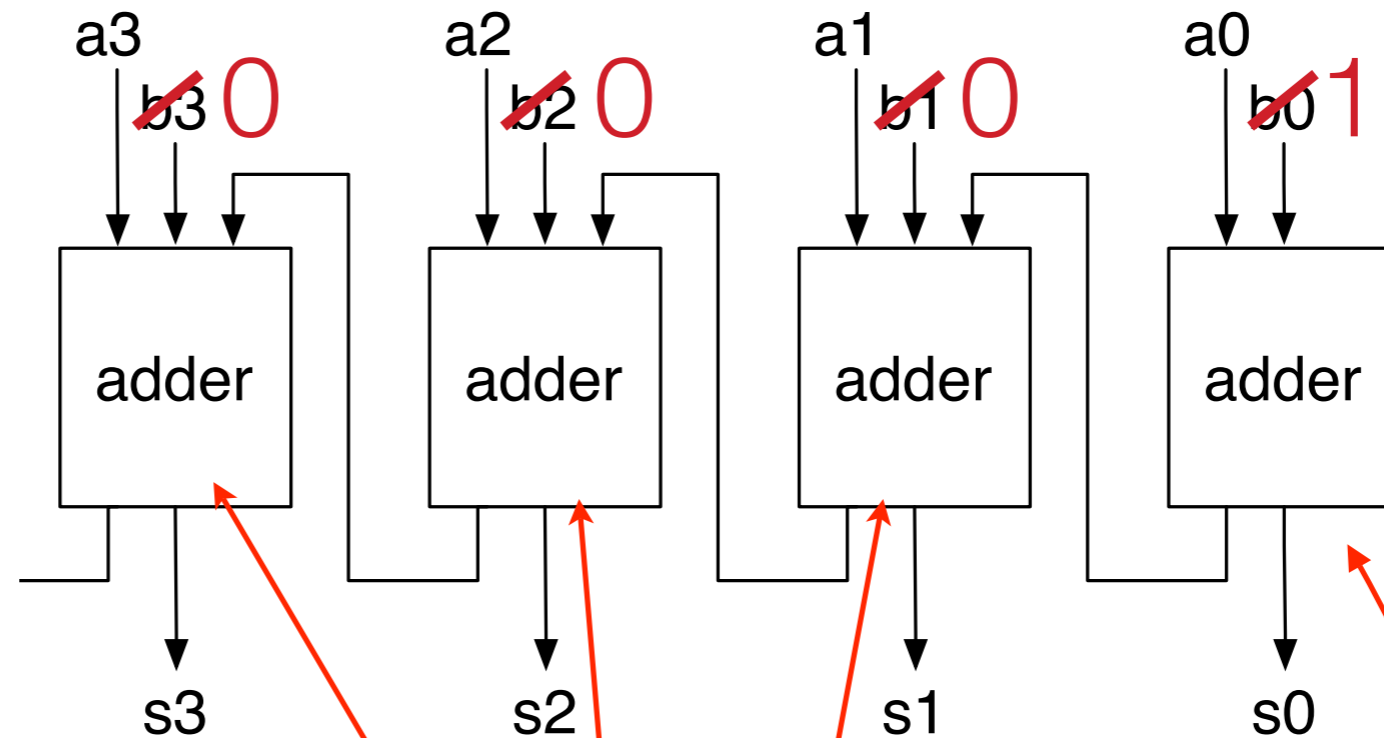- What is the hardware and delay savings of implementing an incrementer using contraction?



Can be reduced to half-adders


Incrementer circuit

| a_0 | S | C |
|-------|---|---|
| 0 | 1 | 0 |
| 1 | 0 | 1 |

$$S_0 = \bar{a}_0, C_0 = a_0$$


Multi-wire notation

 - Useful when running a bunch of bits in parallel to the same (similar place)



Shifter Circuit

 
- Shifts bits of a word: $A_{k-1}A_{k-2}\dots A_2A_1A_0$



$$B_{k-1}B_{k-2}\dots B_2B_1B_0$$


- Various types of shifters
 - Barrel: selector bits indicate (in binary) how “far” bits shift
 - selector value = j , then $B_i = A_{i-j}$
 - bits can “wraparound” $B_i \pmod{2^n} = A_{i-j} \pmod{2^n}$ or rollout ($B_i=0$ for $i < j$)
 - L/R with enable: $n=2$, high bit enables, low bit indicates direction (e.g., 0=left [$B_i = A_{i-1}$], 1=right [$B_i = A_{i+1}$])

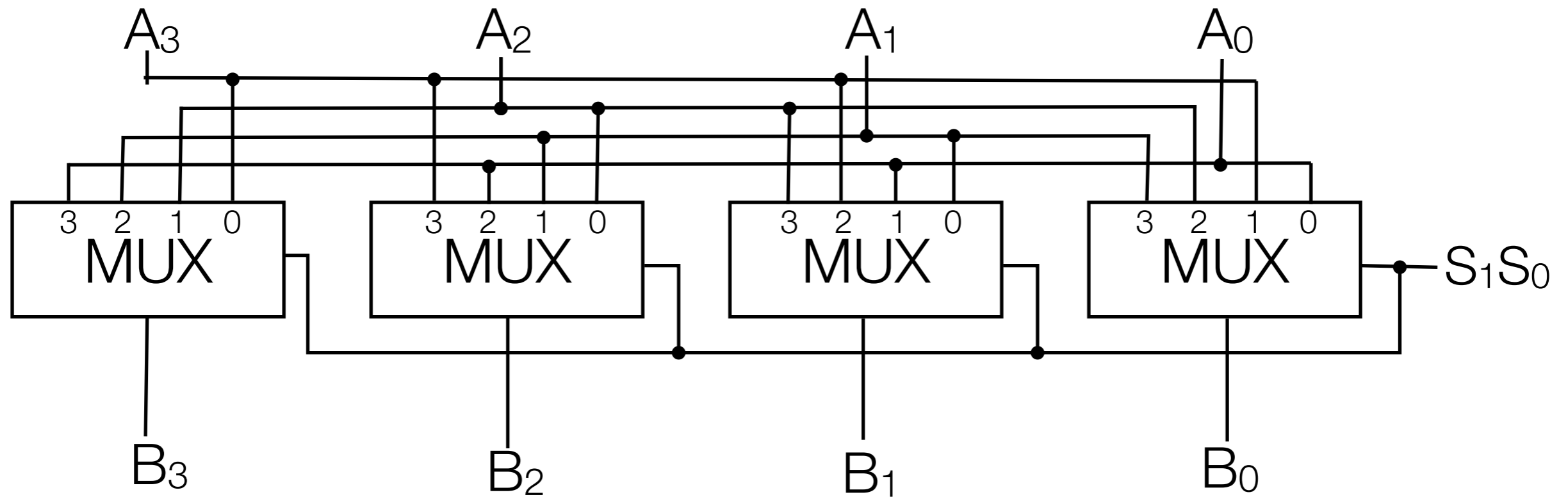Barrel Shifter Design with wraparound (using MUXs)




- Basic form of design: Each A_i feeds into each MUX connecting to B_j into input $(j-i) \bmod 4$

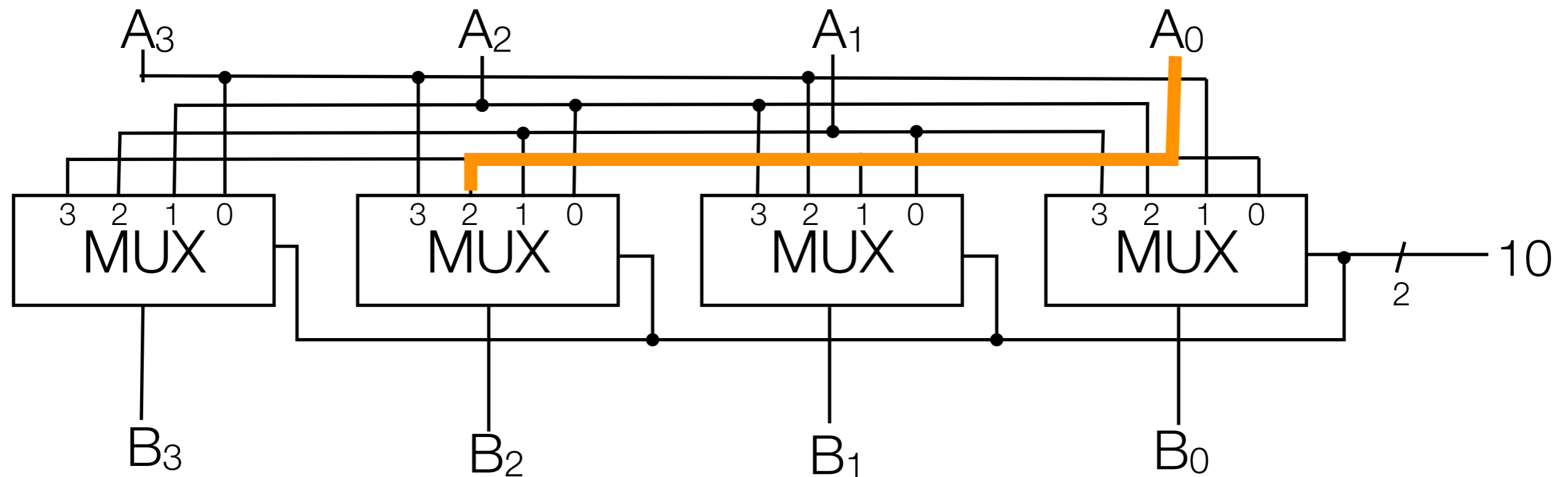Barrel Shifter Design with wraparound (using MUXs)




- Basic form of design: Each A_i feeds into each MUX connecting to B_j into input $(j-i) \bmod 4$
- Selector is 10 (i.e., 2 binary):
- each MUX entry 2 is selected
 - A_0 flows into the '2' input of the MUX whose output is B_2

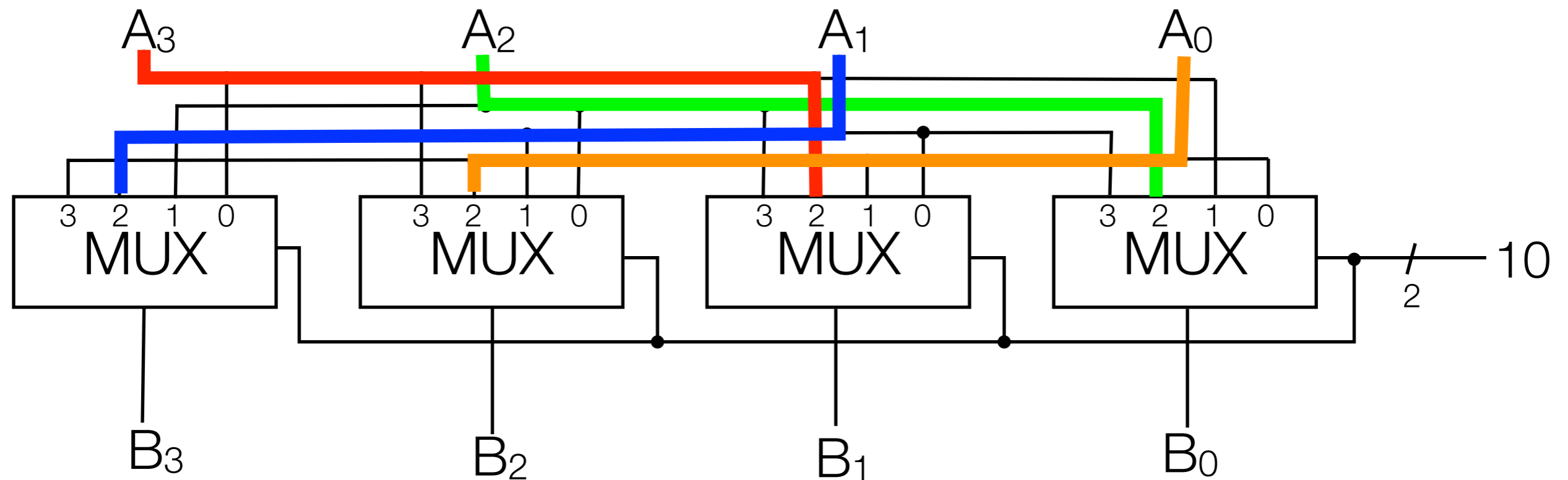Barrel Shifter Design with wraparound (using MUXs)



- Basic form of design: Each A_i feeds into each MUX connecting to B_j into input $(j-i) \bmod 4$
- Selector is 10 (i.e., 2 binary):
- each MUX entry 2 is selected
 - $B_3 B_2 B_1 B_0 = A_1 A_0 A_3 A_2$


L/R Shift w/ Rollout

 

- Basic form of design:

- 0 & 1 MUX selectors ($S_1 = 0$) feed A_i to B_i
- 2 MUX selector feeds from left ($B_i = A_{i-1}$), 3 MUX from right ($B_i = A_{i+1}$)
- Note 0 feeds (0's roll in when bits rollout)

L/R Shift w/ Rollout

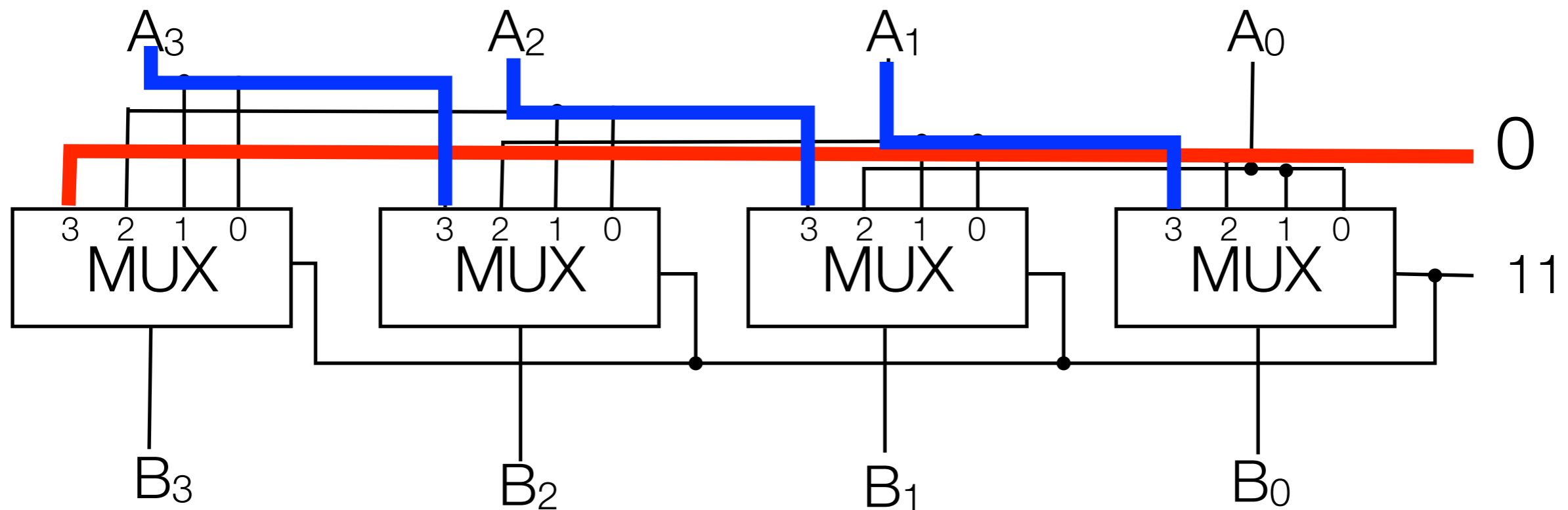

- Basic form of design:

- 0 & 1 MUX selectors ($S_1 = 0$) feed A_i to B_i
- 2 MUX selector feeds from left ($B_i = A_{i-1}$), 3 MUX from right ($B_i = A_{i+1}$)
- Note 0 feeds (0's roll in when bits rollout)