

CSEE 3827: Fundamentals of Computer Systems, Spring 2011

4. Sequential Circuit Elements

Prof. Martha Kim (martha@cs.columbia.edu)

Web: <http://www.cs.columbia.edu/~martha/courses/3827/sp11/>

Outline (H&H 3.1-3.3, 3.5, 5.4)

- Sequential circuit elements
 - Latches
 - SR
 - D
 - Flip-Flops
 - D
 - Enabled
 - Resettable
 - Sync v. Async
 - Timing of Sequential Logic
 - Building blocks
 - Registers
 - Counters
 - Shift Registers

Introduction



- Outputs of sequential logic *depend on current and prior input values* – it has memory.
- Some definitions:
 - **State**: all the information about a circuit necessary to explain its future behavior
 - **Latches and flip-flops**: state elements that store one bit of state
 - **Synchronous sequential circuits**: combinational logic followed by a bank of flip-flops

Sequential Circuits

- Give sequence to events
- Have memory (short-term)
- Use feedback from output to input to store information
- Circuit state is stored in **state elements**, e.g.,
 - Bistable circuit
 - SR Latch
 - D Latch
 - D Flip-flop

Bistable Circuit

 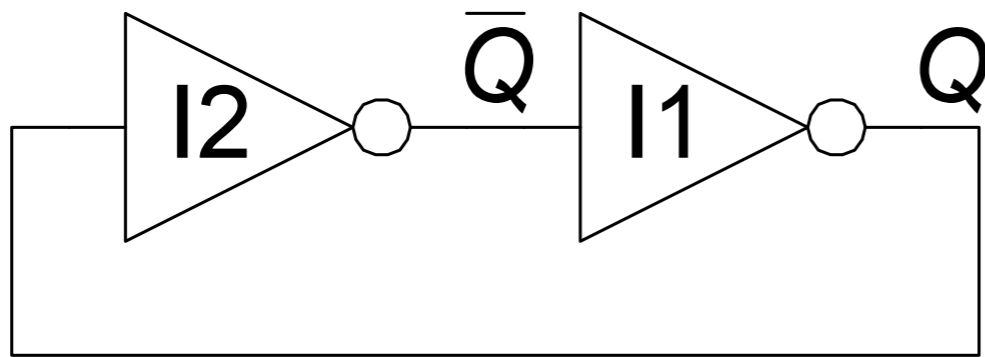
- Fundamental building block of other state elements
- Two outputs: Q , \bar{Q}
- No inputs




Bistable Circuit Analysis

- Consider the two possible cases:

 - $Q = 0$: then $\bar{Q} = 1$ and $Q = 0$ (consistent)



 
- $Q = 1$: then $\bar{Q} = 0$ and $Q = 1$ (consistent)



- Bistable circuit stores 1 bit of state in the state variable, Q (or \bar{Q})
- But there are ***no inputs to control the state***

SR (Set/Reset) Latch

- SR Latch

 

- Consider the four possible cases:

- $S = 1, R = 0$


- $S = 0, R = 1$

- $S = 0, R = 0$

- $S = 1, R = 1$


SR Latch Analysis

- $S = 1, R = 0$: then $Q = 1$

 

set



- $S = 0, R = 1$: then $Q = 0$

 

reset


SR Latch Analysis

- $S = 0, R = 0$: then $Q = Q_{prev}$

  

memory!

 - $S = 1, R = 1$: then $Q = 0$ and $\bar{Q} = 0$




$Q = \bar{Q}$
Invalid state

SR Latch Symbol

- SR stands for Set/Reset Latch, storing one bit of state (Q)
- Control the value being stored with S, R inputs
 - Set (“make the output 1”): $S=1, R=0, Q=1$
 - Reset (“make the output 0”): $S=0, R=1, Q=0$

SR Latch Symbol

 


- Must do something to **avoid invalid state** ($S = R = 1$)


D Latch

- Two inputs: C, D
 - **C**: controls *when* the output changes
 - **D (the data input)**: controls *what* the output changes to
- Function
 - When $C = 1$, D passes through to Q (the latch is transparent)
 - When $C = 0$, Q holds its previous value (the latch is opaque)
- Avoids invalid case when $Q \neq \text{NOT } \bar{Q}$

D Latch
Symbol

 

D Latch Internal Circuit

 

C	D	\bar{D}	S	R	Q	\bar{Q}
0	X					
1	0					
1	1					

Where we are, where we are headed

Latches are circuits that can store “state”

- set the latch to a value (0 or 1)
- put the latch in a “same value” mode to hold the value

To do complicated computations

- intermediate “state” must be maintained
- various steps of the computation must be coordinated

Q: How to coordinate computations and the changing of state values across lots of different parts of a circuit


A: Introduce a **clocking** mechanism

- each clock pulse, combinational computations can be performed, results stored (in latches)

Q: How to introduce clocks into latches?


flip flops: latches on a clock

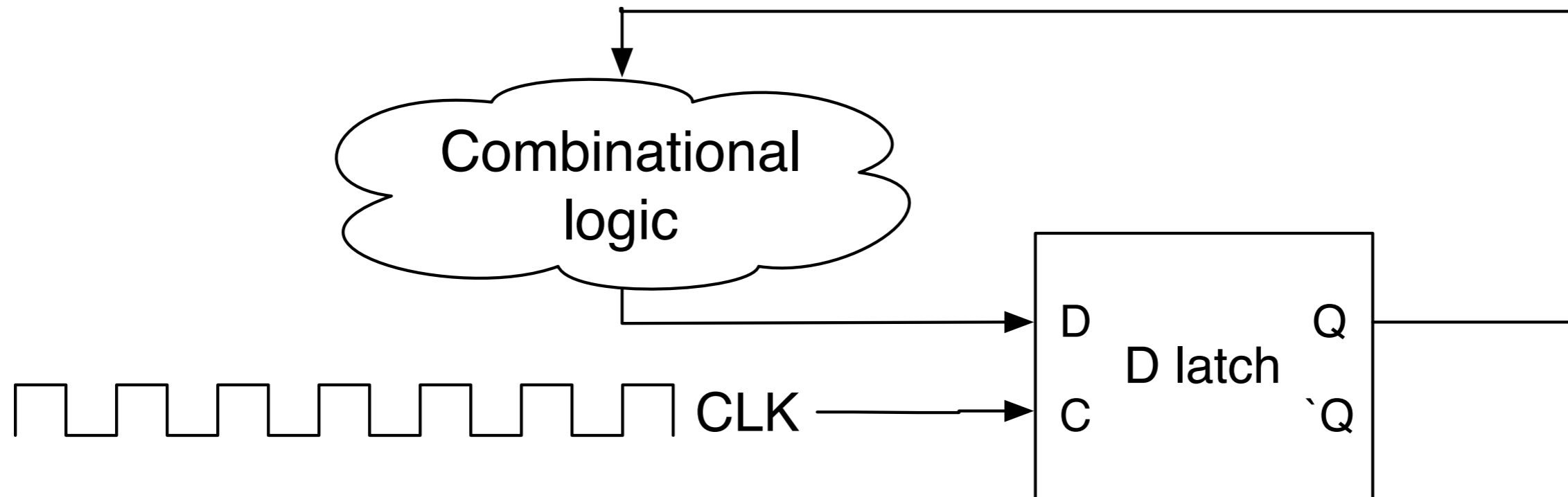- A straightforward latch is not safely (i.e., predictably) synchronous




- The problem is transparency of latches: as soon as the input changes, at some time later the output will change
- Flip flops are designed so that outputs will **not** change within a single clock pulse

Implementing the 1-ride-per-hour

 



- Suppose there is
 - Fun ride
 - People should only ride at most once per hour
 - How to stop someone from riding too often?

Solution #1: Build a gate

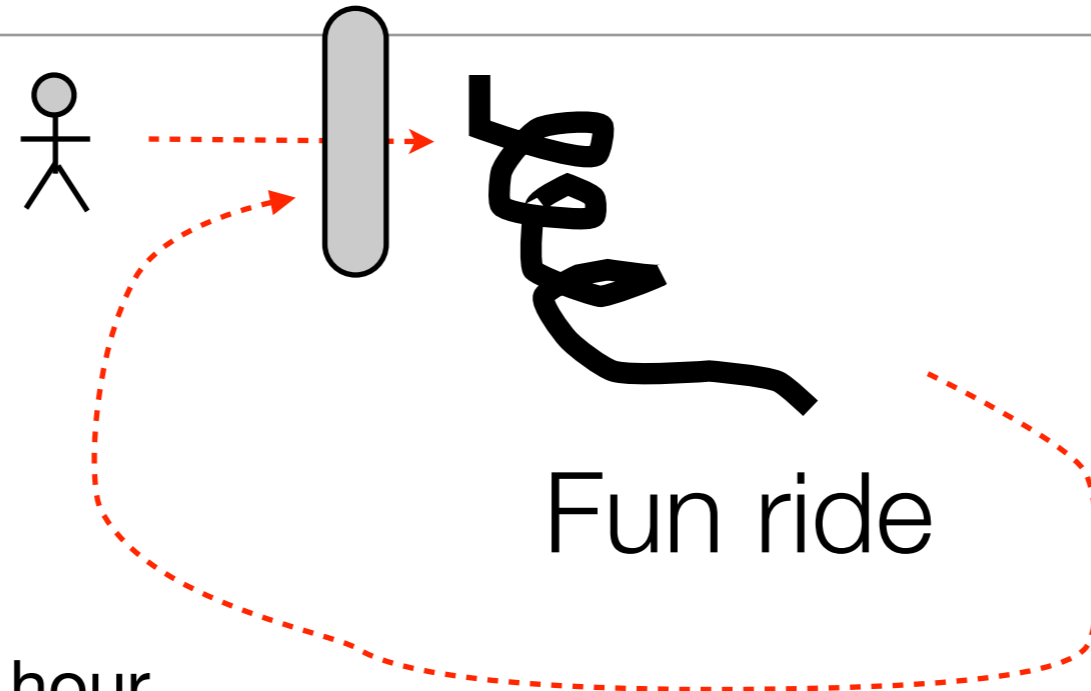


- Gate opens once per hour
 - Problem: how long to leave gate open?
 - Too short: not everyone might make it through in time (limits rideability)
 - Too long: “fast” person can go through, ride, and get through gate again

Solution #2: Pair of alternating gates

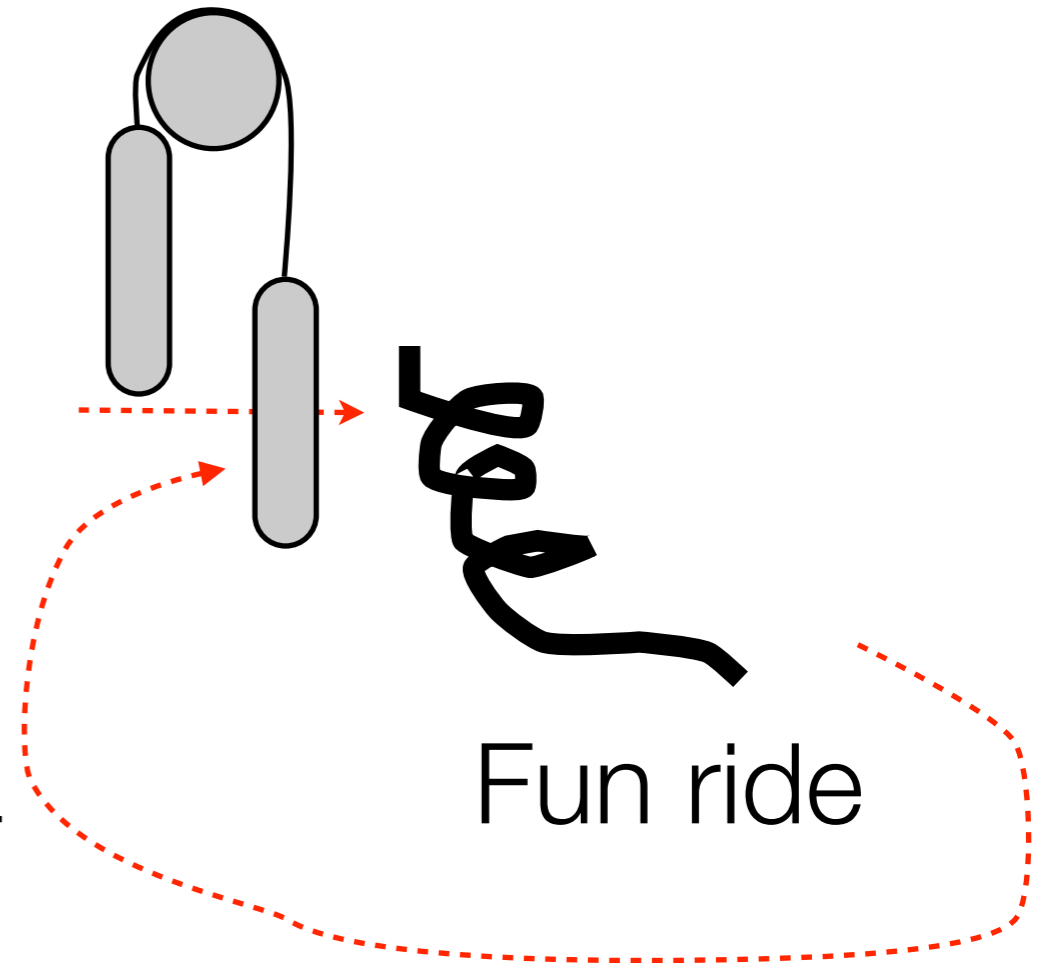 


- Gates alternate being open and closed
 - 1st gate: open on the bottom half of the hour
 - 2nd gate: open on top half of the hour
 - Anyone lined up from $X:00$ to $X:59$ can ride the ride once from $(X+1):00$ to $(X+1):59$
 - $X:00$ - 1st gate closes, people can start waiting in front for ride
 - $X:30$ - 1st gate opens allowing people into middle region
 - $(X+1):00$ - anyone who showed up between $X:00$ - $X:59$ gets through 2nd gate

2 Door system concluded


 


D Flip-Flop Summary

 



- C (Control) is fed a clock pulse (alternates between 0 and 1 with fixed period)
 - C=1: Master latch “on”, Slave latch “off”
 - New D input read into master
 - Previous Q values still emitted (not affected by new D inputs)
 - C=0: Master latch “off”, Slave latch “on”
 - Changing D inputs has no effect on Master (or Slave) latch
 - D inputs from last time C=1 stored safely in Master and transferred into Slave and reflected on output Q

D Flip-Flop Analysis

  



- C=1: Master latch “on”, Slave latch “off”
 - New S & R inputs read into master
 - Previous Q values still emitted (not affected by new S&R inputs)

D Flip-Flop Analysis

  

- C=0: Master latch “off”, Slave latch “on”
 - Changing D inputs has no effect on Master (or Slave) latch
 - D inputs from last time C=1 stored safely in Master and transferred into Slave and reflected on output Q

Flip-Flop Activation over Time

  


- $Q(t)$: value output by Flip-Flop during the t^{th} clock cycle (clock =0, then 1 during a full cycle)
- Depends on input during end of $t-1^{\text{st}}$ cycle

D Flip-Flop Summary

- Two inputs: CLK, D
- Function
 - The flip-flop “samples” D on the rising edge of CLK
 - When CLK rises from 0 to 1, D passes through to Q
 - Otherwise, Q holds its previous value
 - Q changes only on the rising edge of CLK
- A flip-flop is called an edge-triggered device because it is activated on the clock edge


D Flip-Flop Symbols

 




D Flip-Flop Summary

- Two inputs: CLK, D
- Function
 - The flip-flop “samples” D on the ~~rising edge~~ ^{falling edge} of CLK
 - When CLK ~~rises from 0 to 1~~ ^{falls from 1 to 0}, D passes through to Q
 - Otherwise, Q holds its previous value
 - Q changes only on the ~~rising edge~~ ^{falling edge} of CLK
- A flip-flop is called an edge-triggered device because it is activated on the clock edge

D Flip-Flop Symbols


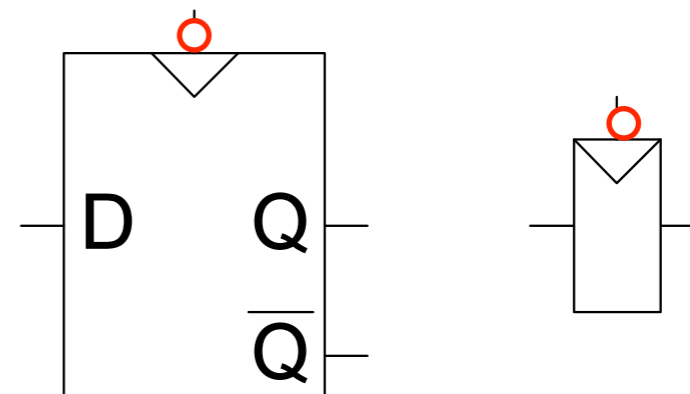


D Flip-Flop vs. D Latch

   


Latch outputs change at any time, flip-flops only during clock transitions

Registers

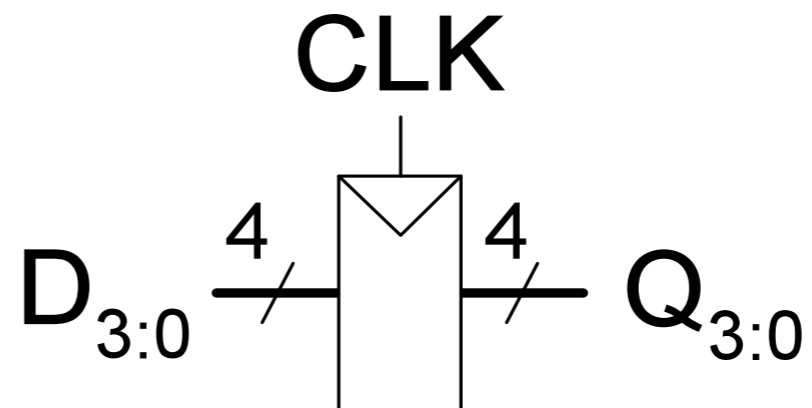 

Enabled Flip-Flops

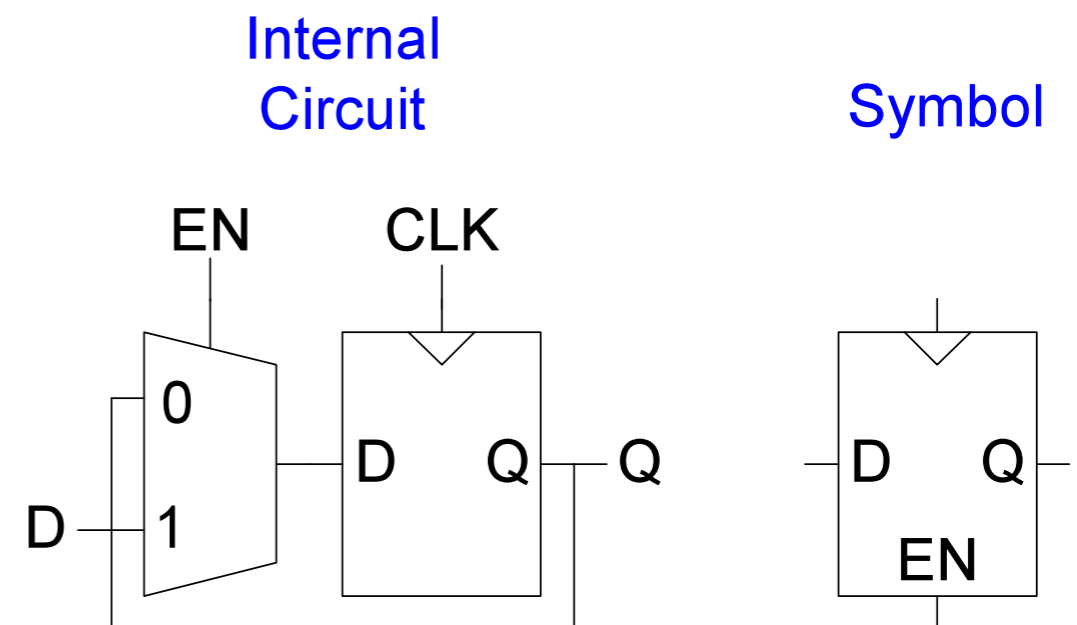
- Inputs: CLK, D, EN
 - The enable input (EN) controls when new data (D) is stored
- Function
 - $EN = 1$: D passes through to Q on the clock edge
 - $EN = 0$: the flip-flop retains its previous state



Resettable Flip Flops


- Inputs: CLK, D, Reset
- Function:
 - **Reset = 1**: Q is forced to 0
 - **Reset = 0**: the flip-flop behaves like an ordinary D flip-flop

Symbols

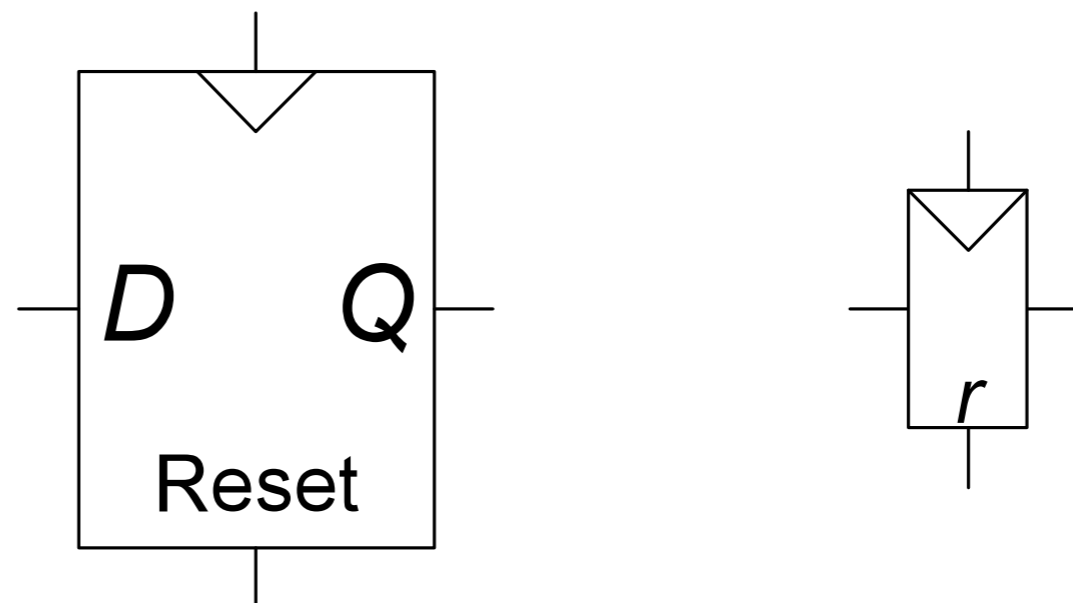

Resettable Flip-Flops (2)


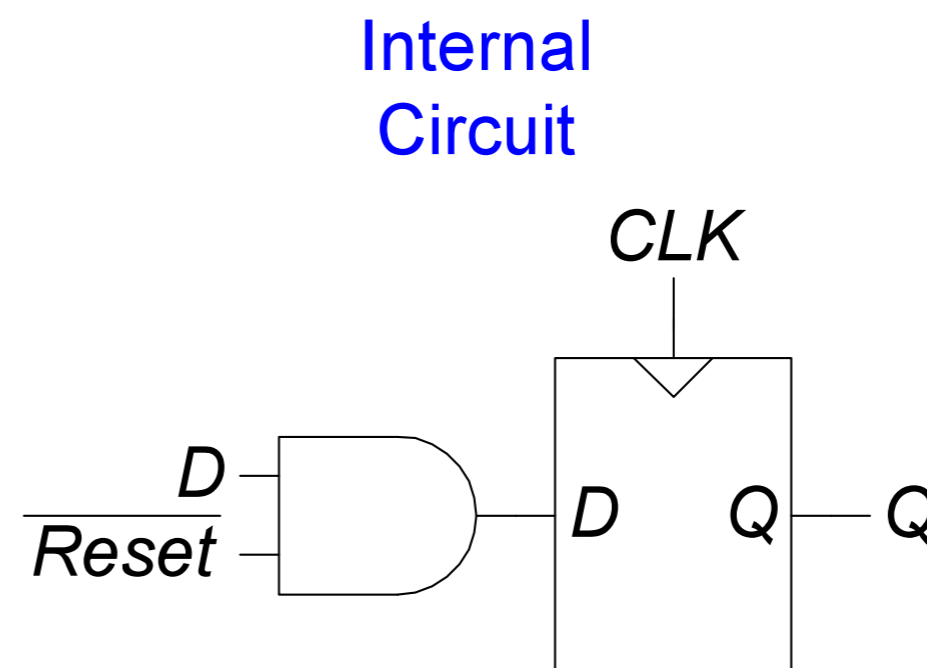
- Two types:
 - Synchronous: resets at the clock edge only
 - Asynchronous: resets immediately when $Reset = 1$
- Asynchronously resettable flip-flop requires changing the internal circuitry of the flip-flop (see Exercise 3.10)
- Synchronously resettable flip-flop?



Sequential Logic

- Sequential circuits: all circuits that aren't combinational

- A problematic circuit:

  

- This circuit has no inputs and 1-3 outputs
- It is an astable circuit that oscillates
- Its period depends on the delay of the inverters – which depends on the manufacturing process, temperature, etc
- The circuit has a **cyclic path**: output fed back to input

Synchronous Sequential Logic Design


- Breaks cyclic paths by inserting registers
- These registers contain the state of the system
- The state changes at the clock edge, so we say the system is **synchronized** to the clock
- Rules of synchronous sequential circuit composition:
 - Every circuit element is either a register or a combinational circuit
 - At least one circuit element is a register
 - All registers receive the same clock signal
 - Every cyclic path contains at least one register
- Two common synchronous sequential circuits
 - Finite State Machines (FSMs)
 - Pipelines

Timing Issues

- Flip-flop samples D at clock edge
- D must be stable when it is sampled
- Similar to a photograph, D must be stable around the clock edge
- If D is changing when it is sampled, metastability can occur


Input Timing Constraints

 - Setup time: t_{setup} = time before the clock edge that data must be stable (i.e. not changing)
- Hold time: t_{hold} = time after the clock edge that data must be stable
- Aperture time: t_a = time around clock edge that data must be stable ($t_a = t_{\text{setup}} + t_{\text{hold}}$)



Output Timing Constraints

 - Propagation delay: t_{pcq} = time after clock edge that the output Q is guaranteed to be stable (i.e., to stop changing)
- Contamination delay: t_{ccq} = time after clock edge that Q might be unstable (i.e., start changing)




Dynamic Discipline

- The input to a synchronous sequential circuit must be stable during the aperture (setup and hold) time around the clock edge.
- Specifically, the input must be stable
 - at least t_{setup} before the clock edge
 - at least until t_{hold} after the clock edge


Dynamic Discipline

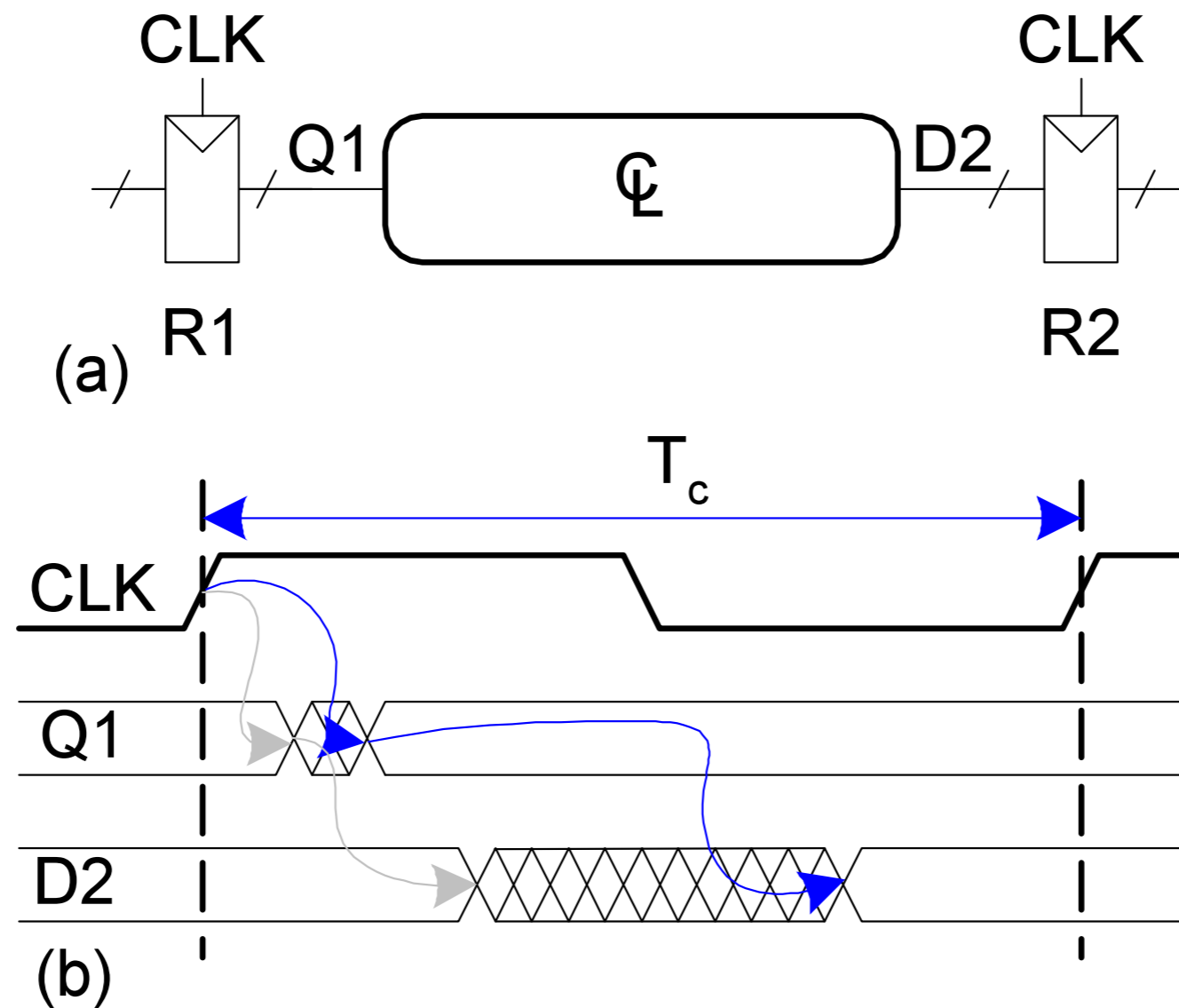- The delay between registers has a **minimum** and **maximum** delay, dependent on the delays of the circuit elements



Setup Time Constraint

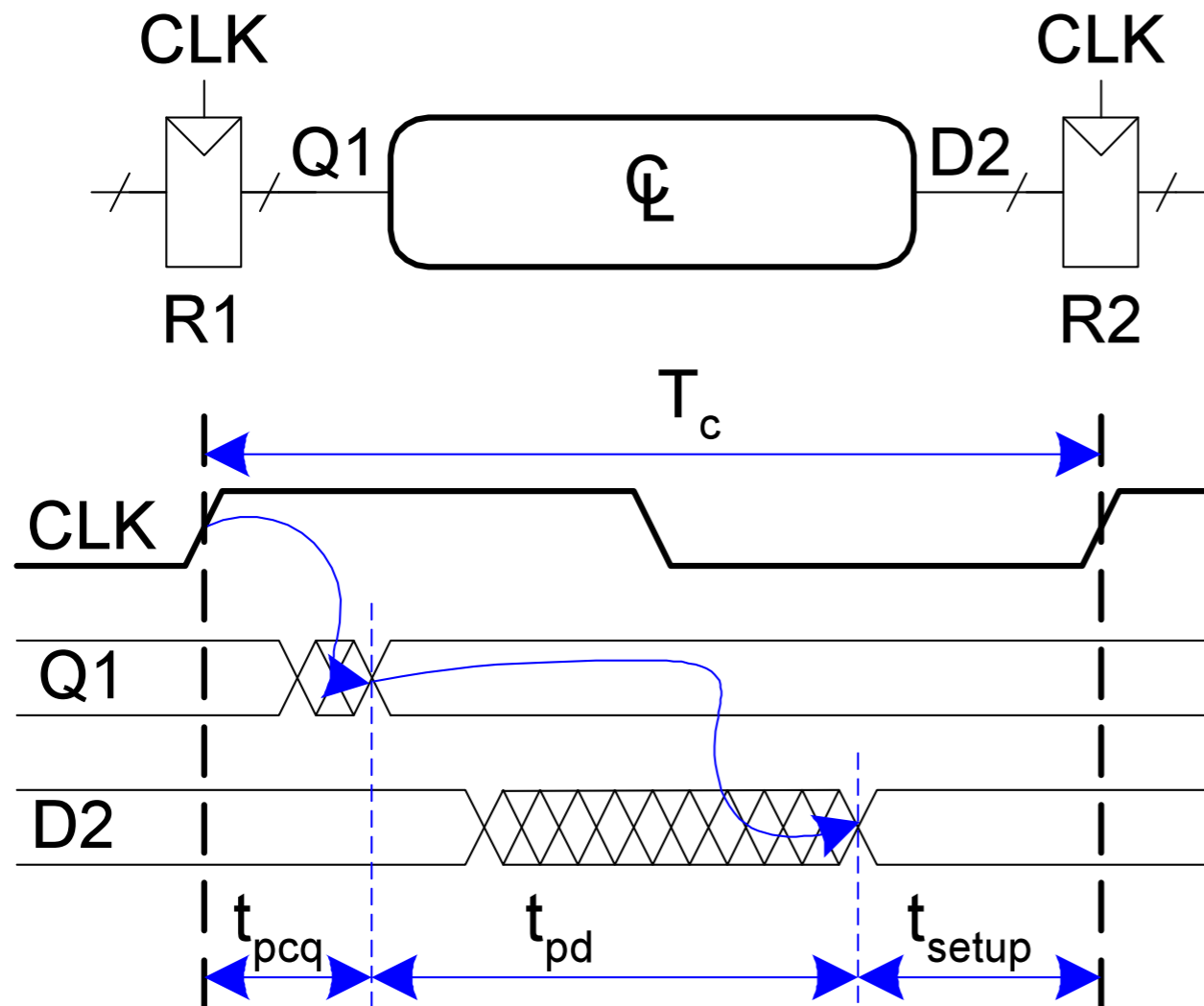
- The setup time constraint depends on the **maximum** delay from register R1 through the combinational logic.
- The input to register R2 must be stable at least t_{setup} before the clock edge.



$$T_c \geq t_{pcq} + t_{pd} + t_{\text{setup}}$$
$$t_{pd} \leq T_c - (t_{pcq} + t_{\text{setup}})$$

Hold Time Constraint

 - The hold time constraint depends on the **minimum** delay from register R1 through the combinational logic.
- The input to register R2 must be stable for at least t_{hold} after the clock edge.




$$t_{\text{hold}} < t_{ccq} + t_{cd}$$

$$t_{cd} > t_{\text{hold}} - t_{ccq}$$


Counters

- Increments on each clock edge.
- Used to cycle through numbers. For example,
 - 000, 001, 010, 011, 100, 101, 110, 111, 000, 001...
- Example uses:
 - Digital clock displays
 - Program counter: keeps track of current instruction executing

Symbol

 


Implementation

 


Shift Register

- Shift a new value in on each clock edge
- Shift a value out on each clock edge
- Serial-to-parallel converter: converts serial input (S_{in}) to parallel output ($Q_{0:N-1}$)

Symbol:

 

Implementation:

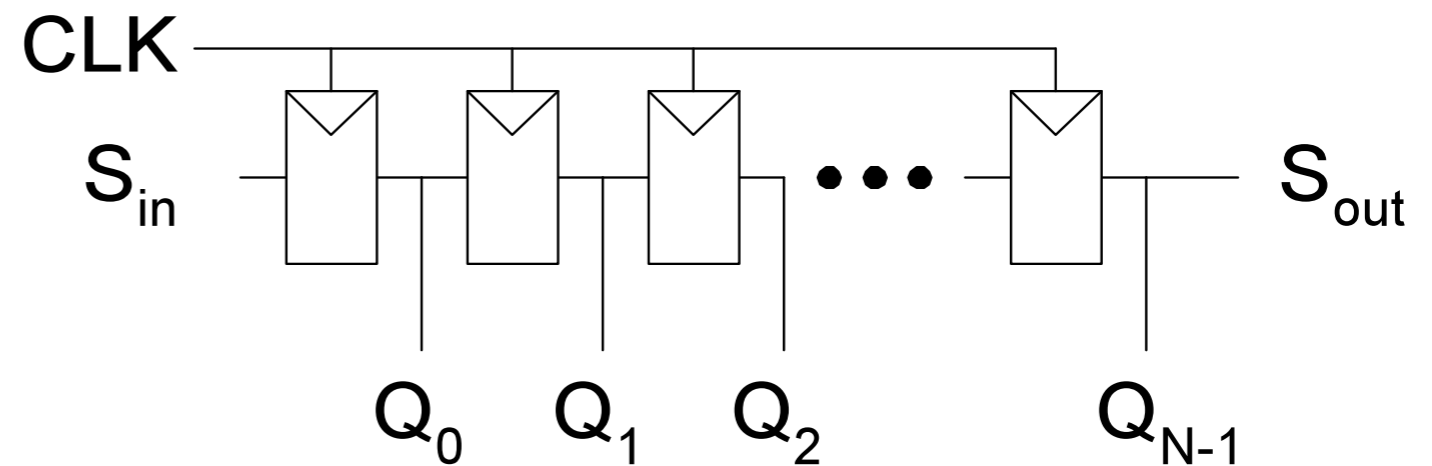

Shift Register with Parallel Load

- When $Load = 1$, acts as a normal N-bit register
- When $Load = 0$, acts as a shift register
- Now can act as a *serial-to-parallel converter* (S_{in} to $Q_{0:N-1}$) or a *parallel-to-serial converter* ($D_{0:N-1}$ to S_{out})

