

# Digital Design with Synthesizable VHDL


Languages for Embedded Systems

Prof. Stephen A. Edwards

Columbia University

March 2009

# Why HDLs?

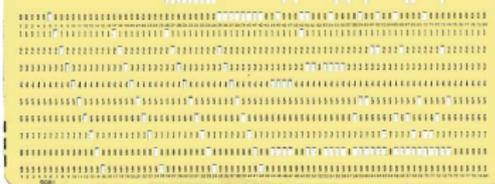



1970s: SPICE transistor-level netlists

An XOR built from four NAND gates

```
.MODEL P PMOS  
.MODEL N NMOS
```


```
.SUBCKT NAND A B Y Vdd Vss  
M1 Y A Vdd Vdd P  
M2 Y B Vdd Vdd P  
M3 Y A X Vss N  
M4 X B Vss Vss N  
.ENDS
```
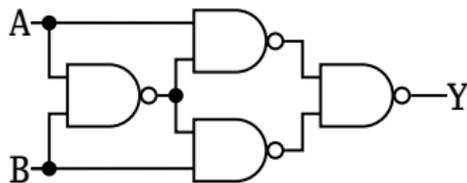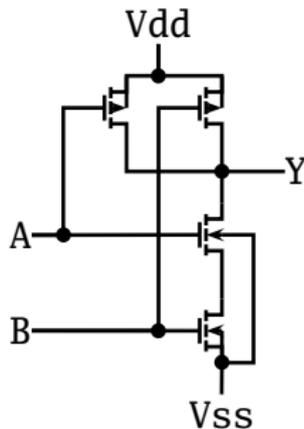
```
X1 A B I1 Vdd 0 NAND  
X2 A I1 I2 Vdd 0 NAND  
X3 B I1 I3 Vdd 0 NAND  
X4 I2 I3 Y Vdd 0 NAND
```


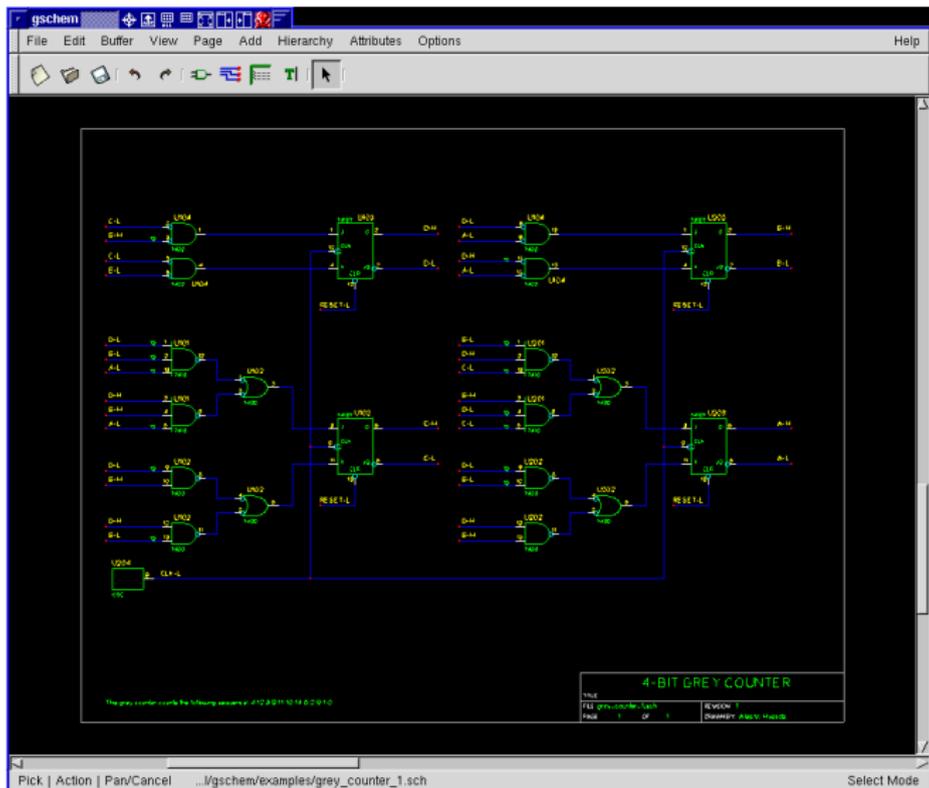
# Why HDLs?

1980s: Graphical schematic capture programs




# Why HDLs?

1990s: HDLs and Logic Synthesis

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity ALU is
port(  A:  in unsigned(1 downto 0);
      B:  in unsigned(1 downto 0);
      Sel: in unsigned(1 downto 0);
      Res: out unsigned(1 downto 0));
end ALU;
architecture behv of ALU is begin
  process (A,B,Sel) begin
    case Sel is
      when "00" => Res <= A + B;
      when "01" => Res <= A + (not B) + 1;
      when "10" => Res <= A and B;
      when "11" => Res <= A or B;
      when others => Res <= "XX";
    end case;
  end process;
end behv;
```

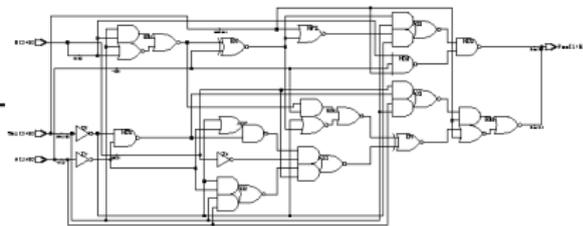

## Two Separate but Equal Languages



Verilog and VHDL

Verilog: More succinct, less flexible, really messy

VHDL: Verbose, very (too?) flexible, fairly messy

Part of languages people actually use identical.

Every synthesis system supports both.

# Basic Lexical Rules of VHDL

- ▶ Free-form: space only separates tokens.
- ▶ Case-insensitive: “VHDL,” “vHdL,” and “vhdl” are equivalent.
- ▶ Comments: from “--” to the end of the line.
- ▶ Identifiers:  $[a-zA-Z](\_?[a-zA-Z0-9])^*$   
Examples: X X\_or\_Y ADDR addr  
Illegal: 14M CLK\_\_4 FOO\_

# Literals in VHDL

- ▶ Decimal integers\*: 1 42 153\_1203
- ▶ Based integers\*: 2#1\_0010# 16#F001D#
- ▶ Characters: '0' '1' 'X'
- ▶ Strings: "101011" "XXXXXX"
- ▶ Bit string literals\*: B"1001\_0101" X"95" mean "10010101"

\*Underscores added for readability are ignored

# Part I

## Combinational Logic in a Dataflow Style

# Bits

|                       |           |         |
|-----------------------|-----------|---------|
| <b>Logical</b>        | True      | False   |
| <b>Binary</b>         | 1         | 0       |
| <b>Voltage</b>        | 1.65–3.3V | 0–1.65V |
| <b>Timing Diagram</b> | ——        | ——      |
| <b>VHDL</b>           | '1'       | '0'     |

In VHDL, zeros and ones on wires are members of an enumerated type. *They are not Boolean.*

# The std\_logic\_1164 package

```
package std_logic_1164 is

    type std_ulogic is
        ( 'U',  -- Uninitialized
          'X',  -- Forcing Unknown
          '0',  -- Forcing 0
          '1',  -- Forcing 1
          'Z',  -- High Impedance
          'W',  -- Weak Unknown
          'L',  -- Weak 0
          'H',  -- Weak 1
          '-'   -- Don't care
        );

    -- The std_logic type allows tri-state drivers
    subtype std_logic is resolved std_ulogic;

    -- Lots more...
```

# Boolean Operators

The basic ones in VHDL:

| <i>a</i> | <i>b</i> | <i>a and b</i> | <i>a or b</i> | <i>not a</i> |
|----------|----------|----------------|---------------|--------------|
| '0'      | '0'      | '0'            | '0'           | '1'          |
| '0'      | '1'      | '0'            | '1'           | '1'          |
| '1'      | '0'      | '0'            | '1'           | '0'          |
| '1'      | '1'      | '1'            | '1'           | '0'          |

| <i>a</i> | <i>b</i> | <i>a nand b</i> | <i>a nor b</i> | <i>a xor b</i> |
|----------|----------|-----------------|----------------|----------------|
| '0'      | '0'      | '1'             | '1'            | '0'            |
| '0'      | '1'      | '1'             | '0'            | '1'            |
| '1'      | '0'      | '1'             | '0'            | '1'            |
| '1'      | '1'      | '0'             | '0'            | '0'            |

# Rules of Boolean Algebra (1)

## -- Precedence

**not**  $a$  **or**  $b$  **and**  $c = (\text{not } a) \text{ or } (b \text{ and } c)$

## -- Basic relationships

**not not**  $a = a$

$a$  **and** '1' =  $a$

$a$  **and** '0' = '0'

$a$  **or** '1' = '1'

$a$  **or** '0' =  $a$

$a$  **and**  $a = a$

$a$  **and not**  $a = \text{'0'}$

$a$  **or**  $a = a$

$a$  **or not**  $a = \text{'1'}$

$a$  **nand**  $b = \text{not } (a \text{ and } b)$

$a$  **nor**  $b = \text{not } (a \text{ or } b)$

$a$  **xor** '0' =  $a$

$a$  **xor** '1' = **not**  $a$

$a$  **xor**  $b = (\text{not } a \text{ and } b) \text{ or } (a \text{ and not } b)$

## Rules of Boolean Algebra (2)

### -- Commutativity

$$a \text{ and } b = b \text{ and } a$$

$$a \text{ or } b = b \text{ or } a$$

### -- Associativity

$$a \text{ and } (b \text{ and } c) = (a \text{ and } b) \text{ and } c$$

$$a \text{ or } (b \text{ or } c) = (a \text{ or } b) \text{ or } c$$

### -- Distributivity

$$a \text{ and } (b \text{ or } c) = a \text{ and } b \text{ or } a \text{ and } c$$

$$a \text{ or } (b \text{ and } c) = (a \text{ or } b) \text{ and } (a \text{ or } c)$$

### -- De Morgan's Law

$$\text{not } (a \text{ and } b) = \text{not } a \text{ or } \text{not } b$$

$$\text{not } (a \text{ or } b) = \text{not } a \text{ and } \text{not } b$$

## A Full Adder: Truth Table

| a | b | c | carry | sum |
|---|---|---|-------|-----|
| 0 | 0 | 0 | 0     | 0   |
| 0 | 0 | 1 | 0     | 1   |
| 0 | 1 | 0 | 0     | 1   |
| 0 | 1 | 1 | 1     | 0   |
| 1 | 0 | 0 | 0     | 1   |
| 1 | 0 | 1 | 1     | 0   |
| 1 | 1 | 0 | 1     | 0   |
| 1 | 1 | 1 | 1     | 1   |

```
carry <=
(not a and b and c) or
(a and not b and c) or
(a and b and not c) or
(a and b and c);
sum <=
(not a and not b and c) or
(not a and b and not c) or
(a and not b and not c) or
(a and b and c);
```

Each row represents a minterm

Sum-of-products form: sum of each minterm in which output is true

## Simplifying Using Boolean Rules

```
carry <= (not a and b and c) or (a and not b and c) or  
          (a and b and not c) or (a and b and c);
```

```
<= (a and b and not c) or (a and b and c) or  
   (not a and b and c) or (a and b and c) or  
   (a and not b and c) or (a and b and c);
```


```
<= (a and b) or (b and c) or (a and c);
```

```
sum <= (not a and not b and c) or (not a and b and not c) or  
        (a and not b and not c) or (a and b and c);
```


```
<= (not a) and ((not b and c) or (b and not c)) or  
   a and ((not b and not c) or (b and c));
```

```
<= a xor b xor c;
```

# Structure of a VHDL Module

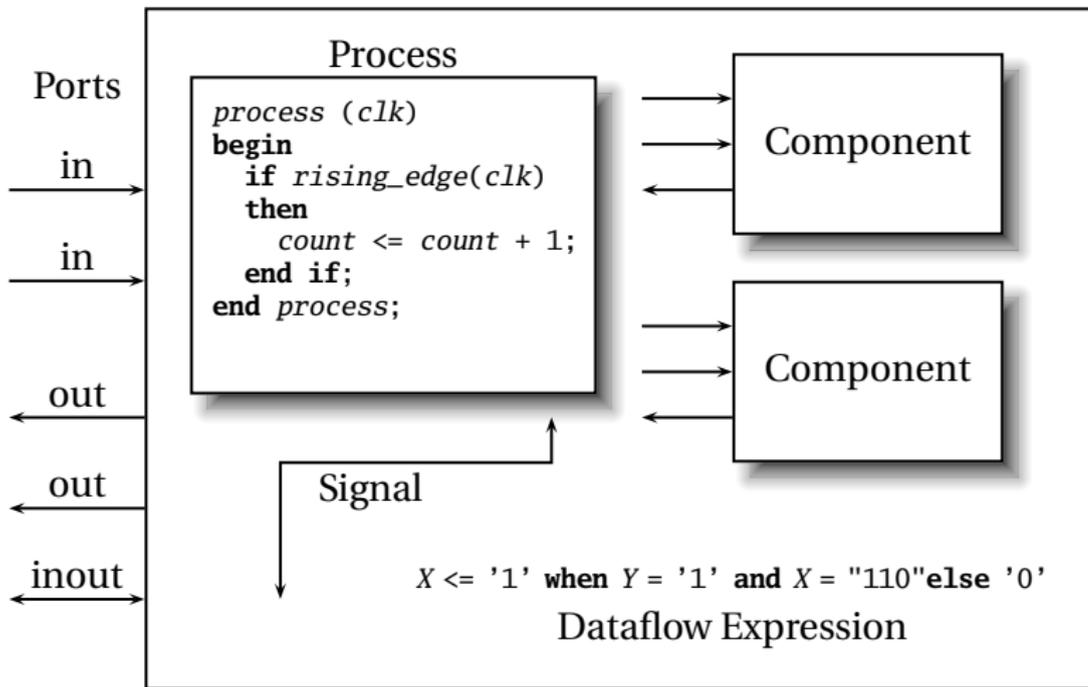

# A Full Adder in VHDL

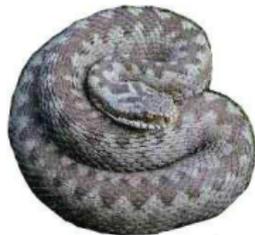


```
library ieee; -- always needed
use ieee.std_logic_1164.all; -- std_logic, et al.

entity full_adder is -- the interface
  port(a, b, c      : in  std_logic;
        sum, carry : out std_logic);
end full_adder;

architecture imp of full_adder is -- the implementation
begin
  sum    <= (a xor b) xor c;    -- combinational logic
  carry <= (a and b) or (a and c) or (b and c);
end imp;
```

## ...After Logic Synthesis

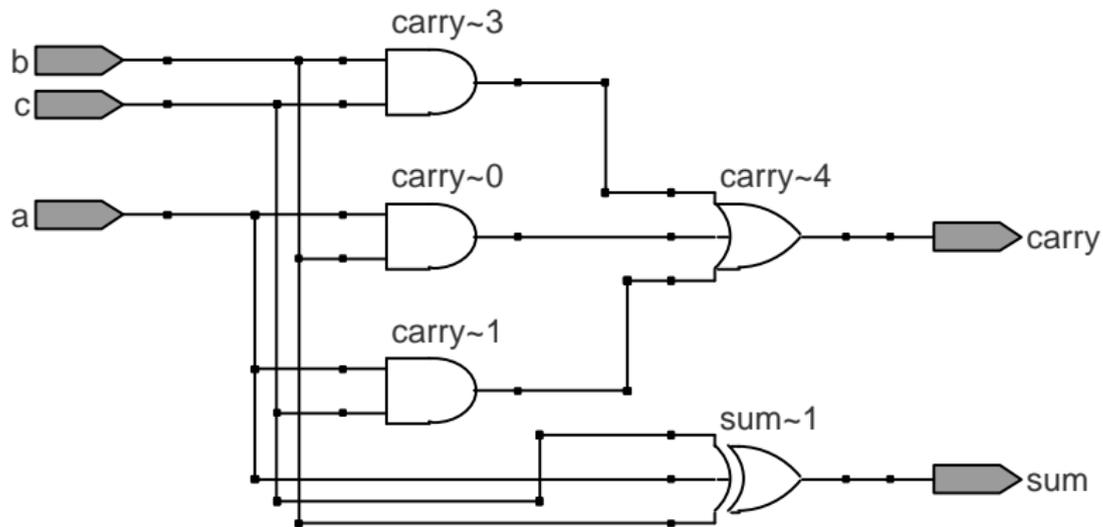

# Vectors of Bits

Three standard synthesizable bit vector types:

| Type                          | Library                    | Logic | Arith. | Neg. |
|-------------------------------|----------------------------|-------|--------|------|
| <code>std_logic_vector</code> | <code>ieee_std_1164</code> | ✓     |        |      |
| <code>unsigned</code>         | <code>numeric_std</code>   | ✓     | ✓      |      |
| <code>signed</code>           | <code>numeric_std</code>   | ✓     | ✓      | ✓    |

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity vectors is
  port(vect : in std_logic_vector(1 downto 0);
       unsi : in unsigned(7 downto 0);
       sign : out unsigned(15 downto 0));
end entity;
```

# Endianness

The perpetual battle: Is “0” most or least significant?

Little Endian    3 2 1 0    *unsigned(3 **down to** 0)*

Big Endian      0 1 2 3    *unsigned(0 **to** 3)*

Arguments on both sides will continue forever.

I suggest using Little Endian for vectors.

# Binary and Hexadecimal in VHDL

| Decimal | Binary  | Hex   |
|---------|---------|-------|
| 0       | "0"     | x"0"  |
| 1       | "1"     | x"1"  |
| 2       | "10"    | x"2"  |
| 3       | "11"    | x"3"  |
| 4       | "100"   | x"4"  |
| 5       | "101"   | x"5"  |
| 6       | "110"   | x"6"  |
| 7       | "111"   | x"7"  |
| 8       | "1000"  | x"8"  |
| 9       | "1001"  | x"9"  |
| 10      | "1010"  | x"A"  |
| 11      | "1011"  | x"B"  |
| 12      | "1100"  | x"C"  |
| 13      | "1101"  | x"D"  |
| 14      | "1110"  | x"E"  |
| 15      | "1111"  | x"F"  |
| 16      | "10000" | x"10" |
| 17      | "10001" | x"11" |
| 18      | "10010" | x"12" |
| 19      | "10011" | x"13" |

Vector types are arrays of `std_logic`

Literals are therefore strings of 0's and 1's

```
-- from std_logic_1164
type std_logic_vector is
    array (natural range <>) of std_logic;

--- from numeric_std
type unsigned is
    array (natural range <>) of std_logic;

type signed is
    array (natural range <>) of std_logic;
```

# Two's Complement

| Decimal | Binary | Hex  |
|---------|--------|------|
| -8      | "1000" | x"8" |
| -7      | "1001" | x"9" |
| -6      | "1010" | x"A" |
| -5      | "1011" | x"B" |
| -4      | "1100" | x"C" |
| -3      | "1101" | x"D" |
| -2      | "1110" | x"E" |
| -1      | "1111" | x"F" |
| 0       | "0000" | x"0" |
| 1       | "0001" | x"1" |
| 2       | "0010" | x"2" |
| 3       | "0011" | x"3" |
| 4       | "0100" | x"4" |
| 5       | "0101" | x"5" |
| 6       | "0110" | x"6" |
| 7       | "0111" | x"7" |

How do you represent negative numbers?


Two's complement produces simpler logic than sign bit alone.

Idea: Add constant  $2^n$  to negative numbers. Simply discard overflow after addition or subtraction.

An  $n$ -bit number represents  $-2^{n-1}$  to  $2^{n-1} - 1$ .

The signed type in `numeric_std` uses this

# A Hex-to-seven-segment Decoder

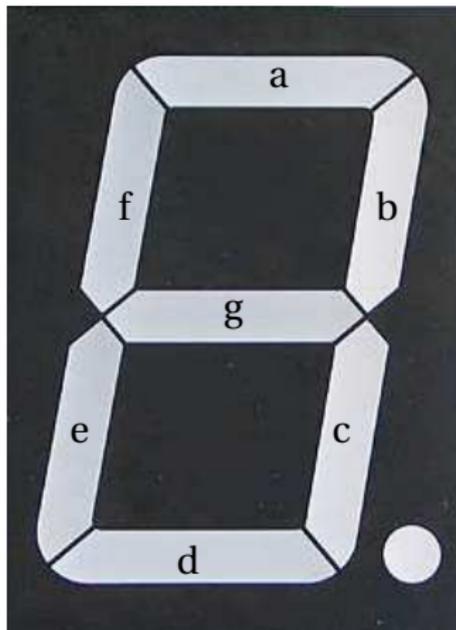

## VHDL: Hex-to-7-segment Decoder

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all; -- Provides the unsigned type
entity hex7seg is
    port ( input  : in  unsigned(3 downto 0); -- A number
          output : out std_logic_vector(6 downto 0));
end hex7seg;
architecture combinational of hex7seg is
begin
    with input select output <=
        "0111111" when x"0", "0000110" when x"1", -- Bad style
        "1011011" when x"2", "1001111" when x"3", -- one case
        "1100110" when x"4", "1101101" when x"5", -- per line
        "1111101" when x"6", "0000111" when x"7", -- preferred
        "1111111" when x"8", "1101111" when x"9",
        "1110111" when x"A", "1111100" when x"B",
        "0111001" when x"C", "1011110" when x"D",
        "1111001" when x"E", "1110001" when x"F",
        "XXXXXXX" when others;
end combinational;
```

## Four-to-one mux: when .. else

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity multiplexer_4_1 is
    port(in0, in1, in2, in3 : in unsigned(15 downto 0);
         s                    : in unsigned(1 downto 0);
         z                    : out unsigned(15 downto 0));
end multiplexer_4_1;

architecture comb of multiplexer_4_1 is
begin
    z <= in0 when s = "00" else
         in1 when s = "01" else
         in2 when s = "10" else
         in3 when s = "11" else
         (others => 'X'); -- Shorthand for "all X's"
end comb;
```

## Four-to-one mux: with...select

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity multiplexer_4_1 is
  port(in0, in1, in2, in3 : in  unsigned(15 downto 0);
        s0, s1             : in  std_logic;
        z                  : out unsigned(15 downto 0));
end multiplexer_4_1;

architecture comb of multiplexer_4_1 is
  signal sels : unsigned(1 downto 0);
begin
  sels <= s1 & s0; -- "&" is vector concatenation
  with sels select -- "with s1 & s0" would not resolve type
    z <= in0          when "00",
        in1          when "01",
        in2          when "10",
        in3          when "11",
        (others => 'X') when others;
end comb;
```

## Three-to-eight Decoder

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity dec1_8 is
port (
    sel : in  unsigned(2 downto 0);
    res : out unsigned(7 downto 0));
end dec1_8;

architecture comb of dec1_8 is
begin
    res <= "00000001" when sel = "000" else
           "00000010" when sel = "001" else
           "00000100" when sel = "010" else
           "00001000" when sel = "011" else
           "00010000" when sel = "100" else
           "00100000" when sel = "101" else
           "01000000" when sel = "110" else
           "10000000";
end comb;
```

# Priority Encoder

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity priority is
  port (
    sel : in  std_logic_vector(7 downto 0);
    code : out unsigned(2 downto 0));
end priority;

architecture imp of priority is
begin
  code <= "000" when sel(0) = '1' else
    "001" when sel(1) = '1' else
    "010" when sel(2) = '1' else
    "011" when sel(3) = '1' else
    "100" when sel(4) = '1' else
    "101" when sel(5) = '1' else
    "110" when sel(6) = '1' else
    "111";
end imp;
```



# Integer Arithmetic

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity adder is
  port (
    A, B : in  unsigned(7 downto 0);
    CI   : in  std_logic;
    SUM  : out unsigned(7 downto 0);
    CO   : out std_logic);
end adder;

architecture imp of adder is
  signal tmp : unsigned(8 downto 0);
begin
  -- trick to promote ci to unsigned
  tmp <= A + B + ("0" & ci);
  SUM <= tmp(7 downto 0);
  CO  <= tmp(8);
end imp;
```



# A Very Simple ALU

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity alu is
  port (
    A, B : in  unsigned(7 downto 0);
    ADD  : in  std_logic;
    RES  : out unsigned(7 downto 0));
end alu;

architecture imp of alu is
begin
  RES <= A + B when ADD = '1' else
        A - B;
end imp;
```

# Arithmetic Comparison

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity comparator is
  port (
    A, B : in  unsigned(7 downto 0);
    GE   : out std_logic);
end comparator;

architecture imp of comparator is
begin
  GE <= '1' when A >= B else '0';
end imp;
```

## Tri-state drivers

How to use a pin as both an input and output.

Not for internal FPGA signals.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity tri_demo is
  port(addr : out unsigned(15 downto 0);    -- output only
        data : inout unsigned(7 downto 0)); -- bidirectional
end tri_demo;

architecture rtl of tri_demo is
  signal oe : std_logic; -- output enable: control direction
  signal d_out : unsigned(7 downto 0);
begin

  data <= d_out when oe = '1' else -- Drive data to chip
    (others => 'Z'); -- Read data from external chip

end rtl;
```

# Syntax of Expressions

Logical operators: **and or xor nand nor**

Relational operators: = /= < <= > >=

Additive operators: + - & (concatenation)

Multiplicative operators: \* / **mod rem**

Others: **abs not \*\*** (exponentiation)

Primaries: identifier

literal

*name*(*expr* **to** *expr*)

*name*(*expr* **downto** *expr*)

( *choice* ( | *choice* ) \* => *expr* )

# Summary of Dataflow Modeling

- ▶ Conditional signal assignment (when...else)

```
target <=  
  (expr when expr else)*  
  expr ;
```

- ▶ Selected signal assignment (with...select)

```
with expr select  
  target <=  
  (expr when choice (| choice)* ,)*  
  expr when choice (| choice)* ;
```

A *choice* is a simple expression (i.e., not logical or comparison) or **others**.

Note: **when** does not nest (i.e., it's not an *expr*).

## Part II

### Hierarchy: Instantiating components (entities)


## Hierarchy: port map positional style

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
entity add2 is  
    port (A, B : in unsigned(1 downto 0);  
          C    : out unsigned(2 downto 0));  
end add2;
```

```
architecture imp of add2 is
```

```
    component full_adder  
    port (a, b, c : in std_logic;  
          sum, carry : out std_logic);  
    end component;
```
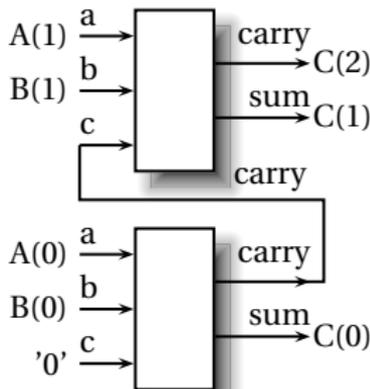
```
    signal carry : std_logic;  
begin  
    bit0 : full_adder port map ( A(0), B(0), '0', C(0), carry );  
    bit1 : full_adder port map ( A(1), B(1), carry, C(1), C(2) );  
end imp;
```



## Hierarchy: port map by-name style

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity add2n is
    port (A, B : in unsigned(1 downto 0);
          C    : out unsigned(2 downto 0));
end add2n;
architecture imp of add2n is
    component full_adder
        port (a, b, c    : in std_logic;
              sum, carry : out std_logic);
    end component;
    signal carry : std_logic;
begin
    bit0 :
        full_adder port map (a => A(0), b => B(0), c => '0',
                             sum => C(0), carry => carry);

    bit1 :
        full_adder port map (a => A(1), b => B(1), c => carry,
                             sum => C(1), carry => C(2));
end imp;
```

## Direct Instantiation (no component)

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity add2 is
  port (A, B : in unsigned(1 downto 0);
        C    : out unsigned(2 downto 0));
end add2;

architecture imp of add2 is
  signal carry : std_logic;
begin
  bit0 : entity work.full_adder -- everything in "work"
    port map ( A(0), B(0), '0', C(0), carry );

  bit1 : entity work.full_adder
    port map ( A(1), B(1), carry, C(1), C(2) );
end imp;
```

Must be compiled after full\_adder.vhd!

## Generate: Ripple-carry adder

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity rippleadder is
    port (a, b : in unsigned(3 downto 0);
          cin : in std_logic;
          sum : out unsigned(3 downto 0);
          cout : out std_logic);
end rippleadder;

architecture imp of rippleadder is
    signal c : unsigned(4 downto 0);
begin
    c(0) <= cin;
    G1: for m in 0 to 3 generate -- expanded at compile time
        sum(m) <= a(m) xor b(m) xor c(m);
        c(m+1) <= (a(m) and b(m)) or (b(m) and c(m)) or
                 (a(m) and c(m));
    end generate G1;
    cout <= c(4);
end imp;
```

## Part III

# Combinational Logic in a Procedural Style

## Processes

Process: sequential code fragment invoked when signal in sensitivity list changes.

A correct, but dumb way to model an inverter:

```
library ieee;
use ieee.std_logic_1164.all;

entity dumb_inv is
  port( a: in std_logic; y : out std_logic );
end dumb_inv;

architecture comb of dumb_inv is
begin
  process (a) -- invoked when signal a changes
  begin
    if a = '1' then y <= '0'; else y <= '1'; end if;
  end process;
end comb;
```

## A 4-to-1 mux in the procedural style

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity pmultiplexer_4_1 is
    port(in0, in1, in2, in3 : in unsigned(15 downto 0);
          s                    : in unsigned(1 downto 0);
          z                    : out unsigned(15 downto 0));
end pmultiplexer_4_1;

architecture comb of pmultiplexer_4_1 is
begin
    process (in0, in1, in2, in3, s)
    begin
        z <= (others => 'X'); -- default
        if s = "00" then z <= in0; -- overrides default
        elsif s = "01" then z <= in1;
        elsif s = "10" then z <= in2;
        elsif s = "11" then z <= in3;
        end if;
    end process;
end comb;
```

## A 4-to-1 mux using case

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity cmultiplexer_4_1 is
    port(in0, in1, in2, in3 : in  unsigned(15 downto 0);
          s                   : in  unsigned(1 downto 0);
          z                   : out unsigned(15 downto 0));
end cmultiplexer_4_1;
architecture comb of cmultiplexer_4_1 is
begin
    process (in0, in1, in2, in3, s)
    begin
        case s is
            when "00" => z <= in0;
            when "01" => z <= in1;
            when "10" => z <= in2;
            when "11" => z <= in3;
            when others => z <= (others => 'X');
        end case;
    end process;
end comb;
```

## An Address Decoder

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity adecoder is
    port(a : in unsigned(15 downto 0);
         ram, rom, video, io : out std_logic);
end adecoder;

architecture proc of adecoder is
begin
    process (a)
    begin
        ram <= '0'; rom <= '0'; video <= '0'; io <= '0';
        if a(15) = '0' then ram <= '1'; -- 0000-7FFF
        elsif a(14 downto 13) = "00" then video <= '1'; -- 8000-9FFF
        elsif a(14 downto 12) = "101" then io <= '1'; -- D000-DFFF
        elsif a(14 downto 13) = "11" then rom <= '1'; -- E000-FFFF
        end if;
    end process;
end proc;
```

# Summary of Procedural Modeling

- ▶ **null**
- ▶ *signal* <= *expr* ;
- ▶ *variable* := *expr* ;
- ▶ **if** *expr* **then** *stmts*  
    (**elsif** *expr* **then** *stmts*)\*  
    (**else** *stmts*)?  
    **end if**;
- ▶ **case** *expr* **is**  
    (**when** *choices* => *stmts*)\*  
    **end case**;

Note: **when...else** and **with...select** *not* allowed

# Part IV

## Sequential Logic


# Basic D Flip-Flop

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity flipflop is  
  port (Clk, D : in  std_logic;  
        Q      : out std_logic);  
end flipflop;
```

```
architecture imp of flipflop is  
begin
```

```
  process (Clk)  -- Sensitive only to Clk  
  begin  
    if rising_edge(Clk) then -- Only on the rising edge of Clk  
      Q <= D;  
    end if;  
  end process;
```


```
end imp;
```

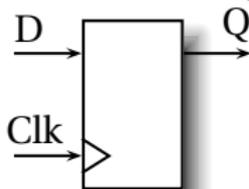
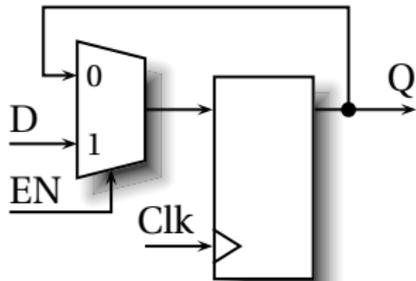
## Flip-Flop with Latch Enable

```
library ieee;
use ieee.std_logic_1164.all;
entity flipflop_enable is
    port (Clk, Reset, D, EN : in std_logic;
          Q                   : out std_logic);
end flipflop_enable;

architecture imp of flipflop_enable is
begin
    process (Clk)
    begin
        if rising_edge(Clk) then
            if EN = '1' then
                Q <= D;
            end if;
        end if;
    end process;
end imp;
```



## Flip-Flop with Synchronous Reset

```
library ieee;
use ieee.std_logic_1164.all;
entity flipflop_reset is
    port (Clk, Reset, D : in std_logic;
          Q           : out std_logic);
end flipflop_reset;

architecture imp of flipflop_reset is
begin
    process (Clk)
    begin
        if rising_edge(Clk) then
            if Reset = '1' then
                Q <= '0';
            else
                Q <= D;
            end if;
        end if;
    end process;
end imp;
```

## Four-bit binary counter



```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity counter is
    port(Clk, Reset : in std_logic;
         Q          : out unsigned(3 downto 0));
end counter;
architecture imp of counter is
    signal count : unsigned(3 downto 0);
begin
    process (Clk)
    begin
        if rising_edge(Clk) then
            if Reset = '1' then count <= (others => '0');
            else count <= count + 1;
            end if;
        end if;
    end process;
    Q <= count;    -- copy count to output
end imp;
```

## Eight-bit serial in/out shift register

```
library ieee;
use ieee.std_logic_1164.all;

entity shifter is
  port ( Clk, SI : in  std_logic;
         SO  : out std_logic);
end shifter;

architecture impl of shifter is
  signal tmp : std_logic_vector(7 downto 0);
begin
  process (Clk)
  begin
    if rising_edge(Clk) then
      tmp <= tmp(6 downto 0) & SI; -- & is concatenation
    end if;
  end process;

  SO <= tmp(7); -- Copy to output
end impl;
```

# Synchronous RAM

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity ram_32_4 is
  port (
    Clk, WE : in std_logic; -- Clock and write enable
    addr    : in unsigned(4 downto 0);
    di      : in unsigned(3 downto 0); -- Data in
    do      : out unsigned(3 downto 0)); -- Data out
end ram_32_4;
architecture imp of ram_32_4 is
  type ram_type is array(0 to 31) of unsigned(3 downto 0);
  signal RAM : ram_type;
begin
  process (Clk) begin
    if rising_edge(Clk) then
      if we = '1' then RAM(TO_INTEGER(addr)) <= di;
                       do <= di; -- write-through
      else do <= RAM(TO_INTEGER(addr));
      end if; end if;
    end process;
end imp;
```



## A small ROM

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity rom_32_4 is
    port (Clk, en : in std_logic;
          addr    : in unsigned(3 downto 0);
          data    : out unsigned(3 downto 0));
end rom_32_4;
architecture imp of rom_32_4 is
type rom_type is array (0 to 15) of unsigned(3 downto 0);
constant ROM : rom_type :=
    (X"1", X"2", X"3", X"4", X"5", X"6", X"7", X"8",
     X"9", X"A", X"B", X"C", X"D", X"E", X"F", X"1");
begin
process (Clk)
begin
    if rising_edge(Clk) then
        if en = '1' then data <= ROM(TO_INTEGER(addr)); end if;
        end if;
end process;
end imp;
```

## Variables and Signals

```
library ieee; use ieee.std_logic_1164.all;
entity twoshiftreg is
  port(clk, si1, si2 : in std_logic;
        so1, so2 : out std_logic);
end twoshiftreg;
architecture imp of twoshiftreg is
  signal sr1 : std_logic_vector(1 downto 0); -- global
begin
  process (clk)
    variable sr2 : std_logic_vector(1 downto 0); -- process-only
  begin
    if rising_edge(clk) then
      sr1(1) <= si1;      -- Effect seen only after next clk
      sr1(0) <= sr1(1); -- Any order works
      so1 <= sr1(0);

      so2 <= sr2(0);
      sr2(0) := sr2(1); -- Effect seen immediately
      sr2(1) := si2;    -- Must be in this order
    end if;
  end process;
end imp;
```

## Variables vs. Signals

| <b>Property</b> | <b>Variables</b>                           | <b>Signals</b>  |
|-----------------|--|---|
| Scope           | Local to process                           | Visible throughout architecture                           |
| Assignment      | Felt immediately (e.g., in next statement) | Only visible after clock rises (i.e., process terminates) |


Lesson: use variables to hold temporary results and state to be hidden within a process. Otherwise, use signals.

## Constants: A VGA sync generator

```
library ieee; use ieee.std_logic_1164.all; use ieee.numeric_std.all;
entity sync_gen is
    port (clk : in std_logic; hs, vs : out std_logic);
end sync_gen;


architecture rtl of sync_gen is
    constant HTOTAL : integer := 800; constant HSYNC : integer := 96;
    constant VTOTAL : integer := 525; constant VSYNC : integer := 2;
    signal hcount, vcount : unsigned(9 downto 0);
begin
    process (clk)
    begin
        if rising_edge(clk) then
            if hcount = HTOTAL - 1 then
                if vcount = VTOTAL - 1 then
                    hcount <= (others => '0'); hs <= '1';
                    if vcount = VSYNC then vs <= '1';
                    vcount <= vcount + 1;
                    end if;
                else
                    if vcount = VSYNC then vs <= '0'; end if;
                    vcount <= vcount + 1;
                    end if;
            else
                if hcount = HSYNC then hs <= '0'; end if;
                hcount <= hcount + 1;
                end if;
            end if;
        end process;
    end rtl;
```

# Rocket Science: FSMs

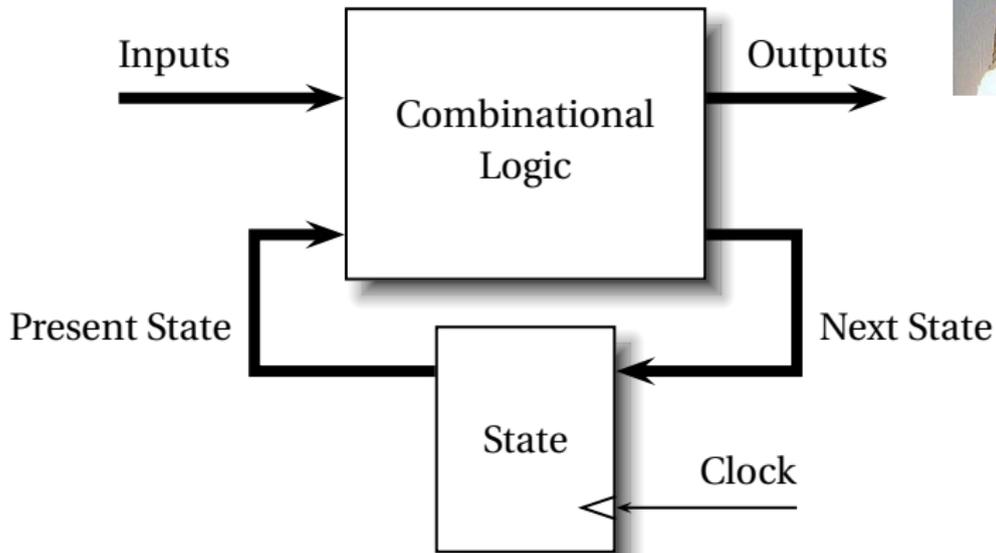

This is a *Mealy* FSM: outputs may depend directly on inputs.

## Moore FSMs

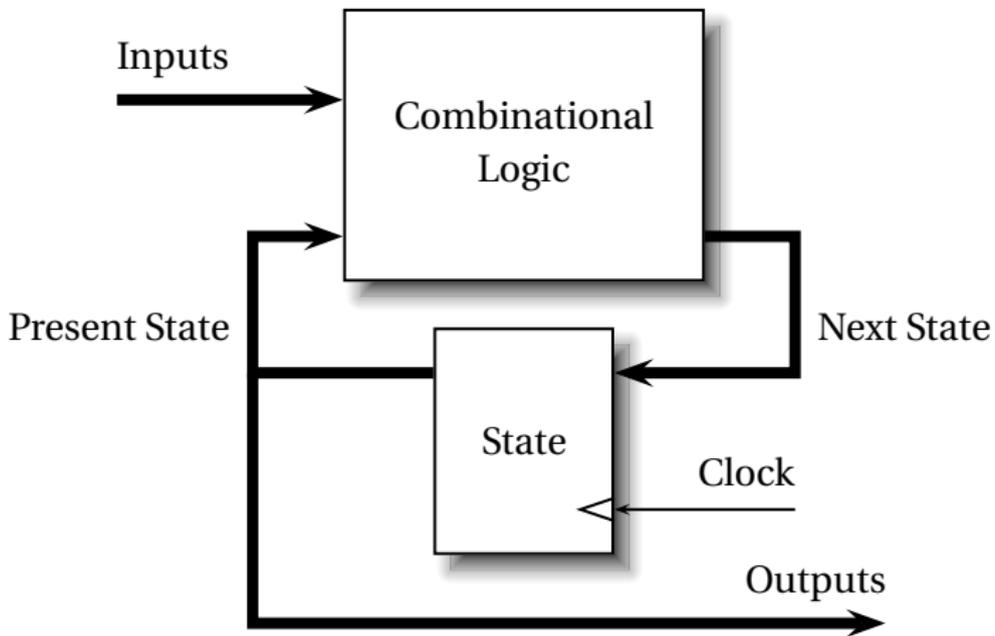

This is a *Moore* FSM: outputs come from state bits.

## Coding Moore State Machines


```
library ieee; use ieee.std_logic_1164.all;
entity threecount is
  port(clk, reset, count : in std_logic; at0 : out std_logic);
end threecount;
architecture moore of threecount is
  type states is (ZERO, ONE, TWO); -- Compiler encodes states
begin
  process (clk)
    variable state : states;
  begin
    if rising_edge(clk) then
      if reset = '1' then state := ZERO;
      else case state is
        when ZERO => if count = '1' then state := ONE; end if;
        when ONE  => if count = '1' then state := TWO; end if;
        when TWO  => if count = '1' then state := ZERO; end if;
      end case;
    end if;
    if state = ZERO then at0 <= '1'; else at0 <= '0'; end if;
  end if;
end process; end moore;
```

## Coding Mealy State Machines

```
architecture mealy of ... is
type states is (IDLE, STATE1, ...);
signal state, next_state : states;
begin
process (clk) -- Sequential process
begin
    if rising_edge(clk) then state <= next_state; end if;
end process;

process (reset, state, i1, i2, ... ) -- Combinational process
begin
    next_state <= state; -- Default: hold
    if reset = '1' then
        next_state <= IDLE;
    else
        case state is
        when IDLE =>
            if i1 = '1' then
                next_state <= STATE1;
            end if;
        when STATE1 =>
```

# The Traffic Light Controller

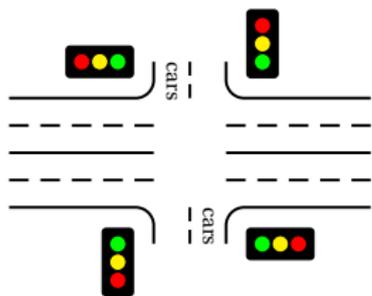


This controls a traffic light at the intersection of a busy highway and a farm road. Normally, the highway light is green but if a sensor detects a car on the farm road, the highway light turns yellow then red. The farm road light then turns green until there are no cars or after a long timeout.

Then, the farm road light turns yellow then red, and the highway light returns to green. The inputs to the machine are the car sensor, a short timeout signal, and a long timeout signal. The outputs are a timer start signal and the colors of the highway and farm road lights.

Source: Mead and Conway, *Introduction to VLSI Systems*, 1980, p. 85.

# FSM for the Traffic Light Controller

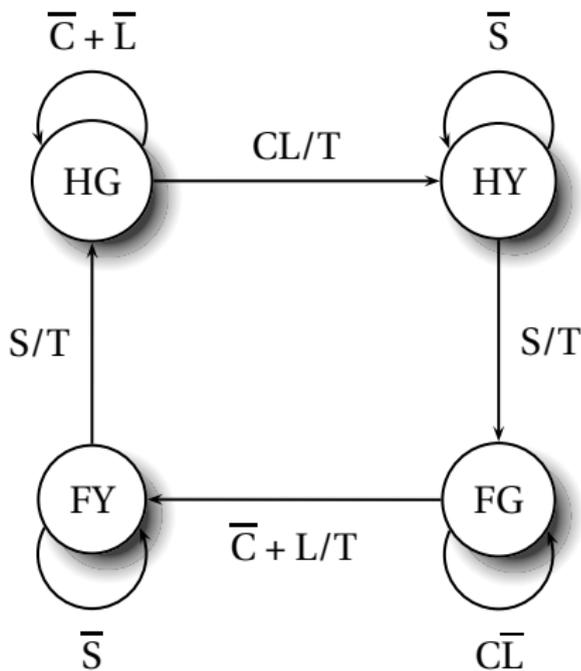

C: Car sensor  
 S: Short timeout  
 L: Long timeout  
 T: Start timer

| St | Hwy | Farm |
|----|-----|------|
| HG | G   | R    |
| HY | Y   | R    |
| FG | R   | G    |
| FY | R   | Y    |

## Traffic Light Controller in VHDL

```
library ieee;
use ieee.std_logic_1164.all;
entity tlc is
    port (clk, reset           : in  std_logic;
          cars, short, long   : in  std_logic;
          highway_yellow, highway_red : out std_logic;
          farm_yellow, farm_red   : out std_logic;
          start_timer          : out std_logic);
end tlc;

architecture imp of tlc is
type states is (HG, HY, FY, FG);
signal state, next_state : states;
begin
    process (clk)    -- Sequential process
    begin
        if rising_edge(clk) then
            state <= next_state;
        end if;
    end process;
end architecture;
```

## TLC in VHDL, continued

```
process (state, reset, cars, short, long)
begin
  if reset = '1' then
    start_timer <= '1'; next_state <= HG;
  else
    case state is
      when HG =>
        highway_yellow <= '0'; highway_red    <= '0';
        farm_yellow    <= '0'; farm_red      <= '1';
        if cars = '1' and long = '1' then
          start_timer <= '1'; next_state <= HY;
        else start_timer <= '0'; next_state <= HG;
        end if;
      when HY =>
        highway_yellow <= '1'; highway_red    <= '0';
        farm_yellow    <= '0'; farm_red      <= '1';
        if short = '1' then
          start_timer <= '1'; next_state <= FG;
        else start_timer <= '0'; next_state <= HY;
        end if;
    end case;
  end if;
end process;
```

## TLC in VHDL, concluded

```
when FG =>
    highway_yellow <= '0'; highway_red    <= '1';
    farm_yellow    <= '0'; farm_red      <= '0';
    if cars = '0' or long = '1' then
        start_timer <= '1'; next_state <= FY;
    else start_timer <= '0'; next_state <= FG;
    end if;
when FY =>
    highway_yellow <= '0'; highway_red    <= '1';
    farm_yellow    <= '1'; farm_red      <= '0';
    if short = '1' then
        start_timer <= '1'; next_state <= HG;
    else start_timer <= '0'; next_state <= FY;
    end if;
end case;
end if;
end process;

end imp;
```

## Part V

# Summary of the Three Modeling Styles

## Three Modeling Styles: Dataflow (1)

Combinational logic described by expressions

```
-- Simple case
a <= x and y;

-- When...else selector
b <= '1' when x = y else
    '0';

--- With..select selector
with x select
c <=
    '1' when '0',
    '0' when '1',
    'X' when others;
```

## Procedural Combinational (2)

Combinational logic described by statements and expressions


```
process (x, y) -- Should be sensitive to every signal it reads
begin
  a <= x and y;
  if x = y then
    b <= '1';
  else
    b <= '0';
  end if;
  case x of
    '0' => c <= '1';
    '1' => c <= '0';
    others => c <= 'X';
  end case;
end process;
```

## Three Styles: Procedural Sequential (3)

Combinational logic driving flip-flops described by statements and expressions.

```
process (clk) -- Sensitive only to the clock
begin
  if rising_edge(clk) then -- Always check for rising edge
    a <= x and y;
    if x = y then
      b <= '1';
    else
      b <= '0';
    end if;
    case x of
      '0' => c <= '1';
      '1' => c <= '0';
      others => c <= 'X';
    end case;
  end if;
end process;
```


# Ten Commandments of VHDL

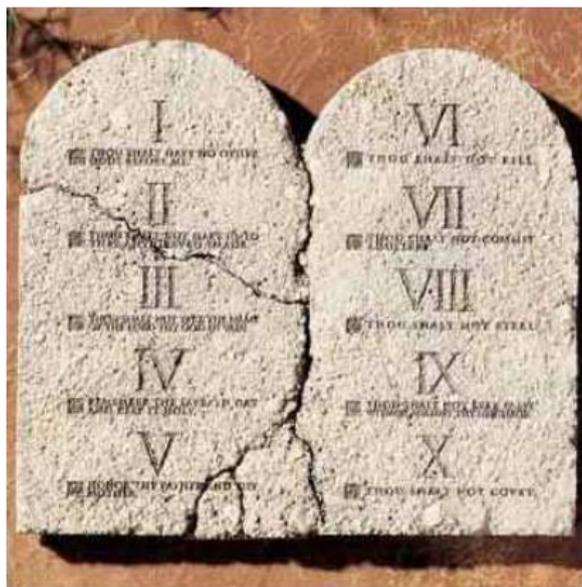


# I: Thou Shalt Design Before Coding

- ▶ Know the structure of what you are designing first.
- ▶ Draw a block diagram of the datapath
- ▶ Understand the timing (draw diagrams)
- ▶ Draw bubble-and-arc diagrams for FSMs
- ▶ Only once you have a design should you start coding in VHDL
- ▶ VHDL is only a way to ask for component


## Block Diagram of a Character Gen.

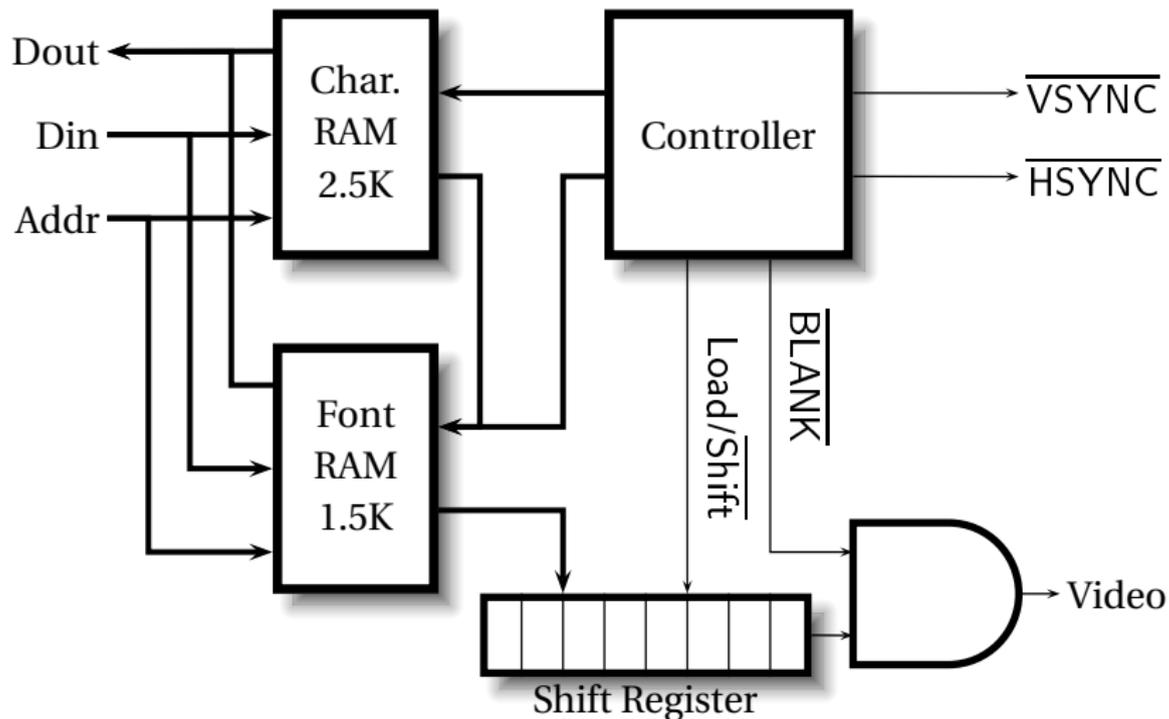


# Pixel-Level Timing

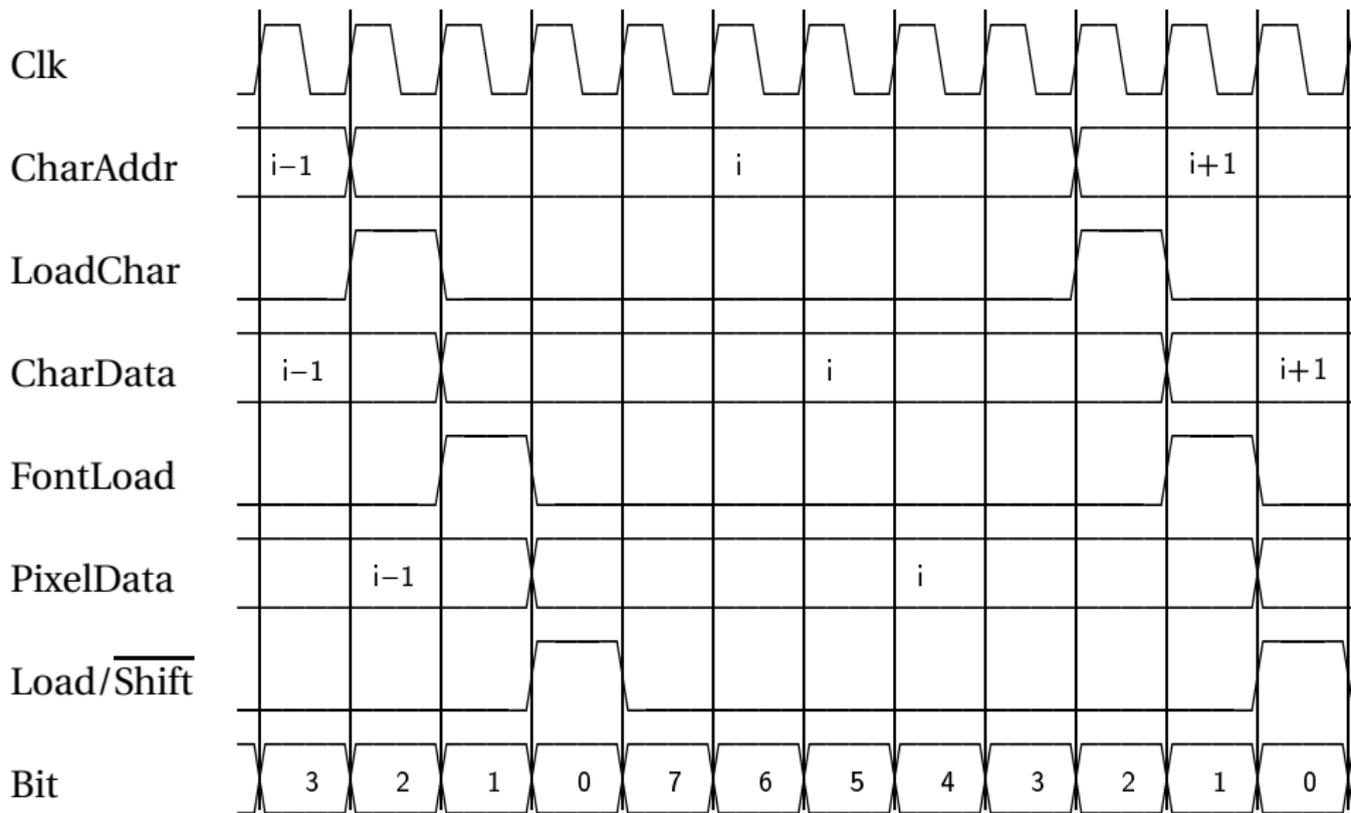

# Start-of-line Detail

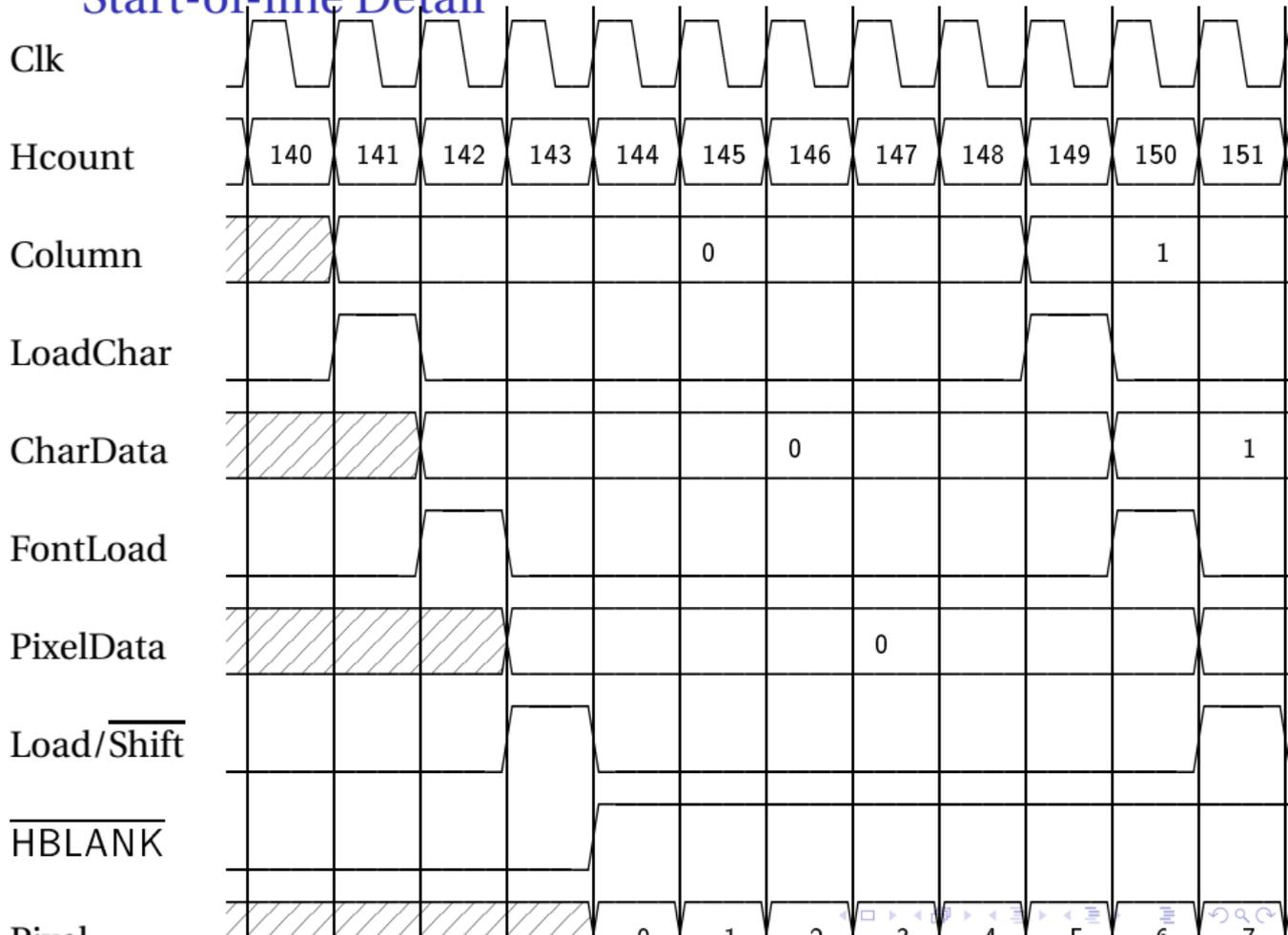

# End-of-line detail

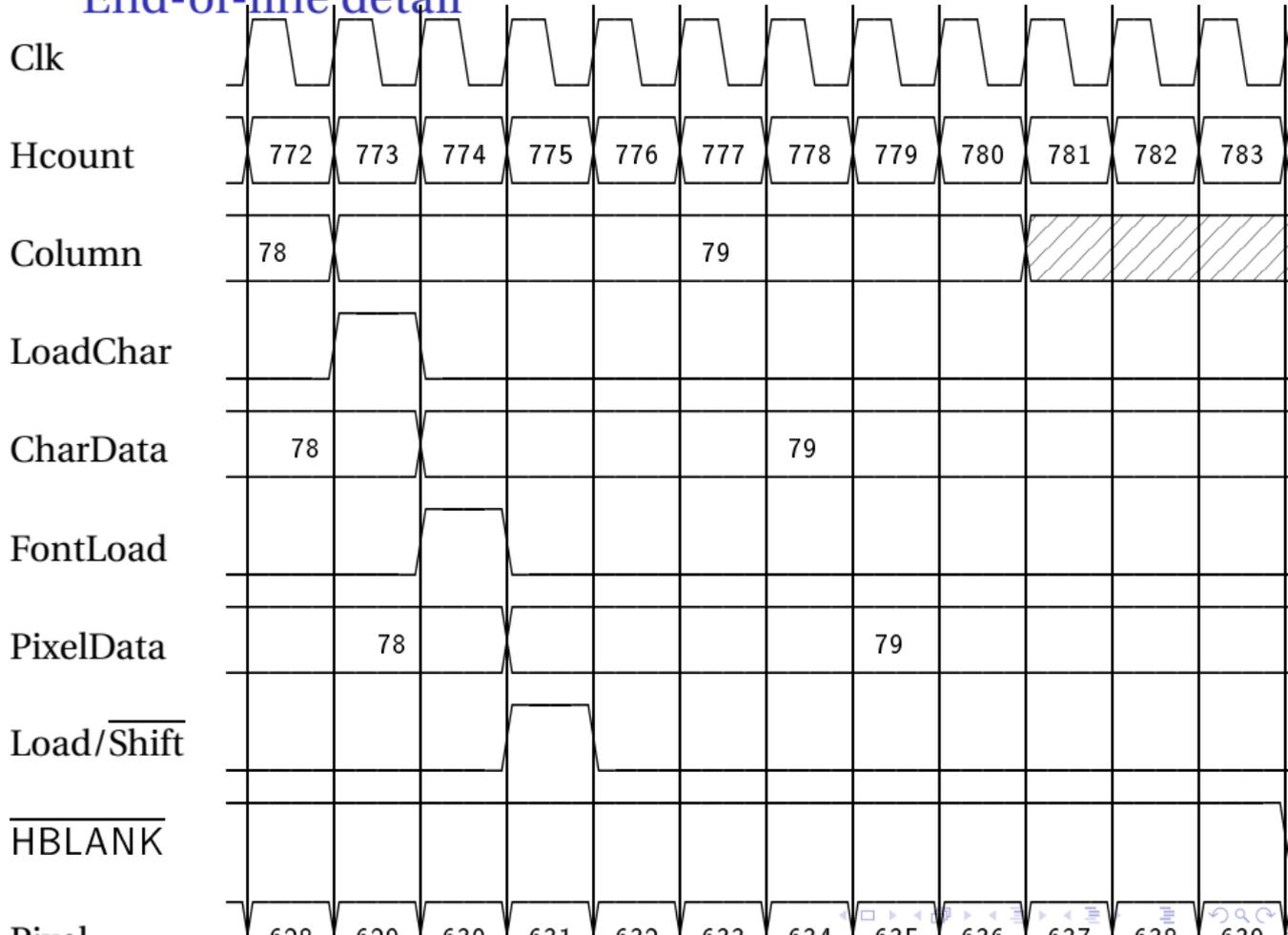

## II: Thou Shalt be Synchronous

- ▶ One global clock
- ▶ Flip-flops generate inputs to combinational logic, which computes inputs to flip-flops
- ▶ Exactly one value per signal per clock cycle
- ▶ Do not generate asynchronous reset signals; only use them if they are external
- ▶ Edge-triggered flip-flops only. Do not use level-sensitive logic.
- ▶ Do not generate clock signals. Use multiplexers to create “load enable” signals on flip-flops.

### III: Thou Shalt Be Sensitive

Combinational processes: list all process inputs

```
process (state, long)
begin
  if reset = '1' then
    next_state <= HG;
    start_timer <= '1';
  else
    case state is
      when HG =>
        farm_yellow <= '0';
        if cars = '1' and long = '1' then
          next_state <= HY;
        else
          next_state <= HG;
        end if;
      when HY =>
        farm_yellow <= '0';
        if short = '1' then
          next_state <= FG;
        else
          next_state <= HY;
        end if;
    end case;
  end if;
end process;
```

```
process (state, reset, cars, short)
begin
  if reset = '1' then
    next_state <= HG;
    start_timer <= '1';
  else
    case state is
      when HG =>
        farm_yellow <= '0';
        if cars = '1' and long = '1' then
          next_state <= HY;
        else
          next_state <= HG;
        end if;
      when HY =>
        farm_yellow <= '0';
        if short = '1' then
          next_state <= FG;
        else
          next_state <= HY;
        end if;
    end case;
  end if;
end process;
```

### III: Thou Shalt Be Sensitive

Sequential processes: always include the clock. Include reset if asynchronous, and nothing else.

```
process (Clk, D)
begin
  if rising_edge(Clk) then
    Q <= D;
  end if;
end process;

process (Clk, D)
begin
  if reset = '1' then
    Q <= '0';
  else
    if rising_edge(Clk) then
      Q <= D;
    end if;
  end if;
end process;
```

```
process (Clk)
begin
  if rising_edge(Clk) then
    Q <= D;
  end if;
end process;

process (Clk, reset)
begin
  if reset = '1' then
    Q <= '0';
  else
    if rising_edge(Clk) then
      Q <= D;
    end if;
  end if;
end process;
```

## IV: Thou Shalt Assign All Outputs

Synthesis infers level-sensitive latches if sometimes you do not assign an output.

```
process (state, input)
begin
  case state is
    when S1 =>
      if input = '1' then
        output <= '0';
      end if;
    when S2 =>
      output <= '1';
    end case;
end process;
```

```
process (state, input)
begin
  case state is
    when S1 =>
      if input = '1' then
        output <= '0';
      else
        output <= '1';
      end if;
    when S2 =>
      output <= '1';
    end case;
end process;
```

## “Default” values are convenient

-- OK

```
process (state, input)
begin
  case state is
    when S1 =>
      if input = '1' then
        output <= '0';
      else
        output <= '1';
      end if;
    when S2 =>
      output <= '1';
  end case;
end process;
```

-- Better

```
process (state, input)
begin
  output <= '1';
  case state is
    when S1 =>
      if input = '1' then
        output <= '0';
      end if;
  end case;
end process;
```

## V: Thou Shalt Enumerate States

Better to use an enumeration to encode states:

```
type states is (START, RUN, IDLE, ZAPHOD);  
signal current, next : states;  
  
process (current)  
  begin  
    case current is  
      when START => ...  
      when RUN => ...  
      when IDLE => ...  
    end case;  
  end process;
```

Running this produces a helpful error:

```
Compiling vhdl file "/home/cristi/cs4840/lab4/main.vhd" in  
Entity <system> compiled.
```

```
ERROR:HDLParasers:813 - "/home/cristi/cs4840/lab4/main.vhd"  
Enumerated value zaphod is missing in case.
```

```
-->
```

VI:



(There is no rule six)

## VII: Thou Shalt Avoid Async

Only use asynchronous reset when there is one global signal from outside.

```
-- OK for external Reset
process (Clk, Reset)
begin
  if Reset = '1' then
    Q <= '0';
  else
    if rising_edge(Clk) then
      Q <= D;
    end if;
  end if;
end process;
```

```
-- Better
process (Clk)
begin
  if rising_edge(Clk) then
    if Reset = '1' then
      Q <= '0';
    else
      Q <= D;
    end if;
  end if;
end process;
```

Never generate your own asynchronous reset. Generating a synchronous reset is fine

## VIII: Thou Shalt Have One Version

- ▶ Never assume signals from the test bench that are not there on the board
- ▶ It is hard enough to make simulation match the design; do not make it any harder
- ▶ If you must slow down hardware, carefully generate a slower clock and only use that clock globally.

## IX: Thou Shalt Not Test For X Or Z

```
architecture behv of ALU is
  process (A,B,Sel) begin
    case Sel is
      when "00" => Res <= A + B;
      when "01" => Res <= A + (B and Z);
      when "1X" => Res <= A and B;
      when "1Z" => Res <= A or B;
      when others => Res <= "XX";
    end case;
  end process;
end behv;
```

```
architecture behv of ALU is begin
  process(A,B,Sel) begin
    case Sel is
      when "00" => Res <= A + B;
      when "01" => Res <= A + (not B);
      when "10" => Res <= A and B;
      when "11" => Res <= A or B;
      when others => Res <= "XX";
    end case;
  end process;
end behv;
```

This is legal VHDL, but the synthesized circuit won't behave like you expect.

## X: Thou Shalt Not Specify Delays

- ▶ The `wait` statement can delay for a certain amount of time, e.g., `wait 10ns;`
- ▶ Only use it in test benches that are not meant to become hardware
- ▶ Do not use them in the design of your hardware

## Pitfalls: Boolean vs. Std\_logic

Don't assign Boolean to std\_logic.

```
signal a : std_logic;
signal b : unsigned(7 downto 0);

a <= b = x"7E"; -- BAD: result is Boolean, not std_logic
a <= '1' when b = x"7E" else '0'; -- OK
```

Don't test std\_logic in a Boolean context.

```
signal a, b, foo : std_logic;

if a then -- BAD: A is not Boolean
  foo <= '1';
end if;
b <= '0' when a else '1'; -- BAD: a is not Boolean

if a = '1' then -- OK
  foo <= '1';
end if;
b <= '0' when a = '1' else '0'; -- OK
```

## Pitfalls: Inferring a Latch

In a combinational process, make sure all output signals are always assigned.

```
process (x, y)
begin
  if x = '1' then
    y <= '0';
  end if;
  -- BAD: y not assigned when x = '0', synthesis infers latch
end process;
```

```
process (x, y)
begin
  y <= '1'; -- OK: y is always assigned
  if x = '1' then
    y <= '0';
  end if;
end process
```

## Pitfalls: Reading Output Port

```
library ieee;
use ieee.std_logic_1164.all;
entity dont_read_output is
  port ( a : in std_logic;
         x, y : out std_logic );
end dont_read_output;

architecture BAD of dont_read_output is
begin
  x <= not a;
  y <= not x; -- Error: can't read an output port
end BAD;

architecture OK of dont_read_output is
signal x_sig : std_logic;
begin
  x_sig <= not a;
  x <= x_sig; -- x_sig just another name for x
  y <= not x_sig; -- OK
end OK;
```

## Pitfalls: Complex Port Map Args

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity bad_port_map is end bad_port_map;

architecture BAD of bad_port_map is
component bar port (x : in unsigned(5 downto 0) );
end component;
signal a : unsigned(3 downto 0);
begin
    mybar : bar port map ( x => "000" & a); -- BAD
end BAD;

architecture OK of bad_port_map is
component bar port (x : in unsigned(5 downto 0) );
end component;
signal a : unsigned(3 downto 0);
signal aa : unsigned(5 downto 0);
begin
    aa <= "000" & a;
    mybar : bar port map ( x => aa ); -- OK
end OK;
```

# Pitfalls: Combinational Loops

You never really need them.

Drive every signal from exactly one process or concurrent assignment.

Don't build SR latches. Use D flip-flops instead.

# Pitfalls: Clock Gating

Dangerous, difficult to get right.

Use a single, global clock and latch enables to perform the same function.

## Pitfalls: Multiple Clock Domains

If you must, vary the phase and drive clocks directly from flip-flops.

# Part VI

## Writing Testbenches

## Testbenches

One of VHDL's key points: can describe hardware and environment together.

```
-- Explicit delays are allowed
clk <= not clk after 50 ns;

process
begin
  reset <= '0';
  wait for 10 ns;      -- Explicit delay
  reset <= '1';
  wait for a = '1'; -- Delay for an event
  assert b = '1' report "b did not rise" severity failure;
  assert c = '1' report "c=0" severity warning; -- error/note
  wait for 50 ns;    -- Delay for some time
  wait;              -- Halt this process
end process;
```

# Testbench Methodology

- ▶ Always put testbench in a separate .vhd file since it cannot be synthesized.
- ▶ Instantiate block under test and apply desired inputs (clocks, other stimulus)
- ▶ Use **assert** to check conditions
- ▶ Try to emulate hardware environment as closely as possible (no special inputs, etc.)

## A Testbench

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity tlc_tb is -- A testbench usually has no ports
end tlc_tb;

architecture tb of tlc_tb is
    signal clk : std_logic := '0'; -- Must initialize!

    -- One signal per port is typical
    signal reset, cars, short, long : std_logic;
    signal farm_red, start_timer : std_logic;
begin

    clk <= not clk after 34.92 ns; -- 14 MHz
```

## A testbench continued

-- Apply stimulus and check the results

```
process
```

```
begin
```

```
cars <= '0'; short <= '0'; long <= '0'; reset <= '1';
```

```
wait for 100 ns;
```

```
assert start_timer = '1' report "No timer" severity error;
```

```
reset <= '0';
```

```
wait for 100 ns;
```

```
assert farm_red = '1' report "Farm not red" severity error;
```

```
wait;
```

```
end process;
```

-- Instantiate the Unit Under Test

```
 uut : entity work.tlc
```

```
 port map ( clk => clk,      reset => reset,
```

```
            cars => cars,   short => short,
```

```
            long => long,   farm_red => farm_red,
```

```
            start_timer => start_timer);
```

```
end tb;
```