

# **CSEE W3827**

## Fundamentals of Computer Systems Homework Assignment 2

Profs. Stephen A. Edwards & Martha Kim  
Columbia University

Due October 9, 2012 at 11:59 PM


Upload your solution to each problem as a Logisim .circ file to CourseWorks.

1. (20 pts.) Create a circuit for a 4-to-16 decoder using AND gates and inverters only. Arrange and name the inputs and outputs as shown below. Treat  $W$  as the most significant bit and let  $A0$  be true when all inputs are false. Only one of the outputs should ever be true.


$W$	$\rightarrow$	$\rightarrow A0$
$X$	$\rightarrow$	$\rightarrow A1$
$Y$	$\rightarrow$	$\vdots$
$Z$	$\rightarrow$	$\rightarrow A15$

Name your solution "hw2-1.circ" and submit it via Courseworks.

## hw2 #1

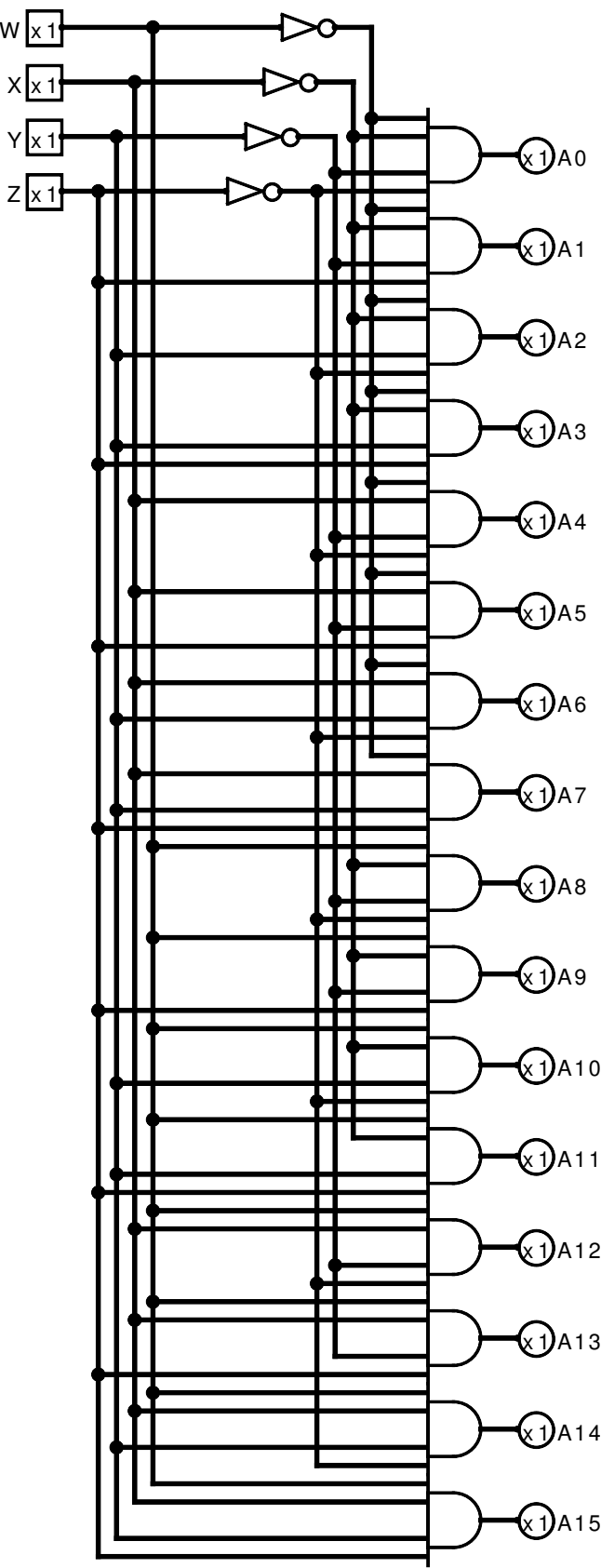

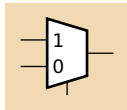2. (10 pts.) In Logisim, implement the logical OR function using just a single two-input MUX (under “Plexers→Multiplexer”; set “include enable” to “no”) and constant “0” and “1” inputs (“Wiring→Constant”). Do not use additional gates.




Draw your inputs and outputs as shown below:

$$\begin{array}{l} A \rightarrow \\ B \rightarrow \end{array} \rightarrow Y$$

Name your solution “hw2-2.circ” and submit it via Courseworks.

hw2 #2

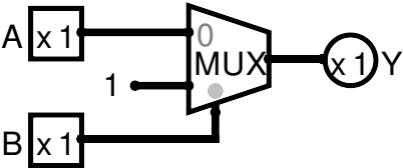


3. (15 pts.) In Logisim, implement  $F = \overline{X}\overline{Y}\overline{Z} + \overline{Y}Z + X\overline{Y}$  using just constants and
- (a) a 3-to-8 decoder (under “Plexers→Decoder.” Set “include enable” to “No” and note the input wires are a bundle at the bottom) and an OR gate;
  - (b) an 8 input mux; and
  - (c) a 4 input mux whose select inputs are  $X$  and  $Y$ , and an inverter.


Arrange your inputs and outputs as shown below and name your files “hw2-3a.circ,” “hw2-3b.circ,” and “hw2-3c.circ.”

$X \rightarrow$   
 $Y \rightarrow \quad \rightarrow F$   
 $Z \rightarrow$

hw2 #3a

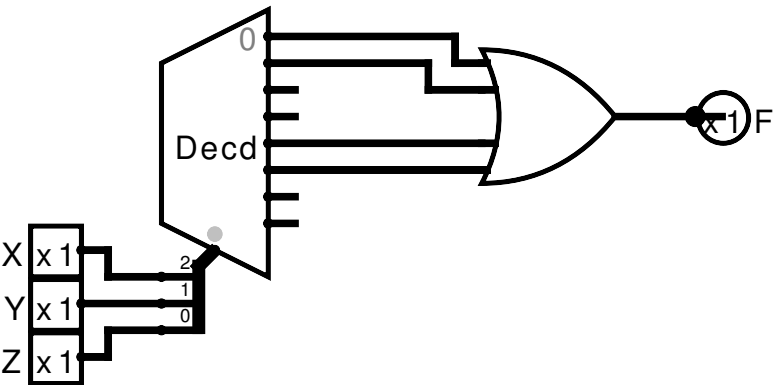


hw2 #3b

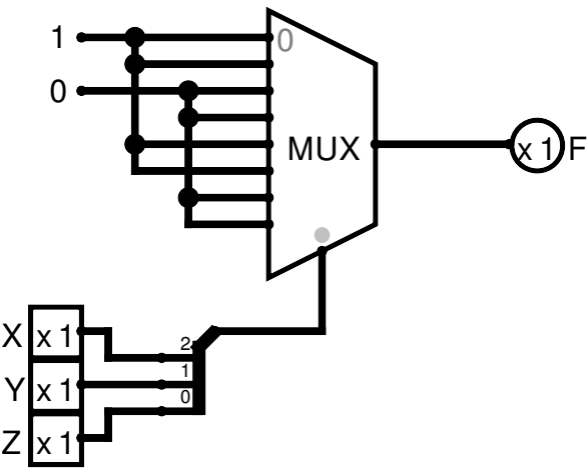



# hw2 #3c

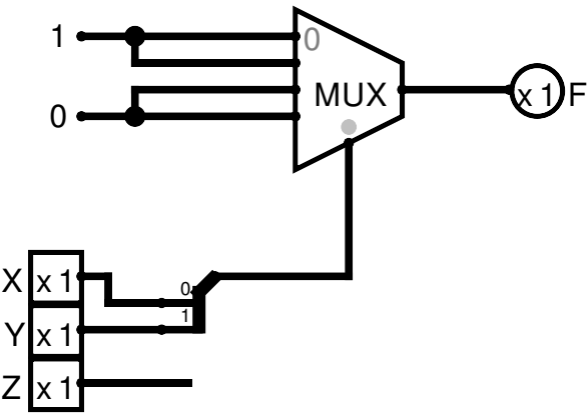

4. (20 pts.) Implement an eight-input mux using three four-input muxes and no other gates (constants are OK).


Arrange your inputs and outputs as shown below and name your solution "hw2-4.circ"

A0 →  
A1 →  
⋮  
A7 →     → F  
X →  
Y →  
Z →

Here, A0 through A7 are the eight inputs, and X, Y, and Z are the three selects. X is the most significant bit, selecting between, e.g., A0 and A4.

Name your solution "hw2-4.circ."

## hw2 #4

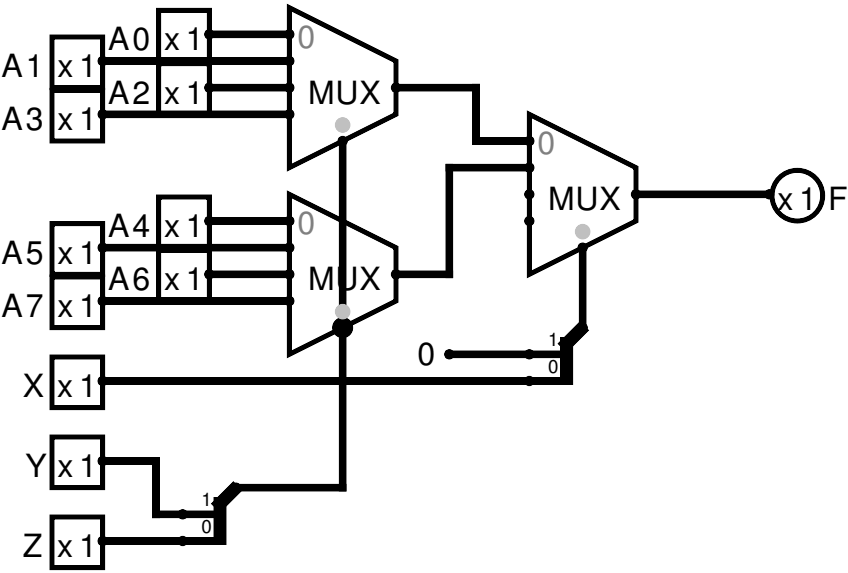

5. (35 pts.) Implement a three-bit binary carry-lookahead adder "hw2-5.circ."  $A_0$  through  $A_2$  and  $B_0$  through  $B_2$  are the two binary inputs ( $A_0$  and  $B_0$  are the LSBs),  $C_0$  is the carry in, and  $Y_0$  through  $Y_3$  is the four-bit output. Arrange your inputs and outputs like this:

$A_2$	$\rightarrow$	
$B_2$	$\rightarrow$	$\rightarrow Y_3$
$A_1$	$\rightarrow$	$\rightarrow Y_2$
$B_1$	$\rightarrow$	$\rightarrow Y_1$
$A_0$	$\rightarrow$	$\rightarrow Y_0$
$B_0$	$\rightarrow$	
$C_0$	$\rightarrow$	

- (a) As text labels in your solution, write expressions for  $G_0, \dots, G_2$  and  $P_0, \dots, P_2$ , the carry generate and propagate functions, in terms of the inputs.
- (b) Write sum-of-product expressions for  $C_1, \dots, C_3$  in terms of the  $G$ 's,  $P$ 's, and  $C_0$ . Use  $+$  for OR,  $\&$  for AND, and  $!$  for NOT.
- (c) Write the equations for the  $Y$ 's in terms of these. Use  $\wedge$  for XOR.
- (d) Implement the carry-lookahead adder circuit corresponding to these equations using inverters, AND, NAND, OR, NOR, and

# hw2 #5

