

CSEE W3827
Fundamentals of Computer Systems
Homework Assignment 1

Prof. Stephen A. Edwards
Columbia University

Due Tuesday, June 9th, 2015 at 5:30 PM

Print this out and turn it in. Enter answers on the computer or manually on the printout.

This homework requires you to use Logisim, which you can download from <http://www.cburch.com/logisim/>

Name: SOLUTION

Uni:

1. (5 pts.) What are the values, in decimal, of the following bytes if they are interpreted as 8-bit numbers in

	00010011	10011010
binary	19	154
one's complement	19	-101
two's complement	19	-102

2. (5 pts.) Complete the truth table for the following Boolean functions:

$$a = X\bar{Y} + \bar{X}YZ + \bar{X}\bar{Z}$$

$$b = (X + \bar{Y})(X + Z)(\bar{X} + Z)$$

X	Y	Z	a	b
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	0
1	0	0	1	0
1	0	1	1	1
1	1	0	0	0
1	1	1	0	1


3. (20 pts.) Consider the function F whose truth table is shown below

W	X	Y	Z	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

(a) Write the function F in sum-of-minterms form. Two are given.

$$\overline{W}\overline{X}Y\overline{Z} + \overline{W}\overline{X}YZ + \overline{W}X\overline{Y}Z + \overline{W}XYZ + WX\overline{Y}\overline{Z} +$$

(b) Fill in this Karnaugh map for F

 

(c) Use your Karnaugh map to write a minimal sum-of-products representation for F

$$WX\overline{Y} + \overline{W}XZ + \overline{W}\overline{X}Y$$

In Logisim,

- (d) Implement the circuit corresponding to your minimal sum-of-products representation. Verify your circuit using Logisim's Combinational Analysis feature (Project→Analyze Circuit).

Print your solution and attach it.


- (e) Use your Karnaugh map to write a minimal product-of-sums representation for F.

$$(!W+!Y)(X+Y)(W+!X+Z)$$


- (f) Implement the circuit corresponding to your minimal product-of-sums. Again, verify your circuit.

Print your solution and attach it.

Circuit for 3(d)

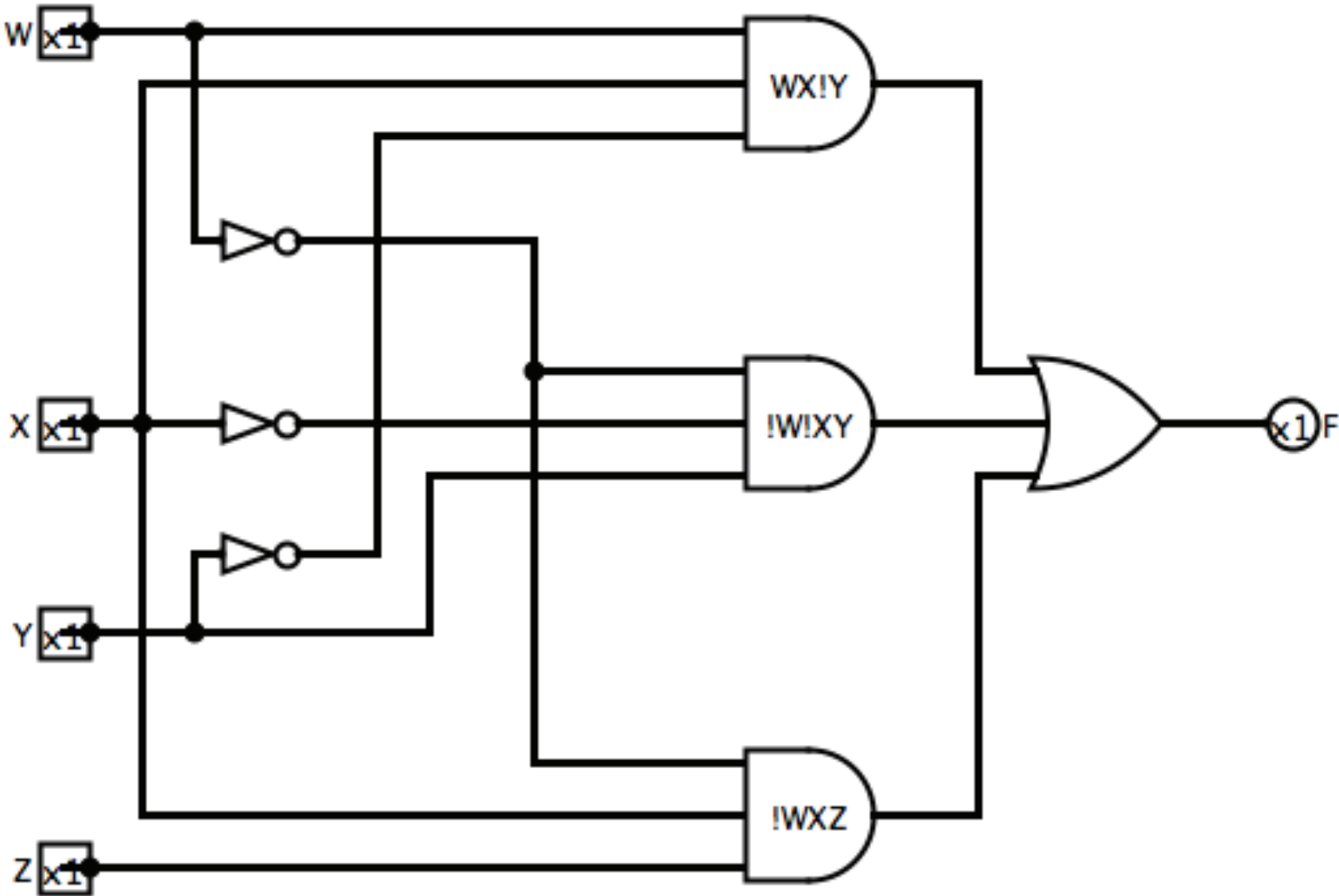


Circuit for 3(f)

 

4. (20 pts.) Create a circuit for a 4-to-10 decoder using AND gates and inverters only. Arrange and name the inputs and outputs as shown below. Treat W as the most significant bit. Only one of the outputs should ever be true.

W	\rightarrow	\rightarrow	$A0$
X	\rightarrow	\rightarrow	$A1$
Y	\rightarrow	\vdots	
Z	\rightarrow	\rightarrow	$A9$

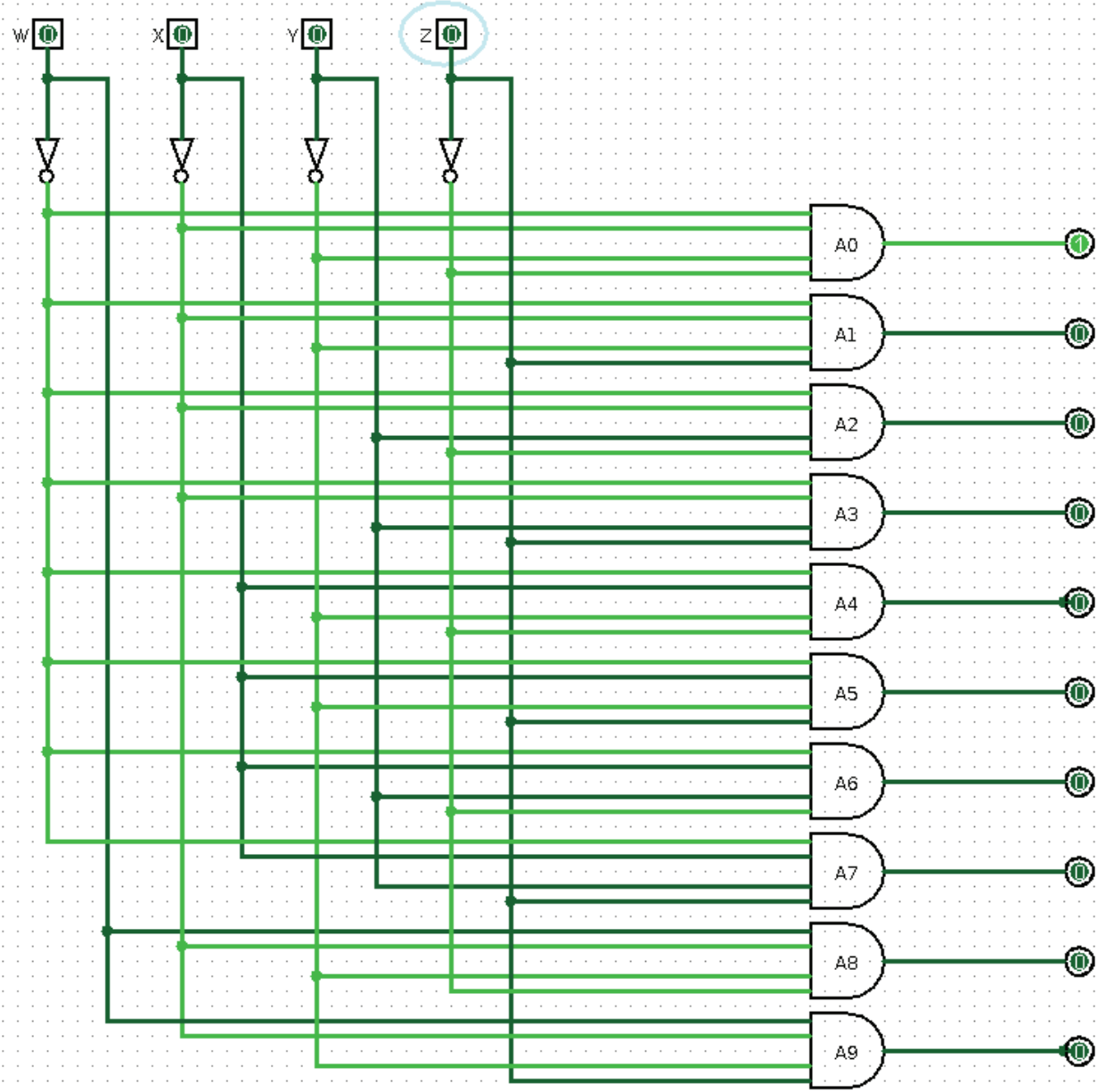
Implement your circuit in Logisim, verify it, and print and attach it.




5. (15 pts.) In Logisim, implement $F = XY\bar{Z} + YZ + \bar{X}Y$ using just constants and

 - (a) a 3-to-8 decoder (under “Plexers→Decoder.” Set “include enable” to “No” and note the input wires are a bundle at the bottom) and an OR gate;
- (b) an 8 input mux; and
- (c) a 4 input mux whose select inputs are X and Y , and an inverter.


Implement each of these circuits in Logisim, verify them, and print and attach them.




Circuit for 5(a)

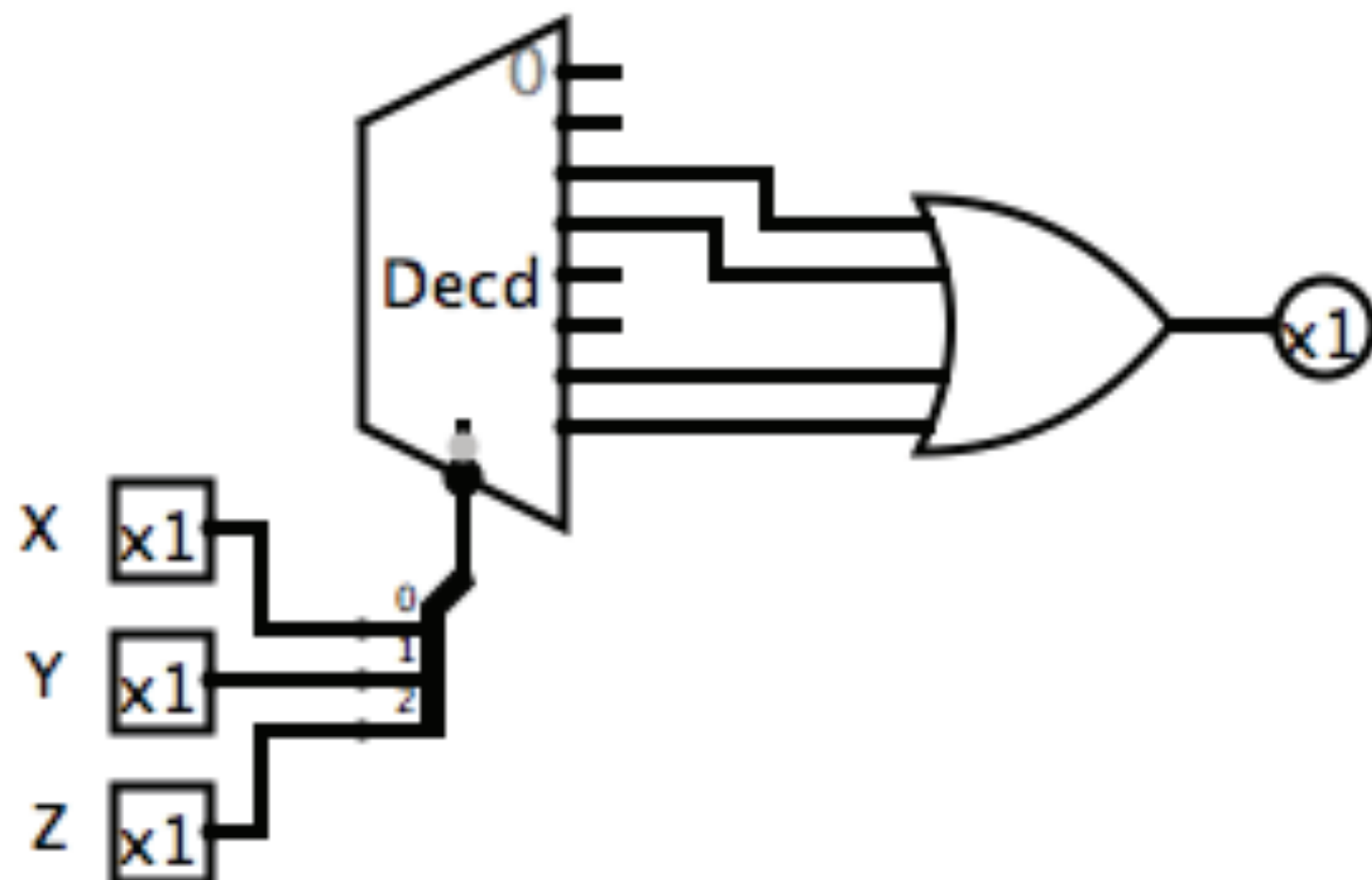

Circuit for 5(b)

 


Circuit for 5(c)

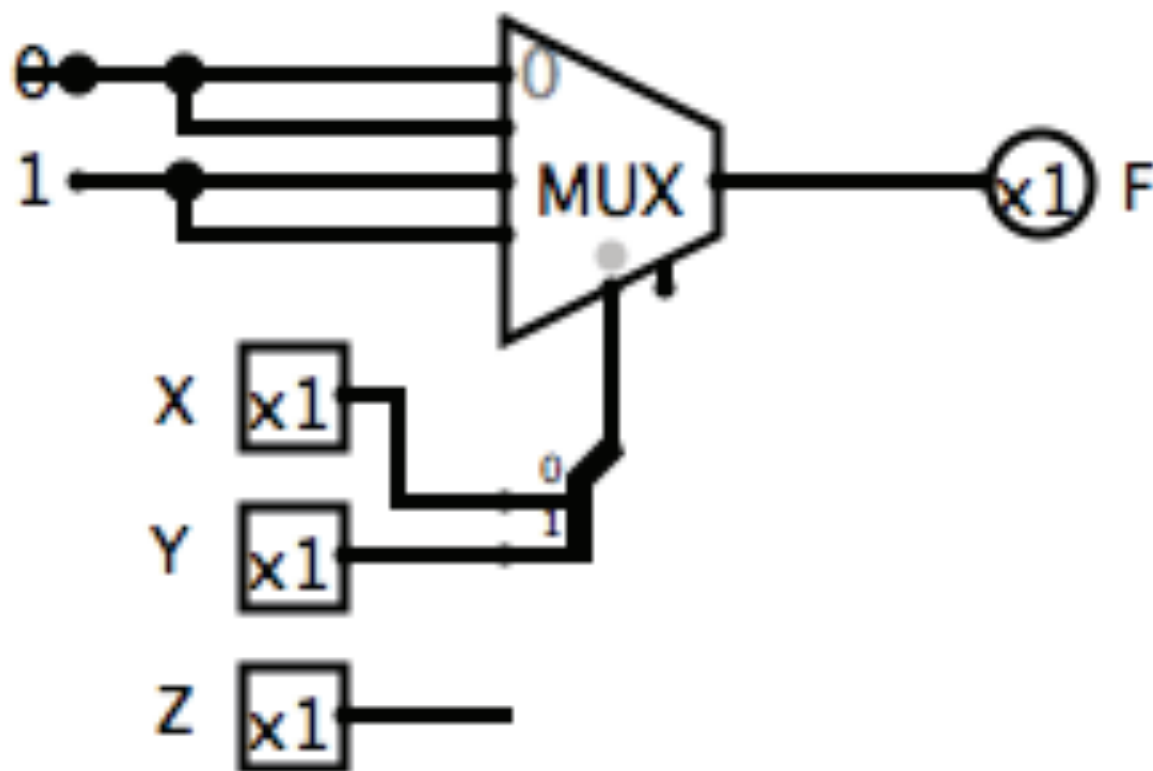

 
6. (15 pts.) Implement an eight-input mux using two-input muxes only (constants are OK).

Arrange your inputs and outputs as shown below.



Here, $A0$ through $A7$ are the eight inputs, and X , Y , and Z are the three selects. X is the most significant bit, selecting between, e.g., $A0$ and $A4$.

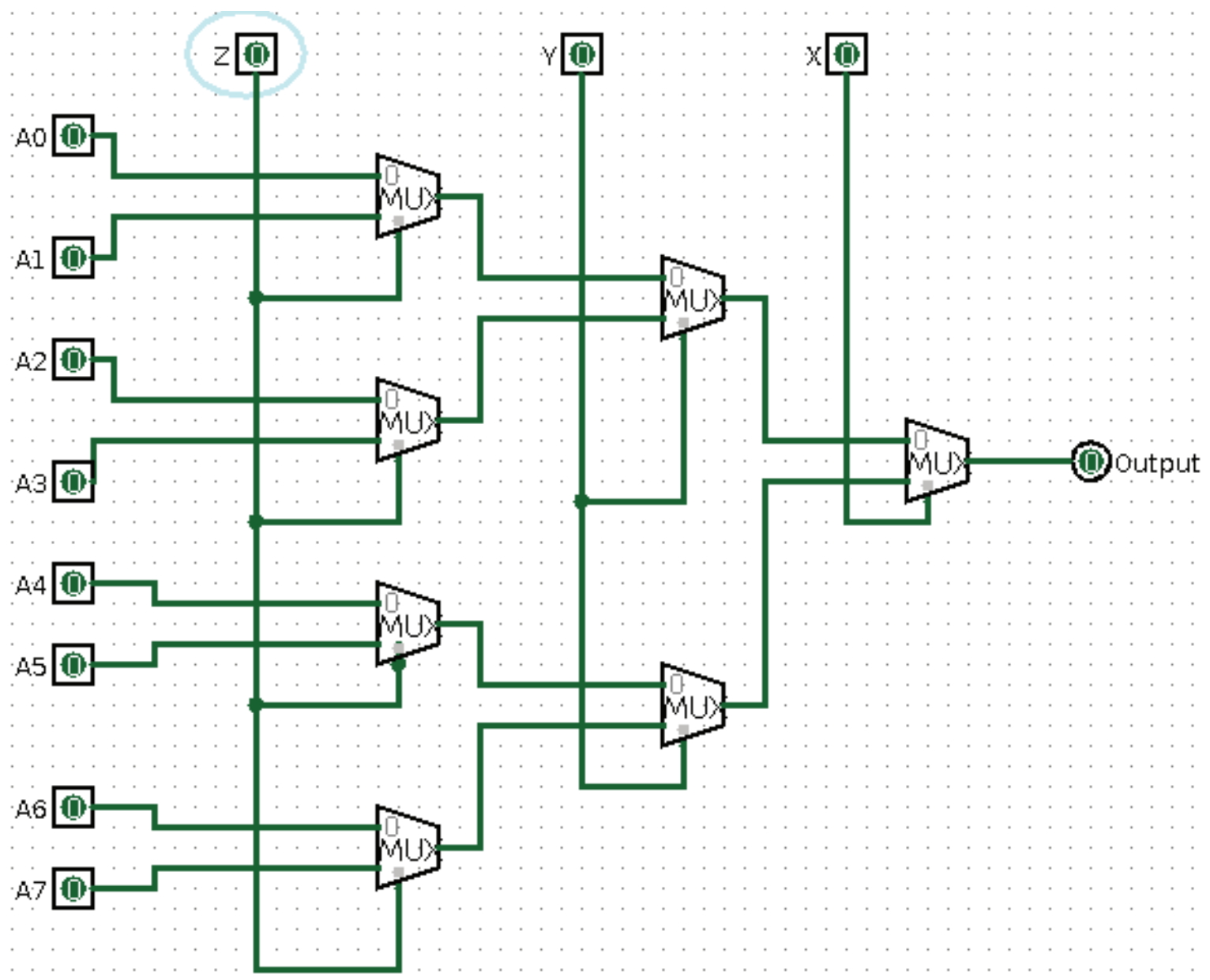Implement your circuit in Logisim, verify it, and print and attach it.



7. (20 pts.) Implement the combinational portion of a three-bit binary counter with an enable input. Give it four inputs, X , Y , Z , and E , and three outputs A , B , and C .

When E is 0, A , B , and C should be X , Y , and Z respectively.

When E is 1, A , B , and C should be X , Y , and Z plus one, with A and X the MSBs.

Your counter should wrap around, i.e., $7 + 1 = 0$.

Implement your circuit in Logisim, verify it, and print and attach it.

Circuit for 7

