# Fundamentals of Computer Systems Transistors, Gates, and ICs

Stephen A. Edwards

**Columbia University** 

Summer 2020

#### Semiconductor

sem·i·con·duc·tor noun

 A substance, such as silicon or germanium, with electrical conductivity intermediate between that of an insulator and a conductor

2. A semiconductor device

#### Sand into Silicon



Silica a.k.a.  $SiO_2$  a.k.a. Quartz  $SiO_2 + 2 C \rightarrow Si + 2 CO$ 



Elemental, amorphous silicon




Monocrystalline Silicon Ingot

## Doping Silicon Makes It a Better Conductor


Undoped (pure) silicon crystal

Not a good conductor

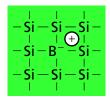

p-type (doped) silicon:


boron atom steals a nearby electron

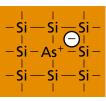


n-type (doped) silicon:

arsenic's extra electron jumps loose


#### A PN Junction aka A Diode

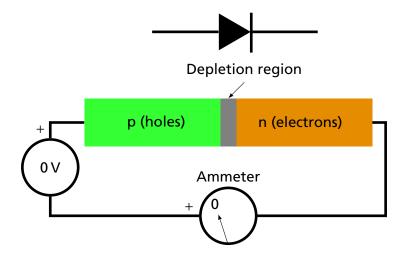


#### A PN Junction aka A Diode

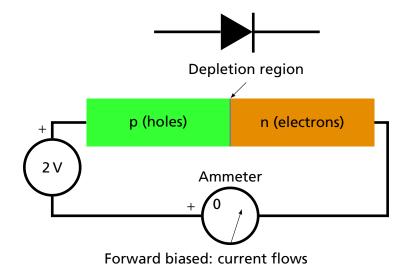


#### A PN Junction aka A Diode

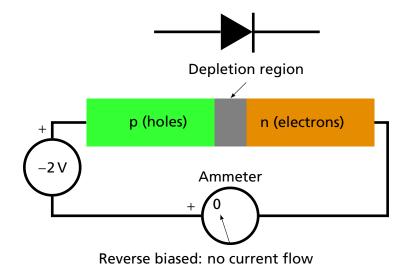


#### An N-Channel MOS Transistor

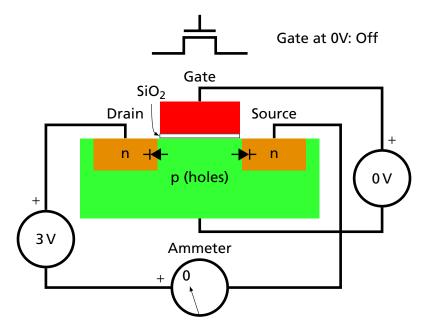

#### An N-Channel MOS Transistor

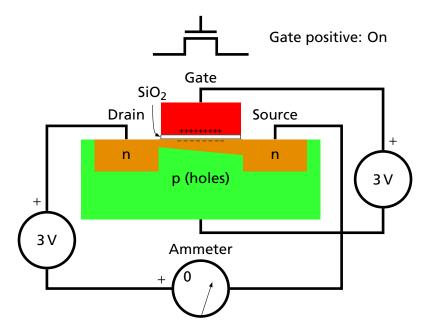

#### The CMOS Inverter

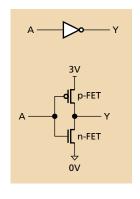


An inverter is built from two MOSFETs:

An n-FET connected to ground

A p-FET connected to the power supply

#### The CMOS Inverter

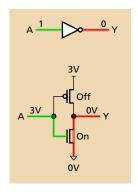


When the input is near the power supply voltage ("1"),

the p-FET is turned off;

the n-FET is turned on, connecting the output to ground ("0").

n-FETs are only good at passing 0's


#### The CMOS Inverter

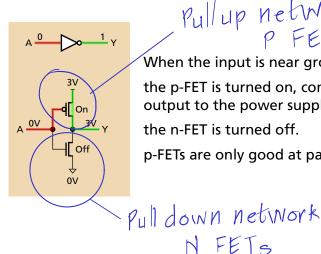



Pullup network

When the input is near ground ("0"), the p-FET is turned on, connecting the output to the power supply ("1"); the n-FET is turned off.

p-FETs are only good at passing 1's

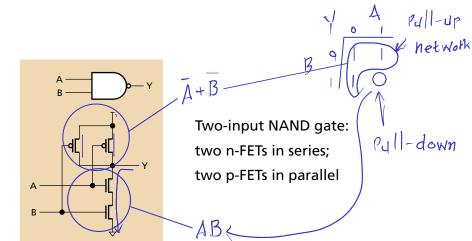

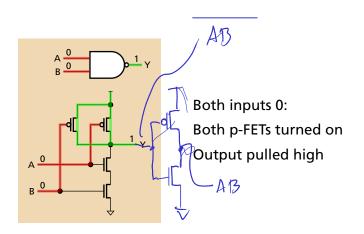

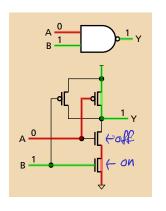


One input 1, the other 0:

One p-FET turned on

Output pulled high

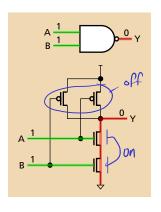One n-FET turned on, but does not control output




Both inputs 1:

Both n-FETs turned on


Output pulled low

Both p-FETs turned off


#### The CMOS NOR Gate

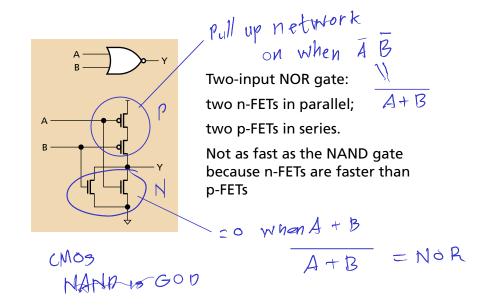

## A CMOS AND-OR-INVERT Gate

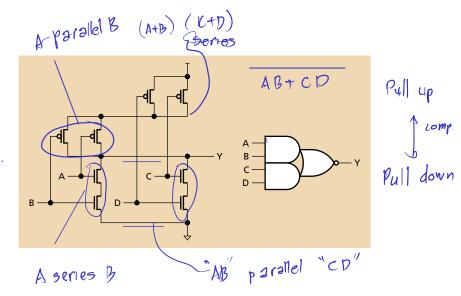


#### Static CMOS Gate Structure

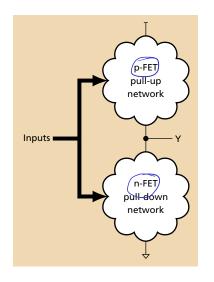


Pull-up and Pull-down networks must be complementary; exactly one should be connected for each input combination.

Series connection in one should be parallel in the other

## **CMOS** Inverter Layout

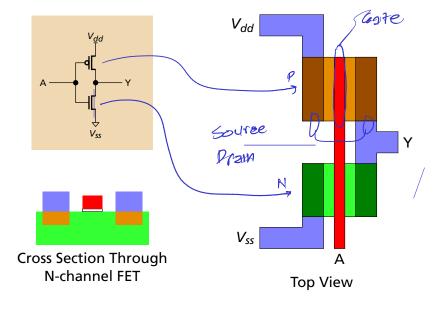


## **Full Adder Layouts**

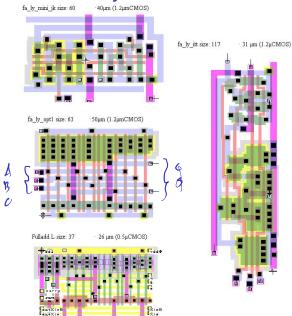

From http://book.huihoo.com/design-of-vlsi-systems
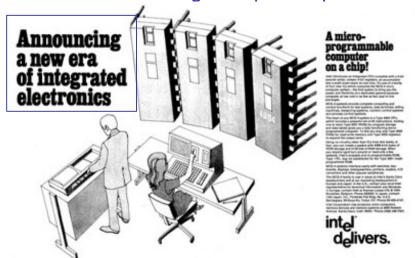
#### Intel 4004: The First Single-Chip Microprocessor




4001: 256-byte ROM + 4-bit IO port

4002: 40-byte RAM

4003: 10-bit shift register

4004: 740 kHz 4-bit CPU w/ 45 instructions (2300 transistors)

## Intel 4004 Masks

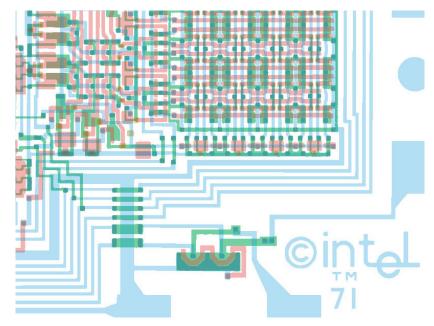

## Intel 4004 Die Photograph

