# Fundamentals of Computer Systems Transistors, Gates, and ICs

Stephen A. Edwards


**Columbia University** 

Summer 2021
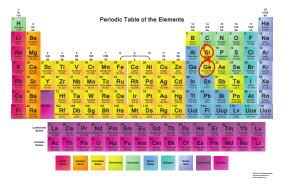
#### Semiconductor

sem·i·con·duc·tor noun

- A substance, such as silicon or germanium, with electrical conductivity intermediate between that of an insulator and a conductor
- 2. A semiconductor device



#### Sand into Silicon



Silica a.k.a.  $SiO_2$  a.k.a. Quartz  $SiO_2 + 2 C \rightarrow Si + 2 CO$ 



Elemental, amorphous silicon




Monocrystalline Silicon Ingot

## Doping Silicon Makes It a Better Conductor


Undoped (pure) silicon crystal

Not a good conductor

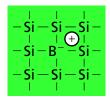

p-type (doped) silicon:


boron atom steals a nearby electron

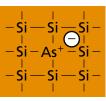


n-type (doped) silicon:

arsenic's extra electron jumps loose


#### A PN Junction aka A Diode

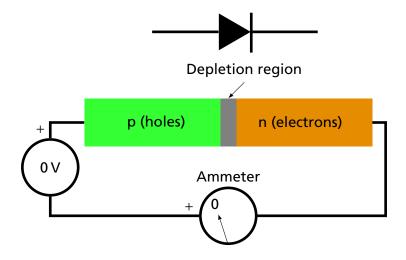


#### A PN Junction aka A Diode

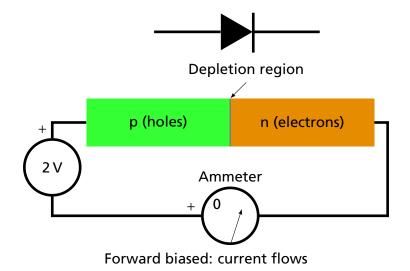


#### A PN Junction aka A Diode

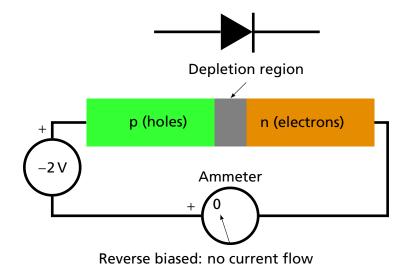


#### An N-Channel MOS Transistor

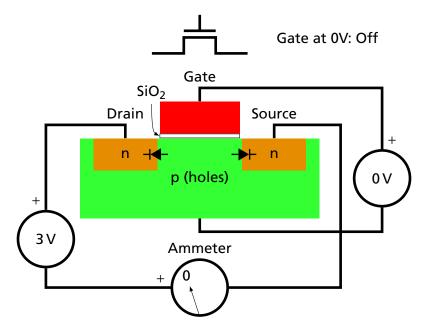


#### An N-Channel MOS Transistor

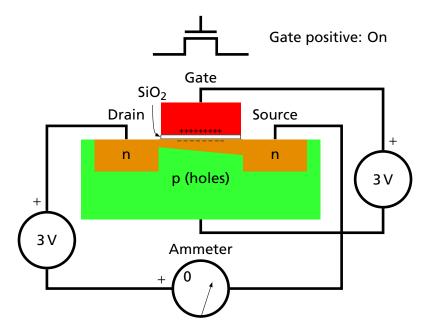


#### The CMOS Inverter

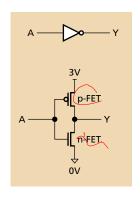

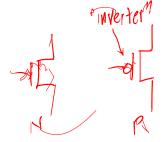An inverter is built from two MOSFETs: An n-FET connected to ground A p-FET connected to the power supply



#### The CMOS Inverter

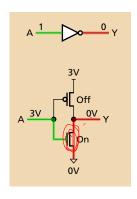


When the input is near the power supply voltage ("1"),

the p-FET is turned off;


the n-FET is turned on, connecting the output to ground ("0").

n-FETs are only good at passing 0's


#### The CMOS Inverter

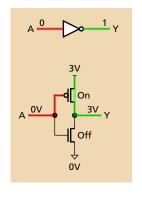

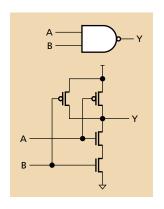
When the input is near ground ("0"), the p-FET is turned on, connecting the output to the power supply ("1"); the n-FET is turned off.
p-FETs are only good at passing 1's



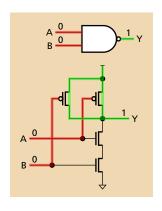Two-input NAND gate: two n-FETs in series; two p-FETs in parallel



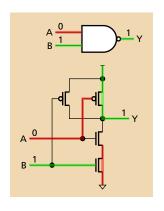Both inputs 0: Both p-FETs turned on Output pulled high




One input 1, the other 0:

One p-FET turned on

Output pulled high

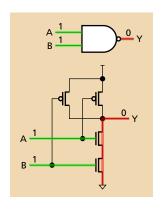One n-FET turned on, but does not control output




Both inputs 1:

Both n-FETs turned on

Output pulled low


Both p-FETs turned off

#### The CMOS NOR Gate

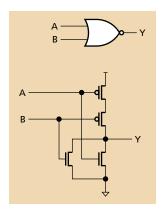


Two-input NOR gate: two n-FETs in parallel; two p-FETs in series.

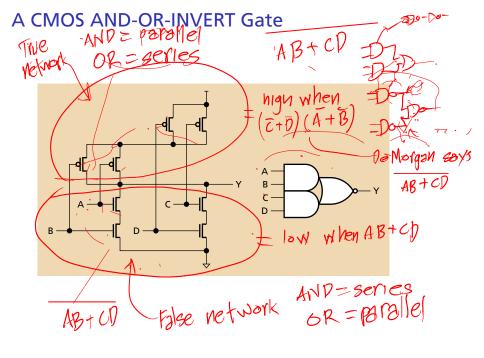
Not as fast as the NAND gate because n-FETs are faster than p-FETs




#### Static CMOS Gate Structure

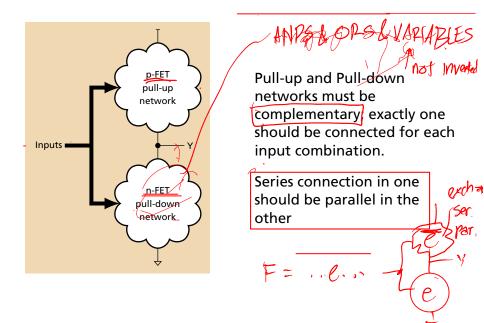


## **CMOS** Inverter Layout

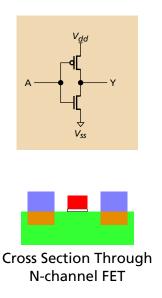

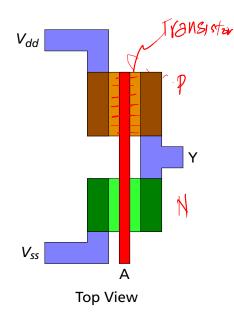


## **Full Adder Layouts**

F. 73

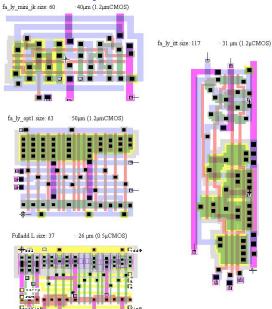

From http://book.huihoo.com/design-of-vlsi-systems
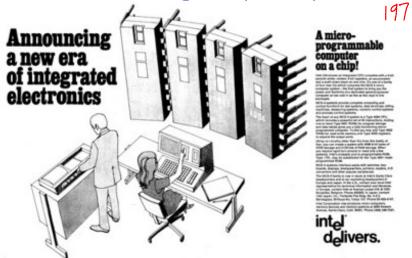
### Intel 4004: The First Single-Chip Microprocessor




4001: 256-byte ROM + 4-bit IO port

4002: 40-byte RAM

4003: 10-bit shift register

4004: 740 kHz 4-bit CPU w/ 45 instructions (2300 transistors)

## Intel 4004 Masks

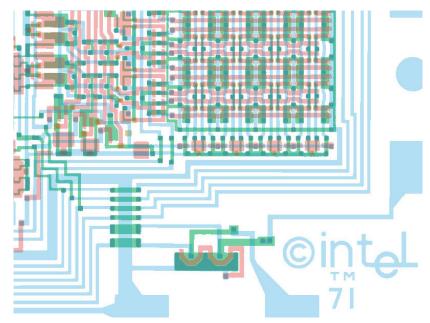

## Intel 4004 Die Photograph

