

Synchronous Digital Logic Systems

Review of Digital Logic

Prof. Stephen A. Edwards

Copyright © 2001 Stephen A. Edwards All rights reserved

- Raw materials: CMOS transistors and wires on ICs
- Wires are excellent conveyors of voltage
 - Little leakage
 - Fast, but not instantaneous propagation
 - Many orders of magnitude more conductive than glass
- CMOS transistors are reasonable switches
 - Finite, mostly-predictable switching times
 - Nonlinear transfer characteristics
 - Voltage gain is in the 100s

Copyright © 2001 Stephen A. Edwards All rights reserved

Philosophy

- Have to deal with unpredictable voltages and unpredictable delays
- Digital: discretize values to avoid voltage noise
 - Only use two values
 - Voltages near these two are “snapped” to remove noise
- Synchronous: discretize time to avoid time noise
 - Use a global, periodic clock
 - Values that become valid before the clock are ignored until the clock arrives

Copyright © 2001 Stephen A. Edwards All rights reserved

Combinational Logic

Copyright © 2001 Stephen A. Edwards All rights reserved

Combinational Logic

- Boolean Logic Gates


			
Inverter	AND	OR	XOR
\overline{A}	AB	$A+B$	$A\overline{B} + \overline{A}B$
0 1	00 0	00 0	00 0
1 0	01 0	01 1	01 1
	10 0	10 1	10 1
	11 1	11 1	11 0

Copyright © 2001 Stephen A. Edwards All rights reserved

A Full Adder

- Typical example of building a more complex function


A	B	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

Copyright © 2001 Stephen A. Edwards All rights reserved

Most Basic Computational Model

 
- Every gate is continuously looking at its inputs and instantaneously setting its outputs accordingly
- Values are communicated instantly from gate outputs to inputs



Copyright © 2001 Stephen A. Edwards All rights reserved

Delays

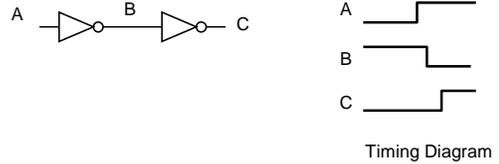
- Real implementations are not quite so perfect
- Computation actually takes some time
- Communication actually takes some time



Copyright © 2001 Stephen A. Edwards All rights reserved

Delays

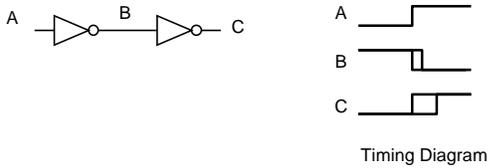- Delays are often partially unpredictable
- Usually modeled with a minimum and maximum



Copyright © 2001 Stephen A. Edwards All rights reserved


Busses

- Wires sometimes used as shared communication medium
- Think “party-line telephone”
- Bus drivers may elect to set the value on a wire or let some other driver set that value
- Electrically disastrous if two drivers “fight” over the value on the bus

Copyright © 2001 Stephen A. Edwards All rights reserved

Implementing Busses

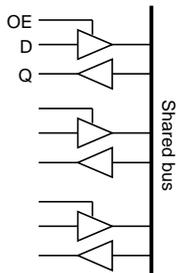- Basic trick is to use a “tri-state” driver
- Data input and output enable



Copyright © 2001 Stephen A. Edwards All rights reserved

- When driver wants to send values on the bus, OE = 1 and D contains the data
- When driver wants to listen and let some other driver set the value, OE = 0 and Q returns the value

Four-Valued Simulation

- Wires in digital logic often modeled with four values
 - 0, 1, X, Z
- X represents an unknown state
 - State of a latch or flip-flop when circuit powers up
 - Result of two gates trying to drive wire to 0 and 1 simultaneously
 - Output of flip-flop when setup or hold time violated
 - Output of a gate reading an “X” or “Z”
- Z represents an undriven state
 - Value on a shared bus when no driver is output-enabled


Copyright © 2001 Stephen A. Edwards All rights reserved

Sequential Logic and Timing

Copyright © 2001 Stephen A. Edwards All rights reserved

Sequential Logic

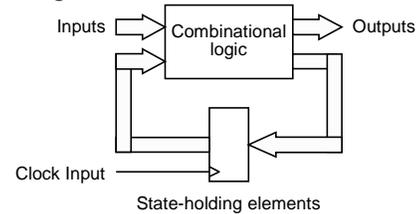
- Simply computing functions usually not enough
- Want more time-varying behavior
- Common model: combinational logic with state-holding elements



Copyright © 2001 Stephen A. Edwards All rights reserved

State Machines

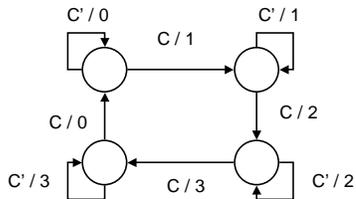- Common use of state-holding elements
- Idea: machine may go to a new state in each cycle
- Output and next state dependent on present state
- E.g., a four-counter



Copyright © 2001 Stephen A. Edwards All rights reserved


Latches & Flip-Flops

- Two common types of state-holding elements
- Latch
 - Level-sensitive
 - Transparent when clock is high
 - Holds last value when clock is low
 - Cheap to implement
 - Somewhat unwieldy to design with
- Flip-flop
 - Edge-sensitive
 - Always holds value
 - New value sampled when clock transitions from 0 to 1
 - More costly to implement
 - Much easier to design with

Copyright © 2001 Stephen A. Edwards All rights reserved

Latches & Flip-Flops

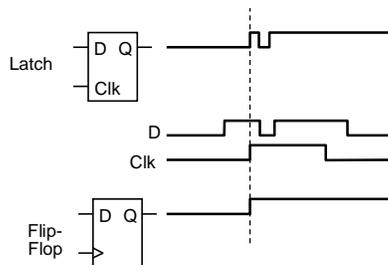
- Timing diagrams for the two common types:



Copyright © 2001 Stephen A. Edwards All rights reserved

RAMs

 
- Another type of state-holding element
- Addressable memory
- Good for storing data like a von Neumann program



Copyright © 2001 Stephen A. Edwards All rights reserved

RAMs

 - **Write cycle**
 - Present Address, data to be written
 - Raise and lower write input
- **Read cycle**
 - Present Address
 - Raise read
 - Contents of address appears on data out



Copyright © 2001 Stephen A. Edwards All rights reserved


Setup & Hold Times

- Flip-flops and latches have two types of timing requirements:
- **Setup time**
 - D input must be stable some time before the clock arrives
- **Hold time**
 - D input must remain stable some time after the clock has arrived

Copyright © 2001 Stephen A. Edwards All rights reserved

Setup & Hold Times


- For a flip-flop (edge-sensitive)

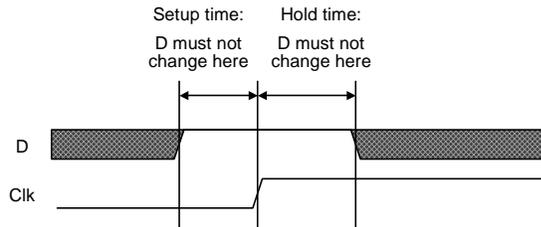

Copyright © 2001 Stephen A. Edwards All rights reserved

Synchronous System Timing

 - Budgeting time in a typical synchronous design



Copyright © 2001 Stephen A. Edwards All rights reserved

Digital Systems

Copyright © 2001 Stephen A. Edwards All rights reserved


Typical System Architecture

- Most large digital systems consist of
 - **Datapath**
 - Arithmetic units (adders, multipliers)
 - Data-steering (multiplexers)
 - **Memory**
 - Places to store data across clock cycles
 - Memories, register files, etc.
 - **Control**
 - Interacting finite state machines
 - Direct how the data moves through the datapath

Copyright © 2001 Stephen A. Edwards All rights reserved

Typical System Architecture

- Primitive datapath plus controller

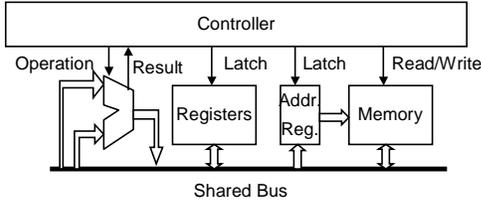

Copyright © 2001 Stephen A. Edwards All rights reserved

Implementing Digital Logic

- Discrete logic chips
 - NAND gates four to a chip and wire them up (e.g., TTL)
- Programmable Logic Arrays (PLAs)
 - Program a chip containing ANDs feeding big OR gates
- Field-Programmable Gate Arrays (FPGAs)
 - Program lookup tables and wiring routes
- Application-Specific Integrated Circuit (ASICs)
 - Feed a logic netlist to a synthesis system
 - Generate masks and hire someone to build the chip
- Full-custom Design
 - Draw every single wire and transistor yourself
 - Hire someone to fabricate the chip or be Intel

Copyright © 2001 Stephen A. Edwards All rights reserved

Implementing Digital Logic

- Discrete logic is dead
 - Too many chips needed compared to other solutions
- PLAs
 - Nice predictable timing, but small and limited
- FPGAs
 - High levels of integration, very convenient
 - Higher power and per-unit cost than ASICs and custom
- ASICs
 - Very high levels of integration, costly to design
 - Low power, low per-unit cost, but huge initial cost
- Full Custom
 - Only cost-effective for very high-volume parts
 - E.g., Intel microprocessors

Copyright © 2001 Stephen A. Edwards All rights reserved

Digital Logic in Embedded Systems

- Low-volume products (1000s or less) typically use FPGAs
- High-volume products usually use ASICs
- Non-custom logic usually implemented using application-specific standard parts
 - Chipsets
 - Graphics controllers
 - PCI bus controllers
 - USB controllers
 - Ethernet interfaces

Copyright © 2001 Stephen A. Edwards All rights reserved