

CSEE W3827

Fundamentals of Computer Systems

Homework Assignment 3

Solutions

Profs. Stephen A. Edwards & Martha Kim

Columbia University

Due February 27th, 2012 at 1:10 PM

Write your name **and UNI** on your solutions


Show your work for each problem; we are more interested in how you get the answer than whether you get the right answer.

1. (25 pts.) A sequential circuit with two D flip-flops S_0 and S_1 , two inputs X and Y , and one output Z behaves according to these equations:


$$S'_0 = \bar{X}S_0 + XY \quad S'_1 = \bar{X}S_1 + XS_0 \quad Z = XS_1$$

- Draw the corresponding circuit. Label each of the signals mentioned above.
- Derive the state table (next state and output as a function of present state and input).
- Draw the corresponding bubble-and-arc diagram.

 
$$S'_0 = \bar{X}S_0 + XY \quad S'_1 = \bar{X}S_1 + XS_0 \quad Z = XS_1$$




S_1S_0	X	Y	$S'_1S'_0$	Z
00	0	0	00	0
00	0	1	00	0
00	1	0	00	0
00	1	1	01	0
01	0	0	01	0
01	0	1	01	0
01	1	0	10	0
01	1	1	11	0
10	0	0	10	0
10	0	1	10	0
10	1	0	00	1
10	1	1	01	1
11	0	0	11	0
11	0	1	11	0
11	1	0	10	1
11	1	1	11	1

 

 
2. (15 pts.) Many serial communication protocols, such as USB, use a signaling protocol known as “non return to zero, inverted” (NRZI) in which a “0” is represented as a transition and a “1” as no transition. Below is an example of a normal bit stream (NRZ) and how it would be encoded in NRZI as a waveform on the left and the corresponding bit streams on the right.



 - Draw a Mealy bubble-and-arc diagram for an NRZ-to-NRZI protocol converter.
- Choose an encoding for your state machine and write its (encoded) state table.
- Design and draw a circuit implementation of your converter using D flip-flops and gates.



S	A	Y	S'
0	0	1	1
0	1	0	0
1	0	0	0
1	1	1	1

 

3. (15 pts.) Determine the logic for a synchronous 4-bit decimal counter that counts $0,1,\dots,9,0,1,\dots$ in binary. It should have four outputs Q_1, Q_2, Q_4, Q_8 , (the subscripts indicate the value of each bit) each driven directly by a flip-flop.

Write Boolean expressions of the form $D_i = Q_i \oplus (\dots)$ for each flip-flop's input. (\oplus is XOR)

0000

0001

0010

0011

0100 $D_1 = Q_1 \oplus 1$

0101 $D_2 = Q_2 \oplus (\overline{Q_8}Q_1)$

0110 $D_4 = Q_4 \oplus (Q_2Q_1)$

0111 $D_8 = Q_8 \oplus (Q_4Q_2Q_1 + Q_8Q_1)$



1000

1001

0000


0001

  4. (15 pts.) Using just three flip-flops and three two-input muxes, draw a circuit for the following Moore state machine with a single input and single output. Use a one-hot encoding. Each state is labeled with the value of the output.




5. (15 pts.)

 - (a) Write a Boolean expression for the function of the following static CMOS gate.



$$Y = \overline{ABC} + D$$

 


- (b) Draw the schematic for a static CMOS gate that implements $Y = \overline{(A + B)C} + D$

6. (15 pts.) Show how to implement a two-bit priority encoder using the PLA drawn below.

Hint: write the expressions for Y and Z in sum-of-products form then draw crosses to indicate connections on the AND plane.

A	B	C	YZ
0	0	0	00
1	0	0	01
X	1	0	10
X	X	1	11

 

$$Y = C + B\bar{C} \text{ or } Y = B + C$$

$$Z = A\bar{B}\bar{C} + C \text{ or } Z = A\bar{B} + C$$