

CSEE W3827  
Fundamentals of Computer Systems  
Homework Assignment 1

Prof. Stephen A. Edwards  
Columbia University

Due Tuesday, June 9th, 2015 at 5:30 PM

Print this out and turn it in. Enter answers on the computer or manually on the printout.

This homework requires you to use Logisim, which you can download from <http://www.cburch.com/logisim/>

Name:

Uni:

1. (5 pts.) What are the values, in decimal, of the following bytes if they are interpreted as 8-bit numbers in

00010011 10011010

binary

one's complement

two's complement

2. (5 pts.) Complete the truth table for the following Boolean functions:

$$a = X\bar{Y} + \bar{X}YZ + \bar{X}\bar{Z}$$

$$b = (X + \bar{Y})(X + Z)(\bar{X} + Z)$$


<b>X</b>	<b>Y</b>	<b>Z</b>	<b>a</b>	<b>b</b>
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

3. (20 pts.) Consider the function  $F$  whose truth table is shown below

W	X	Y	Z	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

(a) Write the function  $F$  in sum-of-minterms form. Two are given.

(b) Fill in this Karnaugh map for  $F$

 

(c) Use your Karnaugh map to write a minimal sum-of-products representation for  $F$

In Logisim,

- (d) Implement the circuit corresponding to your minimal sum-of-products representation. Verify your circuit using Logisim's Combinational Analysis feature (Project→Analyze Circuit).

Print your solution and attach it.

- (e) Use your Karnaugh map to write a minimal product-of-sums representation for F.

- (f) Implement the circuit corresponding to your minimal product-of-sums. Again, verify your circuit.

Print your solution and attach it.

4. (20 pts.) Create a circuit for a 4-to-10 decoder using AND gates and inverters only. Arrange and name the inputs and outputs as shown below. Treat  $W$  as the most significant bit. Only one of the outputs should ever be true.

$W$	$\rightarrow$	$\rightarrow A0$
$X$	$\rightarrow$	$\rightarrow A1$
$Y$	$\rightarrow$	$:$
$Z$	$\rightarrow$	$\rightarrow A9$

Implement your circuit in Logisim, verify it, and print and attach it.


5. (15 pts.) In Logisim, implement  $F = XY\bar{Z} + YZ + \bar{X}Y$  using just constants and
- (a) a 3-to-8 decoder (under “Plexers→Decoder.” Set “include enable” to “No” and note the input wires are a bundle at the bottom) and an OR gate;
  - (b) an 8 input mux; and
  - (c) a 4 input mux whose select inputs are  $X$  and  $Y$ , and an inverter.

Implement each of these circuits in Logisim, verify them, and print and attach them.



 6. (15 pts.) Implement an eight-input mux using two-input muxes only (constants are OK).

Arrange your inputs and outputs as shown below.



Here,  $A0$  through  $A7$  are the eight inputs, and  $X$ ,  $Y$ , and  $Z$  are the three selects.  $X$  is the most significant bit, selecting between, e.g.,  $A0$  and  $A4$ .

Implement your circuit in Logisim, verify it, and print and attach it.

7. (20 pts.) Implement the combinational portion of a three-bit binary counter with an enable input. Give it four inputs,  $X$ ,  $Y$ ,  $Z$ , and  $E$ , and three outputs  $A$ ,  $B$ , and  $C$ .

When  $E$  is 0,  $A$ ,  $B$ , and  $C$  should be  $X$ ,  $Y$ , and  $Z$  respectively.

When  $E$  is 1,  $A$ ,  $B$ , and  $C$  should be  $X$ ,  $Y$ , and  $Z$  plus one, with  $A$  and  $X$  the MSBs.

Your counter should wrap around, i.e.,  $7 + 1 = 0$ .

Implement your circuit in Logisim, verify it, and print and attach it.