

Digital Design with SystemVerilog

Prof. Stephen A. Edwards

Columbia University

Spring 2019

Synchronous Digital Design

Combinational Logic

Sequential Logic

Summary of Modeling Styles

Testbenches

Why HDLs?




1970s: SPICE transistor-level netlists

An XOR built from four NAND gates

```
.MODEL P PMOS
.MODEL N NMOS

.SUBCKT NAND A B Y Vdd Vss
M1 Y A Vdd Vdd P
M2 Y B Vdd Vdd P
M3 Y A X Vss N
M4 X B Vss Vss N
.ENDS

   X1 A B I1 Vdd 0 NAND
X2 A I1 I2 Vdd 0 NAND
X3 B I1 I3 Vdd 0 NAND
X4 I2 I3 Y Vdd 0 NAND
```



Why HDLs?

1980s: Graphical schematic capture programs

The screenshot displays the gschem graphical schematic capture program. The window title is "gschem" and the menu bar includes "File", "Edit", "Buffer", "View", "Page", "Add", "Hierarchy", "Attributes", "Options", and "Help". The toolbar contains various icons for file operations and editing. The main workspace shows a complex digital circuit diagram for a 4-bit grey counter. The circuit consists of several logic gates (AND, OR, XOR) and flip-flops (D-type), interconnected to produce four outputs: C-H, D-H, E-H, and F-H. A clock input (CLK-L) is connected to a D-type flip-flop (U024). The circuit is labeled "4-BIT GREY COUNTER" in green text. A status bar at the bottom indicates the file path: ".../gschem/examples/grey_counter_1.sch".

The circuit diagram shows a 4-bit grey counter implemented using logic gates and flip-flops. The inputs are labeled C-L, B-L, A-L, D-L, E-L, and F-L. The outputs are labeled C-H, D-H, E-H, and F-H. The circuit includes several logic gates (AND, OR, XOR) and flip-flops (D-type). A clock input (CLK-L) is connected to a D-type flip-flop (U024). The circuit is labeled "4-BIT GREY COUNTER" in green text.

The grey counter counts the following sequence: 0101 0110 0100 0111

| File | gschem-1.sch | VIEW: 1 |
|------|--------------|------------------------------|
| Proj | OF | Document: 4-bit Grey Counter |


Pick | Action | Pan/Cancel .../gschem/examples/grey_counter_1.sch Select Mode

Why HDLs?


1990s: HDLs and Logic Synthesis

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity ALU is
port(A:    in unsigned(1 downto 0);
     B:    in unsigned(1 downto 0);
     Sel:  in unsigned(1 downto 0);
     Res:  out unsigned(1 downto 0));
end ALU;
architecture behv of ALU is begin
  process (A,B,Sel) begin
    case Sel is
      when "00" => Res <= A + B;
      when "01" => Res <= A + (not B) + 1;
      when "10" => Res <= A and B;
      when "11" => Res <= A or B;
      when others => Res <= "XX";
    end case;
  end process;
end behv;
```

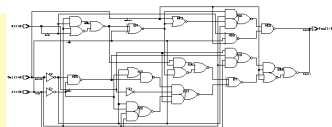

Separate but Equal: Verilog and VHDL

 

Verilog: More succinct, really messy

VHDL: Verbose, overly flexible, fairly messy

Part of languages people actually use identical

Every synthesis system supports both

SystemVerilog a newer version. Supports many more features.

Synchronous Digital Design

The Synchronous Digital Logic Paradigm

Gates and D
flip-flops only


No level-sensitive
latches

All flip-flops
driven by the
same clock



No other clock
signals

Every cyclic path
contains at least
one flip-flop

No combinational
loops

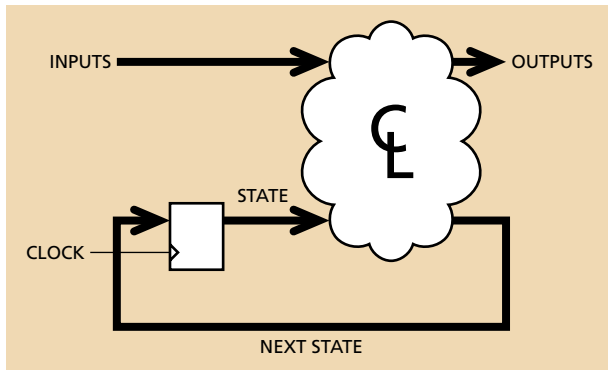


Timing in Synchronous Circuits

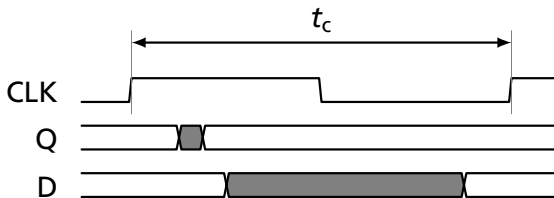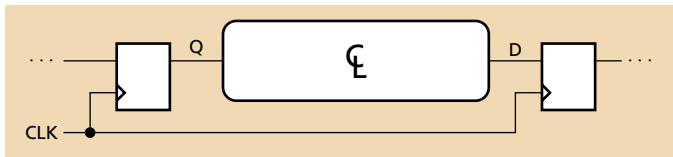


t_c : Clock period. E.g., 10 ns for a 100 MHz clock

Timing in Synchronous Circuits


 


Sufficient Hold Time?

 

Hold time constraint: how soon after the clock edge can D start changing? Min. FF delay + min. logic delay

Timing in Synchronous Circuits

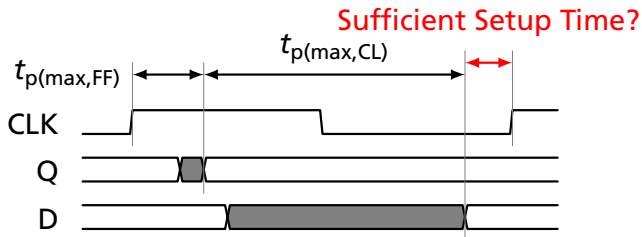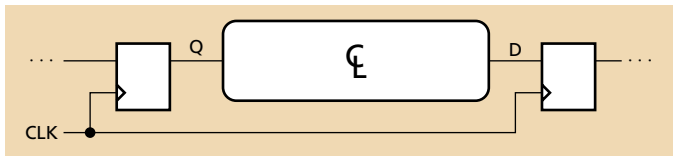

Setup time constraint: when before the clock edge is D guaranteed stable? Max. FF delay + max. logic delay

Combinational Logic

Full Adder

Single-line comment

Systems are built from modules

Module name


Input port

Data type: single bit

Port name

```
// Full adder  
module full_adder(input logic a, b, c,  
                 output logic sum, carry);  
  
    assign sum = a ^ b ^ c;  
    assign carry = a & b | a & c | b & c;  
endmodule
```

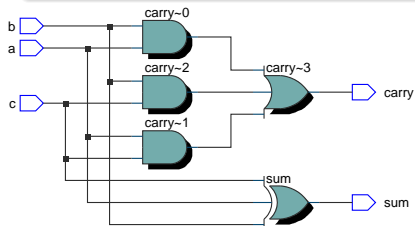"Continuous assignment" expresses combinational logic



Logical Expression

Operators and Vectors

Four-bit vector,
little-endian style

```
module gates(input  logic [3:0] a, b,  
            output logic [3:0] y1, y2, y3,  
            y4, y5);  
  
    /* Five groups of two-input logic gates  
       acting on 4-bit busses */  
    assign y1 = a & b;    // AND  
    assign y2 = a | b;    // OR  
    assign y3 = a ^ b;    // XOR  
    assign y4 = ~(a & b); // NAND  
    assign y5 = ~(a | b); // NOR  
endmodule
```

Multi-line
comment

Reduction AND Operator


```
module and8(input logic [7:0] a,  
            output logic      y);  
  
    assign y = &a; // Reduction AND  
  
    // Equivalent to  
    // assign y = a[7] & a[6] & a[5] & a[4] &  
    //           a[3] & a[2] & a[1] & a[0];  
  
    // Also ~|a  NAND  
    //         |a  OR  
    //        ~|a  NOR  
    //         ^a  XOR  
    //        ~^a  XNOR  
endmodule
```

The Conditional Operator: A Two-Input Mux

```
module mux2(input  logic [3:0] d0, d1,
            input  logic      s,
            output logic [3:0] y);

    // Array of two-input muxes

    assign y = s ? d1 : d0;
endmodule
```

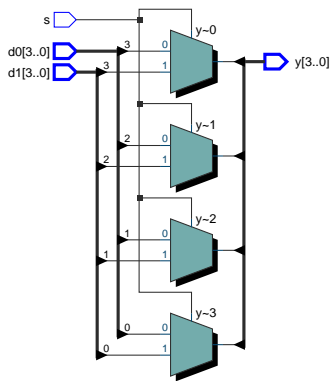

Operators in Precedence Order

| | |
|-------------------|----------------------------------|
| !c -c &c ~&c | NOT, Negate, Reduction AND, NAND |
| c ~ c ^c ~^c | OR, NOR, XOR, XNOR |
| a*b a/b a%b | Multiply, Divide, Modulus |
| a+b a-b | Add, Subtract |
| a<<b a>>b | Logical Shift |
| a<<<b a>>>b | Arithmetic Shift |
| a<b a<=b a>b a>=b | Relational |
| a==b a!=b | Equality |
| a&b a^&b | AND |
| a^b a~^b | XOR, XNOR |
| a b | OR |
| a?b:c | Conditional |
| {a,b,c,d} | Concatenation |


An XOR Built Hierarchically

```
module mynand2(input logic a, b,  
              output logic y);  
  assign y = ~(a & b);  
endmodule
```

```
module myxor2(input logic a, b,  
            output logic y);  
  logic abn, aa, bb;  
  
  mynand2 n1(a, b, abn),  
         n2(a, abn, aa),  
         n3(abn, b, bb),  
         n4(aa, bb, y);  
endmodule
```

Declare internal wires

n1: A mynand2
connected to a, b, and abn

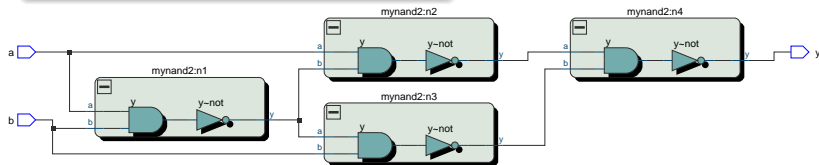

A Decimal-to-Seven-Segment Decoder

always_comb:
combinational
logic in an
imperative style

```
module dec7seg(input logic [3:0] a,  
              output logic [6:0] y);  
    always_comb  
    case (a)  
        4'd0:    y = 7'b111_1110;  
        4'd1:    y = 7'b011_0000;  
        4'd2:    y = 7'b110_1101;  
        4'd3:    y = 7'b111_1001;  
        4'd4:    y = 7'b011_0011;  
        4'd5:    y = 7'b101_1011;  
        4'd6:    y = 7'b101_1111;  
        4'd7:    y = 7'b111_0000;  
        4'd8:    y = 7'b111_1111;  
        4'd9:    y = 7'b111_0011;  
        default: y = 7'b000_0000;  
    endcase  
endmodule
```

Multiway
conditional


4'd5: decimal "5"
as a four-bit
binary number

Mandatory

seven-bit
binary vector
(_ is ignored)

"blocking
assignment":
use in always_comb


Verilog Numbers

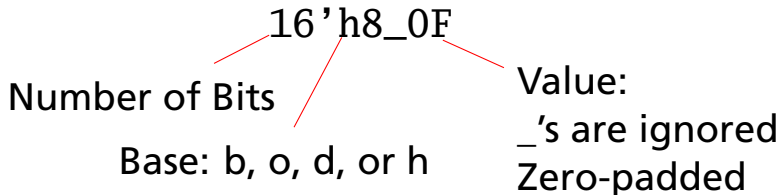

4'b1010 = 4'o12 = 4'd10 = 4'ha
16'h4840 = 16'b 100_1000_0100_0000

Imperative Combinational Logic

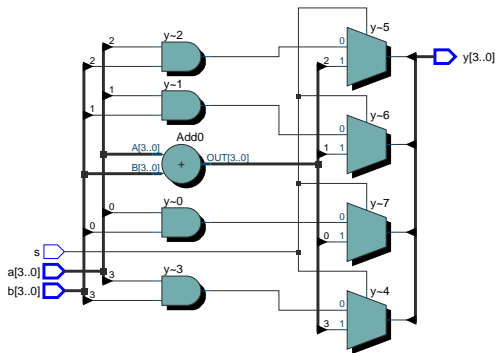
```
module comb1(  
    input logic [3:0] a, b,  
    input logic s,  
    output logic [3:0] y);  
  
    always_comb  
        if (s)  
            y = a + b;  
        else  
            y = a & b;  
  
endmodule
```



Both $a + b$ and $a \& b$ computed, mux selects the result.

Imperative Combinational Logic

```
module comb2(  
    input logic [3:0] a, b,  
    input logic s, t,  
    output logic [3:0] y);  
  
    always_comb  
        if (s)  
            y = a + b;  
        else if (t)  
            y = a & b;  
        else  
            y = a | b;  
  
endmodule
```

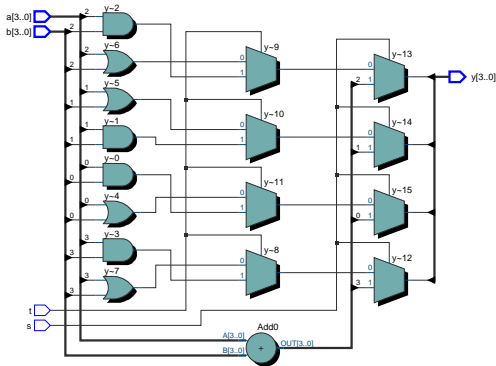


All three expressions
computed in parallel.
Cascaded muxes
implement priority
(s over t).

| s | t | y |
|---|---|-------|
| 1 | — | a + b |
| 0 | 1 | a & b |
| 0 | 0 | a b |

Imperative Combinational Logic

```
module comb3(  
    input logic [3:0] a, b,  
    input logic s, t,  
    output logic [3:0] y, z);  
  
    always_comb begin  
        z = 4'b0;  
        if (s) begin  
            y = a + b;  
            z = a - b;  
        end else if (t) begin  
            y = a & b;  
            z = a + b;  
        end else  
            y = a | b;  
        end  
    end  
endmodule
```

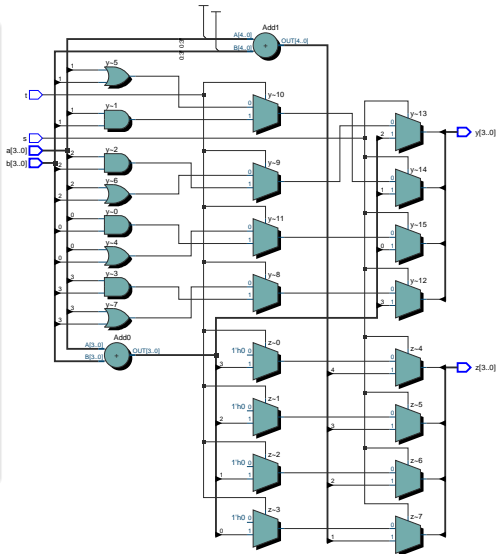

Separate mux cascades
for y and z.
One copy of a + b.

An Address Decoder

```
module adecode(input logic [15:0] address,
               output logic RAM, ROM,
               output logic VIDEO, IO);

  always_comb begin
    {RAM, ROM, VIDEO, IO} = 4'b 0;
    if (address[15])
      RAM = 1;
    else if (address[14:13] == 2'b 00 )
      VIDEO = 1;
    else if (address[14:12] == 3'b 101)
      IO = 1;
    else if (address[14:13] == 2'b 11 )
      ROM = 1;
  end
endmodule
```

Vector concatenation

Default:
all zeros

Select bit 15

Select bits 14, 13, & 12

Omitting defaults for *RAM*, etc. will give “construct does not infer purely combinational logic.”

Sequential Logic

A D-Flip-Flop


always_ff introduces sequential logic

Triggered by the rising edge of clk

```
module mydff(input logic clk,  
             input logic d,  
             output logic q);  
  
    always_ff @(posedge clk)  
        q <= d;  
  
endmodule
```

Copy d to q

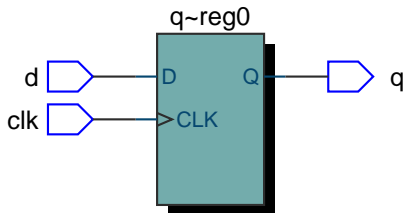
Non-blocking assignment:
happens "just after" the rising edge




A Four-Bit Binary Counter

```
module count4(input logic clk,  
              output logic [3:0] count);  
  
  always_ff @(posedge clk)  
    count <= count + 4'd 1;  
  
endmodule
```

Width optional
but good style

 


Moore and Mealy Finite-State Machines

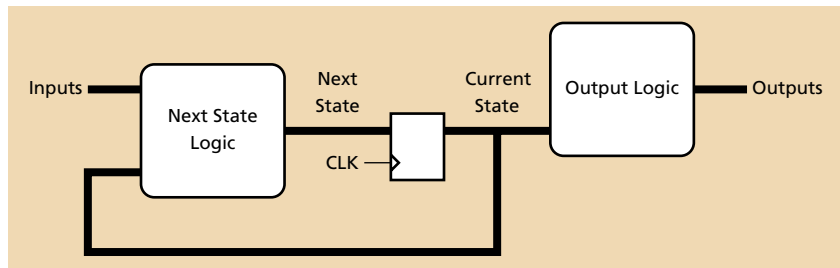

The Moore Form:

Outputs are a function of *only* the current state.

Moore and Mealy Finite-State Machines

 

The Mealy Form:

Outputs may be a function of *both* the current state and the inputs.

A mnemonic: *Moore* machines often need *more* states.

Moore-style: Sequential Next-State Logic

```
module moore_tlc(input logic  clk, reset,
                 input logic  advance,
                 output logic  red, yellow, green);

enum logic [2:0] {R, Y, G} state; // Symbolic state names

always_ff @(posedge clk) // Moore-style next-state logic
  if (reset)          state <= R;
  else case (state)
    R: if (advance) state <= G;
    G: if (advance) state <= Y;
    Y: if (advance) state <= R;
    default:         state <= R;
  endcase

assign red    = state == R; // Combinational output logic
assign yellow = state == Y; // separated from next-state logic
assign green  = state == G;

endmodule
```

Mealy-style: Combinational output/next state logic

```
module mealy_tlc(input logic  clk, reset,
                input logic  advance,
                output logic  red, yellow, green);

typedef enum logic [2:0] {R, Y, G} state_t;
state_t state, next_state;

always_ff @(posedge clk) state <= next_state;

always_comb begin // Mealy-style next state and output logic
    {red, yellow, green} = 3'b0; // Default: all off and
    next_state = state;          // hold state
    if (reset)                   next_state = R;
    else case (state)
        R: begin red = 1;
                if (advance) next_state = G; end
        G: begin green = 1;
                if (advance) next_state = Y; end
        Y: begin yellow = 1;
                if (advance) next_state = R; end
        default: next_state = R;
    endcase
end

endmodule
```


Blocking vs. Nonblocking assignment

```
module nonblock(input    clk,  
               input logic a,  
               output logic d);
```

```
  logic b, c;
```

```
  always_ff @(posedge clk)
```

```
  begin
```

```
    b <= a;
```


```
    c <= b;
```

```
    d <= c;
```

```
  end
```

```
endmodule
```

 Nonblocking
assignment:
All run on the
clock edge



```
module blocking(input    clk,  
               input logic a,  
               output logic d);
```

```
  logic b, c;
```

```
  always_ff @(posedge clk)
```

```
  begin
```

```
    b = a;
```


```
    c = b;
```

```
    d = c;
```

```
  end
```

```
endmodule
```

 Blocking
assignment:
Effect felt by
next statement



Summary of Modeling Styles

A Contrived Example

```
module styles_tlc(input logic  clk, reset,
                 input logic  advance,
                 output logic  red, yellow, green);
enum logic [2:0] {R, Y, G} state;

always_ff @(posedge clk)           // Imperative sequential
  if (reset) state <= R;           // Non-blocking assignment
  else case (state)                // Case
    R: if (advance) state <= G;    // If-else
    G: if (advance) state <= Y;
    Y: if (advance) state <= R;
    default: state <= R;
  endcase

always_comb begin                  // Imperative combinational
  {red, yellow} = 2'b 0;           // Blocking assignment
  if (state == R) red = 1;         // If-else
  case (state)                     // Case
    Y: yellow = 1;
    default: ;
  endcase;
end

assign green = state == G;        // Cont. assign. (comb)
endmodule
```

Testbenches

Testbenches

A model of the environment; exercises the module.

```
// Module to test:  
// Three-bit  
// binary counter  
  
module count3(  
    input logic clk,  
             reset,  
    output logic [2:0]  
             count);  
  
    always_ff  
        @(posedge clk)  
            if (reset)  
                count <= 3'd 0;  
            else  
                count <=  
                    count + 3'd 1;  
  
endmodule
```

```
module count3_tb;  No ports  
    logic clk, reset;  Signals for each DUT port  
    logic [2:0] count;  "Device Under Test"  
  
    count3 dut(.*)  Connect everything  
  
    initial begin  Initial block:  
        clk = 0;  Imperative code  
        forever  runs once  
            #20ns clk = ~clk;  Infinite loop  
        end  Delay  
  
        initial begin // Reset  Counted loop  
            reset = 0;  
            repeat (2)  Wait for a  
                @(posedge clk);  clock cycle  
            reset = 1;  
            repeat (2)  
                @(posedge clk);  
            reset = 0;  
        end  
  
endmodule
```

Running this in ModelSim

